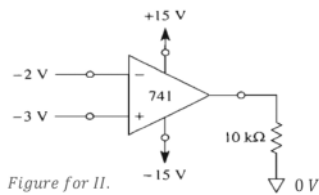


1.3 Comparator Examples

1.3.1 Finding output with constant inputs

Mohammed Radoan, Adjunct Lecturer, BRAC University


- II. Determine the voltage across the $10\text{ k}\Omega$ resistor for the circuit shown below. Assume the op-amp to be ideal except with a finite gain $A = 10^4$.



Ans: I. $-140\text{ }\mu\text{V}$; II. -15 V

$$\begin{aligned}
 V_{\text{out}} &= A(V_{\text{+in}} - V_{\text{-in}}) = 10^4(-3 - (-2)) \\
 &= 10^4 \times (-1) \\
 &= -10,000\text{ V (Not possible)} \\
 &= -V_{\text{sat}} \\
 &= -15\text{ V}
 \end{aligned}$$

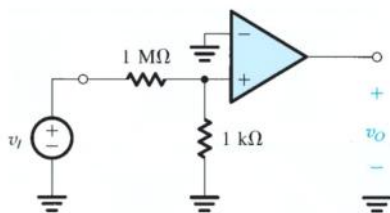The following circuit uses an op amp that is ideal except for having a finite gain A . Measurements indicate $v_O = 4.0\text{ V}$ when $v_I = 2.0\text{ V}$. What is the op-amp gain A ?



Ans: $A = 2002$



$$\begin{aligned}
 V_{\text{+in}} &= \frac{1\text{ k}}{1\text{ k} + 1\text{ M}} \times V_I \\
 &= \frac{1000}{1000 + 10^6} \times 2 = 1.998\text{ mV}
 \end{aligned}$$

$$\begin{aligned}
 V_O &= A V_{\text{+in}} - A(1.998\text{ m} - 0) \\
 \Rightarrow 4 &= A \times 1.998\text{ m} \\
 \Rightarrow A &= \frac{4}{1.998\text{ m}} = 2002\text{ V/V}
 \end{aligned}$$

1.3 Comparator Examples 1.3.2 Finding output with time varying inputs


Mohammed Radoan, Adjunct Lecturer, BRAC University

- Sketch V_o vs. t and V_o vs. E_i .

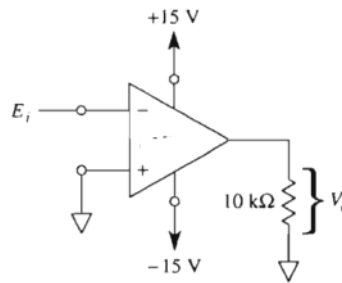
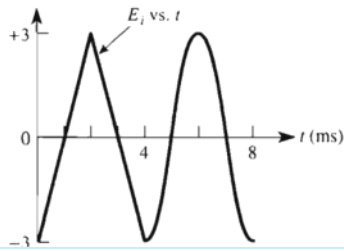


Ans

Cond	V_{out}
$E_i > 0$	$-V_{sat}$
$E_i < 0$	$+V_{sat}$

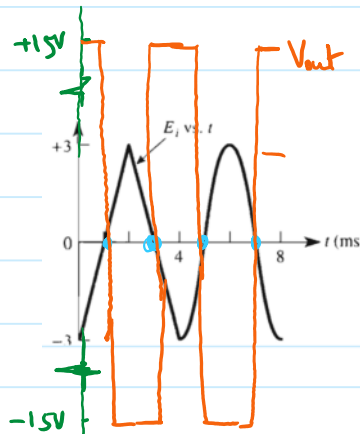


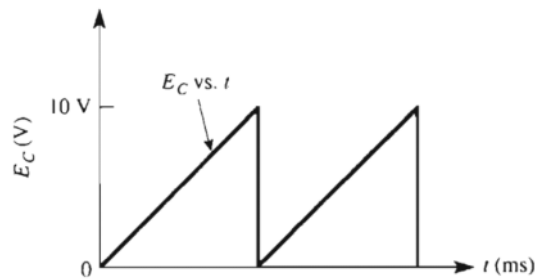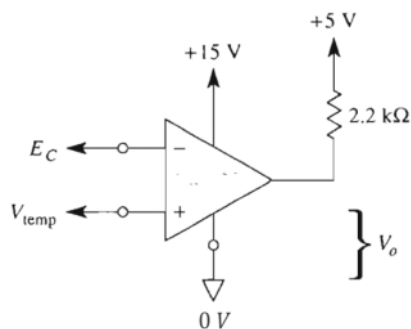- The frequency of E_C is constant at 50 Hz. If $V_{temp} = 4$ V, (a) plot V_o vs. E_C , (b) plot V_o vs. t , and (c) calculate the high time of V_o .



Ans

Cond	V_{out}
$E_c > 4V$	$-V_{sat} = 0V$
$E_c < 4V$	$+V_{sat} = +15V$


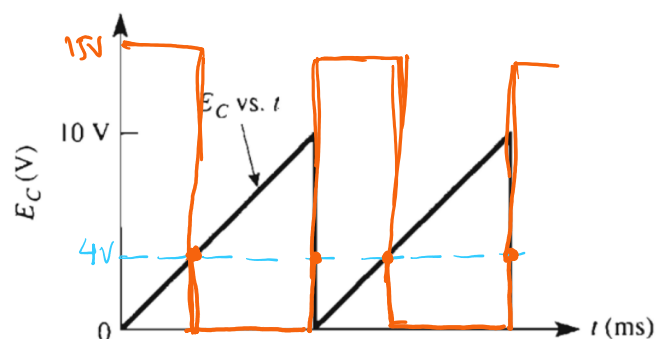


1.3 Comparator Examples

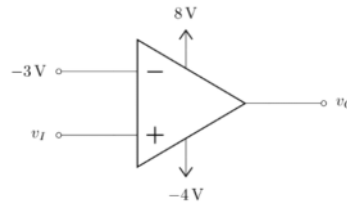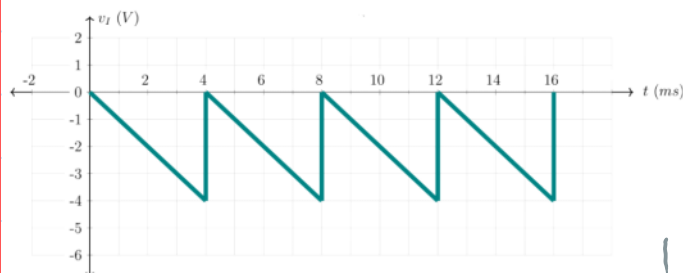1.3.2 Finding output with time varying inputs


Mohammed Radoan, Adjunct Lecturer, BRAC University

- In the adjacent circuit, v_I is a time varying voltage as plotted below. Sketch the graphs of (a) V_o vs. t and (b) V_o vs. v_I .





Ans

Cond	Output
$V_I > -3V$	$+V_{sat} = 8V$
$V_I < -3V$	$-V_{sat} = -4V$

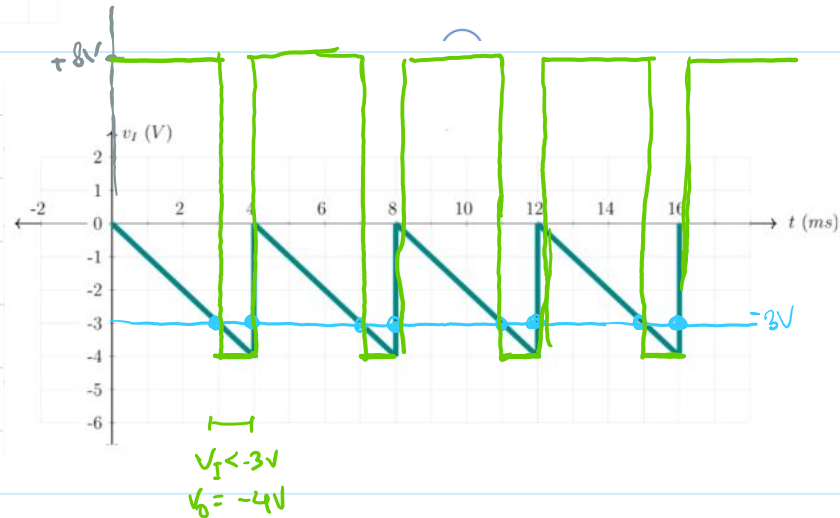

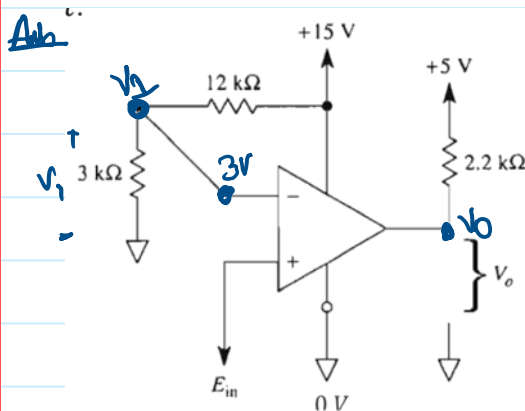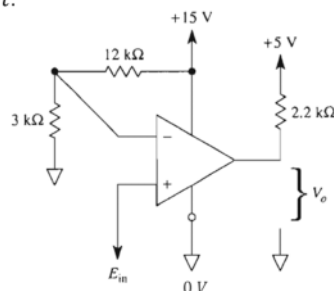- In the following circuit, E_{in} is a triangular wave of 100 Hz frequency with an amplitude of 5 V. Sketch, with appropriate levels of axes crossings, the graphs of (a) V_o vs. E_{in} and (b) V_o vs. t .





$$V_I = \frac{3k}{12k+3k} \times 15 = 3V$$

Cond	Output
$E_{in} > 3$	$+V_{sat} = +15V$
$E_{in} < 3$	$-V_{sat} = 0V$

$$f = 100 \text{ Hz}$$

$$T = \frac{1}{100} = 0.01 \text{ s}$$



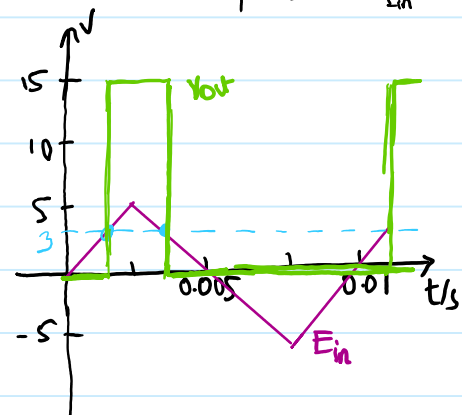
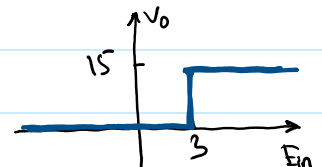


1.3 Comparator Examples







1.3.3 Designing circuit

Mohammed Radoan, Adjunct Lecturer, BRAC University

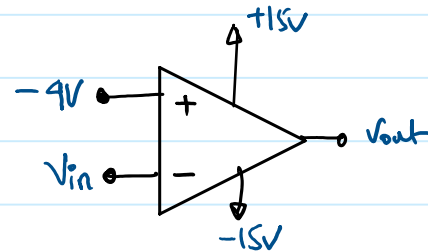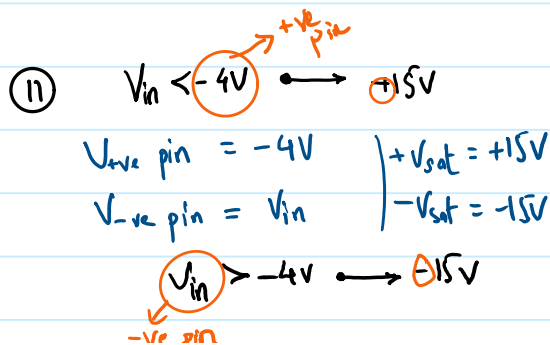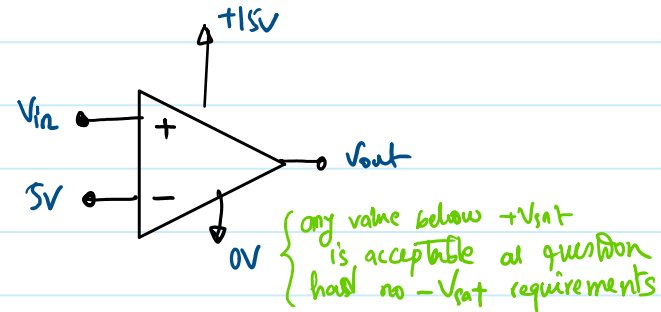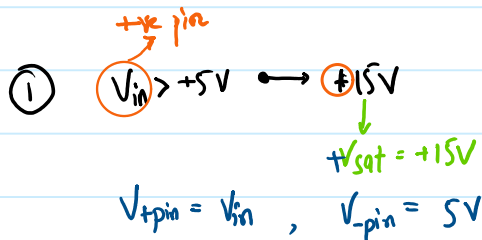- I. Draw the schematics of a circuit whose output voltage will go positive to $+15\text{ V}$, when the input signal crosses $+5\text{ V}$ in the positive direction.
- II. Draw the schematics of a circuit whose output voltage will go positive to $+15\text{ V}$, when the input signal is below -4 V . The output should be at -15 V when the input is above -4 V .



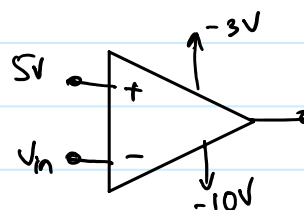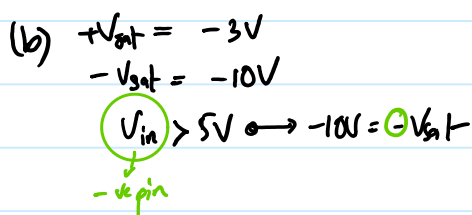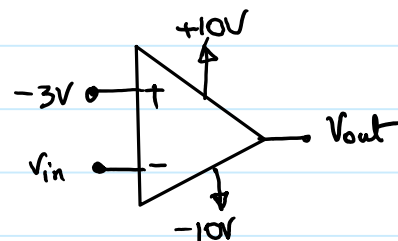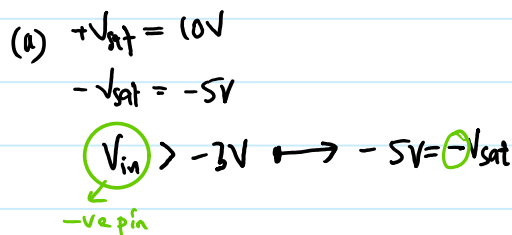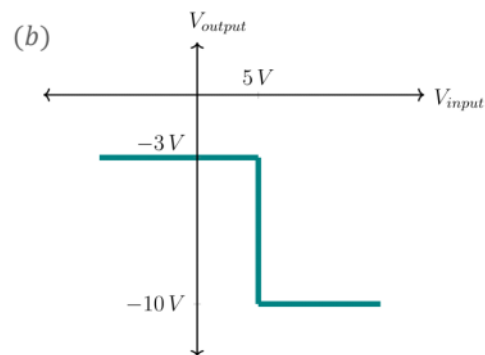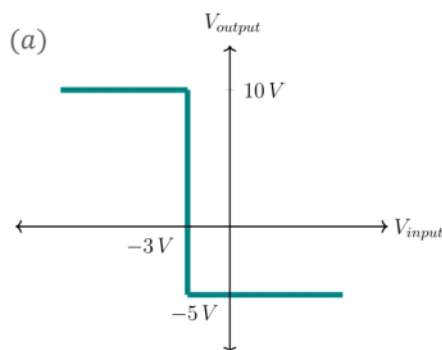
- Design a circuit with a single ideal op-amp for each of the VTC plots shown below. V_{output} and V_{input} are the output voltage and the input voltage respectively.



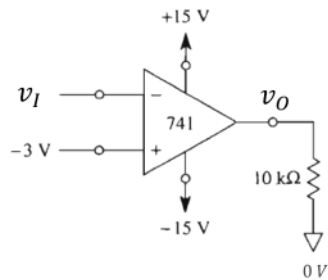1.3 Comparator Examples 1.3.4 Drawing VTC


Mohammed Radoan, Adjunct Lecturer, BRAC University

- Draw the Voltage Transfer Characteristics (v_o vs. v_i) of the following circuit.




v_i	v_o
$v_i > -3$	$-v_{sat} = -15V$
$v_i < -3$	$+v_{sat} = +15V$

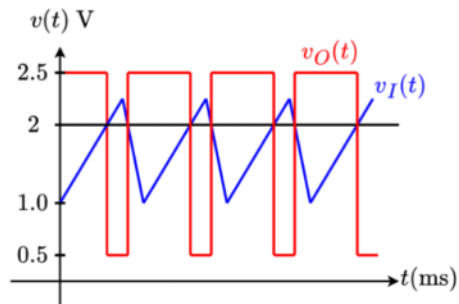- Draw the Voltage Transfer Characteristics (v_o vs. v_i) of the following circuit.
- Also design a circuit that would give rise to the VTC you plotted in I.



(i)

	v_{out}
$v_i > 2V$	$+0.5V$ ($-v_{sat}$)
$v_i < 2V$	$+2.5V$ ($+v_{sat}$)

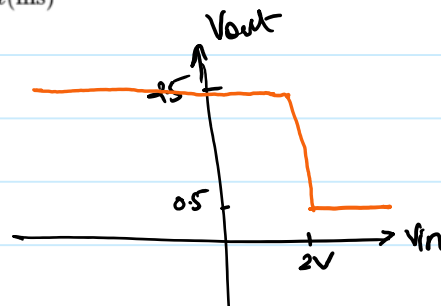

(ii)

$v_i > 2V \rightarrow 0.5V = -v_{sat}$
 -ve pin
 $v_i < 2V \rightarrow +2.5V = +v_{sat}$
 +ve pin

