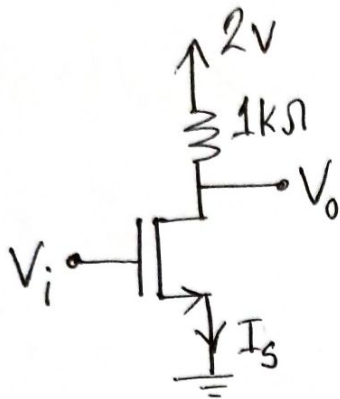


Lets start simple — one resistor connected to the 'Drain' terminal

Example 1



Find V_o & I_s when —

(i) $V_i = 0.1V$


(ii) $V_i = 0.3V$

(iii) $V_i = 1V$

$$V_T = 0.2V$$
$$K = 4mA/V^2$$

(i) for $V_i = 0.1V \rightarrow V_{GS} = 0.1V < V_T (0.2V)$

\therefore MOSFET in cut off —

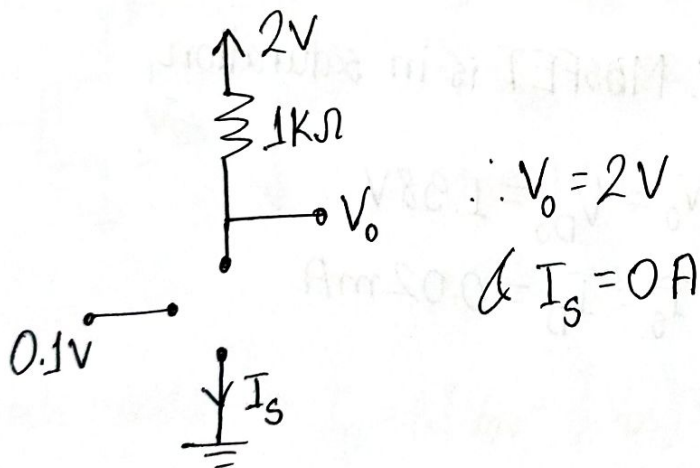

$\therefore V_o = 2V$

& $I_s = 0A$

② for $v_i = 0.3V \rightarrow V_{GS} = 0.3V \geq V_T (0.2V)$


\therefore MOSFET in either saturation or triode.

Assuming saturation \rightarrow we have to show $V_{DS} \geq V_{ov}$ given $I_D = \frac{1}{2} k V_{ov}^2$

Here, $V_{ov} = V_{GS} - V_T = 0.1V$

$\therefore I_D = 0.02mA$

in the ckt —

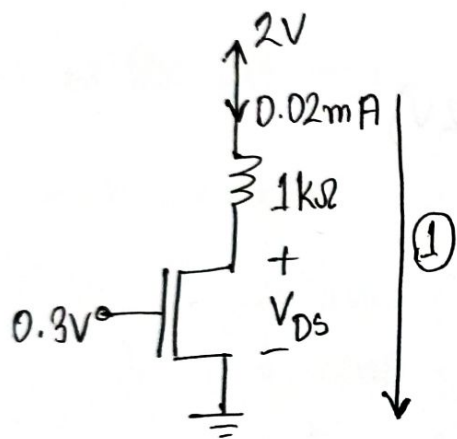

KVL in line 1 —

$$0.02 + V_{DS} = 2$$

$$\Rightarrow V_{DS} = 1.98V \geq V_{ov} (0.1V)$$

\therefore MOSFET is in saturation

$$\therefore V_o = V_{DS} = 1.98V$$

$$\angle I_s = I_D = 0.02mA$$

iii) for $v_i = 1V \rightarrow V_{GS} = 1V \geq V_T (0.2V)$

\therefore MOSFET in either saturation or triode.


Assuming saturation —

$$I_D = \frac{1}{2} V_{ov}^2 \cdot K$$

$$V_{ov} = V_{GS} - V_T = 0.8V$$

$$\therefore I_D = \frac{1}{2} \times 4 \times 0.8^2 = 1.28mA$$

in the ckt —

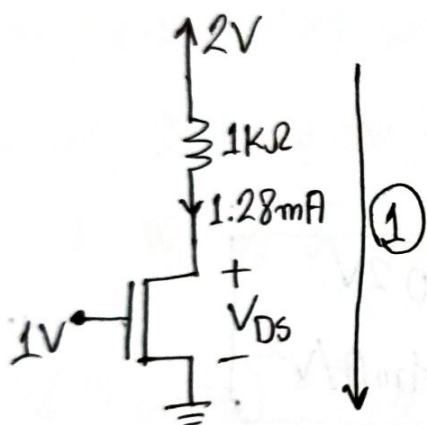

KVL in line 1 —

$$1.28 + V_{DS} = 2$$

$$\Rightarrow V_{DS} = 0.72V < V_{ov} (0.8V)$$

\therefore MOSFET cannot be in saturation, it has to be in triode mode.

In triode mode $\rightarrow I_D = K(V_{ov} - \frac{1}{2}V_{DS})V_{DS}$

in the ckt — $I_D = \frac{2 - V_{DS}}{1} \left[\text{using Ohm's law across the } 1k\Omega \right]$

$$\therefore 2 - V_{DS} = K(V_{ov} - \frac{1}{2}V_{DS}) \cdot V_{DS} \text{ for this ckt}$$

$$\Rightarrow 2 - V_{DS} = 4(0.8 - \frac{1}{2}V_{DS})V_{DS}$$

$$\Rightarrow 2 - V_{DS} = (3.2 - 2V_{DS})V_{DS}$$

(3)

$$\Rightarrow 2V_{DS}^2 - 4.2V_{DS} + 2 = 0$$

$$\therefore V_{DS} = 0.73V \text{ or } 1.37V$$

Now the rule is to take the value that better fits your hypothesis.


Here if you take $1.37V \geq V_{OV}$, your triode assumption fails.

So instead take $V_{DS} = 0.73V$

$$\therefore V_O = 0.73V \text{ \& } I_S = I_D = 2 - V_{DS} = 1.27mA$$

Now lets try out one resistor connected to the 'Source' terminal.

Example 2

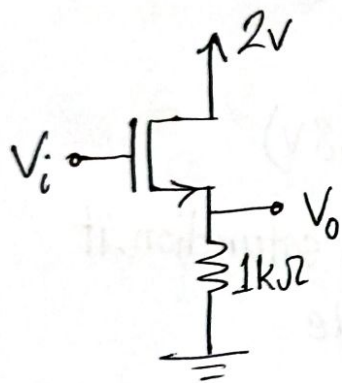

Find V_O for

(i) $V_i = 0.3V$

(ii) $V_i = 1V$

(iii) $V_i = 3V$

$V_T = 0.2V$ $K = 4mA/V^2$

(i) for $V_i = 0.3V$, lets assume cut-off $\rightarrow I_D = 0$

then $V_S = 0V$

$$\therefore V_{GS} = 0.3V \geq V_T (0.2V)$$


So, MOSFET will not be in cut off.

Assuming saturation now —

$$I_D = \frac{1}{2} k V_{ov}^2$$

from the ckt —
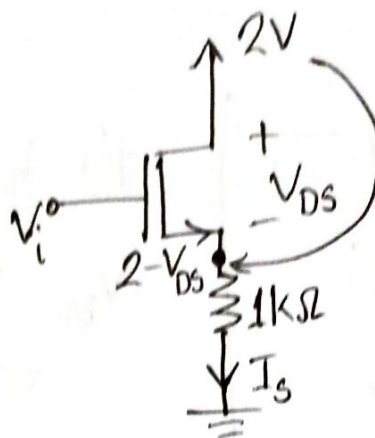
$$I_D = I_S = \frac{2 - V_{DS} - 0}{1} \\ = 2 - V_{DS}$$



$$\therefore I_D = \frac{1}{2} k V_{ov}^2$$

$$\Rightarrow 2 - V_{DS} = \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2$$

Now problem is that we do not have the values of V_{DS} or V_{GS} , but we do know the values of V_D & V_G . So, we have to split V_{DS} to $V_D - V_S$ & V_{GS} to $V_G - V_S$.

$$\Rightarrow 2 - (V_D - V_S) = \frac{1}{2} \times 4 \times (V_G - V_S - V_T)^2$$

$$\Rightarrow 2 - (2 - V_S) = 2 (0.3 - 0.2 - V_S)^2$$

$$\Rightarrow V_S = 2 (0.1 - V_S)^2$$

$$\Rightarrow V_S = 2V_S^2 - 0.4V_S + 0.02 \Rightarrow 2V_S^2 - 1.4V_S + 0.02 = 0$$

$$\therefore V_S = 0.0146 \text{ V or } 0.685 \text{ V}$$

Now, we cannot directly say which one we should pick. So let's do a bit more work —

for $V_s = 0.0146 \text{ V}$ —

$$V_{Ds} = 2 - 0.0146 \\ = 1.9854 \text{ V}$$

$$\& V_{Gs} = 0.3 - 0.0146 \\ = 0.2854 \text{ V}$$

$$\therefore V_{ov} = 0.0854 \text{ V} \leq V_{Ds}$$

So, $V_s = 0.0146 \text{ V}$ is the correct value

for $V_s = 0.685 \text{ V}$ —

$$V_{Ds} = 2 - 0.685 \\ = 1.315$$

$$\& V_{Gs} = 0.3 - 0.685 \\ = -0.385 \text{ V}$$

We can discard $V_s = 0.685 \text{ V}$ directly from V_{Gs} being -ve.

\therefore MOSFET is in saturation mode & $V_o = V_s = 0.0146 \text{ V}$

(6)

(ii) for $V_i = 1V$, let's assume MOSFET is in saturation —

$$I_D = \frac{1}{2} K V_{ov}^2$$

$$\Rightarrow 2 - V_{DS} = \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2 \quad [\text{Just like before}]$$

$$\Rightarrow 2 - 2 + V_S = 2(0.8 - V_S)^2$$

$$\Rightarrow V_S = 2V_S^2 - 3.2V_S + 1.28$$

$$\Rightarrow 2V_S^2 - 4.2V_S + 1.28 = 0$$

$$\therefore V_S = 0.37V \text{ or } 1.73V$$

for $V_S = 0.37V$

$$V_{DS} = 2 - 0.37 \\ = 1.63V$$

$$\& V_{GS} = 1 - 0.37 \\ = 0.63V$$

$$V_{DS} \gg V_{GS} - 0.2$$

\therefore correct value &
correct assumption

$$\therefore V_0 = V_S = 0.37V$$

for $V_S = 1.73V$

$$V_{DS} = 2 - 1.73 \\ = 0.27V$$

$$\& V_{GS} = 1 - 1.73 \\ = -0.73$$

\therefore wrong value

iii) for $V_i = 3V \rightarrow$ lets assume saturation

$$I_D = \frac{1}{2} K V_{ov}^2$$

$$\Rightarrow 2 - V_{DS} = 2(V_{GS} - V_T)^2$$

$$\Rightarrow V_S = 2(2.8 - V_S)^2$$

$$\Rightarrow V_S = 2(V_S^2 - 5.6V_S + 7.84)$$

$$\Rightarrow V_S^2 - 6.1V_S + 7.84 = 0$$

$$\Rightarrow V_S = 1.84V \text{ or } 4.26V$$

V_S cannot be $4.26V$ because the supply is $2V$.

$$\therefore V_S = 1.84V$$

$$\therefore V_{DS} = 0.16V$$

$$\& V_{GS} = 1.16V$$

$$\therefore V_{DS} < V_{GS} - V_T$$

\therefore assumption for saturation is wrong

\therefore the MOSFET is in triode mode —

$$I_D = K(V_{GS} - \frac{1}{2}V_{DS}) \cdot V_{DS}$$

$$\Rightarrow -V_{DS} + 2 = 4(V_{GS} - V_T - \frac{1}{2}V_{DS}) \cdot V_{DS}$$

$$\Rightarrow V_S = 4(2.8 - V_S - \frac{1}{2}(2 - V_S)) \cdot (2 - V_S)$$

$$\Rightarrow V_S = 4(1.8 - 0.5V_S) \cdot (2 - V_S)$$

$$\Rightarrow V_S = (7.2 - 2V_S)(2 - V_S)$$

$$\Rightarrow V_S = 14.4 - 4V_S - 7.2V_S + 2V_S^2$$

$$\Rightarrow 2V_S^2 - 12.2V_S + 14.4 = 0$$

$$\Rightarrow V_S = 1.6V \text{ or } V_S = 4.5V$$

V_S cannot be 4.5V because supply is 2V.

$$\therefore V_S = 1.6V$$

$$\therefore V_{DS} = 0.4V$$


$$\& V_{GS} = 1.4V$$

$$\therefore V_{DS} < V_{GS} - V_T$$

\therefore assumption is correct. $\therefore V_0 = V_S = 1.6V$

Lets make our problem harder. We are going to add one resistor to the 'Drain' and also one to the 'Source'.

Example 3

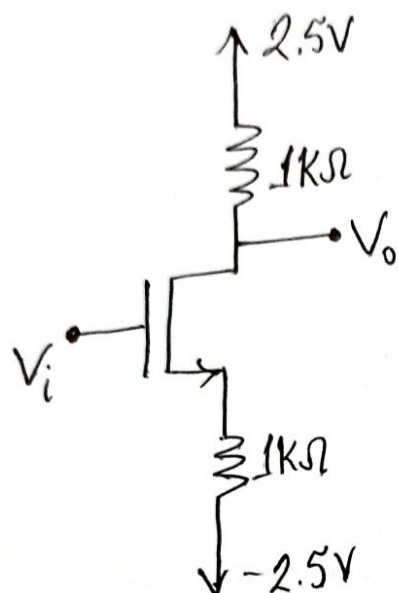

Find v_o for

- (i) $V_i = -2V$
- (ii) $V_i = 0V$
- (iii) $V_i = 2V$

$$V_T = 0.7V$$
$$K = 4mA/V^2$$

(i) for $V_i = -2V$ lets assume cut off.

$$\text{then } I_D = I_S = 0A$$

$$\therefore V_D = 2.5V \text{ \& } V_S = -2.5V$$

$$\therefore V_{GS} = -2 - (-2.5) = 0.5V < V_T (0.7V)$$

\therefore assumption is correct.

(ii) for $v_i = 0V$, let's assume saturation —

$$\begin{aligned} I_D &= \frac{1}{2} K V_{ov}^2 \\ &= \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2 \\ &= 2(V_G - V_S - V_T)^2 \\ &= 2(-0.7 - V_S)^2 \\ &= 2V_S^2 + 2.8V_S + 0.98 \end{aligned}$$

Now we need I_D in terms of V_S to solve the problem —

$$I_D = I_S = \frac{V_S - (-2.5)}{1} = V_S + 2.5$$

$$\therefore V_S + 2.5 = 2V_S^2 + 2.8V_S + 0.98$$

$$\Rightarrow 2V_S^2 + 1.8V_S - 1.52 = 0$$

$$\therefore V_S = -1.43V \text{ or } 0.53V$$

$$\text{for } V_S = 0.53 \rightarrow V_{GS} = -0.53V \text{ [not possible]}$$

$$\therefore V_S = -1.43V$$

$$\therefore V_{GS} = 1.43V$$

$$\text{Now, } I_D = \frac{2.5 - V_D}{1} = I_S = V_S + 2.5$$

$$\therefore V_D = -V_S = 1.43V \quad \therefore V_{DS} = 2.86V \geq V_{GS} - V_T (0.73V)$$

(11)

So, our assumption is correct

$$\therefore V_0 = V_D = 1.43V$$

(iii) for $V_i = 2V$, let's assume saturation —

$$I_D = \frac{1}{2} k V_{ov}^2$$

$$\Rightarrow V_S + 2.5 = 2(2 - 0.7 - V_S)^2 \text{ [same as before]}$$

$$\Rightarrow V_S^2 - 3.1V_S + 0.44 = 0$$

$$\therefore V_S = 0.15V \text{ or } 2.95V$$

$V_S = 2.95V$ isn't possible because the max node voltage in the main line is $2.5V$.

$$\therefore V_S = 0.15V \rightarrow V_{GS} = 1.85V$$

$$\therefore \text{Ohm's law} \rightarrow I_D = \frac{2.5 - V_D}{1} = I_S = V_S + 2.5$$

$$\Rightarrow V_D = -V_S \Rightarrow V_D = -0.15V$$

$$\therefore V_{DS} = -0.3V < V_{GS} - V_T$$

\therefore saturation assumption is wrong; MOSFET has to be in triode mode.

$$I_D = k(V_{ov} - \frac{1}{2}V_{DS})V_{DS}$$

$$= 4(V_{GS} - V_S - V_T - \frac{1}{2}V_D + \frac{1}{2}V_S)(V_D - V_S)$$

$$= 4(1.3 - \frac{1}{2}V_D - \frac{1}{2}V_S)(V_D - V_S)$$

$$\text{Now, we know, } I_D = 2.5 - V_D = I_S = V_S + 2.5$$

$$\therefore V_D = -V_S$$

$$\therefore 2.5 - V_D = 4 \left(1.3 - \frac{1}{2} V_D + \frac{1}{2} V_D \right) \cdot (V_D + V_D)$$

$$\Rightarrow 2.5 - V_D = 5.2 \times 2 V_D$$

$$\Rightarrow 2.5 = 11.4 V_D$$

$$\Rightarrow V_D = 0.22V$$

$$\therefore V_{DS} = 0.44V$$

$$\& V_{GS} = 2.22V$$


$$\therefore V_{DS} < V_{GS} - V_T (1.52V)$$

\therefore assumption is correct

$$\therefore V_o = V_D = 0.22V$$


Special cases —

(i)

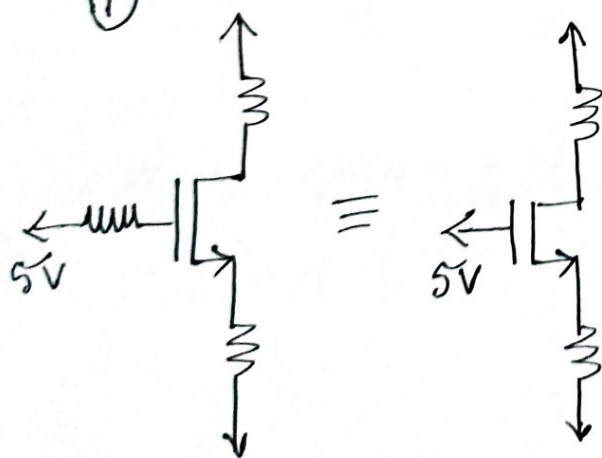


Resistance connected in series to gate terminal doesn't change anything since $I_G = 0$ all the time.

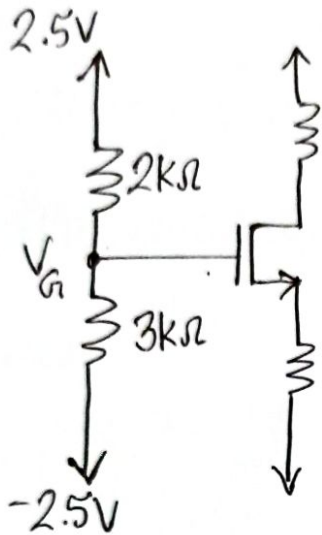However, this property of $I_G = 0$ allows us to put complex ckts on the gate terminal from which we have to solve for V_G . The most common case —




Find V_G .

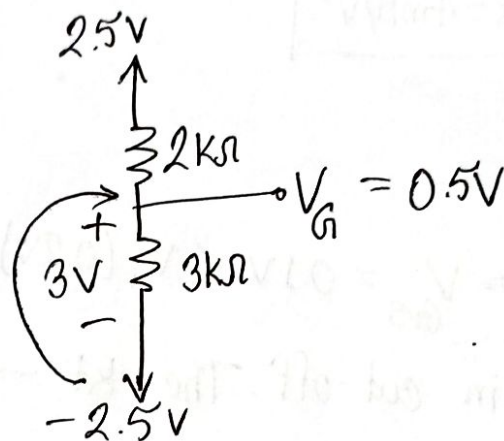→ Just a simple voltage divider suffices —




Same ckt with one small complication —

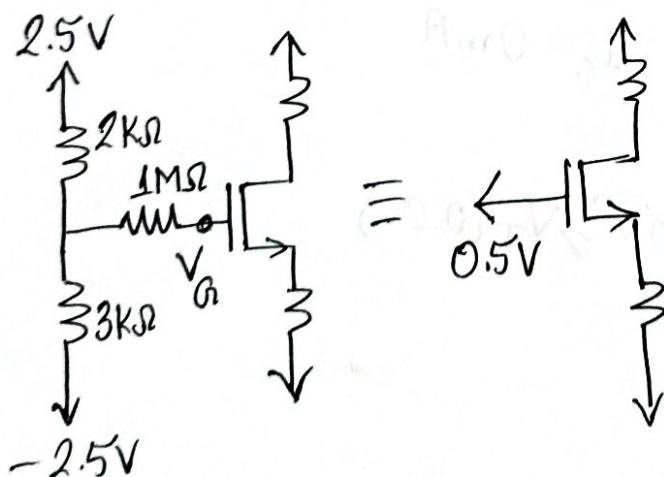

Just like before, the $1M\Omega$ doesn't matter as $I_G = 0A$

(ii)

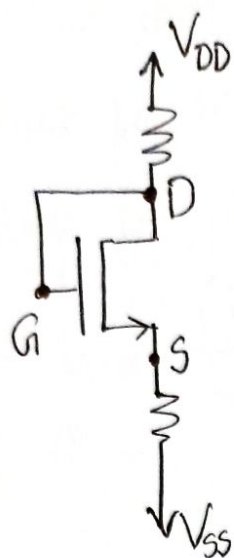

This type of residual connection from drain to gate forces the MOSFET to be in saturation mode, when $V_{DD} \geq V_T$.

In this config, $V_D = V_G$


$$\therefore V_{DS} = V_{GS}$$

Since, V_T is always positive,

$$V_{DS} \geq V_{GS} - V_T \text{ [criteria for saturation]}$$

This proof was set in last final [Fall 24]

(iii)

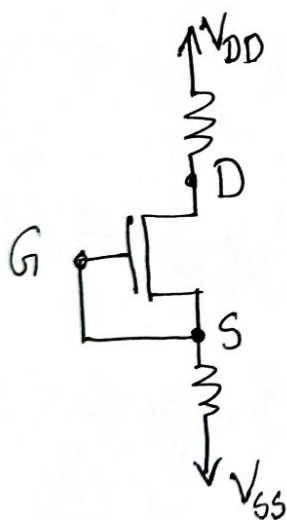


This config will always result in cut-off if $V_T > 0$.

$$\text{Here, } V_G = V_S$$

$$\therefore V_{GS} = 0V$$

So, unless $V_T = 0V$, the MOSFET will remain in cut-off.

Example 4

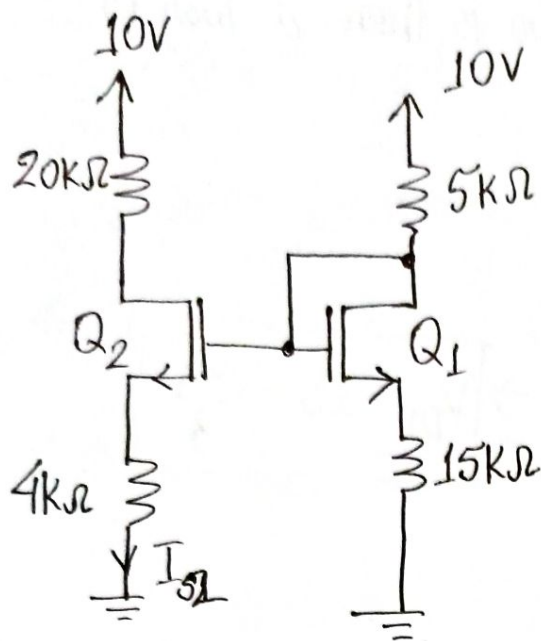

Find I_{S2} .

Assume $V_T = 1V$ & $K = 4mA/V^2$
for both MOSFETs.

Q_1 is in saturation because of the configuration. So it will be easier to work with Q_1 first.

$$I_{D1} = \frac{1}{2} K V_{ov1}^2$$

$$\Rightarrow I_{D1} = 2 (V_G - V_{S1} - V_T)^2$$
$$= 2 (V_G - V_{S1} - 1)^2$$

$$I_{D1} = I_{S1} = \frac{10 - V_{D1}}{5} = \frac{V_{S1}}{15}$$

$$\therefore \frac{V_{S1}}{15} = 2 (V_G - V_{S1} - 1)^2$$

$$\Rightarrow V_{S1} = 30 (V_G - V_{S1} - 1)^2 \text{ --- (i)}$$

Now, we have to understand that we cannot solve the equation

① because we have two unknowns — V_G & V_{S1} . So, is there a way to replace V_G with V_{S1} ?

Because of the residual connection, $V_G = V_{D1}$

and we know $\frac{10 - V_{D1}}{5} = \frac{V_{S1}}{15}$ [From $I_{D1} = I_{S1}$]

$$\Rightarrow V_{D1} = 10 - \frac{V_{S1}}{3}$$

$$\therefore \textcircled{1} \Rightarrow V_{S1} = 30 \left(10 - \frac{V_{S1}}{3} - V_{S1} - 1 \right)^2$$

$$\Rightarrow V_{S1} = 30 \left(9 - \frac{4}{3} V_{S1} \right)^2$$

solving $\rightarrow V_{S1} = 6.4V$ or $7.11V$

for $V_{S1} = 6.4V$

$$V_{DS1} = 1.467V = V_{GS1}$$

for $V_{S1} = 7.11V$


$$V_{DS1} = 0.52V = V_{GS1} < V_T$$

So this value is wrong

Now, $V_{D1} = 7.867V = V_G$

Now we move to Q2.

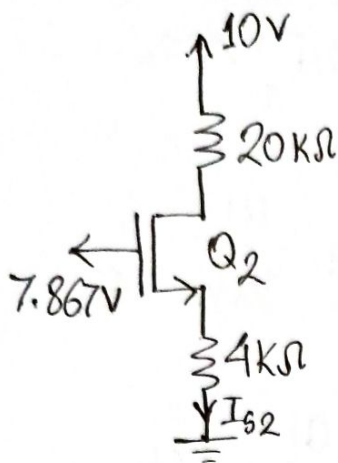After solving for Q_1 , our problem is simplified to —



Assuming Q_2 is in saturation —

$$I_{D2} = \frac{1}{2} K V_{ov2}^2$$

$$\Rightarrow \frac{V_{s2}}{4} = 2 (7.867 - 1 - V_{s2})^2$$

$$\Rightarrow \frac{V_{s2}}{8} = V_{s2}^2 + 61.889 - 15.734 V_{s2}$$

$$\Rightarrow V_{s2}^2 - 15.859 V_{s2} + 61.889 = 0$$

$$\therefore V_{s2} = 6.935 \text{ V or } 8.92 \text{ V}$$

$$V_{D2} \neq 8.92 \text{ V [goes to cutoff, } V_{GS} < 0]$$

$$\therefore V_{s2} = 6.935 \text{ V}$$

$$\text{We know, } \frac{10 - V_{D2}}{20} = \frac{V_{s2}}{4}$$

$$\Rightarrow V_{D2} = 10 - 5V_{s2} = -24.675 \text{ V [not possible, lowest voltage is 0V]}$$

You can still go ahead and check if $V_{Ds2} < V_{ov}$

Either ways, the MOSFET is in Triode mode

In triode mode —

$$I_{D2} = K(V_{ov2} - \frac{1}{2}V_{DS2}) \cdot V_{DS2}$$

$$\Rightarrow \frac{V_{S2}}{4} = 4 \left(6.867 - V_{S2} - \frac{1}{2}V_D + \frac{1}{2}V_{S2} \right) \cdot (V_{D2} - V_{S2})$$

$$\text{Now, } V_{D2} = 10 - 5V_{S2}$$

$$\therefore \frac{V_{S2}}{16} = \left(6.867 - \frac{1}{2}V_{S2} - 5 + 2.5V_{S2} \right) (10 - 6V_{S2})$$

$$\Rightarrow \frac{V_{S2}}{16} = (1.867 + 2V_{S2})(10 - 6V_{S2})$$

$$\Rightarrow \frac{V_{S2}}{16} = 18.67 + 20V_{S2} - 11.202V_{S2} - 12V_{S2}^2 \quad \therefore$$

$$\Rightarrow 12V_{S2}^2 - 8.7355V_{S2} - 18.67 = 0$$

$$\therefore V_{S2} = -0.935V \text{ or } 1.66V$$

$$V_{S2} \neq -0.935V \text{ [lowest voltage is } 0V]$$

$$\therefore V_{S2} = 1.66V$$

$$\therefore V_{D2} = 1.7V$$

$$\therefore V_{DS2} = 0.04V$$

$$\text{and } V_{GS2} = 6.207 \text{ V}$$

$$\therefore V_{DS2} < V_{GS2} - V_T$$

So assumption is correct.

$$\therefore I_{S2} = \frac{1.66}{4} = 0.415 \text{ mA}$$