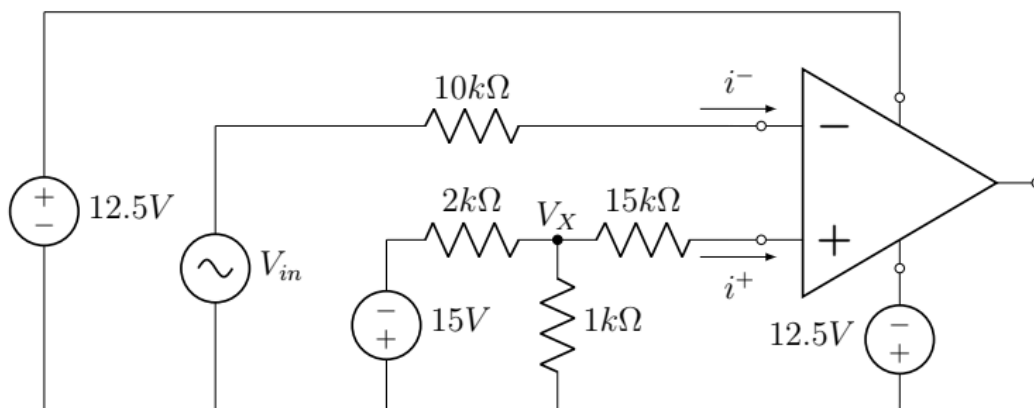


The goal of this assignment is to test your concept and knowledge of:

- Alternative representation of circuits (Line diagrams),
- Application of KCL and KVL in aforementioned representation.
- Op Amp circuit solving



1. For the op-amp circuit shown below:

- Draw the alternative representation. (ground node first...)
- Given that $i^+ = 0$ A, write down the KCL equation at node V_x . Hence, find V_x .
- What did you notice about the equation you wrote in part (b)? What rule is this?



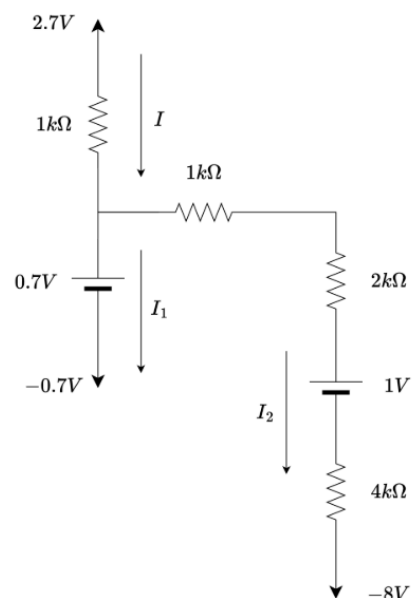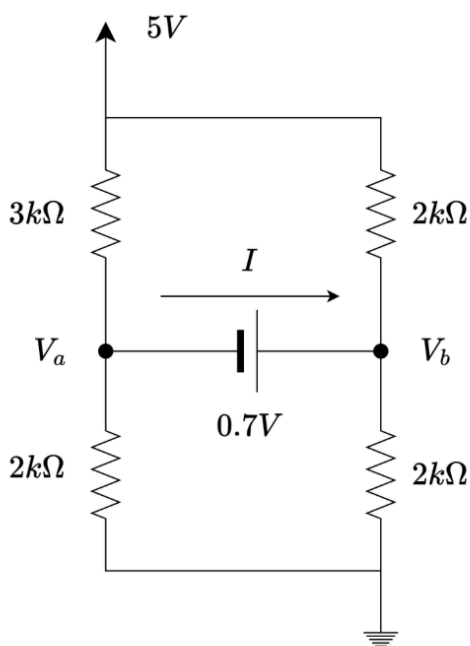2. Two circuits, in alternative representation, are shown below.

- For the circuit on the left, find the values of V_a and V_b . Hence, write down the value of I (Any method is fine, either KCL or KVL. Avoid nodal and mesh.).
- For the circuit on the right, find all unknown node voltages (mark all the nodes in the circuit first). Also, find the currents I , I_1 , and I_2 .



3. Design a device to implement the following function, f where x , y , and z are the inputs of the device. Assume any value if necessary.

$$f = \frac{d^2x}{dt^2} + 10y + \int (10z - 9)dt$$

4. Analyze the circuit in Figure-5, and determine the expression of the function, f where x , y and z are the input of the circuit.

