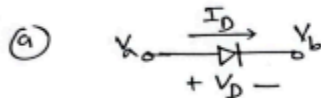


Solutions


Q2

Set-02



to verify ON states $I_D > 0$


to verify off states $V_{ab} < V_{D0}$

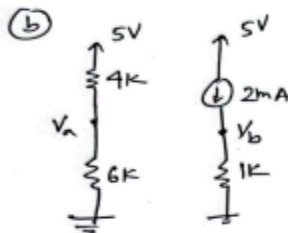

$$V_a = 5 \times \frac{6}{6+4} = 3V$$

$$V_b = 1 \times 2 = 2V$$

(c) Assume D_1 ON, D_2 off

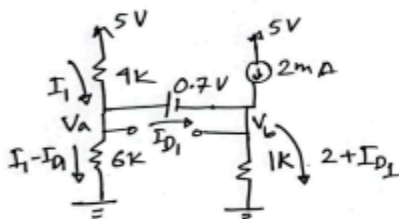

$$5 = 4I_1 + 0.7 + (2 + I_{D1}) \times 1$$

$$5 = 4I_1 + 6(I_1 - I_{D1})$$

$$\therefore I_1 = 0.553 \text{ mA}$$

$$I_{D1} = 0.088 \text{ mA}$$

$$\therefore I_{D1} = 0.088 \text{ mA} \quad I_{D2} = 0 \text{ mA}$$

Verify

I_{D1} is positive $\therefore D_1$ ON

$$V_a = 6(I_1 - I_{D1}) = 2.79V$$

$$V_b = 1(2 + I_{D1}) = 2.088$$

$V_{ba} = -0.7 < 0.7 \therefore D_2$ off

So our assumption OK

- (d) if two diodes are in a opposite direction in a series ckt the overall network is off
so current in line $I_{ab} = 0$.


~~Set 01~~ Set 01 .

(a) Same as set 02

(b) $V_a = 5 \times \frac{3}{2+3}$
 $= 5V$

$V_b = 1 \times 2 = 2V$

$V_a = 3V$ (here it's a mistake)

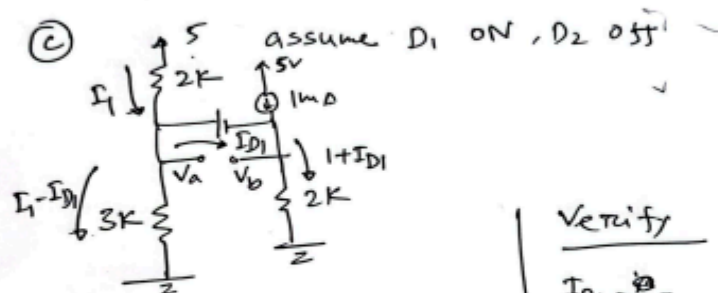

$5 = 2I_1 + 0.7 + (1 + I_{D1}) \times 2$

$5 = 2I_1 + 3(I_1 - I_{D1})$

$\therefore I_1 = 1.056$

$I_{D1} = 0.093$

Verify

$I_{D1} > 0 \therefore D_1 \text{ ON}$

$V_{ba} = -0.7V < 0.7V$

$\therefore D_2 \text{ OFF}$

\therefore (d) same as set 02.

Set- A/ Set-1

(a) $\text{Gain} = -\frac{R_F}{R_1}$

(b) Nodal Analysis at V_a node: $\frac{V_a-5}{2} + \frac{V_a}{10} + 1 = 0 \Rightarrow V_a = 2.5 \text{ V}$. Also, $V_a = V^+ = 2.5 \text{ V}$

(c) When S1 is **closed**, the op-amp is in **closed** loop.

$$V^+ = V^- = 2.5 \text{ V}.$$

Nodal Analysis at V^- node: $\frac{V^- - 3.3}{4} + \frac{V^- - V_0}{0.33} = 0$

$$\Rightarrow V_0 = 2.434 \text{ V}$$

(d) When S1 is **open**, the op-amp is in **open** loop.

$$V^+ = 2.5 \text{ V (from 'b')}$$

$$V^- = 3.3 \text{ V (from the left side of } 4k\Omega)$$

$$\text{Since, } V^+ < V^-$$

$$\Rightarrow V_0 = -8 \text{ V}$$

(e) A **differentiator** ($RC=0.2$) series with an **inverting amplifier** ($R_1=R_F$). Or, any other appropriate choices for R and C which finally gives +0.2 factor.

Set- B/ Set-2

(a) $\text{Gain} = 1 + \frac{R_F}{R_1}$

(b) Nodal Analysis at V_a node: $\frac{V_a-5}{2} + \frac{V_a}{10} = 1 \Rightarrow V_a = 5.83 \text{ V}$. Also, $V_a = V^+ = 5.83 \text{ V}$

(c) When S1 is **closed**, the op-amp is in **closed** loop.

$$V^+ = V^- = 5.83 \text{ V}.$$

Nodal Analysis at V^- node: $\frac{V^- - 3.3}{4} + \frac{V^- - V_0}{0.48} = 0$

$$\Rightarrow V_0 = 6.134 \text{ V}$$

(d) When S1 is **open**, the op-amp is in **open** loop.

$$V^+ = 5.83 \text{ V (from 'b')}$$

$$V^- = 3.3 \text{ V (from the left side of } 4k\Omega)$$

$$\text{Since, } V^+ > V^-$$

$$\Rightarrow V_0 = +10 \text{ V}$$

(e) A **differentiator** ($RC=0.8$) series with an **inverting amplifier** ($R_1=R_F$). Or, any other appropriate choices for R and C which finally gives +0.8 factor.

Q4

Set 01

- a. Open Circuit
- b. $V_x = 4.56 \text{ V}$, $I_{D1} = 0 \text{ mA}$, $I_{D2} = 1.36 \text{ mA}$
- c. $V_O = 7 \text{ V}$. ($9.12 \text{ V} > 7 \text{ V}$)

Set 02

- d. Short Circuit
- e. $V_x = 4.48 \text{ V}$, $I_{D1} = 1.38 \text{ mA}$, $I_{D2} = 0 \text{ mA}$
- f. $V_O = 7 \text{ V}$. ($8.96 \text{ V} > 7 \text{ V}$)

Q5

Set 01

- a. CVD+R diode I-V graph
- b. $V_{o1} = 1.7 \text{ V}$, $V_{o2} = 1.9 \text{ V}$
- c. $V_o = 2.7 \text{ V}$
- d. D3, D4 -> Reverse Bias. $V_{o2} = (10 * (5-1) / (10+30)) = 1 \text{ V}$. $V_O = 2 \text{ V}$

Set 02

- a. Diode I-V graph
- b. $V_{o1} = 1.7 \text{ V}$, $V_{o2} = 1.9 \text{ V}$
- c. $V_o = 2.7 \text{ V}$
- d. D3, D4 -> Reverse Bias. $V_{o2} = (10 * (5-1) / (10+30)) = 1 \text{ V}$. $V_O = 2 \text{ V}$