

Set
A

Extra → 2 copies
 Present → 22
 Absent → 3

Assessment: Quiz 1
 Duration: 25 minutes
 Date: July 9, 2025
 Full Marks: 20

Farhan, Anika, Munasib

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the answer script and the question paper must be returned to the invigilator.
- ✓ All the questions are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

Question 1 of 2

[CO2] [8 marks]

- (a) [2.5 marks] Show the alternative representation (i.e. line representation/diagram) of the circuit in Figure-1.
 (b) [1.5 marks] Analyze the circuit in an alternative representation from part-(a), and calculate V_x .
 (c) [2.5 marks] Analyze the circuit in an alternative representation from part-(a) & the waveform of V_{in} in Figure-2, and draw the waveform of the output voltage on Figure-2. Label the graph properly.
 (d) [1.5 marks] Draw the VTC of this comparator (V_o vs V_{in}).

Rubric:

(a) Ground taken → 1
 V_{set}^+ , V_{set}^- taken → 1
 V_{in} , +15 shown → 0.5

(b) Using VDR → 1
 Correct ans → 0.5

(c) Correct Transition → 1
 u voltage label → 0.5

(d) Zero Crossing shape → 0.5
 Label → 0.5

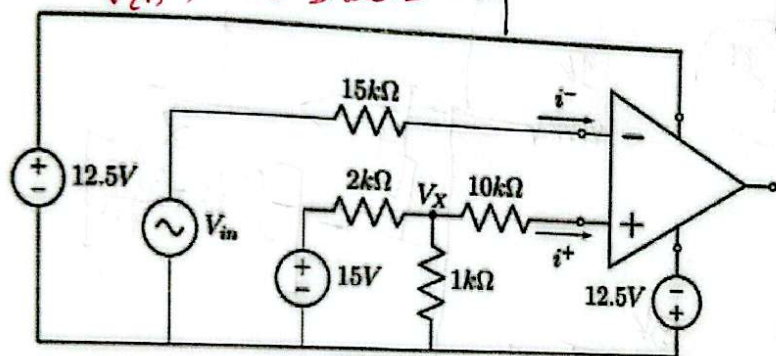


Figure-1


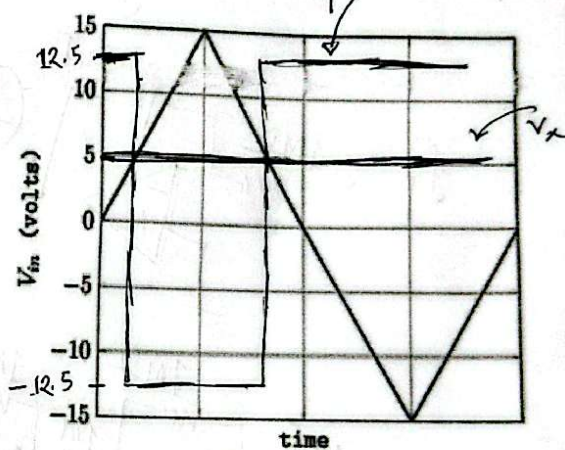


Figure-2

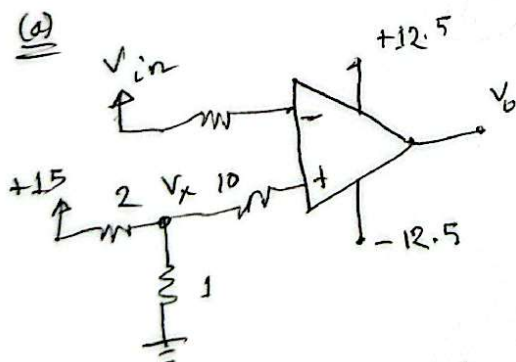

(b) $V_x = \frac{1}{1+2} \times 15$
 $= 5V$

(c) $V_- = V_{in}$
 $V_+ = V_x = 5V$

V_{in} range:
 $-15 \rightarrow +15$


(d) Open loop,
 $V_o = A(V_+ - V_-)$

If $V_o = 0$, $V_+ = V_- = 5V$

If $V_- < V_+ \Rightarrow V_{in} < 5$

$V_o = V_{set}^+ = +12.5$

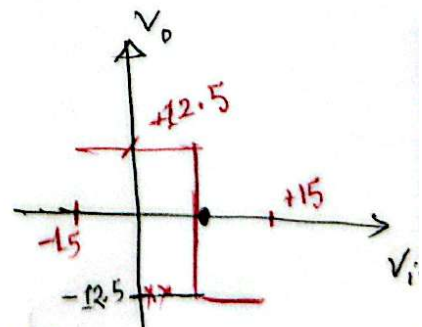If $V_- > V_+ \Rightarrow V_{in} > 5 \rightarrow V_o = V_{set}^- = -12.5$





2(a)

Summer has (-) in formula, so taking one (-) voluntarily

$$f = \left[\int (6x - y) dt - 3 \frac{d^2 z}{dt^2} \right]$$

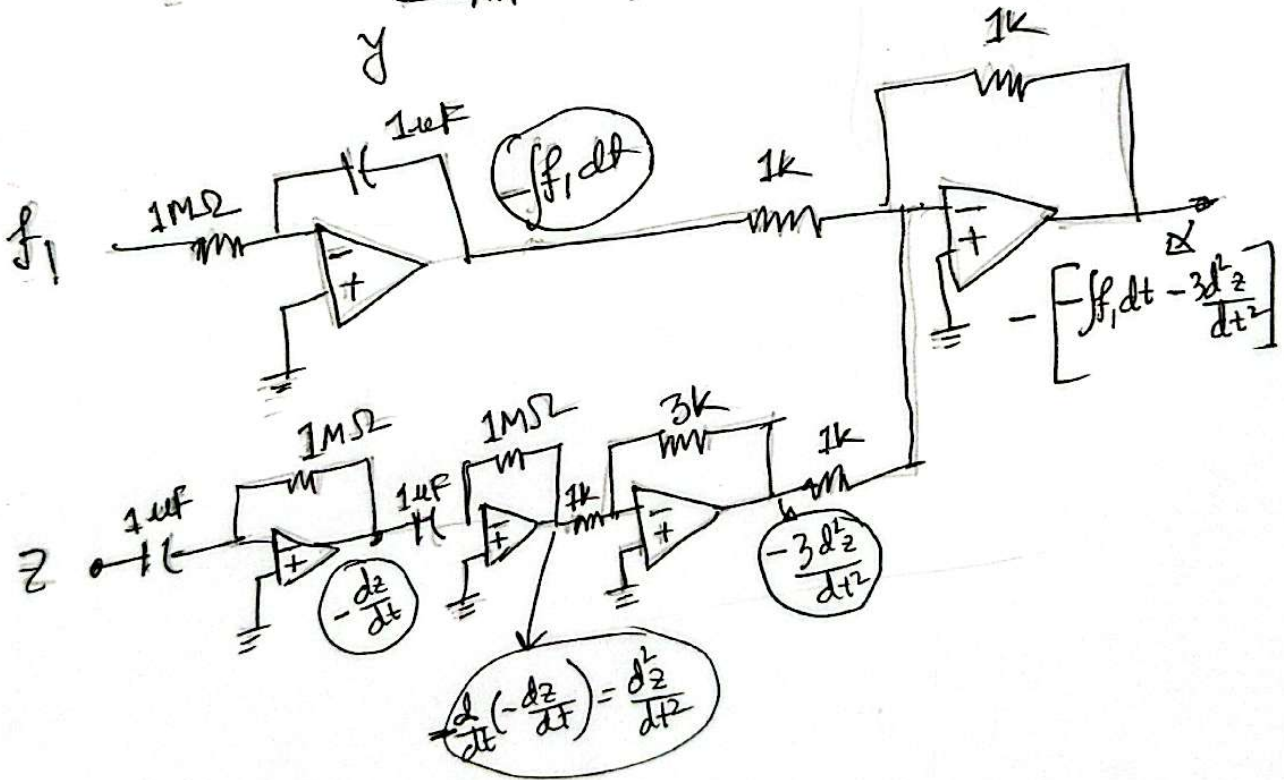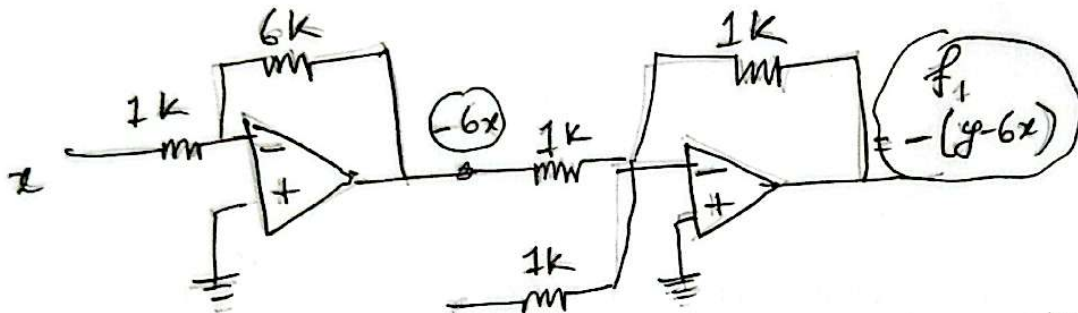Integration formula has (-) $-\int (6x - y) dt$
 $-\int [-(y - 6x)] dt$
 summer formula has (-)




■ Question 2 of 2

(a)

[CO3+CO2] [7+5 marks]

$$f = \int (6x - y) dt + 3 \frac{d^2}{dt^2} z$$

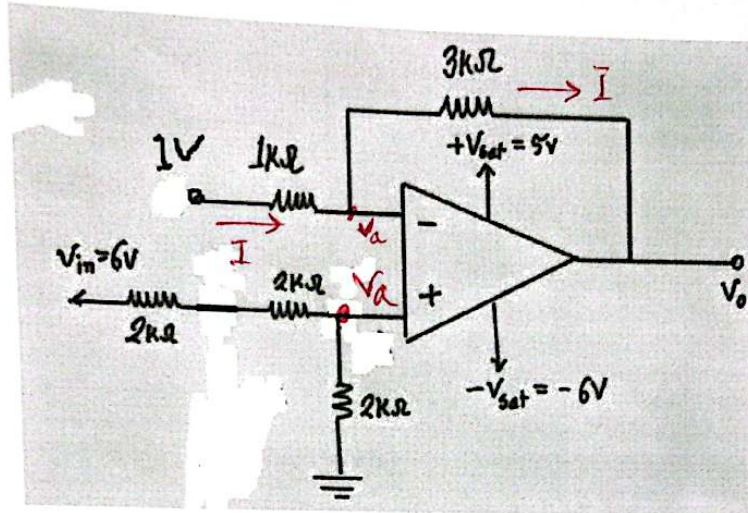2 Differentiators $\rightarrow 2 \times 1$ 1 integrator $\rightarrow 1$ 2 Adder $\rightarrow 2 \times 1$ Integration of the components $\rightarrow 2$ (b) Find the value of V_o .

$$V_a = \frac{2}{2+2+2} \times 6$$

$$= 2V$$

$$V_+ = V_- = 2V \text{ [Virtual Short]}$$

$$I = \frac{1 - V_a}{1} = \frac{V_a - V_o}{3}$$

$$\Rightarrow \frac{1-2}{1} = \frac{2-V_o}{3}$$

$$\Rightarrow -3 = 2 - V_o$$

$$\Rightarrow V_o = 5V$$

Rubric:

VDR for $V_a \rightarrow 1$ Virtual short ($V_+ = V_-$) $\rightarrow 1.5$ Equal current through $1k\Omega$ & $3k\Omega \rightarrow 1.5$ V_o value $\rightarrow 1$