

Diode Rectifiers

* pn junction \rightarrow diode \rightarrow diode ckt model \rightarrow applications

* Applications : ① DL gates (Diode Logic Gates)


② Rectification

process of converting ac signals into one with unidirectional/limited polarity.
 (+ve polarity will remain +ve, or -ve to -ve)
 /convert to

Uses of rectification : ① power supply (electronics require DC)
 ↳ providing \approx suitable DC.

* rms \rightarrow root mean squared



↳ used for AC power calculation.

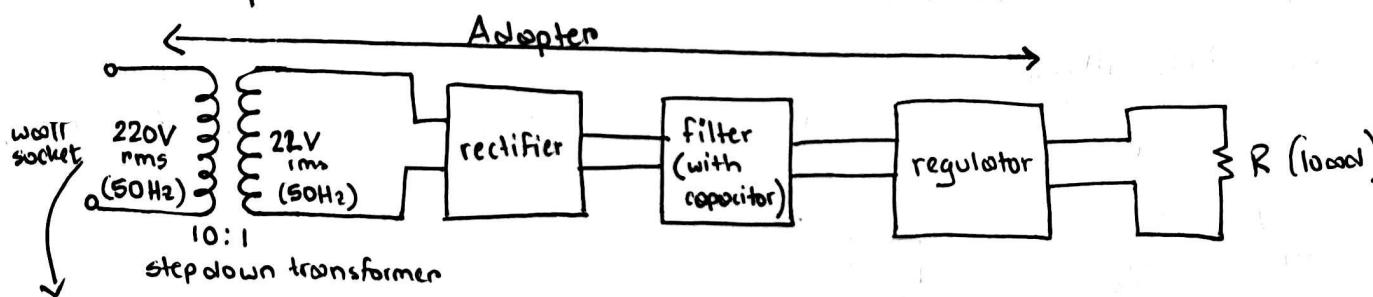

220V_{rms} sinusoidal

$$\Rightarrow 220 = \frac{V_m}{\sqrt{2}}$$

$$V_m = 220\sqrt{2}$$

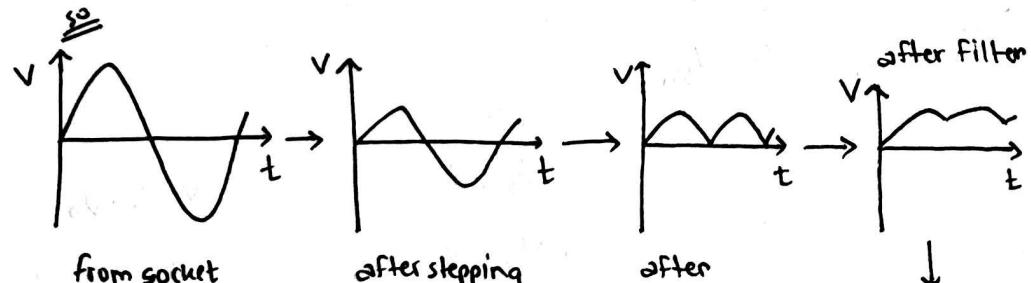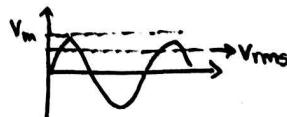


$$\text{DC power: } P = VI$$

$$\text{AC power: } P(t) = V(t)i(t)$$

↳ function of time,
not a useful measurement.

$$V_{\text{rms}} = V_m/\sqrt{2}$$


(Vm is peak voltage of sinusoidal wave)

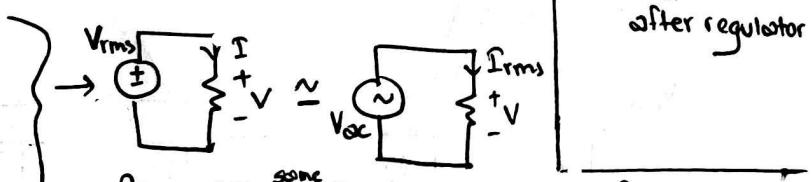


$$P_{\text{out}} = V I \xrightarrow{\text{same}} P_{\text{out}} = V_{\text{rms}} I_{\text{rms}} = P_{\text{avg}}$$

$$(V = V_{\text{dc}})$$

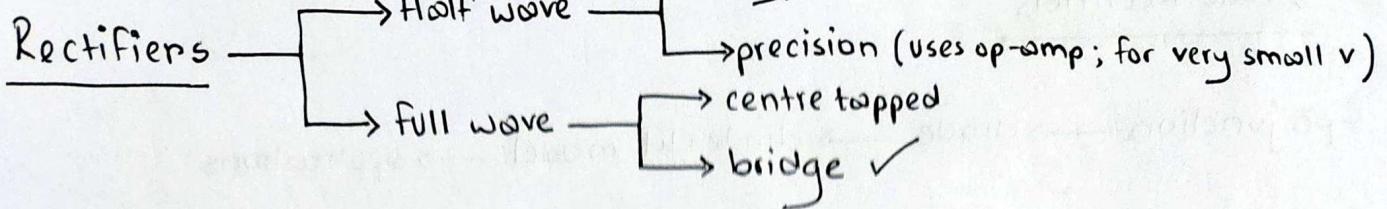* V_{rms} is the effective value of AC signal that would result in some power dissipation for both ckt's.



Half-wave Rectifier

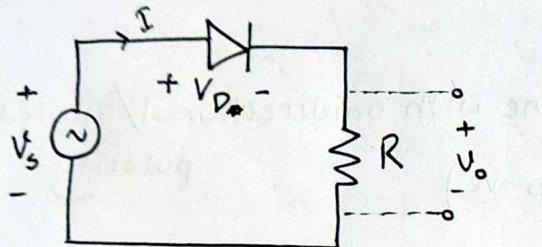

V_s = source voltage

$$= V_m \sin \omega t \text{ (for this analysis)}$$


V_o = output voltage [V_p = peak output]

V_{D_0} = diode cut-in voltage = 0.7 for si

V_D = diode voltage


CVD model

ON	OFF
$I_D > 0$	$I_D = 0$
$V_D > V_{D_0}$	$V_D < V_{D_0}$

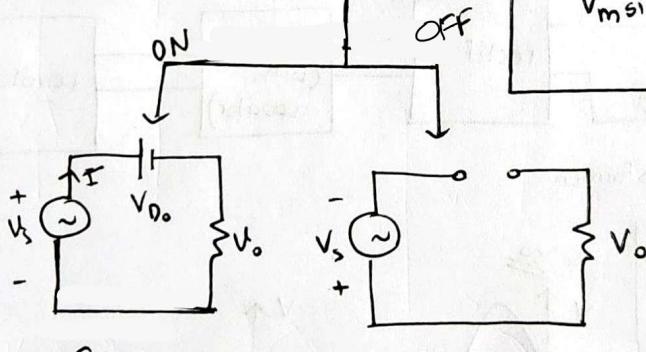

$$* V_o = V_s - V_{D_0}$$

$$* V_o = 0 \text{ (no current)}$$

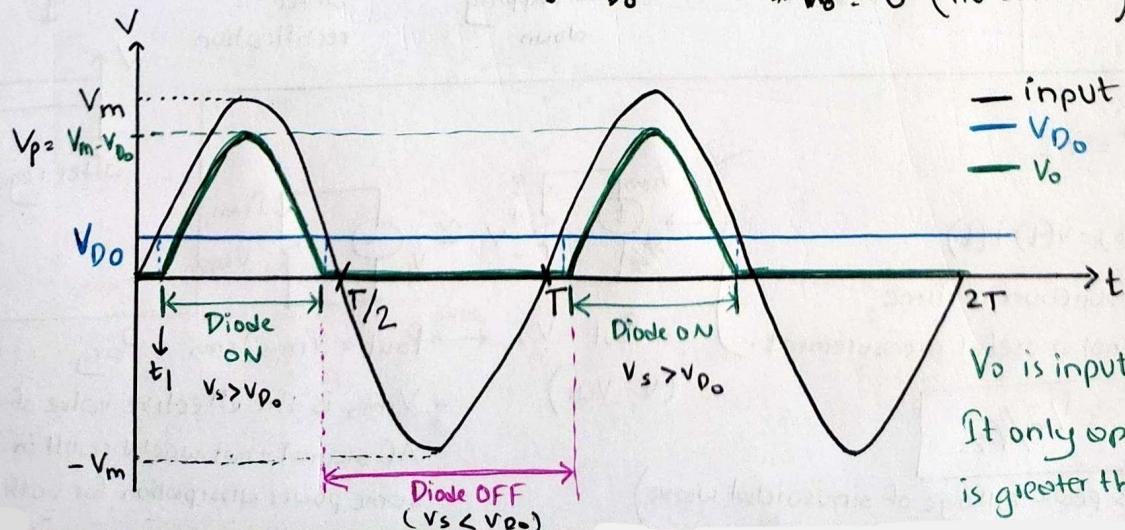

- input
- V_{D_0}
- V_o

V_o is input minus V_{D_0} .

It only appears when input is greater than V_{D_0} .

AC revision:

$$V_s = V_m \sin(\omega t + \varphi)$$


V_m = amplitude

$$\omega = 2\pi f = \frac{2\pi}{T} = \text{angular frequency}$$


f = natural frequency

$$T = \text{time period} = \frac{1}{f}$$

φ = initial phase

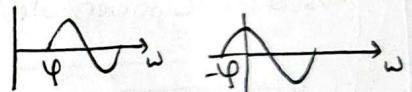
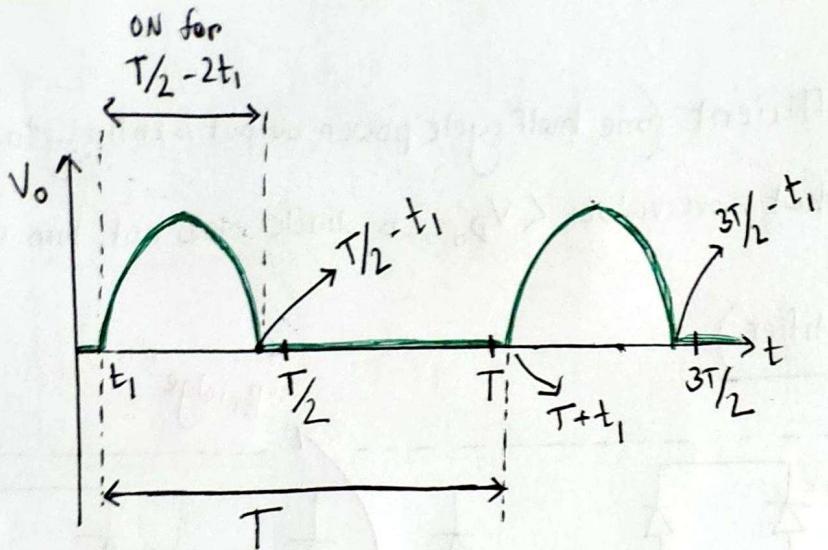
$$V_m \sin(\omega t - \varphi) \quad V_m \sin(\omega t + \varphi)$$



* input T = output T

To find t_1 -

at $t=t_1$

$$V_m \sin \omega t_1 = V_{D_0}$$

$$\therefore t_1 = \frac{1}{\omega} \sin^{-1} \left(\frac{V_{D_0}}{V_m} \right)$$

To find the DC component or average,

$$V_{DC} = \frac{1}{T} \int_0^T V_o(t) dt \quad (\text{integrate over given time period})$$

$$= \frac{1}{T} \int_0^T (V_s(t) - V_{D_0}) dt$$

$$= \frac{1}{T} \int_{t_1}^{T/2-t_1} \{ V_m \sin \omega t - V_{D_0} \} dt \quad (\text{change the limits to fit the function})$$

$$\approx \frac{1}{T} \int_0^{T/2} \{ V_m \sin \omega t - V_{D_0} \} dt \rightarrow * \text{conditions:}$$

$$= - \frac{V_m}{\omega T} [\cos \omega t]_0^{T/2} - \frac{V_{D_0}}{T} [t]_0^{T/2}$$

$$= - \frac{V_m}{\omega T} \times \left(\cos \frac{2\pi}{T} \times \frac{T}{2} - \cos 0 \right) - \frac{V_{D_0}}{T} [T/2 - 0]$$

$$= - \frac{V_m}{\omega T} \times (-1 - 1) - \frac{V_{D_0}}{T}$$


$$= + \frac{V_m}{\omega T} - \frac{V_{D_0}}{T}$$

* V_{rms}

$$= \sqrt{\frac{1}{T} \int_{t_1}^{T/2-t_1} V_o^2(t) dt}$$

root
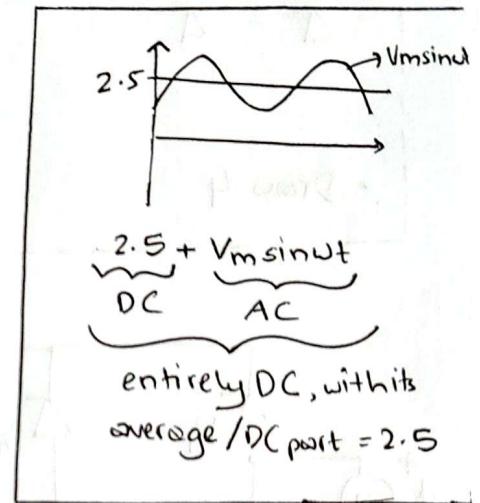
$$= \sqrt{\frac{V_m^2}{4} - \frac{2V_m V_{D_0}}{\pi} - \frac{V_{D_0}^2}{2}}$$



- ① $t_1 \ll T$ ↗ ① is a consequence of ②.
- or ② $V_{D_0} \ll V_m$ ↗ or $V_D \approx V_m$

Even though V_o is on for $(T/2 - 2t_1)$ amount of time,

* if t_1 is small enough, we can ignore for an approximate result.


* if V_{D_0} was large...

Approx. would not work.


- * HW rectifiers are very inefficient (one half cycle power output is entirely lost!)
- * cannot rectify signals that have values $< V_{D_0}$, as diode does not turn ON at all.

Full-wave (bridge rectifier)


HOW TO REMEMBER

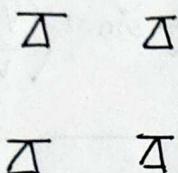


• Draw 4

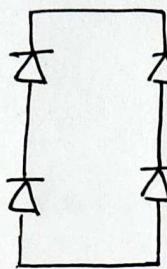

• connect

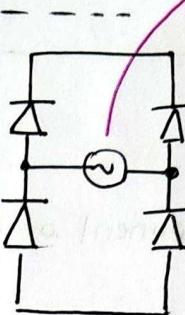





"Bridge"

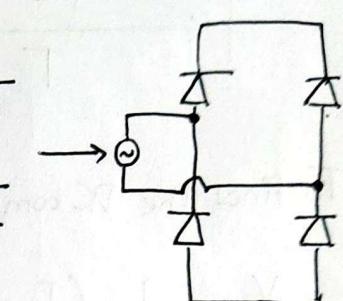

• bridge

• formal orientation


• (this is fine!)

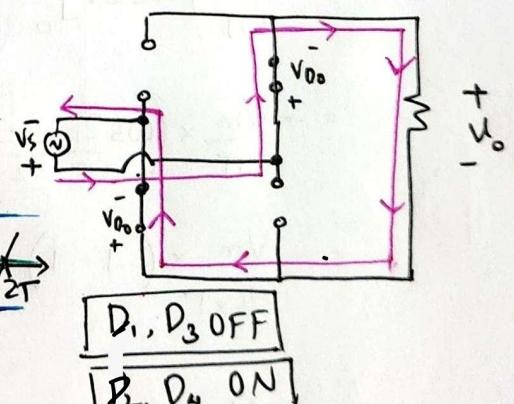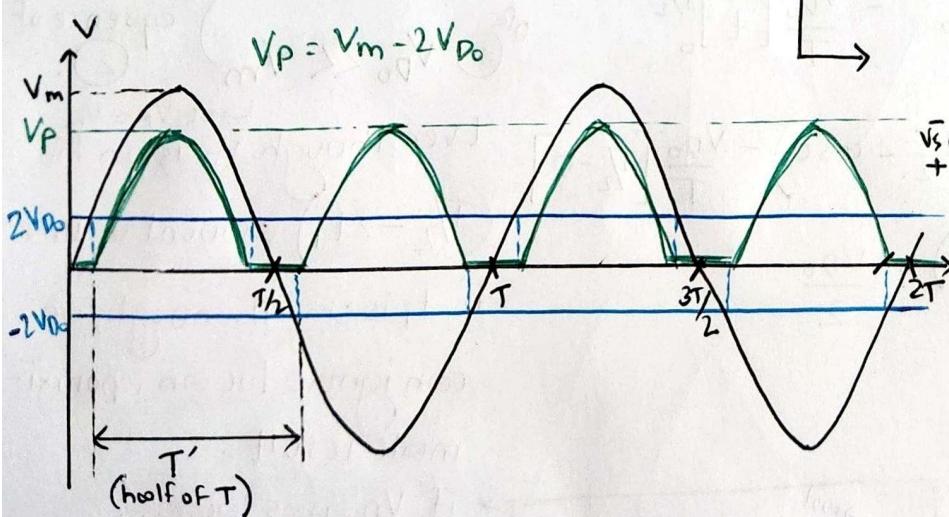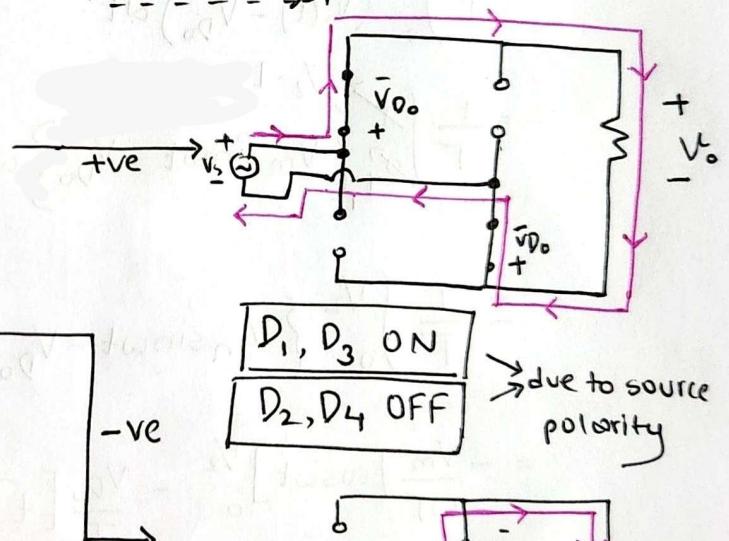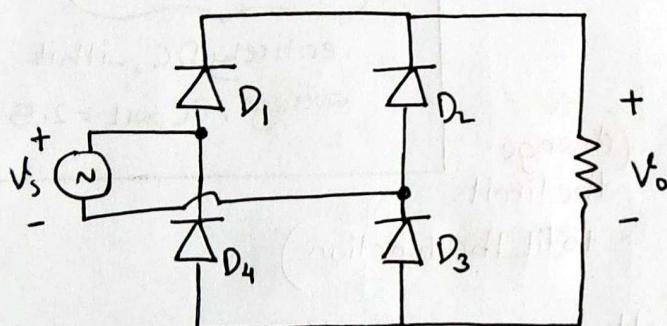

in both + and - cycles,
the current direction through
the load remains same.

$$V_0 = V_s - 2V_{D_0} \quad \begin{cases} + \\ - \end{cases} \quad V_0 = +V_s - 2V_{D_0}$$

mathematically same

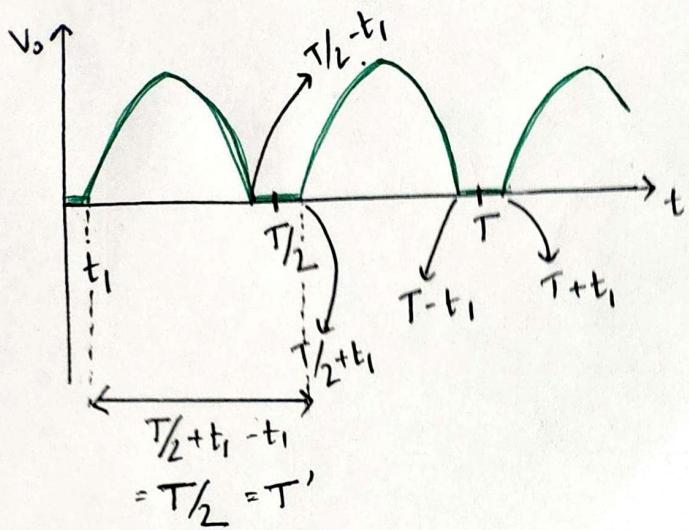

T' = time period of output

$$T' = \frac{1}{2} \times T$$

$$= \frac{T}{2}$$

To find t_1 -

$$V_{ms} \sin \omega t_1 = 2V_{D_o}$$

$$\therefore t_1 = \frac{1}{\omega} \sin^{-1} \left(\frac{2V_{D_o}}{V_m} \right)$$

* the obtained output is called pulsating DC.

* DC component,

$$V_{DC} = \frac{1}{T/2} \int_0^{T/2} V_o(t) dt$$

$$= \frac{1}{T/2} \int_{t_1}^{T/2 - t_1} \{ V_m \sin \omega t - 2V_{D_o} \} dt$$

$$\approx \frac{2}{T} \int_0^{T/2} \{ V_m \sin \omega t - 2V_{D_o} \} dt \quad [\text{assuming } V_{D_o} \ll V_m / t_1 \ll T]$$

: (similar to before)

$$= \frac{2V_m}{\pi} - 2V_{D_o}$$