

Practice Problem Set 3.3

CSE251 - Electronic Devices and Circuits

DIODE LOGIC CIRCUITS

OR Gate, AND Gate, and Cascaded Logic Circuits

[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)

Problem 1

- Implement the following logic functions using diodes.

I. $A.C + B + D$




II. $A.C + B.D$

III. $(A + C).(B + D)$

IV. $A.C.(B + D)$

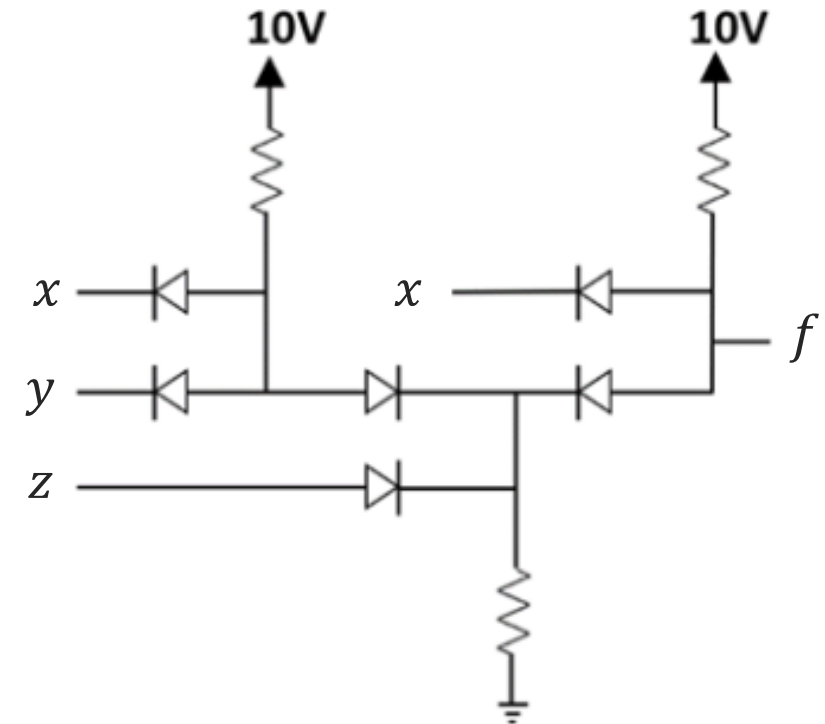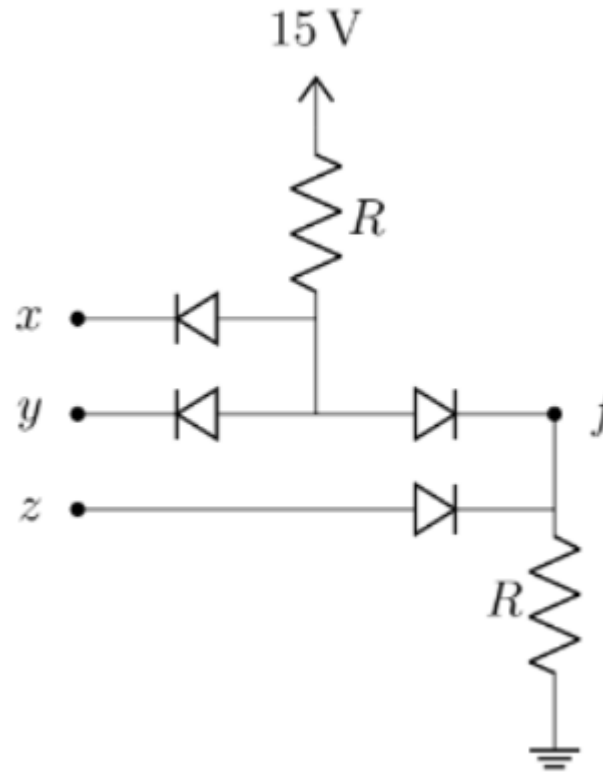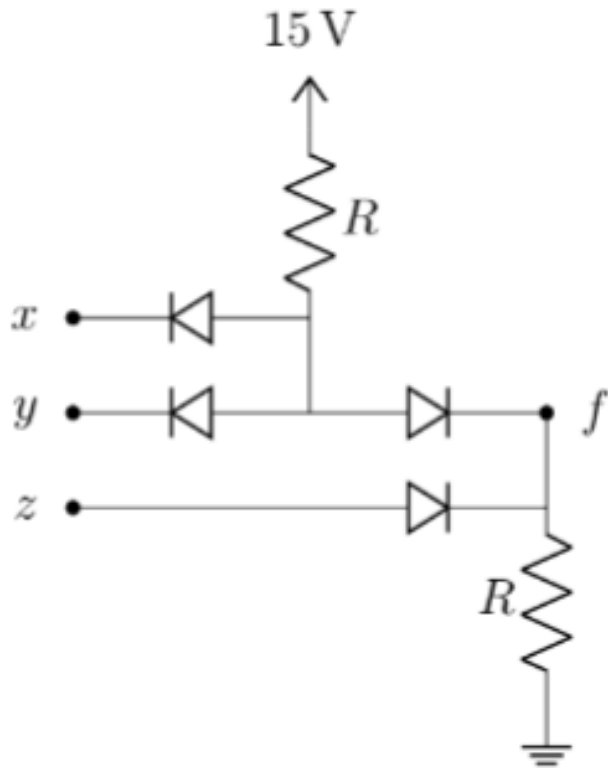
Problem 2

- For each of the circuits shown below, assuming x , y , and z are Boolean inputs, express f in terms of x , y , and z .





100

- 
- BRAC
UNIVERSITY
- Inspiring Excellence

 4

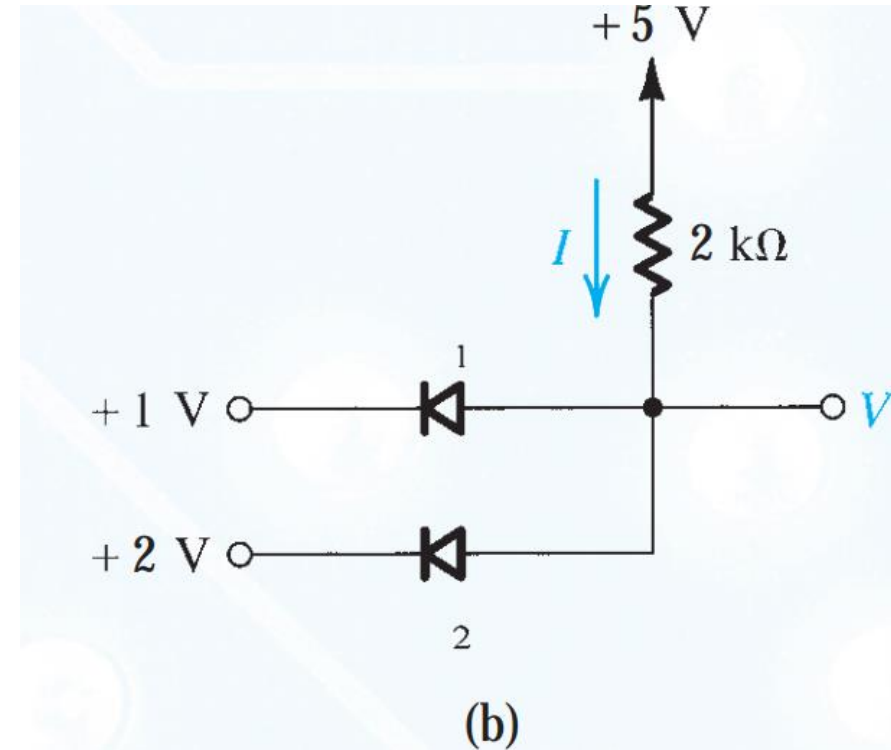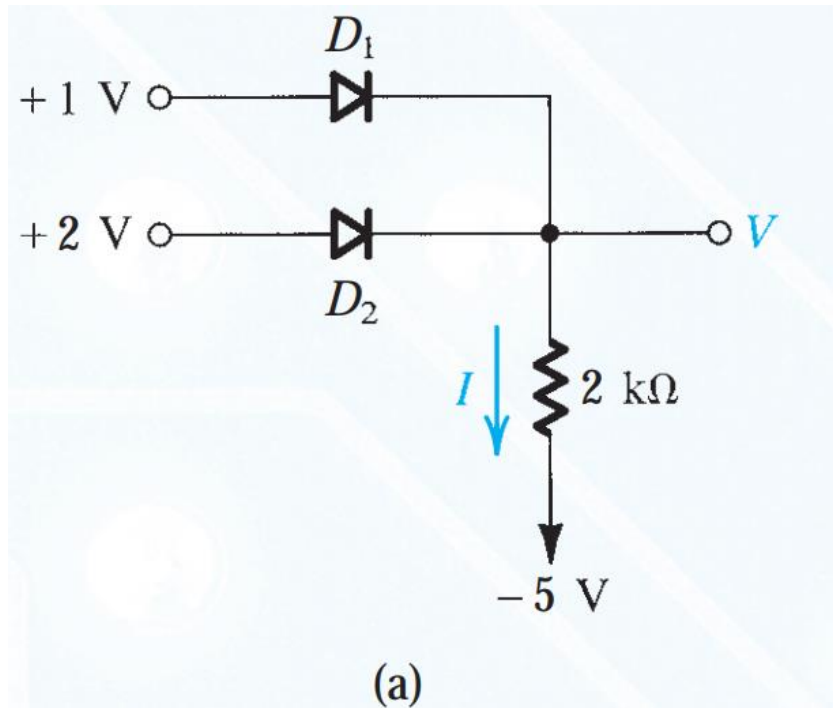Problem 4


- For the logic circuits shown below, use ideal diode model, find the values of the voltages and currents indicated.




Ans: (a) $V = 2\text{ V}$, $I = 2.5\text{ mA}$; (b) $V = 1\text{ V}$, $I = 2\text{ mA}$

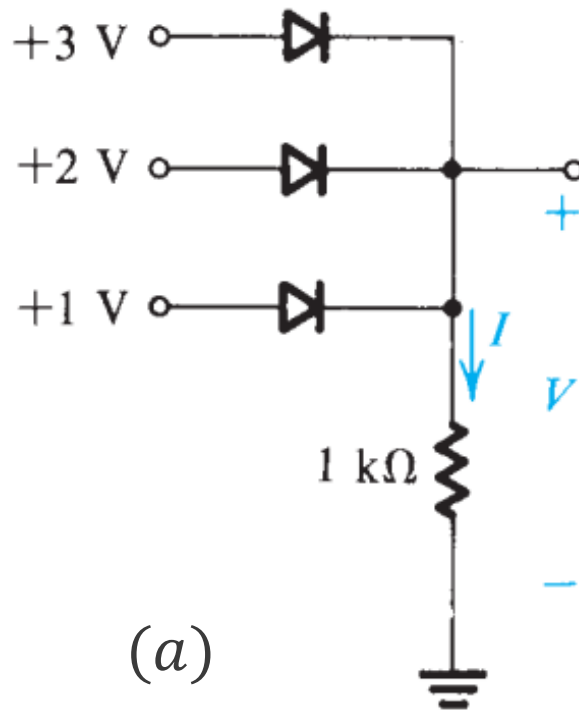Problem 5

- For the logic circuits shown below, use ideal diode model, find the values of the voltages and currents indicated.



(a)

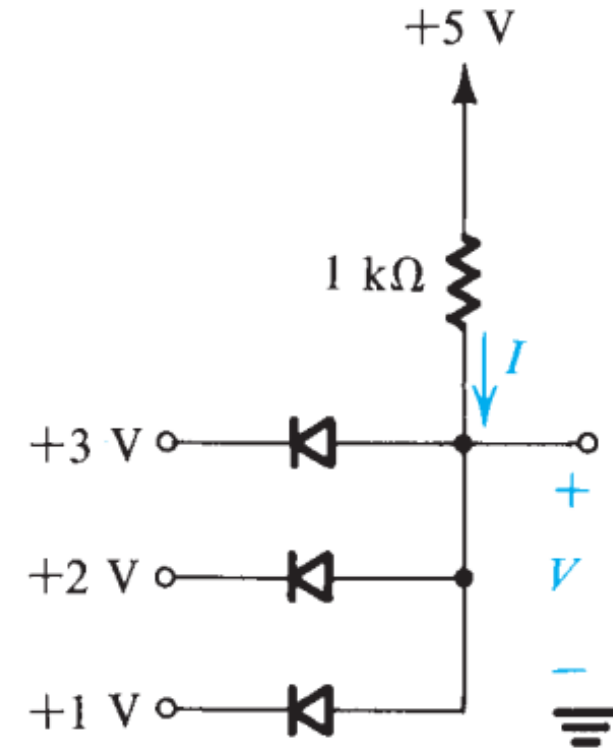


(b)


Ans: (a) $V = 3\text{ V}$, $I = 3\text{ mA}$; (b) $V = 1\text{ V}$, $I = 4\text{ mA}$

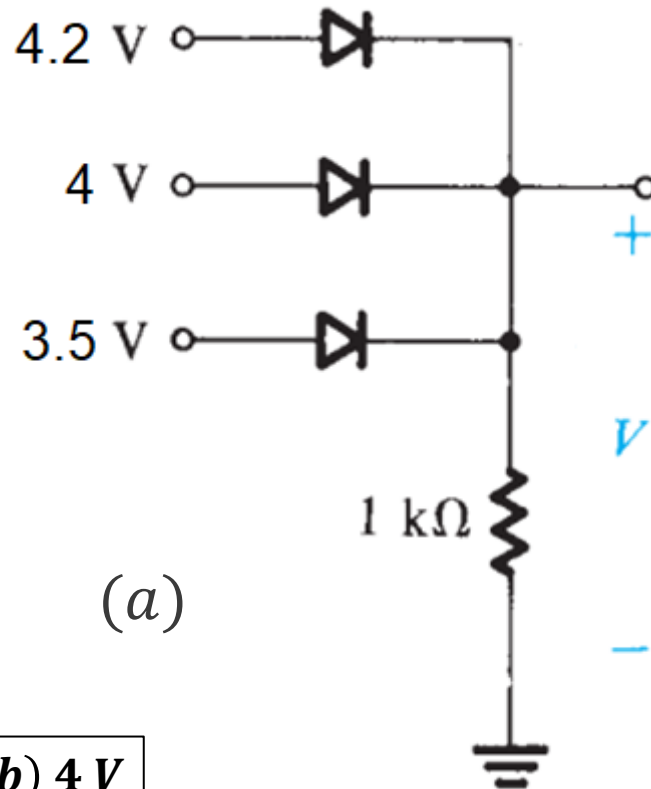Problem 6

- For each of the circuits shown below, use CVD model, find the values of the voltages and currents indicated. Take $V_{D_{o1}} = 1\text{ V}$, $V_{D_{o2}} = 0.7\text{ V}$, and $V_{D_{o3}} = 0.5\text{ V}$.



(a)


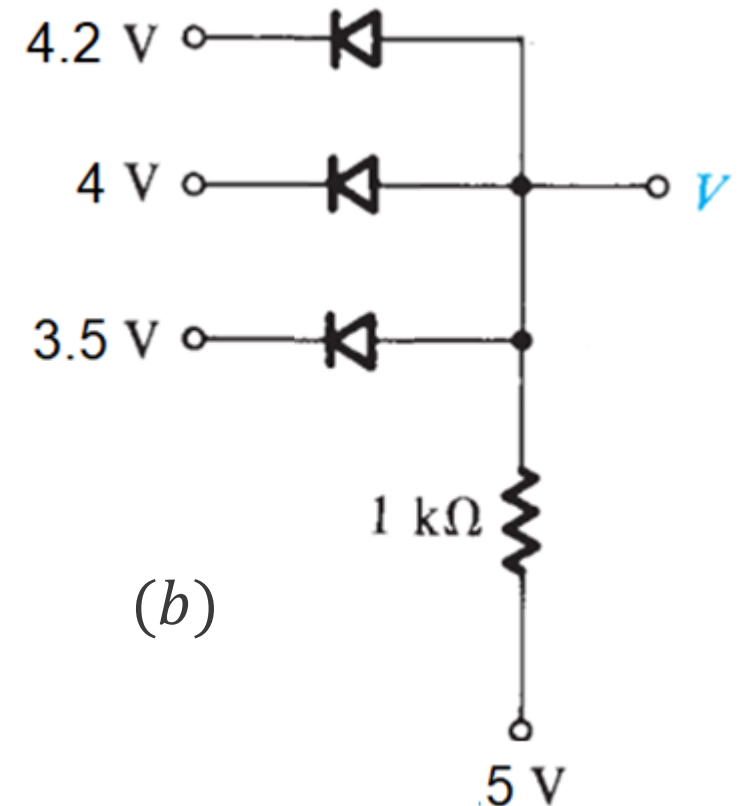


(b)

Ans: (a) $V = 3.3\text{ V}$; (b) 4 V

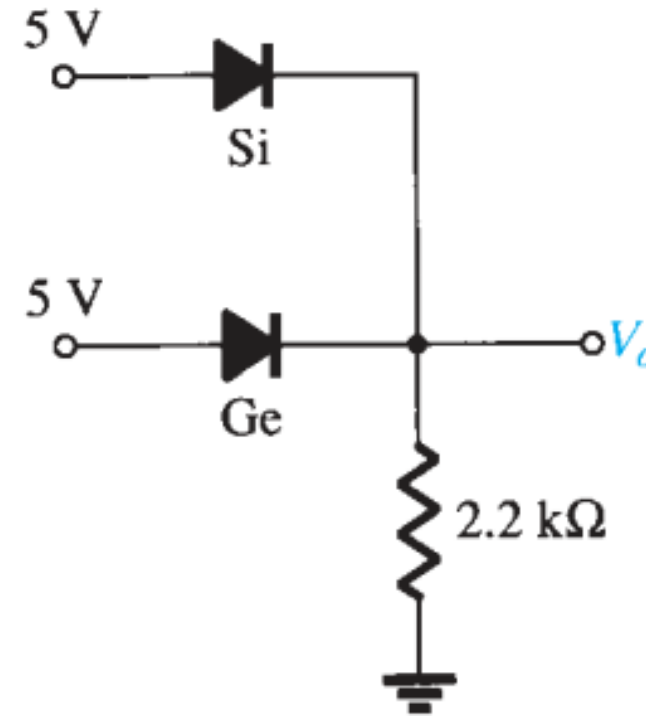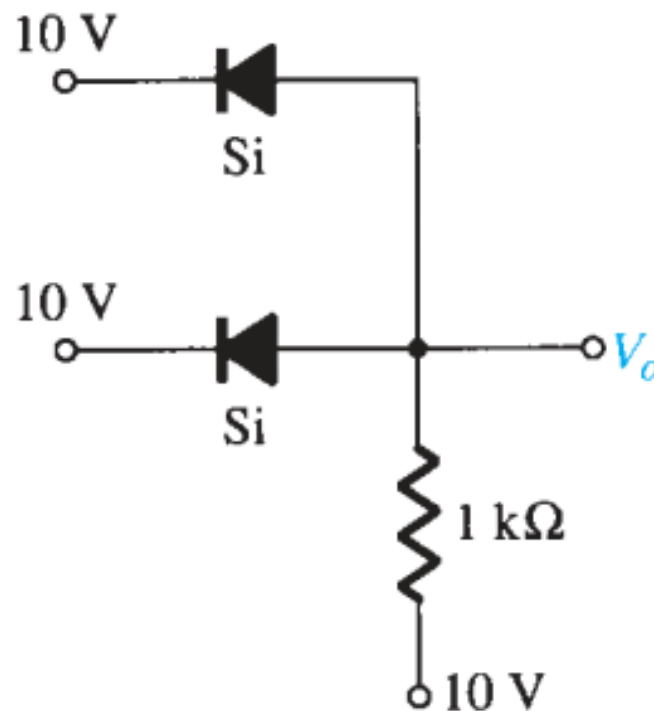Problem 7


- For the logic circuits shown below, determine. Use CVD+R model with $V_{D_o, Si} = 0.7\text{ V}$ and $V_{D_o, Ge} = 0.3\text{ V}$ and $r_o = 10\ \Omega$ for both.



Ans: (a) $V_o = 10.7\text{ V}$; (b) $V_o = 4.7\text{ V}$

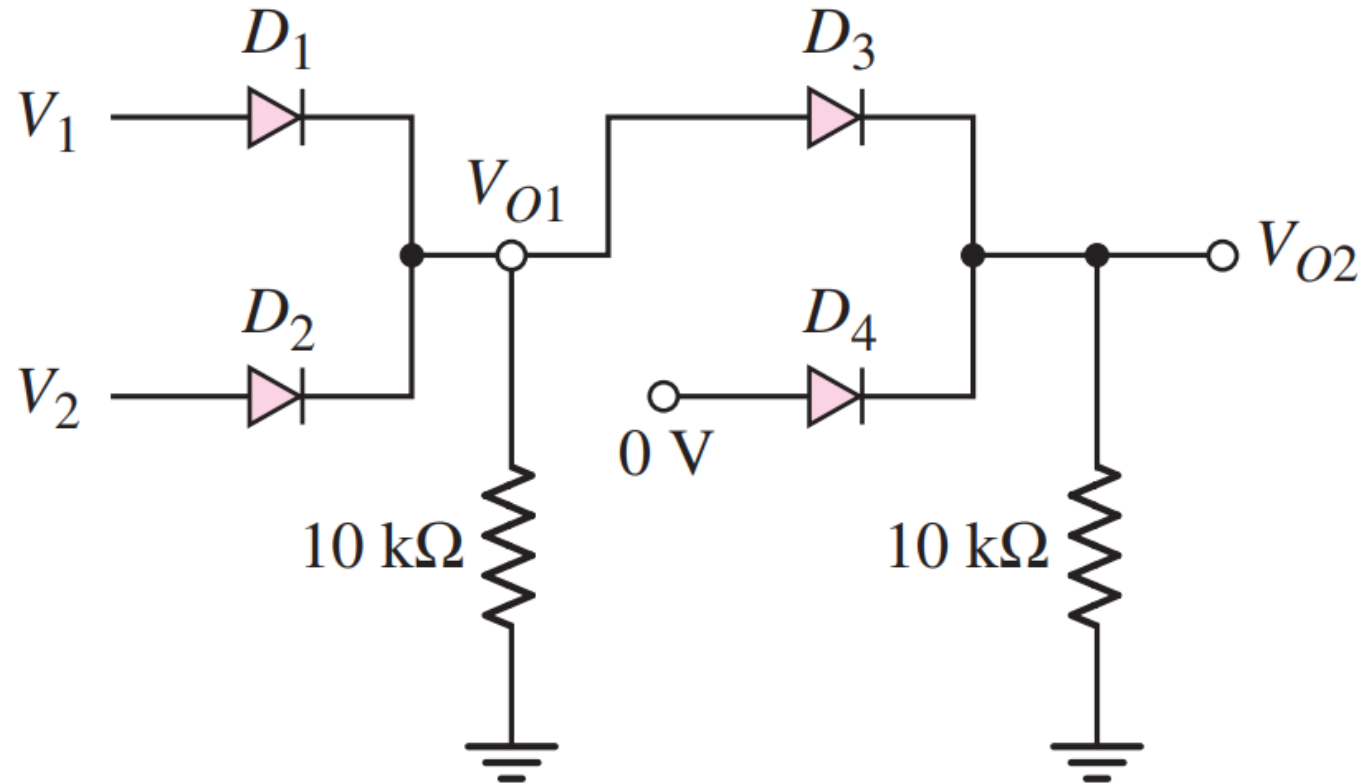Problem 8


- From the logic network shown, express V_{O2} as a Boolean expression of V_1 and V_2 . Determine V_{O2} if $V_1 = 3\text{ V}$ and $V_2 = 1\text{ V}$. Use CVD model with $V_{D_o} = 0.7\text{ V}$.



Ans: $V_{O2} = 2\text{ V}$

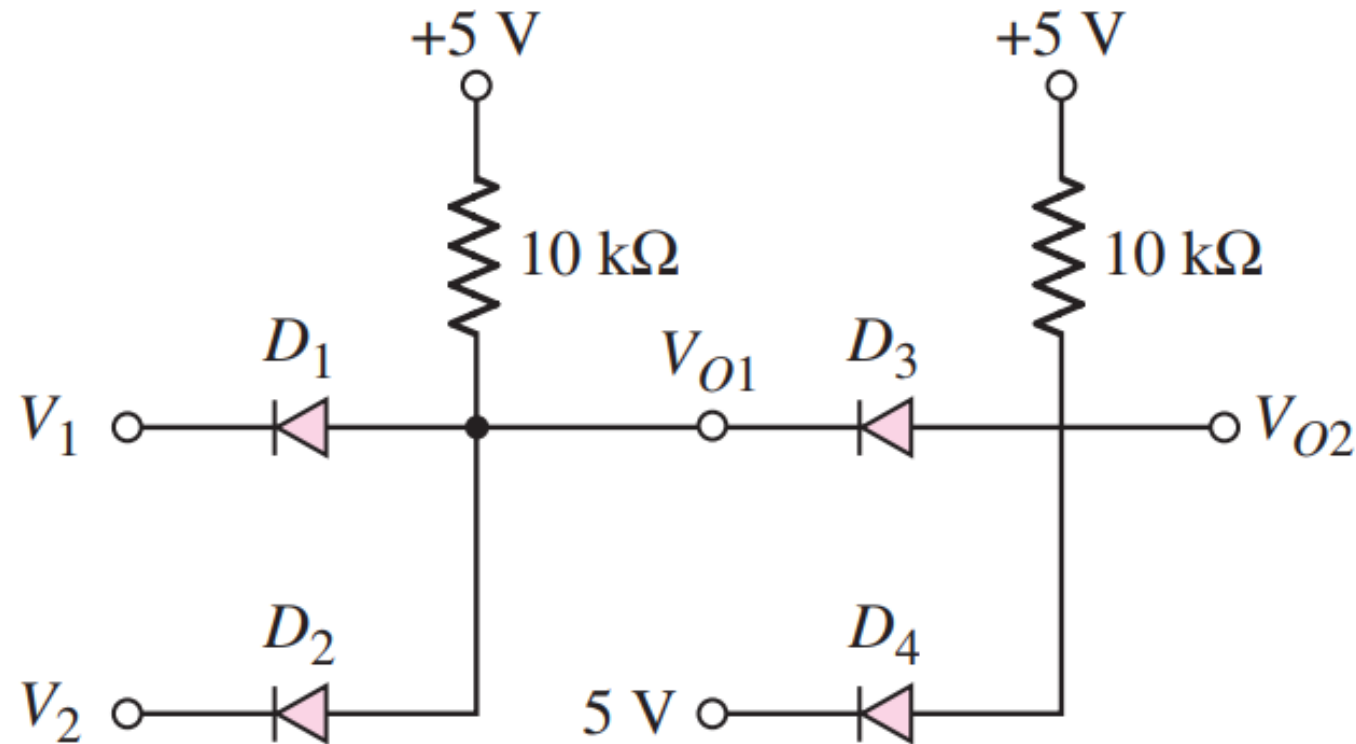Problem 9


- From the logic network shown, express V_{O2} as a Boolean expression of V_1 and V_2 . Determine V_{O2} if $V_1 = 3\text{ V}$ and $V_2 = 1\text{ V}$. Use CVD model with $V_{D_o} = 0.7\text{ V}$.



Ans: $V_{O2} = 2.4\text{ V}$

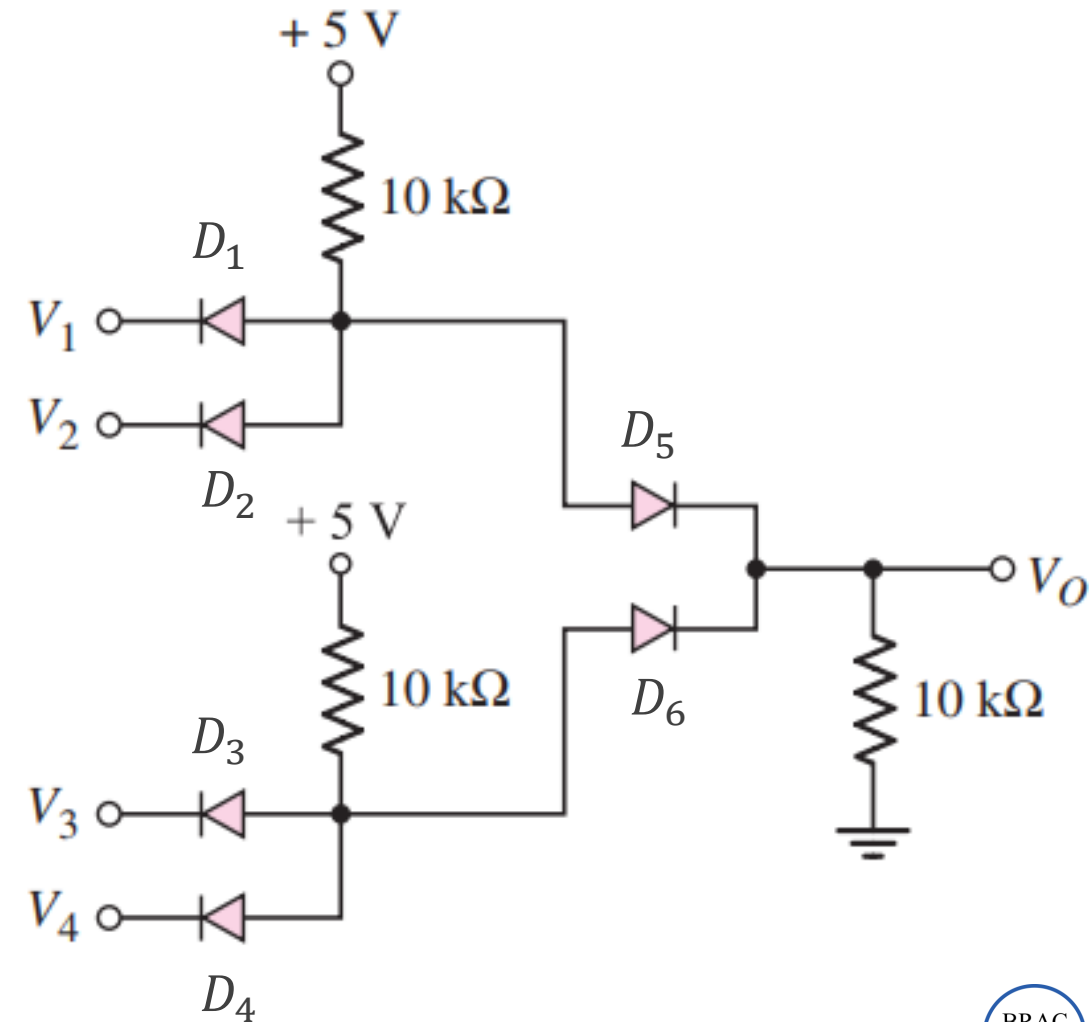Problem 10

- From the logic network shown, determine V_O if $V_1 = 2\text{ V}$, $V_2 = 2.2\text{ V}$, $V_3 = 2.4\text{ V}$, and $V_4 = 2.5\text{ V}$. Use CVD model with $V_{D_{o1}} = 0.3\text{ V}$, $V_{D_{o2}} = 0.5\text{ V}$, $V_{D_{o3}} = 0.7\text{ V}$, $V_{D_{o4}} = 0.9\text{ V}$, $V_{D_{o5}} = 1\text{ V}$, and $V_{D_{o6}} = 1.5\text{ V}$.




Ans: $V_O = 1.6\text{ V}$

Problem 11

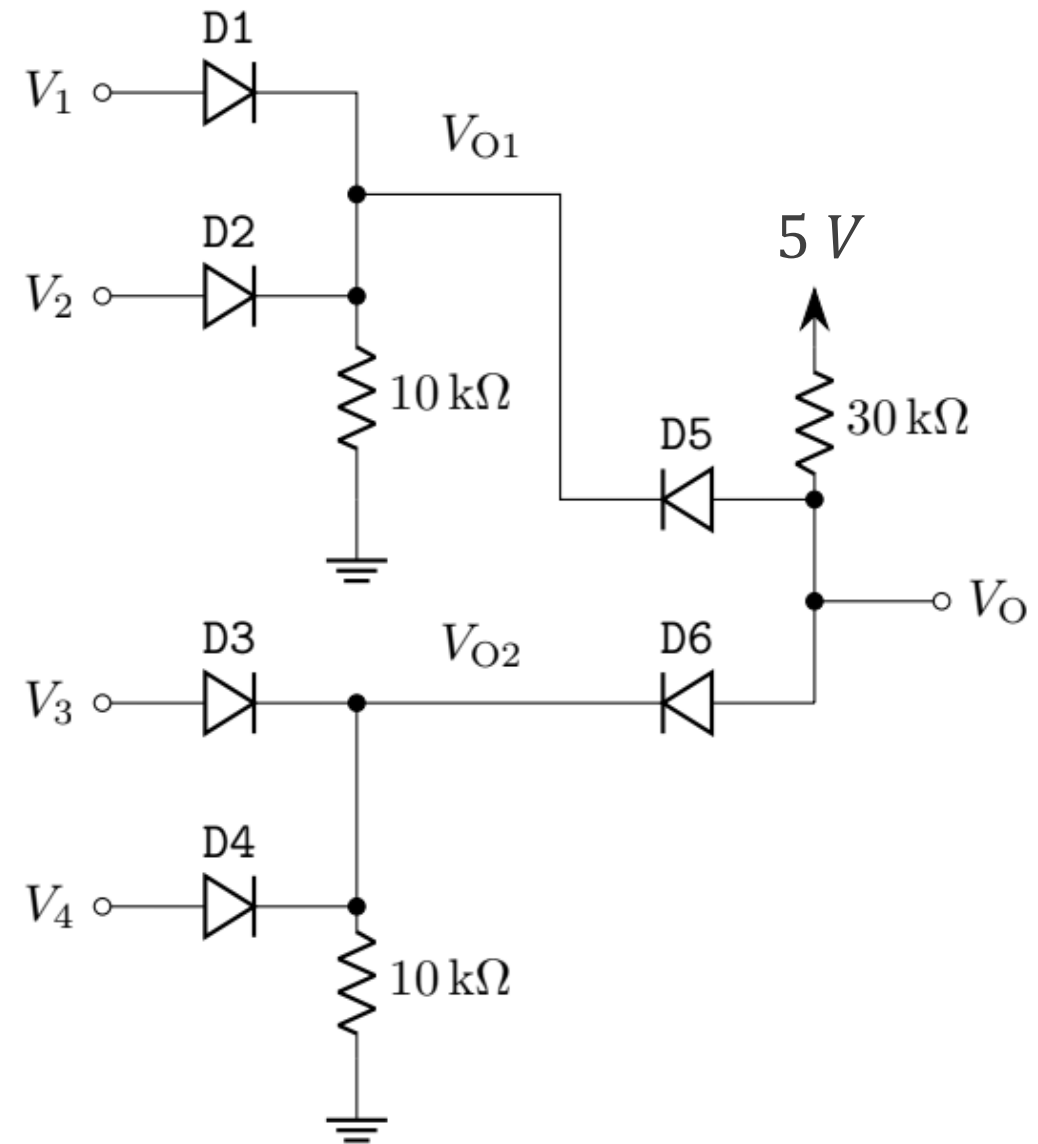- a. From the logic network shown, determine V_{O1} and V_{O2} if $V_1 = 2\text{ V}$, $V_2 = 2.2\text{ V}$, $V_3 = 2.4\text{ V}$, and $V_4 = 2.5\text{ V}$. Use CVD model with $V_{D_{o1}} = 0.3\text{ V}$, $V_{D_{o2}} = 0.5\text{ V}$, $V_{D_{o3}} = 0.7\text{ V}$, $V_{D_{o4}} = 0.9\text{ V}$, and $V_{D_{o5}} = V_{D_{o6}} = 1\text{ V}$.
- b. Now if V_3 and V_4 are changed to -2 V and -3 V while keeping all other parameters unchanged, identify the states of the diodes D_3 and D_4 . Determine V_O .

[Hint: V_{O1} is as it is for (a). However, you don't know V_{O2} now. You need to apply method of assumed states to check the states of D_5 and D_6 .]



Ans: (a) $V_{O1} = 1.7\text{ V}$, $V_{O2} = 1.7\text{ V}$; (b) $V_{O1} = 1.7\text{ V}$, $V_{O2} = 1\text{ V}$, $V_O = 2\text{ V}$