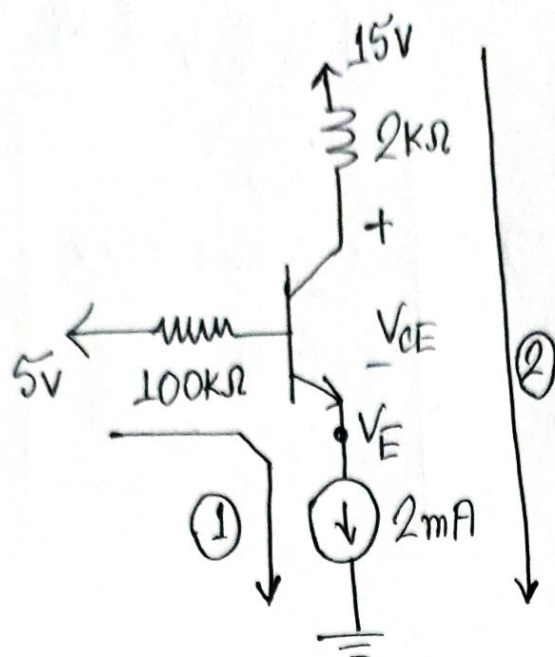


①



Find I_B, I_C, I_E & V_{CE}

$$\beta = 100$$

$$V_{BE(\text{active})} = 0.7V$$

$$V_{BE(\text{sat})} = 0.8V$$

$$V_{CE(\text{sat})} = 0.2V$$

Assuming active —

$$I_E = 2\text{mA} \quad \because I_E = (\beta + 1)I_B \text{ in active mode}$$

$$\therefore I_B = \frac{2}{101} \text{ mA} = 0.0198 \text{ mA}$$

$$\therefore I_C = 1.98 \text{ mA}$$

$$\text{KVL in ②} — 2 \times 1.98 + V_{CE} = 15 - V_E \quad [\text{KVL upto node E}] \text{---①}$$

To solve for V_{CE} we need the value of V_E .

$$\text{KVL in ①} — 100 \times 0.0198 + V_{BE(\text{active})} = 5 - V_E \quad [\text{upto node E}]$$

$$\Rightarrow 1.98 + 0.7 = 5 - V_E \Rightarrow V_E = 2.32V$$


$$\therefore \text{①} \Rightarrow V_{CE} = 15 - 2.32 - 3.96 = 8.72V > V_{CE(\text{sat})}$$

\therefore assumption is correct

$$\text{Required quantities} \rightarrow I_B = 0.0198 \text{ mA}; I_C = 1.98 \text{ mA}; I_E = 2 \text{ mA};$$

$$V_{CE} = 8.72V$$

②

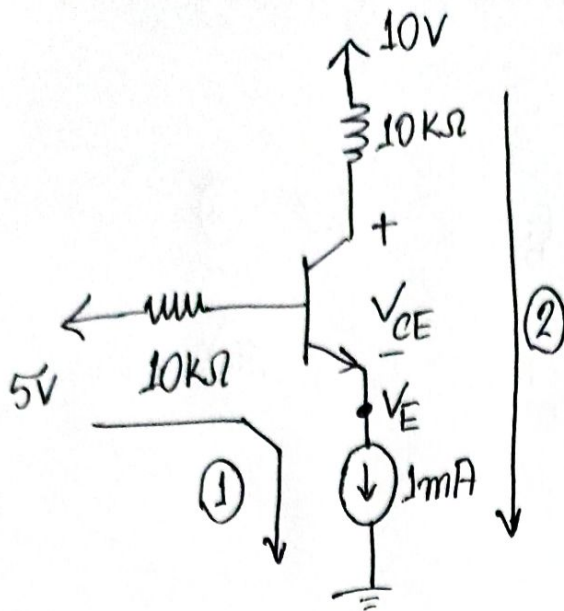

Find I_B, I_C, I_E & V_{CE}

$$\beta = 100$$

$$V_{BE}(\text{active}) = 0.7V$$

$$V_{BE}(\text{sat}) = 0.8V$$

$$V_{CE}(\text{sat}) = 0.2V$$

Assuming active —

$$I_E = 1mA \quad \therefore I_B = \frac{1}{\beta+1} = 0.99 \times 10^{-2} mA \quad \therefore I_C = \beta I_B = 0.99 mA$$

KVL in line ② upto node E —

$$10 \times 0.99 + V_{CE} = 10 - V_E \quad \text{--- (i)}$$

KVL in line ① upto node E —

$$10 \times 0.99 \times 10^{-2} + 0.7 = 5 - V_E$$

$$\Rightarrow V_E = 5 - 0.7 - 0.099 = 4.201 V$$

$$\therefore \text{(i)} \Rightarrow V_{CE} = 10 - 9.9 - 4.201 = -4.101 \leq V_{\text{sat}CE}$$

\therefore active assumption wrong.

Assuming saturation —

KVL in ② —

$$10 I_C + V_{CE}(\text{sat}) = 10 - V_E \quad [\text{upto node E}] \Rightarrow 10 I_C + V_E = 9.8 \quad \text{--- (i)}$$

KVL in ① upto node E —

$$10I_B + V_{BE}(\text{sat}) = 5 - V_E \Rightarrow 10I_B + V_E = 4.2 \text{ --- ②}$$

$$\text{also we know, } I_E = I_B + I_C \Rightarrow I_B + I_C = 1 \text{ --- ③}$$

Solving ①, ② & ③, we get,

$$I_B = 0.22 \text{ mA}$$

$$I_C = 0.78 \text{ mA}$$

$$V_{CE} = 2 \text{ V}$$

$$\therefore \frac{I_C}{I_B} = 3.54 = \beta_{\text{forced}} < \beta$$

\therefore assumption correct


required quantities $\rightarrow I_B = 0.22 \text{ mA}$

$$I_C = 0.78 \text{ mA}$$

$$I_E = 1 \text{ mA}$$

$$V_{CE} = 2 \text{ V}$$

③

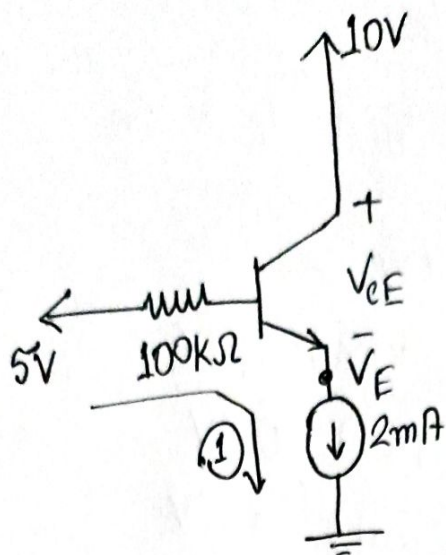

Find I_B, I_C, I_E & V_{CE}

$$\beta = 100$$

$$V_{BE}(\text{active}) = 0.7V$$

$$V_{BE}(\text{sat}) = 0.8V$$

$$V_{CE}(\text{sat}) = 0.2$$

Assuming active —

$$I_E = 2mA \quad \therefore I_B = \frac{2}{\beta + 1} = 0.0198mA \quad \therefore I_C = 1.98mA$$

KVL in ① —

$$100 \times 0.0198 + V_{BE}(\text{active}) = 5 - V_E \quad [\text{upto node E}]$$

$$\Rightarrow V_E = 5 - 1.98 - 0.7 = 2.32V$$

$$\therefore V_{CE} = 10 - V_E = 10 - 2.32 = 7.68V > V_{CE}(\text{sat})$$

\therefore assumption correct


Required quantities $\rightarrow I_B = 0.0198mA$

$$I_C = 1.98mA$$

$$I_E = 2mA$$

$$V_{CE} = 7.68V$$

④

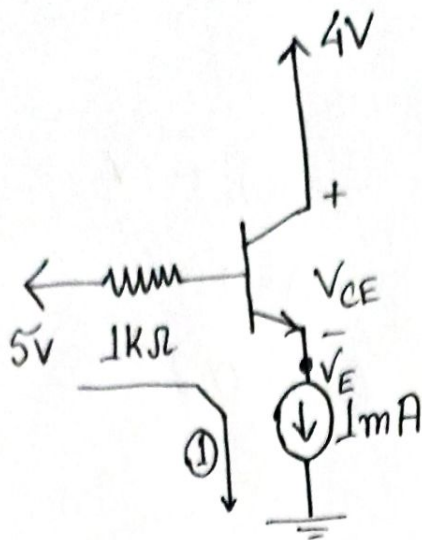

Find I_B , I_C , I_E & V_{CE}

$$\beta = 100$$

$$V_{BE(\text{active})} = 0.7V$$

$$V_{BE(\text{sat})} = 0.8V$$

$$V_{CE(\text{sat})} = 0.2V$$

Assuming active mode —

$$I_E = 1mA \quad \therefore I_B = \frac{1}{\beta + 1} = 0.0099mA$$

KVL in ① —

$$0.0099 + V_{BE(\text{active})} = 5 - V_E \text{ (upto node E)}$$

$$\Rightarrow V_E = 5 - 0.7 - 0.0099 = 4.29V$$

$$\therefore V_{CE} = 4 - 4.29 = -0.29 \leq V_{CE(\text{sat})}$$

So, assumption is wrong

Assuming saturation —

$$\therefore V_{CE(\text{sat})} = 0.2V \quad \therefore V_E = 4 - 0.2 = 3.8V$$

KVL in ① —


$$I_B + V_{BE(\text{sat})} = 5 - V_E \text{ [upto node E]} \Rightarrow I_B = 5 - 3.8 - 0.8 = 0.4mA$$

$$\therefore I_E = I_B + I_C \quad \therefore I_C = 0.6mA$$

$$\therefore \beta_{\text{forced}} = \frac{I_c}{I_B} = \frac{0.6}{0.4} = 1.5 < \beta \text{ [assumption correct]}$$

$$\therefore \text{required quantities} \rightarrow I_B = 0.4 \text{ mA}; I_c = 0.6 \text{ mA}; I_E = 1 \text{ mA}; V_{CE} = 0.2 \text{ V}$$

(5)

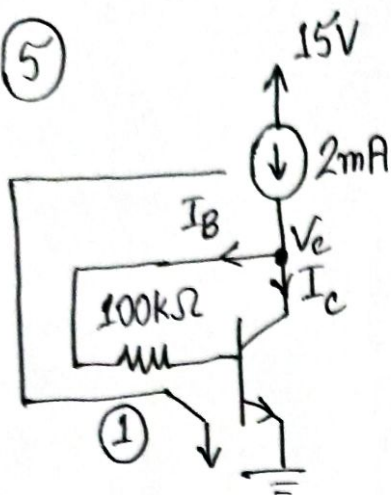

Find I_B, I_c, I_E & V_{CE}

$$\beta = 100$$

$$V_{BE}(\text{active}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$V_{BE}(\text{sat}) = 0.8 \text{ V}$$

Assuming active —

$$\text{KCL @ node C} - I_B + I_c = 2 \Rightarrow I_B + 100I_B = 2 \text{ [}\because I_c = \beta I_B \text{ in active]} \\ \Rightarrow I_B = 0.0198 \text{ mA}$$

KVL in line (1) starting from node C —


$$100 \times 0.0198 + V_{BE}(\text{active}) = V_c - 0 \Rightarrow V_c = 1.98 + 0.7 = 2.68 \text{ V}$$

$$\therefore V_{CE} = V_c - V_E = 2.68 \text{ V} > V_{CE}(\text{sat}) \text{ [assumption correct]}$$

Required quantities —

$$I_B = 0.0198 \text{ mA}; I_c = 1.98 \text{ mA}; I_E = 2 \text{ mA}; V_{CE} = 2.68 \text{ V}$$

⑥

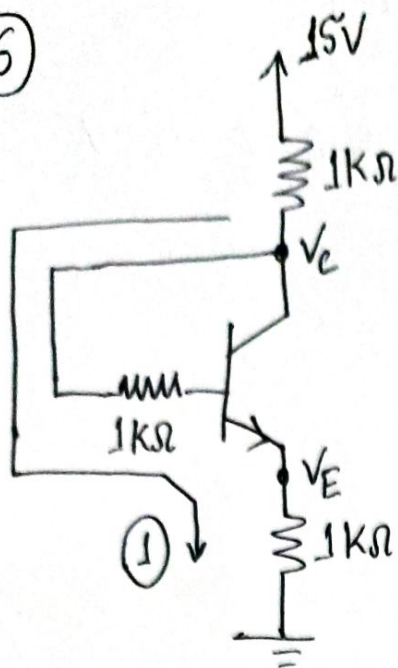

Find I_B, I_C, I_E & V_{CE}

$$\beta = 100$$

$$V_{BE(\text{active})} = 0.7 \text{ V}$$

$$V_{BE(\text{sat})} = 0.8 \text{ V}$$

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$

Assuming active —

$$I_C = \beta I_B \Rightarrow 100 I_B - I_C = 0 \text{ — (i)}$$

applying KCL @ node c —

$$\frac{15 - V_C}{1} = I_B + I_C \Rightarrow I_B + I_C + V_C = 15 \text{ — (ii)}$$

applying KVL in line ① starting @ node c —

$$I_B + V_{BE(\text{active})} + I_E = V_C - 0 \Rightarrow I_B + I_E - V_C = -0.7$$

$$\Rightarrow 2I_B + I_C - V_C = -0.7 \quad [I_E = I_B + I_C] \text{ — (iii)}$$

Solving (i), (ii) & (iii) we get,

$$I_B = 0.07044 \text{ mA} ; I_C = 7.044 \text{ mA} ; V_C = 7.885 \text{ V}$$


$$V_{CE} = V_C - V_E = 7.885 - 1 \times I_E = 7.885 - 7.044 - 0.07044$$

$$= 0.77056 \text{ V} > V_{CE(\text{sat})} \text{ [correct]}$$

required quantities $\rightarrow I_B = 0.07044 \text{ mA} ; I_C = 7.044 \text{ mA} ; I_E = 7.114 \text{ mA}$

$$V_{CE} = 7.885 \text{ V}$$

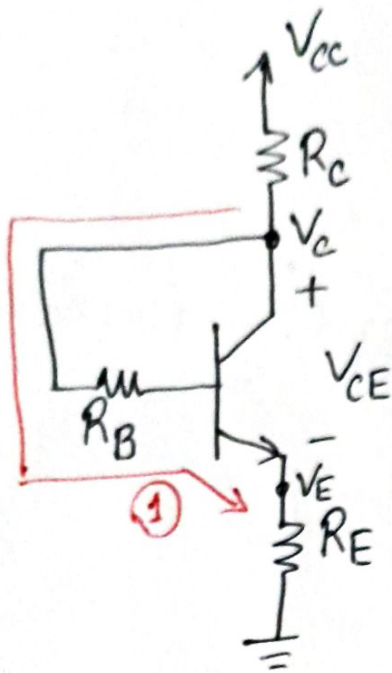Note — This type of connection as in problem 5 & 6 will always be in active mode, if the BJT is ON.



KVL in line (1) from node C to E —

$$I_B R_B + V_{BE} = V_C - V_E$$

$$\Rightarrow V_{CE} = V_{BE} + I_B R_B$$

When BJT is ON — V_{BE} is at least 0.7V
& $I_B > 0$

$\therefore V_{CE}$ must be greater than 0.7V


$$\therefore V_{CE(sat)} = 0.2 \sim 0.3 \text{ V}$$

The BJT must be in active mode

V_{CC} must be large enough to ensure $I_B > 0$
which implies $V_{BE} \neq 0.7 \text{ V}$

ps — You still have to find values and verify

⑦

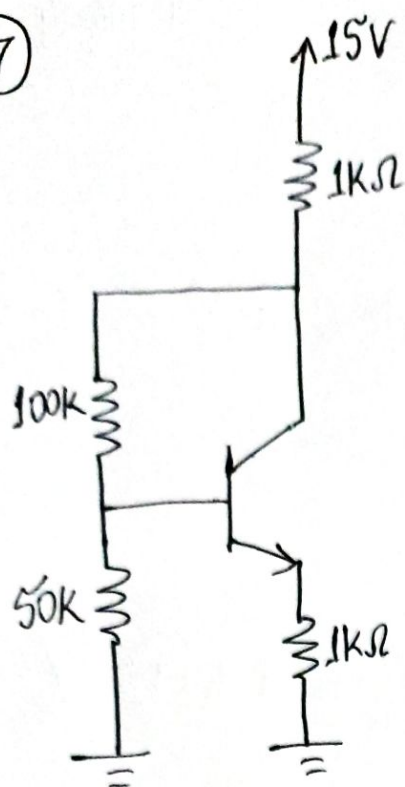

Find I_c, I_B, I_E & V_{CE}

$$\beta = 100$$


$$V_{BE} = 0.7V(\text{active})$$

$$0.8V(\text{saturation})$$

$$V_{CE}(\text{sat}) = 0.2V$$

High difficulty. Will probably not be set in exam

Labelling some circuit variables —

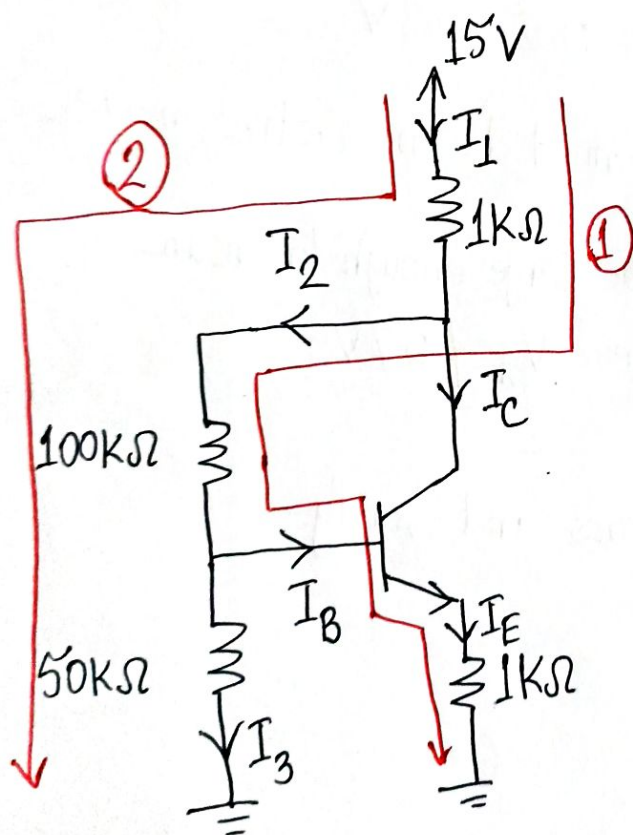

Assuming active —

KVL in ① —

$$I_1 + 100I_2 + V_{BE}(\text{active}) + I_E = 15 - 0$$

$$\Rightarrow I_2 + I_C + 100I_2 + I_B + I_C = 15 - 0.7$$

$$\Rightarrow I_2 + 100I_2 + I_B + I_C + I_C = 14.3$$

$$\Rightarrow 101I_2 + I_B + 2 \times 100I_B = 14.3$$

$$[\because I_C = \beta I_B]$$

$$\Rightarrow 101I_2 + 201I_B = 14.3 \text{ --- (i)}$$

KVL in ② —

$$I_1 + 100I_2 + 50I_3 = 15 \Rightarrow I_2 + I_C + 100I_2 + 50I_2 - 50I_B = 15$$

$$\Rightarrow 151I_2 + 50I_B = 15 \text{ --- (ii) } [\because I_C = \beta I_B]$$

Solving (i) & (ii) —

$$I_2 = 0.0909 \text{ mA}$$


$$I_B = 0.0255 \text{ mA}$$

$$\therefore I_C = 2.55 \text{ mA}$$

$$\therefore I_1 = I_2 + I_C = 2.6409 \text{ mA}$$

$$\& I_E = I_B + I_C = 2.5755 \text{ mA}$$

\therefore the ckt —

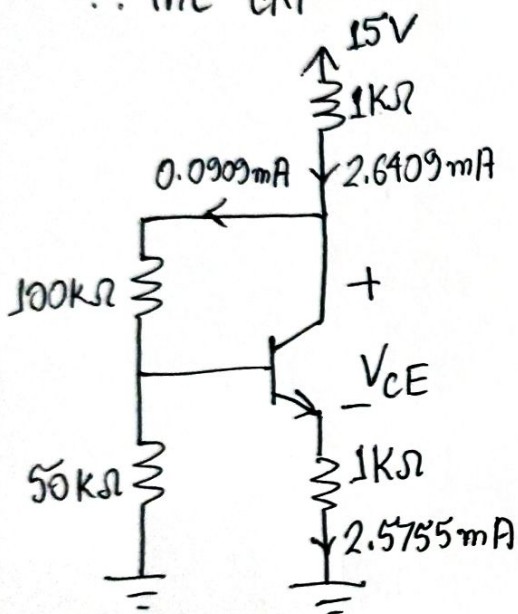

To verify assumption —

Applying KVL in (3) —

$$2.6409 + V_{CE} + 2.5755 = 15 - 0$$

$$\Rightarrow V_{CE} = 15 - 5.2164$$

$$= 9.7836 \text{ V} > V_{CE}(\text{sat})$$

\therefore assumption is correct

Required quantities — $I_B = 0.0255 \text{ mA}$

$$I_C = 2.55 \text{ mA}$$

$$I_E = 2.5755 \text{ mA}$$

$$V_{CE} = 9.7836 \text{ V}$$