

'Assignment - 03'

Amirun Nahin

ID: 23201416

Sec: 07

Course: CSE251


Semester: Summer 2025

Date: 07/09/2025

Ans. to the ques. no - 04

(a)

Given circuit,

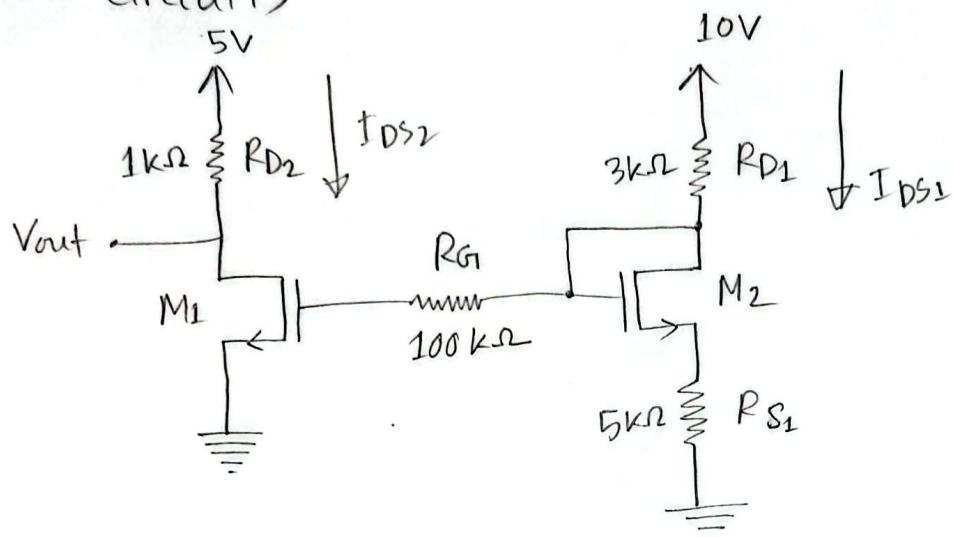

Here, in M₂ MOSFET, the gate and drain are shorted. So, in M₂ MOSFET, $V_{GS} = V_{DS}$. Also, as $I_G = 0$, I_{D2} will be the current through M₂ MOSFET. Now, to be in saturation mode,

$$V_{DS} \geq V_{ov}$$

$$\Rightarrow V_{DS} \geq V_{GS} - V_T$$

$$\Rightarrow V_{DS} \geq V_{DS} - V_T \quad [\text{as } V_{GS} = V_{DS}]$$


$$\Rightarrow 0 \geq -V_T$$

$$\Rightarrow V_T \geq 0 \quad [\text{Multiplying by } (-1)]$$

We see that, to be in saturation mode V_T has to be more than 0. Our given V_T for M₂ is 1V.

Therefore, M₂ MOSFET will operate in saturation mode.

Given circuit,

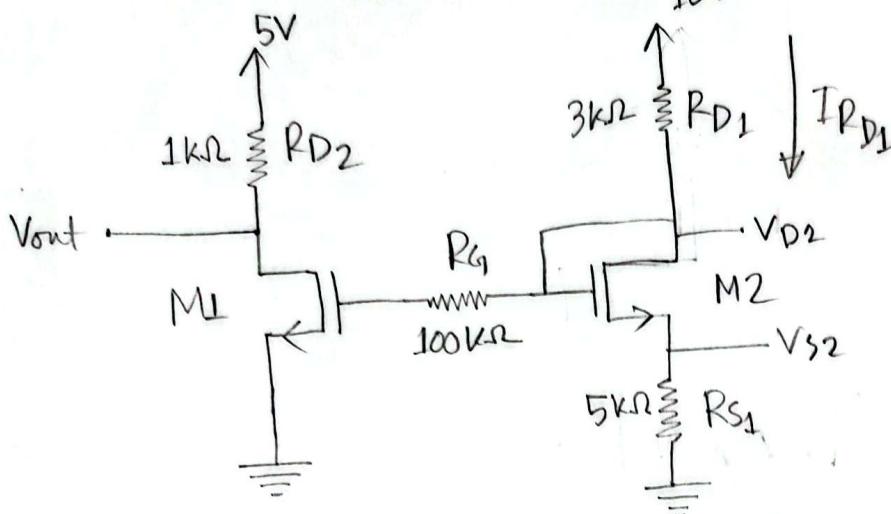

(b)

$$V_T = 1 \text{ V} \text{ (for both)}$$

for M1,

$$K_1 = 0.5 \text{ mA/V}^2$$

for M2,

$$K_2 = 2 \text{ mA/V}^2$$

for M2 MOSFET, assuming saturation,

$$I_{RD1} = \frac{1}{2} \times K_2 \times (V_{DS2})^2$$

~~$$I_{RD1} = \frac{1}{2} \times 2 \times (V_{GS2} - V_T)^2$$~~

$$I_{RD1} = (V_{DS2} - V_T)^2 \quad \text{(i)}$$

Again,

$$I_{RD1} = \frac{10 - V_{DS2}}{3} \quad \text{(ii)}$$

$$I_{RD1} = \frac{V_{DS2} - 0}{5}$$

$$= \frac{V_{DS2}}{5} \quad \text{(iii)}$$

from (ii) and (iii)

$$\frac{10 - V_{DS2}}{3} = \frac{V_{DS2}}{5}$$

$$\Rightarrow 50 - 5V_{DS2} = 3V_{DS2}$$

$$\Rightarrow 5V_{D2} = 50 - 3V_{S2}$$

$$\Rightarrow V_{D2} = \frac{50 - 3V_{S2}}{5} \quad \text{--- (iv)}$$

Now, we can see that, Gate and Drain are shorted in M₂ MOSFET. So,

$$V_G = V_{D2}$$

also, as $I_G = 0$ through R_G , both MOSFET has

same V_{G1} .

Now, from (iv)

$$V_G = \frac{50 - 3V_{S2}}{5}$$

and, from (i) and (iii)

$$\frac{V_{S2}}{5} = \left(\frac{50 - 3V_{S2}}{5} - V_{S2} - V_T \right)^2$$

$$\Rightarrow \frac{V_{S2}}{5} = \left(\frac{50 - 3V_{S2} - 5V_{S2} - 1}{5} \right)^2$$

$$\Rightarrow 5V_{S2} = (-8V_{S2} + 45)^2$$

$$\Rightarrow 5V_{S2} = 64V_{S2}^2 - 720V_{S2} + 2025$$

$$\Rightarrow 64V_{S2}^2 - 725V_{S2} + 2025 = 0$$

$$\therefore V_{S2} = 6.33V, 5V$$

Taking $V_{S2} = 5V$ as to V_{GS} to be more, we need less value of V_{S2} .

So,

$$V_G = \frac{50 - (3 \times 5)}{5}$$

$$= 7V$$

from (i),

$$I_{RD1} = (7 - 5 - 1)^2$$

$$= 1mA$$

Verify, as $V_{DS} = V_{GS}$

$$\therefore V_{DS} = V_G - V_{S2}$$

$$= 7 - 5$$

$$= 2V$$

since, $V_{DS} > V_T$; saturation mode assumption is right.

Now, for M2 MOSFET,

the V_G is the same as M1. So, $V_G = 7V$. and $V_{S1} = 0V$.

Assuming saturation,

$$I_{RD2} = \frac{1}{2} \times k_1 \times (V_{GS})^2$$

$$\Rightarrow I_{RD2} = \frac{1}{2} \times 0.5 \times (V_{GS2} - V_T)^2$$

$$\Rightarrow I_{RD2} = \frac{1}{4} \times (V_G - V_{SL} - V_T)^2$$

$$= \frac{1}{4} \times (7 - 0 - 1)^2$$

$$= 9 \text{ mA}$$

Again, this is wrong, because negative voltage is there.

$$I_{RD2} = \frac{5 - V_{out}}{1}$$

$$\therefore 9 = 5 - V_{out}$$

$$\therefore V_{out} = -4 \text{ V}$$

verify, $I_{RD2} = 1$

$$V_{DS} = V_D - V_{SL}$$

$$V_{DS} = -V_{out} - V_{SL}$$

$$= -4 - 0$$

$$= -4$$

since, $V_{DS} < V_T$; assumption is wrong.

Now, assuming Triode,

$$I_{RD2} = k \times \left(V_{ov} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\Rightarrow I_{RD2} = 0.5 \times \left(V_G - V_{SL} - V_T - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\Rightarrow I_{RD2} = 0.5 \times \left(7 - 0 - 1 - \frac{V_{out} - V_{SL}}{2} \right) \times \left(V_{out} - V_{SL} \right)$$

$$\Rightarrow I_{RD_2} = 0.5 \times \left(6 - \frac{V_{out}}{2} \right) \times V_{out}$$

$$\Rightarrow I_{RD_2} = 0.5 \times \frac{(12 - V_{out})}{2} \times V_{out}$$

$$\Rightarrow I_{RD_2} = \frac{12V_{out} - V_{out}^2}{4} \quad \text{--- (i)}$$

Again,

$$I_{RD_2} = \frac{5 - V_{out}}{1}$$

$$\Rightarrow I_{RD_2} = 5 - V_{out} \quad \text{--- (ii)}$$

from (i) and (ii),

$$5 - V_{out} = \frac{12V_{out} - V_{out}^2}{4}$$

$$\Rightarrow 20 - 4V_{out} = 12V_{out} + V_{out}^2$$

$$\Rightarrow V_{out}^2 - 16V_{out} + 20 = 0$$

$$\therefore V_{out} = 14.633 \text{ V}, 1.366 \text{ V}$$

Verify, let $V_{out} = 1.366 \text{ V}$

$$\begin{aligned} \text{So, } V_{DS} &= V_D - V_{S1} \\ &= V_{out} - V_{S1} \\ &= 1.336 - 0 \\ &= 1.336 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{OV} &= V_{GS} - V_T \\ &= V_G - V_{S1} - V_T \\ &= 7 - 0 - 1 \\ &= 6 \text{ V} \end{aligned}$$

Since, $V_{DS} < V_T$; Triode mode assumption is right.

Finally, from (i),

$$\text{from (i),}$$
$$I_{RD2} = \frac{12 V_{out} - V_{out}^2}{4}$$
$$= \frac{12 \times (1.336) - (1.336)^2}{4}$$
$$= 3.56 \text{ mA}$$

So, We get,

$$V_{out} = 1.336 \text{ V}$$

$$I_{RD1} = 1 \text{ mA}$$

$$I_{RD2} = 3.56 \text{ mA}$$

(Ans.)

Ans. to the que. no-02


①

Given,

$$f = \overline{A \cdot B \cdot C + D \cdot E}$$

$V_{DD} = 5V$


$$f = (\overline{ABC} + DE)$$

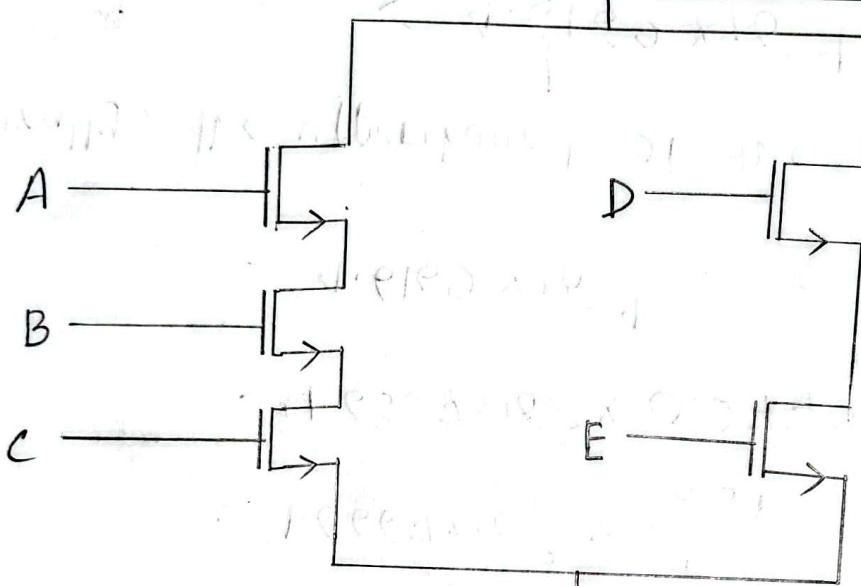

ii


Given,

$$g = A \cdot B \cdot (C + D)$$

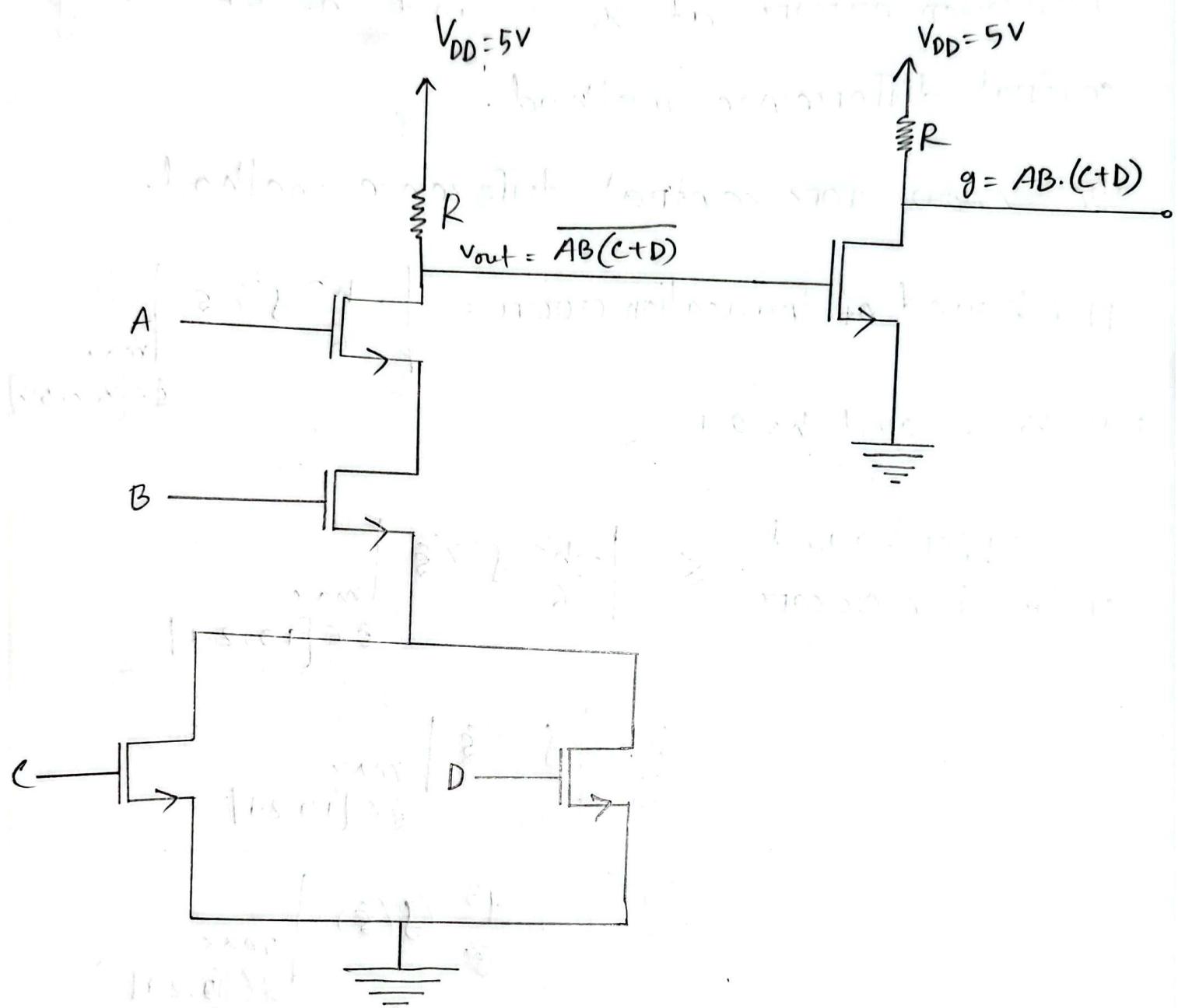

Ans. to the ques. no-03

Given,

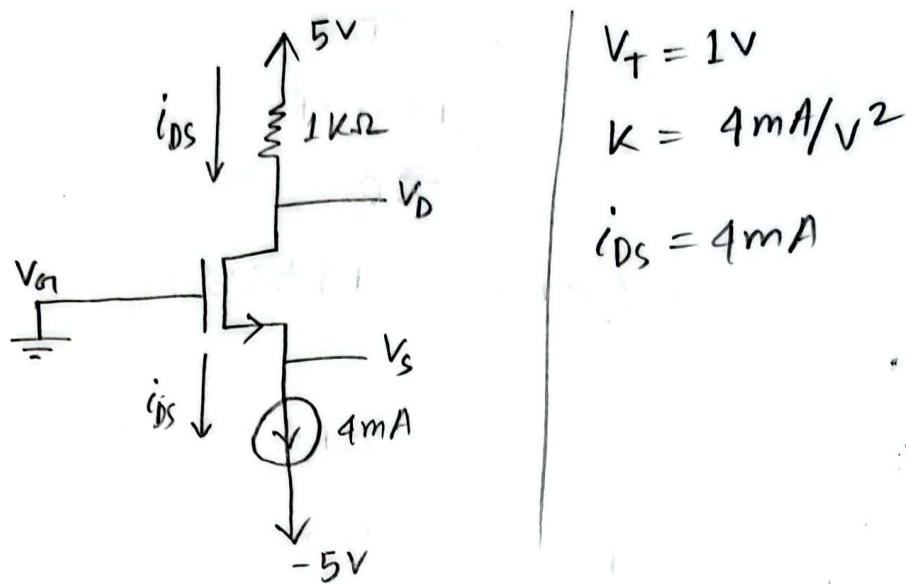

Assuming Saturation,

here, $i_{DS} = 4mA$. So,

$$i_{DS} = \frac{1}{2} K n \frac{W}{L} \cdot (V_{GS})^2$$

$$\Rightarrow 4 = \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2$$

$$\Rightarrow 4 = 2 \times (V_{GS} - V_S - V_T)^2$$

$$\Rightarrow 4 = 2 \times (0 - V_S - 1)^2$$

$$\Rightarrow 2 = (-V_S - 1)^2$$

$$\Rightarrow \sqrt{2} = -V_S - 1$$

$$\Rightarrow V_S = -1 - \sqrt{2}$$

$$\Rightarrow V_S = -2.414 V$$

Now,

$$i_{DS} = \frac{5 - V_D}{1}$$

$$\Rightarrow 4 = \frac{5 - V_D}{1}$$

$$\Rightarrow 4 = 5 - V_D$$

$$\Rightarrow V_D = 5 - 4$$

$$\Rightarrow V_D = 1V$$

Verify,

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= 1 + 2.414 \\ &= 3.414 V \end{aligned}$$

$$\text{and, } V_{ov} = V_{GS} - V_T$$

$$= V_G - V_S - V_T$$

$$= 0 + 2.414 - 1$$

$$= 1.414 V$$

$$\therefore V_{DS} > V_{ov}$$

So, assumption is right.

Therefore, the MOSFET is in Saturation mode.

$$\text{and, } V_S = -2.414 V. \quad (\underline{\text{Ans.}})$$

Ans. to the ques. no. 04


(a)

In saturation mode, the MOSFET will have,

$$\left. \begin{aligned} V_{GS} &\geq V_{TN} \\ \text{and, } V_{DS} &\geq V_{ov} \end{aligned} \right\} \text{ whence, } V_{ov} = V_{GS} - V_{TN}$$

(b)

Given,

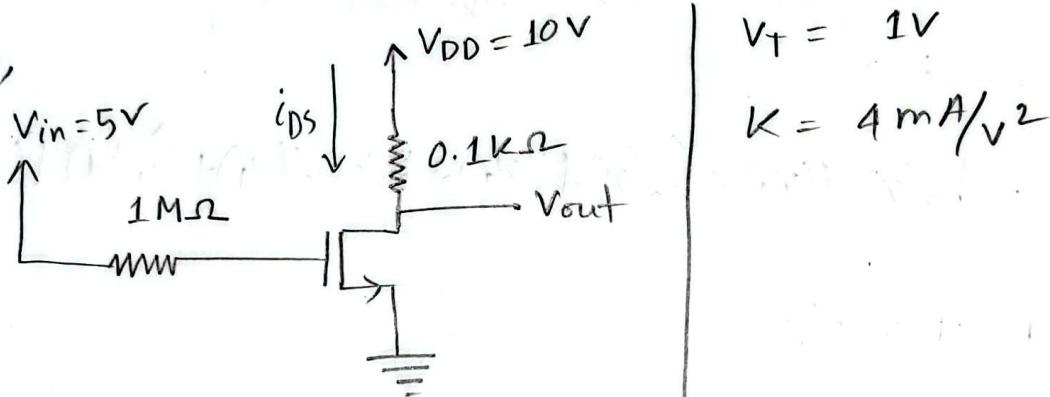

Assuming Saturation,

$$\begin{aligned} i_{DS} &= \frac{1}{2} \times K \times \frac{W}{L} \times (V_{ov})^2 \\ &= \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2 \\ &= 2 \times (V_G - V_S - V_T)^2 \\ &= 2 \times (5 - 0 - 1)^2 \\ &= 32 \text{ mA} \end{aligned}$$

$$\text{So, } i_{DS} = \frac{V_{DD} - V_{out}}{0.1}$$

$$\Rightarrow 32 \times 0.1 = 10 - V_{out}$$

$$\Rightarrow 3.2 = 10 - V_{out}$$

$$\Rightarrow V_{out} = 10 - 3.2$$

$$\Rightarrow V_{out} = 6.8 \text{ V}$$

Verify,

$$V_{GS} = V_G - V_S$$

$$= 5 - 0$$

$$= 5 \text{ V}$$

$$\therefore V_{GS} > V_T$$

$$\text{and, } V_{DS} = V_D - V_S$$

$$= V_{out} + V_S$$

$$= 6.8 - 0$$

$$= 6.8 \text{ V}$$

$$V_{ov} = V_{GS} - V_T$$

$$= V_G - V_S - V_T$$

$$= 5 - 0 - 1$$


$$= 4 \text{ V}$$

As, $V_{DS} > V_{ov}$, the assumption is correct and the

MOSFET is in saturation mode.

As, we're given logic HIGH as input and got $V_{out} = 6.8 \text{ V}_{\text{II}}$, which is also logic HIGH, Normal was correct. (Ans.)

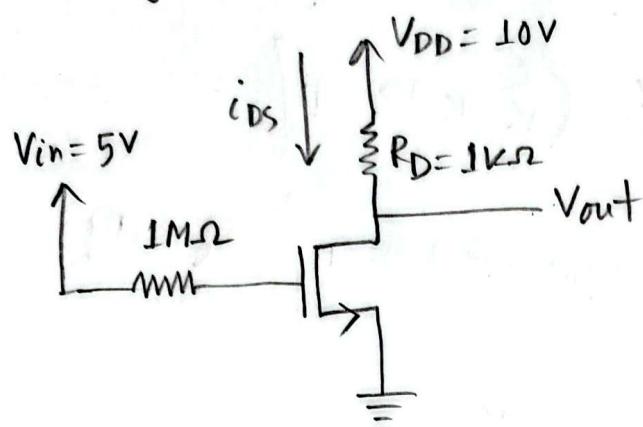Nizmol changed the value of R_D to $1\text{k}\Omega$. So, circuit,



$$V_T = 1\text{V}$$

$$K_n = 4 \text{ mA/V}^2$$

Assuming saturation,

$$\begin{aligned} i_{DS} &= \frac{1}{2} \times K_n \times \frac{W}{L} \times (V_{GS})^2 \\ &= \frac{1}{2} \times 4 \times (V_{GS} - V_T)^2 \\ &= \frac{1}{2} \times 4 \times (V_G - V_S - V_T)^2 \\ &= 2 \times (5 - 0 - 1)^2 \\ &= 32 \text{ mA} \end{aligned}$$

$$\text{So, } i_{DS} = \frac{V_{DD} - V_{out}}{R_D}$$

$$\Rightarrow 32 = 10 - V_{out}$$

$$\Rightarrow V_{out} = -22\text{V}$$

$$\text{Verify, } V_{GS} = V_G - V_S$$

$$= 5 - 0$$

$$= 5\text{V}$$

$$\therefore V_{GS} > V_T$$

$$\text{and, } V_{DS} = V_D - V_S$$

$$= V_{out} - V_S$$

$$= -22 - 0$$

$$= -22 \text{ V}$$

$$\therefore V_{ov} = V_{GS} - V_T = V_G - V_S - V_T$$

$$= 5 - 0 - 1$$

$$= 4 \text{ V}$$

As, $V_{DS} < V_{ov}$, assumption is wrong.

Assuming Triode Mode,

$$i_{DS} = k_n \cdot \frac{W}{L} \times \left[V_{ov} - \frac{V_{DS}}{2} \right] V_{DS}$$

$$\Rightarrow i_{DS} = 4 \times \left[V_G - V_S - V_T - \frac{(V_D - V_S)}{2} \right] (V_D - V_S)$$

$$\Rightarrow i_{DS} = 4 \times \left[5 - 0 - 1 - \frac{(V_D - 0)}{2} \right] (V_D - 0)$$

$$\Rightarrow i_{DS} = 4 \times \left(4 - \frac{V_D}{2} \right) V_D$$

$$\Rightarrow i_{DS} = 4 \times \left(\frac{8 - V_{out}}{2} \right) V_{out}$$

$$\Rightarrow i_{DS} = (16 - 2V_{out}) V_{out}$$

$$\Rightarrow i_{DS} = 16V_{out} - 2V_{out}^2 \quad \text{--- (1)}$$

Again,

$$i_{DS} = \frac{V_{DD} - V_{out}}{R_D}$$

$$\Rightarrow i_{DS} = \frac{10 - V_{out}}{1}$$

$$\Rightarrow i_{DS} = 10 - V_{out} \quad \text{(ii)}$$

from (i) and (ii)

$$16 V_{out} - 2 V_{out}^2 = 10 - V_{out}$$

$$\Rightarrow 2 V_{out}^2 - 17 V_{out} + 10 = 0$$

$$\therefore V_{out} = 0.635 \text{ V}$$

Verify,

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= V_{out} - V_S \\ &= 0.635 - 0 \\ &= 0.635 \text{ V} \end{aligned}$$

$$\text{and, } V_{ov} = V_{GS} - V_T$$

$$\begin{aligned} &= V_G - V_S - V_T \\ &= 5 - 0 - 1 \\ &= 4 \text{ V} \end{aligned}$$

As $V_{DS} < V_{ov}$; so, assumption is right. So, the MOSFET is in Triode Mode.

Now, As $V_{out} = 0.635 \text{ V}$ which is less than 5V, the output is logic Low. So, Yes, the inverter was working properly.

(Ans.)

(d)

At the edge of saturation,

$$V_{DS} = V_{ov}$$

Now,

$$\begin{aligned}V_{ov} &= V_{GS} - V_T \\&= V_G - V_S - V_T \\&= 5 - 0 - 1 \\&= 4 \text{ V}\end{aligned}$$

$$\therefore V_{DS} = 4 \text{ V}$$

$$\Rightarrow V_D - V_S = 4$$

$$\Rightarrow V_D - 0 = 4$$

$$\Rightarrow V_D = 4 \text{ V}$$

Now, at the saturation mode,

$$\begin{aligned}i_{DS} &= \frac{1}{2} \times k_n \times \frac{W}{L} \times (V_{ov})^2 \\&= \frac{1}{2} \times 4 \times (4)^2 \\&= 32 \text{ mA}\end{aligned}$$

again,

$$\begin{aligned}i_{DS} &= \frac{V_{PD} - V_{out}}{R_D} \\&\Rightarrow R_D = \frac{10 - 6}{32}\end{aligned}$$

$$\Rightarrow R_D = 0.1875 \text{ k}\Omega$$

Therefore, for $R_D = 0.1875 \text{ k}\Omega$, the MOSFET operates at the edge of saturation. (Ans.)