

The goal of this assignment is to test your concept and knowledge of:

- Diode Circuits
- Diode Logic Gates

1. [5 marks] Analyze the circuit in Figure-2, and calculate V_X , V_Y , I_{D1} , and I_{D2} using the method of assumed states. You must validate your assumptions. Use $V_{D0} = 0.7V$ for both diodes.

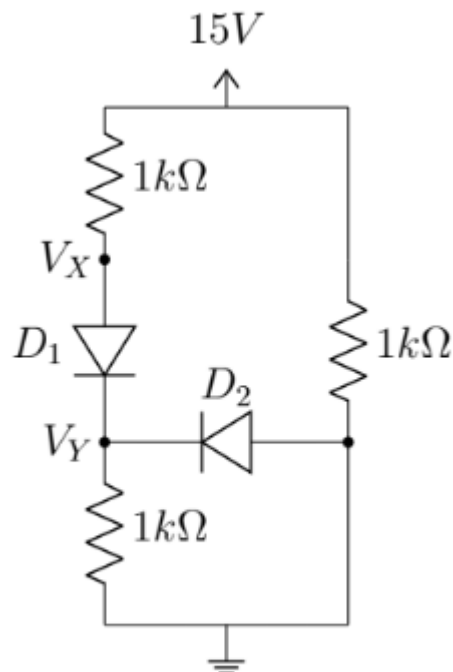


Figure-2

2. [5 marks] In the adjacent circuit $V_{DD} = 5V$ and other parameters are as follows:

Input Voltages	Diode Barrier Voltages
----------------	------------------------


$V_1 = 2.0V$	For D1: $V_{D1} = 0.3V$
--------------	-------------------------

$V_2 = 2.2V$	For D2: $V_{D2} = 0.7V$
--------------	-------------------------

$V_3 = 2.4V$	For D3: $V_{D3} = 0.5V$
--------------	-------------------------

$V_4 = 2.5V$	For D4: $V_{D4} = 0.9V$
--------------	-------------------------

For D5 & D6: $V_{D5} = V_{D6} = 1V$

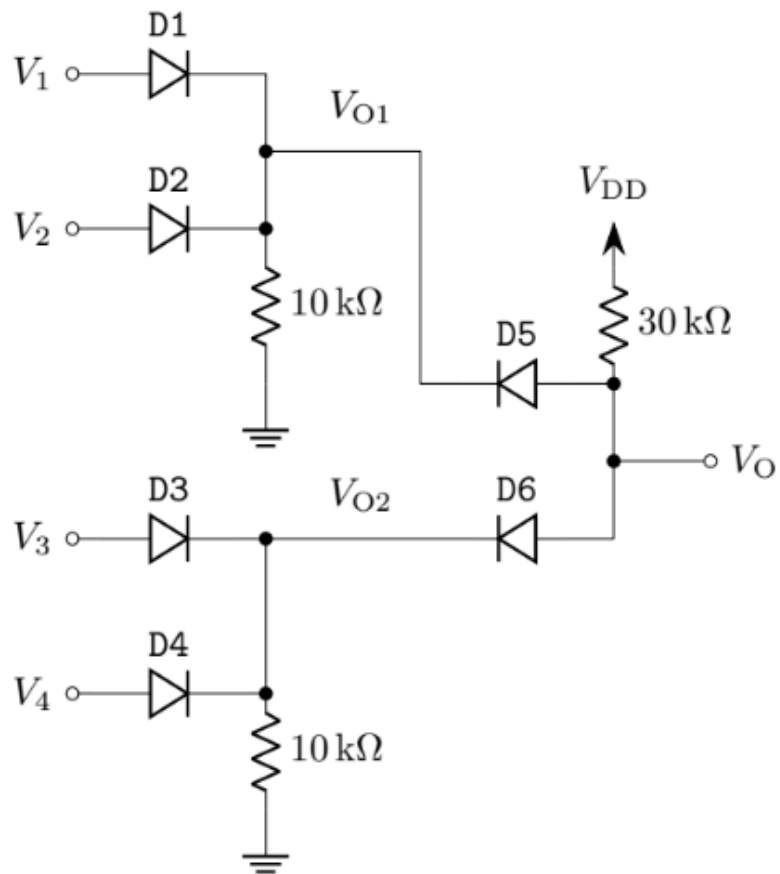

(a) [3 marks] Determine the values of V_{O1} and V_{O2} .

(b) [2 marks] Calculate the value of V_O .