

Brac University**Set: 01**

Semester: Fall 2022

Course No: CSE251

Course Title: Electronic Devices and Circuits

Section: 1 to 14


Midterm

Full Marks: 30

Time: 1 hour 30 minutes

Date: November 11, 2022

Answer **any 3 out of 4** questions. All the questions carry equal marks.

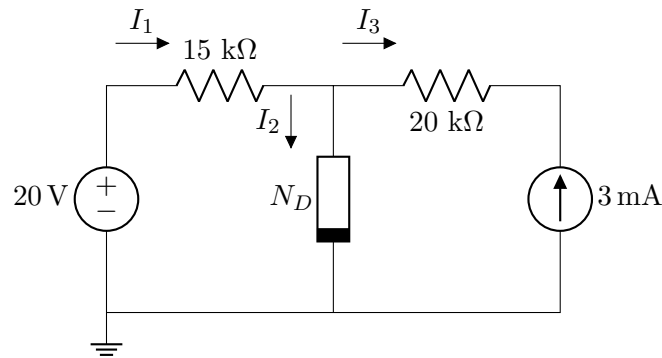Question 1 [CO1]**10**Figure 1: A circuit with a non-linear device N_D


- (a) **Draw** the IV characteristics of a voltage source $V_o = 10\text{ V}$ in series with a resistor $R = 15\text{ k}\Omega$. Also, **determine** the IV equation and **calculate** the slope, m . [1.5+1.5]
- (b) You are tasked to design a non-linear electronic device with following characteristics (here V_D is the voltage across the device and I_D is the current through the device):
- (i) for $-5\text{ mA} < I_D \leq -1\text{ mA}$, the device should behave like a voltage source with $V_o = -2\text{ V}$
 - (ii) for $-2\text{ V} < V_D \leq 3\text{ V}$, the I_D should increase linearly with V_D with a slope of 2 mA/V
 - (iii) for $3\text{ V} < V_D \leq 5\text{ V}$, the device should act like a current source. [**Hint**: calculate I_o from (ii)]

Draw the IV characteristics of the non-linear device with appropriate labelling. [1.5+0.5]

- (c) **Show** the alternative representation of the circuit in Fig 1 above. **Analyze** the alternative representation to **deduce** any two KVL equations and one KCL equation. [4]

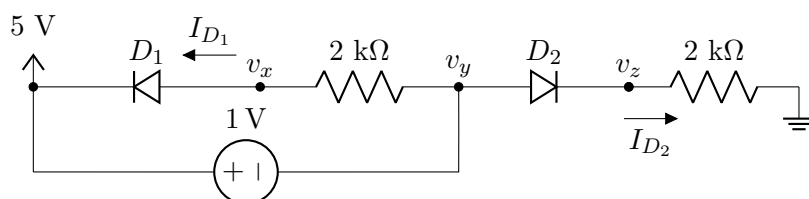
Question 2 [CO1]**7+3**

Analyze the circuit to find the values of I_{D1} , I_{D2} , v_x , v_y , and v_z . Use the diode's CVD Model with $V_{D0} = 0.5\text{ V}$. You must **validate** your assumptions. [**Hint**: Start by calculating the node voltages first]




Question 3 [CO2]


10

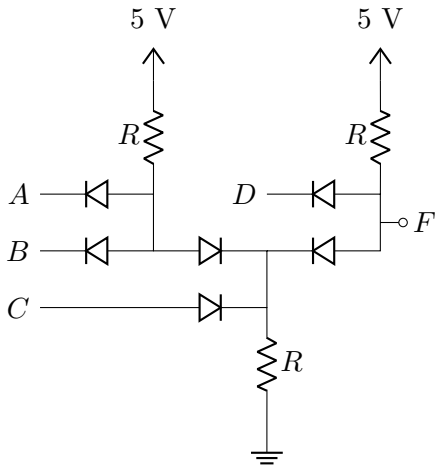

(a) Circuit-1

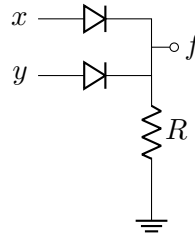

(b) Circuit-2

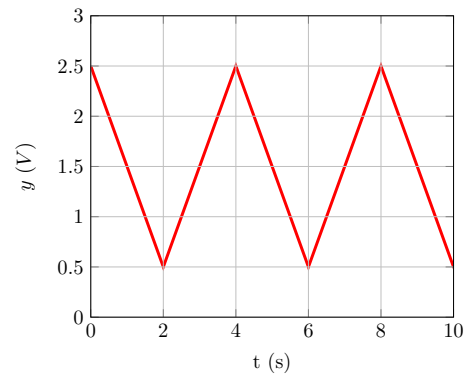

(c) Graph-1

For this question, assume all of the diodes are ideal.

- Analyze** Circuit-1 to find the logical expression of F in terms of boolean inputs A, B, C, D . [4]
- Design** a circuit to implement the logic function $F = (A + B).(C + D)$. Here “+” and “.” denotes logical OR and AND, respectively, and A, B, C, D are boolean inputs. [4]
- Analyze** the Circuit-2 to find the waveform (voltage vs time graph) of f assuming x and y are voltage signals, where $x = 1.5$ V and y has a waveform as shown in the Graph-1. [2]

Question 4 [CO2]

10

A voltage waveform $v_i = 8 \sin(100\pi t)$ V is fed into a rectifier with a load resistance $R = 10$ k Ω . Silicon diodes are used in this circuit for which the forward drop is $V_{D_0} = 0.8$ V. The output frequency of the rectifier is 100 Hz.

- Identify** the type of rectifier used (full-wave or half-wave). Give proper reasoning. [2]
- Show** the circuit with proper input and output labels. [2]
- Illustrate** the input and output waveforms in separate graphs. Label the graph and **indicate** the voltage levels properly. [2]
- Calculate** the DC value of the output. [1]

A capacitor is now added to reduce the fluctuation of the output voltage, which makes the peak to peak ripple voltage 5% of the maximum output voltage V_P .

- Deduce** is the value of the capacitor from the given data. [2]
- Calculate** the DC value of the output after adding the capacitor and **compare** the result with that found in part (d). [1]