

# ' Assignment - 01 '

Amirun Nahin

ID: 23201416

Sec: 07

Course: CSE251


Date: 08/07/2025

Semester: Summer 2025

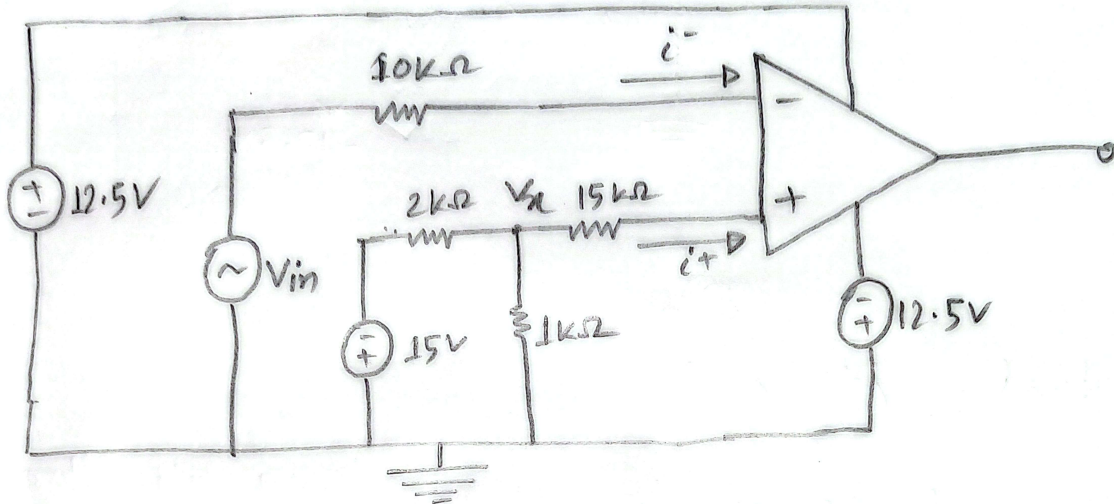
# Ans. to the que. no - 1

(a)


The given circuit with ground node at the bottom node,



At first, with ground node,

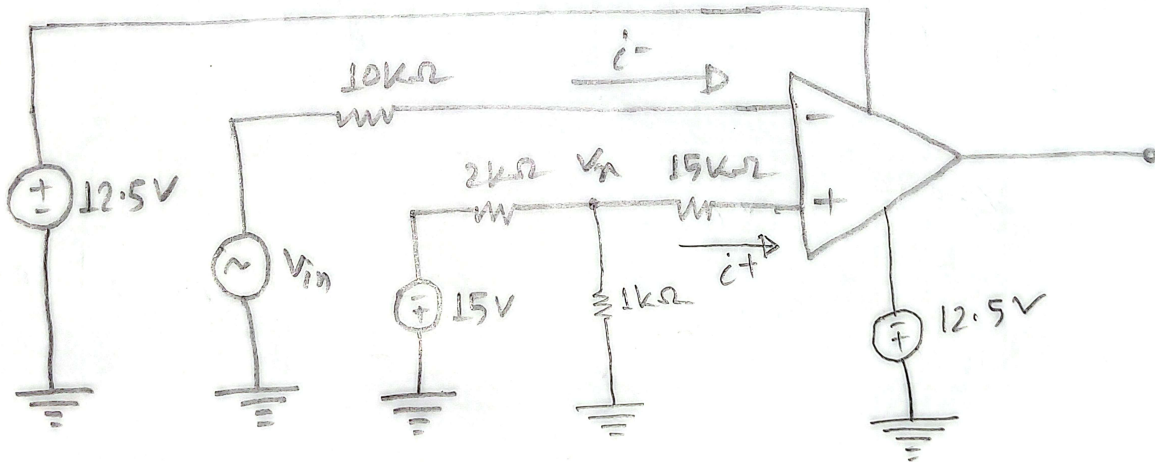

Finally,

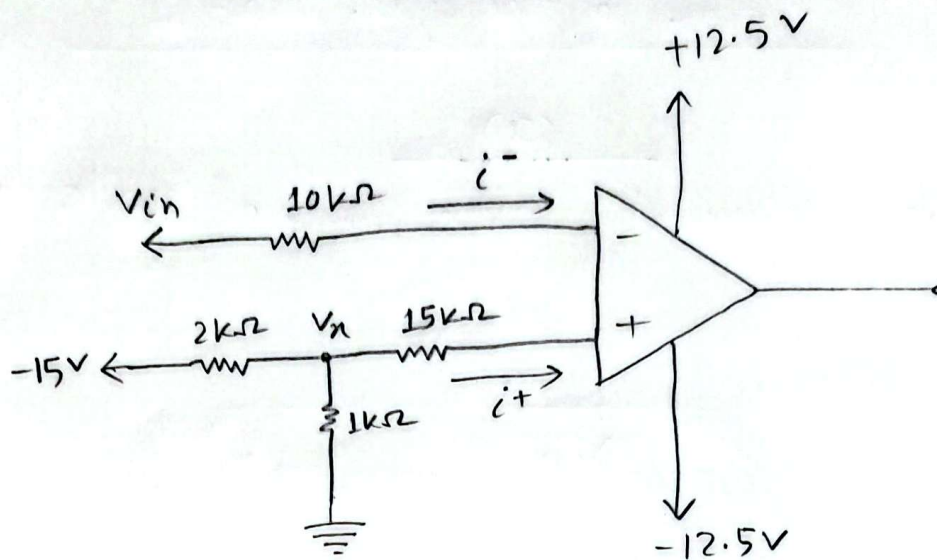

(b)

Given that,  $i^+ = 0 A$ .

So, KCL at  $V_n$  node, assuming all the currents are outgoing,

$$\frac{V_n - (-15)}{2} + \frac{V_n - 0}{1} = 0$$

$$\Rightarrow \frac{V_n + 15}{2} + V_n = 0$$

So, This is the KCL equation at node  $V_n$ .

Now,

$$\frac{V_n + 15 + 2V_n}{2} = 0$$

$$\Rightarrow 3V_n = -15$$

$$\Rightarrow V_n = -5 V$$

$$V_n = -5 V$$

(Ans.)

(c)

From the equation of part (b), we see that as the  $i^+ = 0$ , the  $2k\Omega$  and  $1k\Omega$  resistors are in series. Hence, the equation that we have is the same as 'Voltage Divider Rule' equation on  $1k\Omega$  resistor.

So, we can say that, this equation is similar to Voltage Divider Rule equation.


(Ans.)



Ans. to the que. no - 02

(a)

Given circuit,

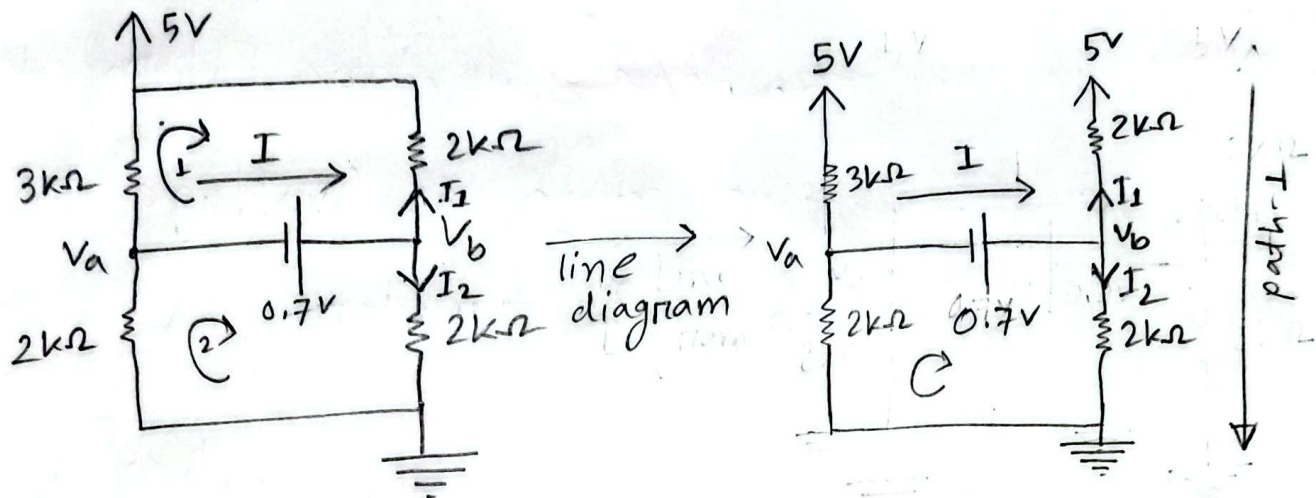

KVL at path-1,

$$-2I_1 + 2I_2 = 5 - 0$$

$$\Rightarrow -2I_1 + 2I_2 = 5$$

Now, KVL at loop,

$$-2I_2 - 0.7 + 2I_2 = 0$$

$$\Rightarrow I_2 = 0.175 \text{ mA}$$

$$\text{So, } -2I_1 + 2I_2 = 5$$

$$\Rightarrow 2I_1 = 2I_2 - 5$$

$$\Rightarrow I_1 = \frac{2I_2 - 5}{2}$$

$$\Rightarrow I_1 = -2.325 \text{ mA}$$

KCL at  $V_b$ ,

$$I = I_1 + I_2$$

$$= -2.325 + 0.175$$

$$= -2.15 \text{ mA}$$

Now,

$$\therefore \frac{V_b - 0}{2} = I_2 = 0.175$$

$$\Rightarrow V_b = 2 \times 0.175 = 0.35 \text{ V}$$

again,

$$\frac{V_a - 0}{2} = -I_2$$

$$\Rightarrow V_a = -2I_2$$

$$\Rightarrow V_a = -2 \times 0.175$$

$$\Rightarrow V_a = -0.35 \text{ V}$$

$$\text{So, } V_a = -0.35 \text{ V}$$


$$V_b = 0.35 \text{ V}$$

$$I = -2.15 \text{ mA}$$

(Ans.)

(b)

given circuit,

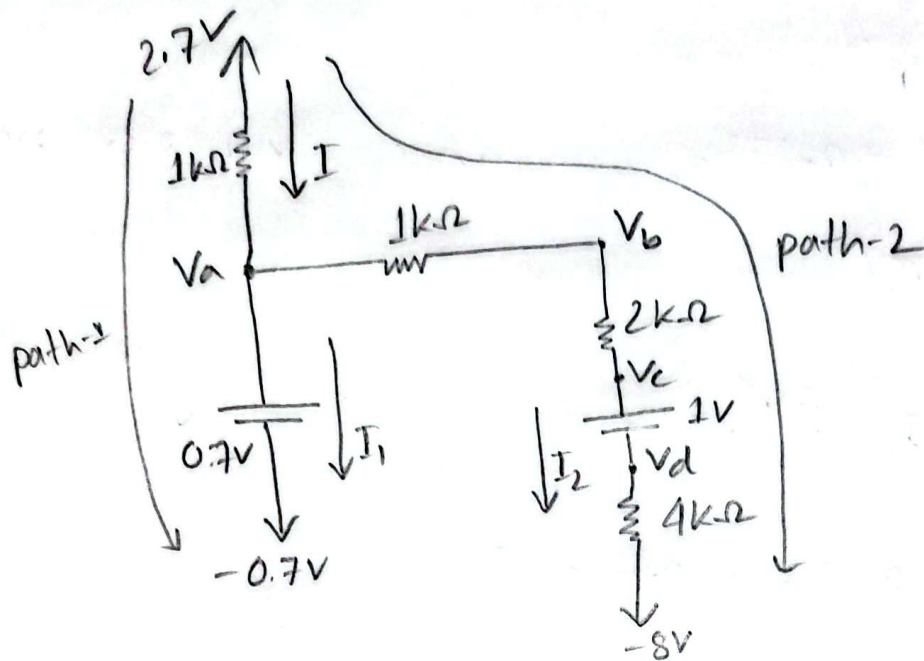

KVL at path-1,

$$1I + 0.7 = 2.7 - (-0.7)$$

$$\Rightarrow I = 2.7 \text{ mA}$$

KVL at path-2,

$$I + I_2 + 2I_2 + 1 + 4I_2 = 2.7 - (-8)$$

$$\Rightarrow I + 7I_2 = 9.7$$

$$\Rightarrow 7I_2 = 9.7 - I = 9.7 - 2.7$$

$$\Rightarrow 7I_2 = 7$$

$$\Rightarrow I_2 = 1 \text{ mA}$$

Now, KCL at  $V_a$ ,

$$I = I_1 + I_2$$

$$\Rightarrow I_1 = I - I_2$$

$$\text{So, } I_1 = 2.7 - 1 \\ = 1.7 \text{ mA}$$

Again,  $V_a, V_b, V_c, V_d$  are 4 unknown voltages. So,

for  $V_a$ ,

$$\frac{V_a - 2.7}{1} = -1$$

$$\Rightarrow V_a - 2.7 = -2.7$$

$$\Rightarrow V_a = 0 \text{ V}$$

for  $V_b$ ,

$$\frac{V_a - V_b}{1} = I_2$$

$$\Rightarrow V_a - V_b = 1$$

$$\Rightarrow V_b = -1 \text{ V}$$

for  $V_c$ ,

$$\frac{V_b - V_c}{2} = I_2$$

$$\Rightarrow V_b - V_c = 2$$

$$\Rightarrow -V_c = 3$$

$$\Rightarrow V_c = -3 \text{ V}$$



for  $V_d$ ,

$$\frac{V_d - (-8)}{4} = 1$$

$$\Rightarrow V_d + 8 = 4$$

$$\Rightarrow V_d = -4 \text{ V}$$

Finally,

$$I = 2.7 \text{ mA}$$

$$I_1 = 1.7 \text{ mA}$$

$$I_2 = 1 \text{ mA}$$

$$V_a = 0 \text{ V}$$

$$V_b = -1 \text{ V}$$

$$V_c = -3 \text{ V}$$

$$V_d = -4 \text{ V}$$

(Ans.)

Ans. to the que. no-03

Given,

$$f = \frac{d^2x}{dt^2} + 10y + \int (10z - 9) dt$$


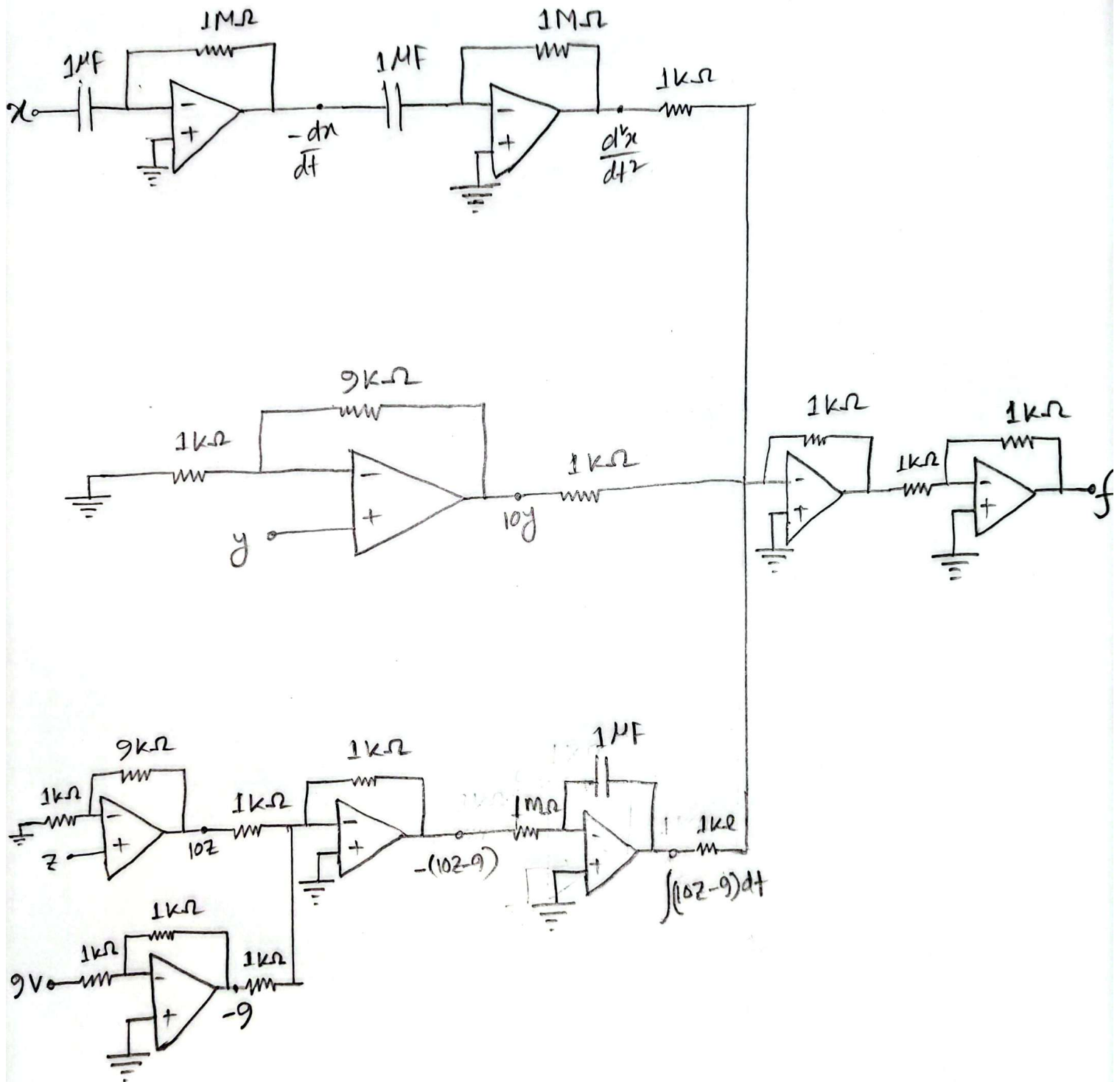


fig: circuit for function f

# Ans. to the que. no-4


Firstly,

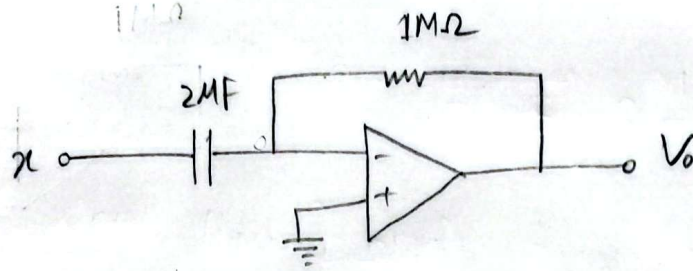

$$\therefore V_o = -(2 \times 10^{-6} \times 1 \times 10^6) \times \frac{dx}{dt}$$

$$= -2 \cdot \frac{dx}{dt}$$


again,

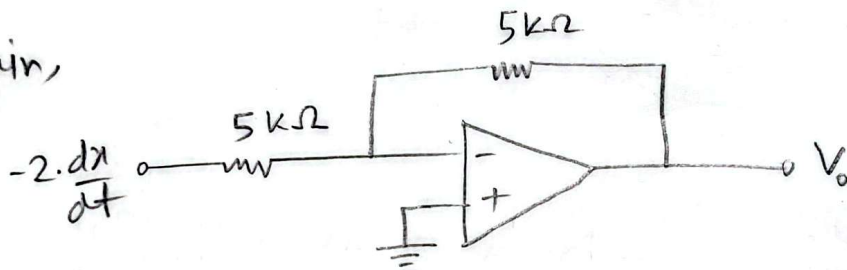

$$\therefore V_o = -\frac{5}{5} \times -2 \cdot \frac{dx}{dt}$$


$$= 2 \cdot \frac{dx}{dt}$$

Then,

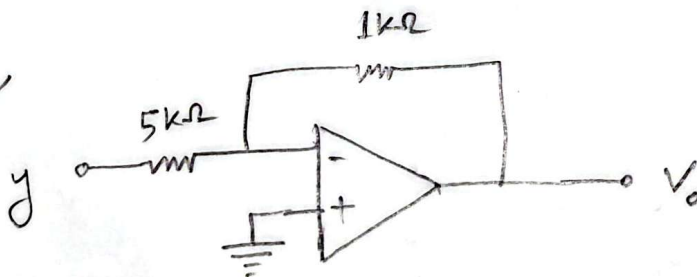

$$\therefore V_o = -\frac{1}{5} \cdot y$$


again,

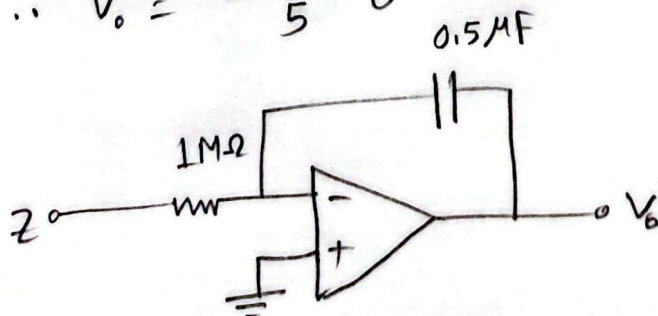

$$\therefore V_0 = \frac{-1}{(0.5 \times 10^{-6} \times 1 \times 10^6)} \int z dt$$

$$= -2 \int z dt$$

Lastly,

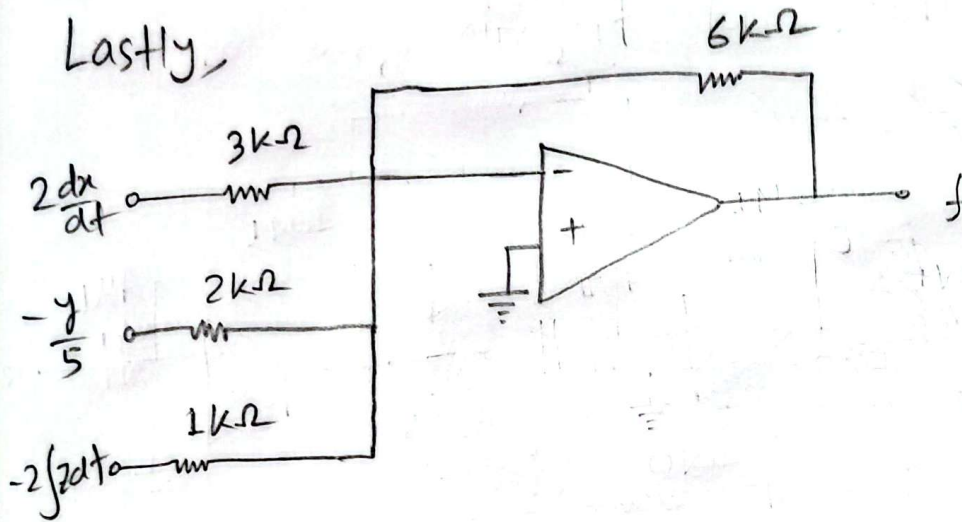

$$\therefore f = -6 \times \left\{ \frac{2 \frac{dx}{dt}}{3} + \frac{\left(-\frac{y}{5}\right)}{2} + \frac{\left(-2 \int z dt\right)}{1} \right\}$$

$$= -4 \frac{dx}{dt} + \frac{3y}{5} + 12 \int z dt$$

$$\text{So, } f = 12 \int z dt + \frac{3y}{5} - 4 \frac{dx}{dt}$$

(Ans.)