

Practice Problem Set 2.2

CSE251 - Electronic Devices and Circuits

CLOSE LOOP CONFIGURATIONS OF OP-AMP

Inv and Non-inv Amplifiers, Inv Adder, Integrator and
Differentiator, Function Implementation, and VTC

For every problem, assume the op-amps to be ideal having infinite open loop gain, zero input currents, and zero output resistance.

[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)

Problem 1

- Design circuits using op-amps to implement the following operational functions. x , y , and z are the inputs and f is the output.

I. $f = -4x + 5y$

II. $f = -7x + \frac{d}{dt}y$

III. $f = \frac{3}{4}x + 7y - \frac{d}{dt}z$

IV. $f = -7 \int x dt + \frac{4}{3}y - 3 \frac{d}{dt}z$

V. $f = \int (6x - y) dt + 3 \frac{d^2}{dt^2}z$

VI. $f = \int (6x - 3 \frac{d^2y}{dt^2}) dt - 3 \frac{dz}{dt}$

VII. $f = \frac{d}{dt} \left(3x - \frac{3}{2} \int y dt \right) + \int 4z dt$

VIII. ** $f = -\frac{1}{3} \int x dt + 2 \ln y + 4z$

IX. ** $f = -3 \frac{d}{dt}x + 2e^y + 4z$

X. ** $f = xy/z$

Note: Problems marked with an asterisk (**) are a bit more advanced for this course. However, attempting them can help you develop a stronger grasp of the topic.

Problem 2


- I. Using not more than two op-amps, design a circuit to implement the following expression. v_1 , v_2 , and v_3 are the inputs and v_o is the output.

$$-v_o = \frac{v_3 - v_1}{5} + \frac{v_1 - v_2}{2}$$

- II. Design a circuit that will average three voltages.



Problem 3

- Prove that the following circuit is a subtractor which produces an output equal to the difference between v_2 and v_1 .

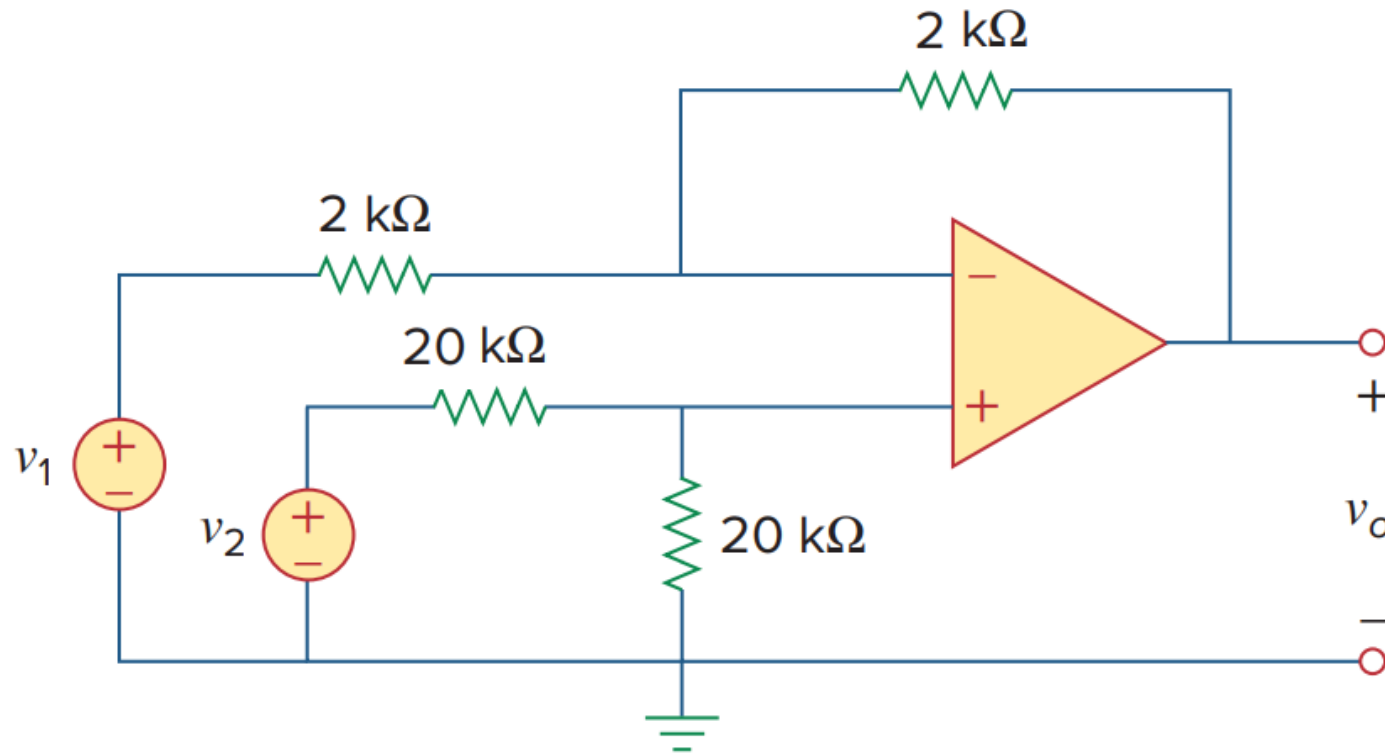

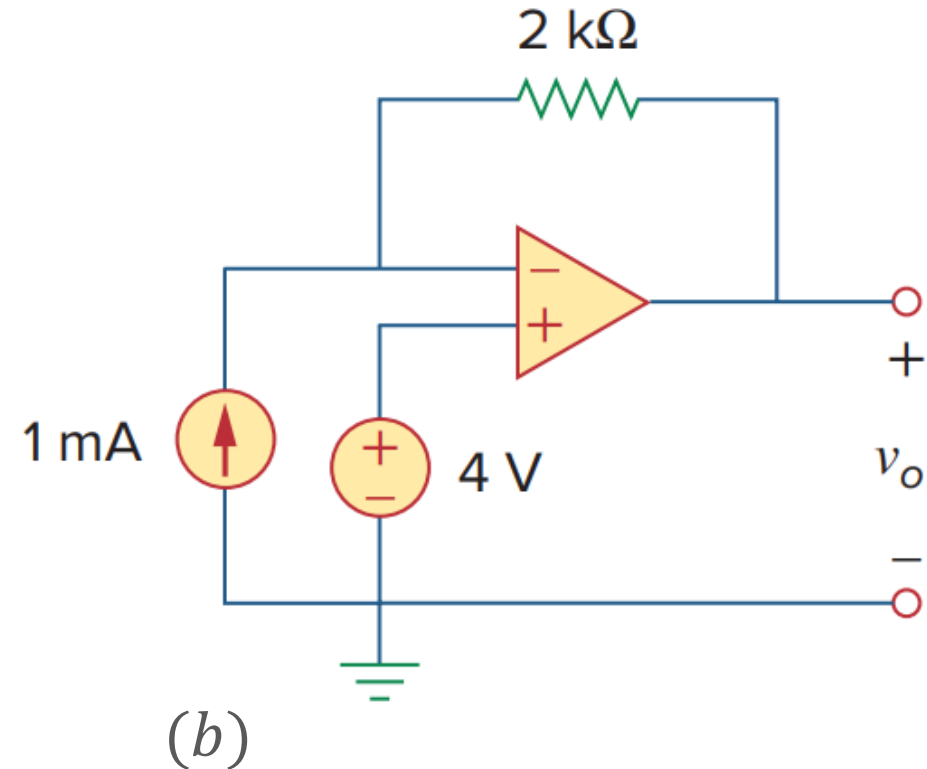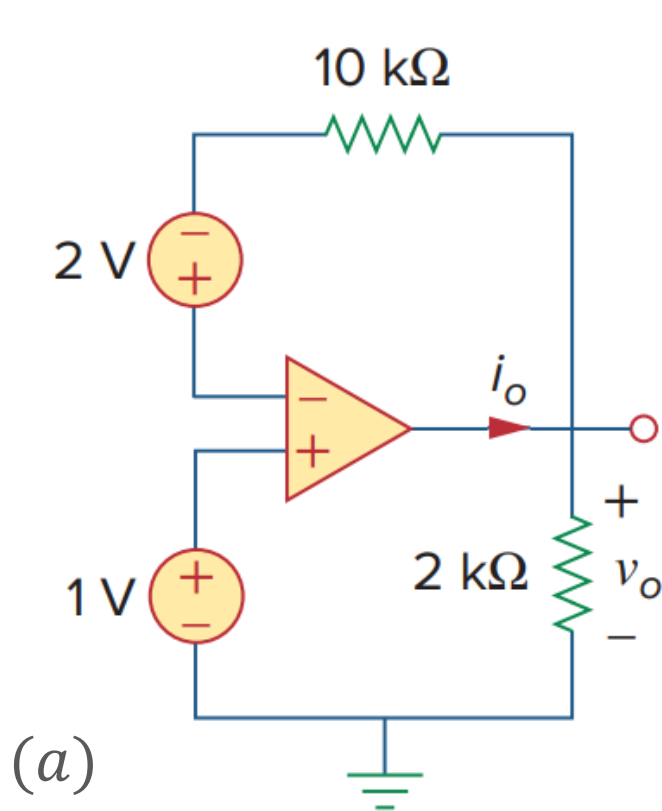Problem 4



- Determine v_o and i_o for the circuits shown below.



Ans: (a) $v_o = -1\text{ V}$, $i_o = -0.5\text{ mA}$; (b) $v_o = 2\text{ V}$

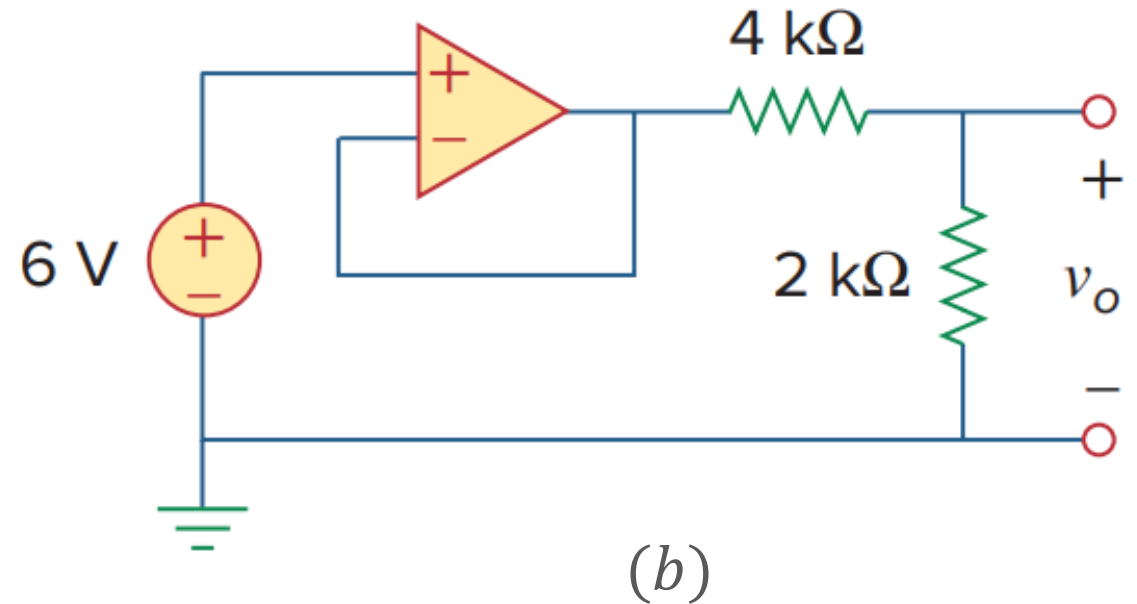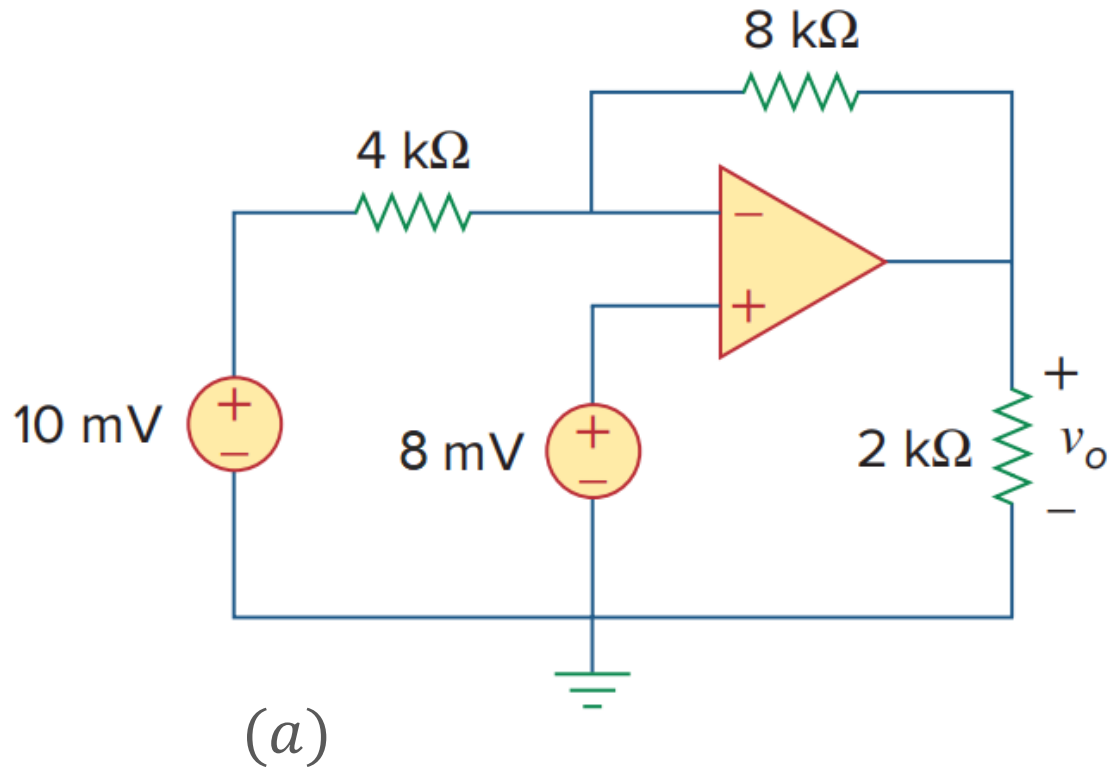Problem 5


- For the circuits shown below, determine v_o .



Ans: (a) 4 mV; (b) 2 V

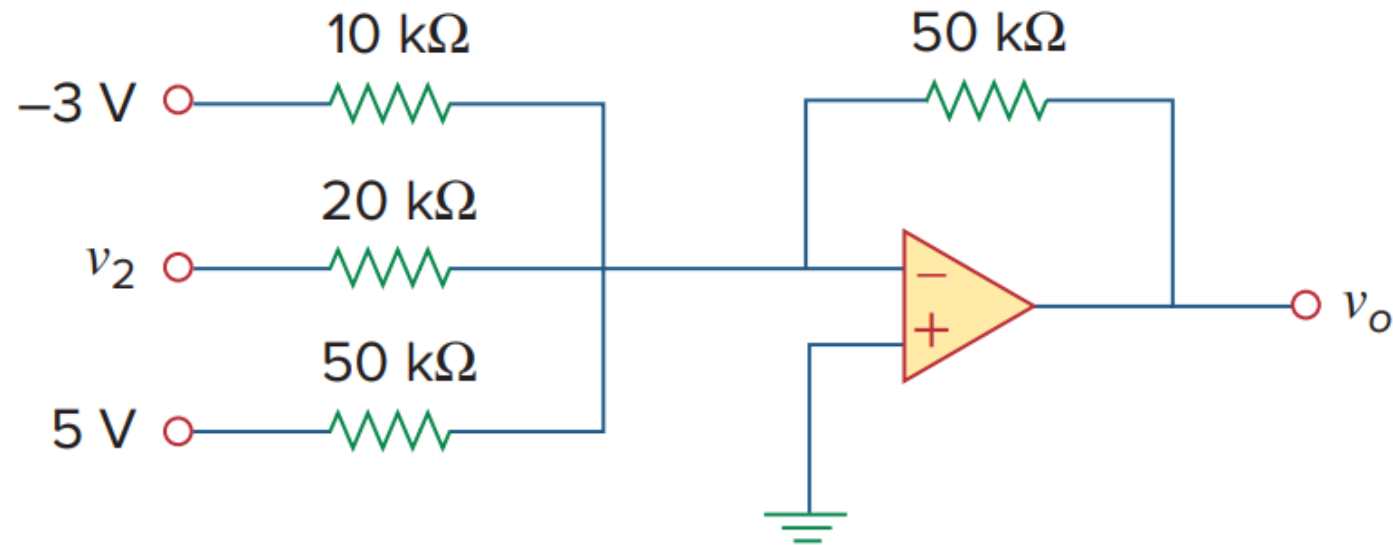Problem 6


- Determine the value of v_2 in order to make $v_o = -16.5\text{ V}$.



Ans: $v_2 = 10.6\text{ V}$

Problem 7


- Determine v_o from the circuit shown.

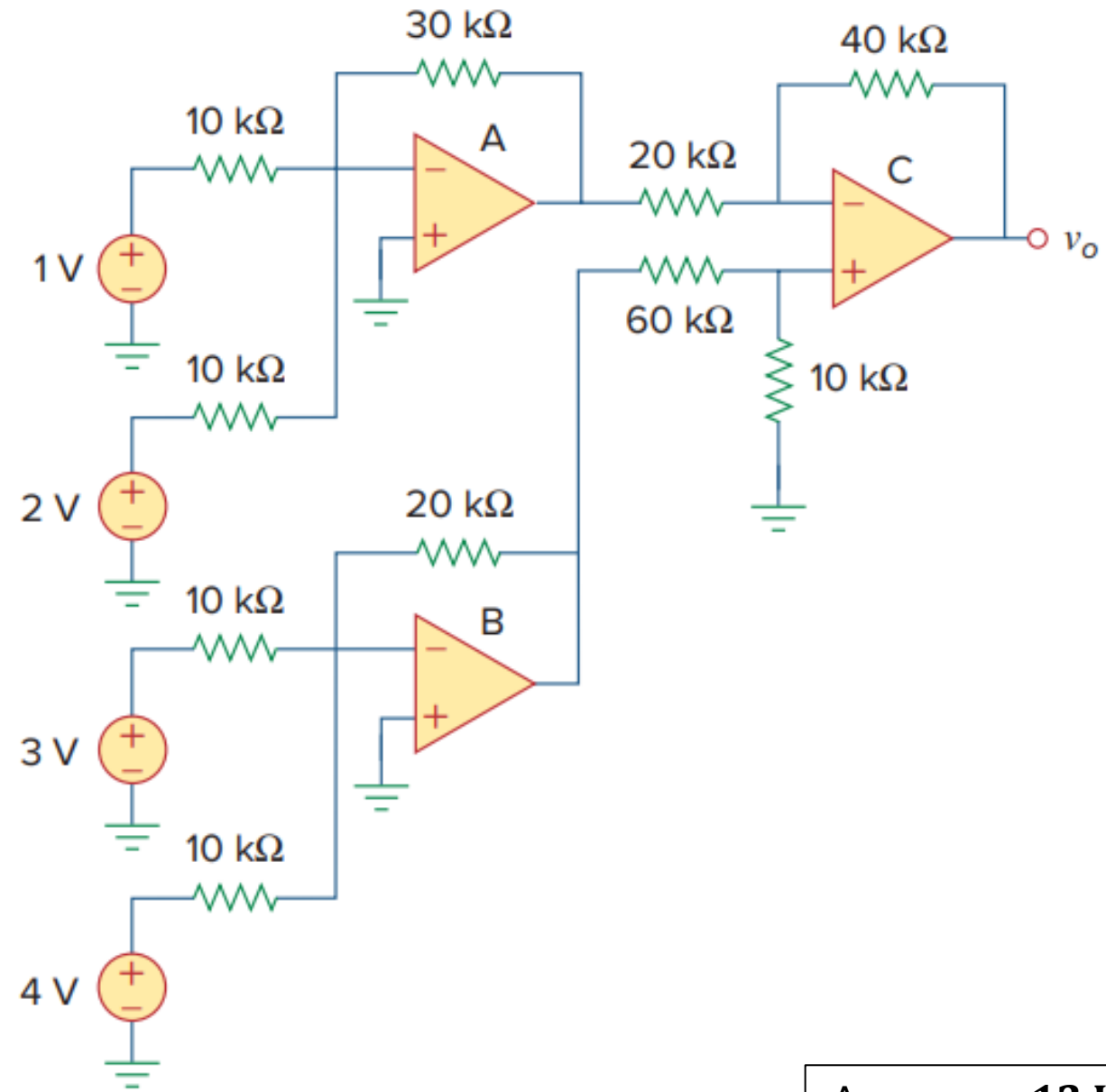

Ans: $v_o = 12 V$

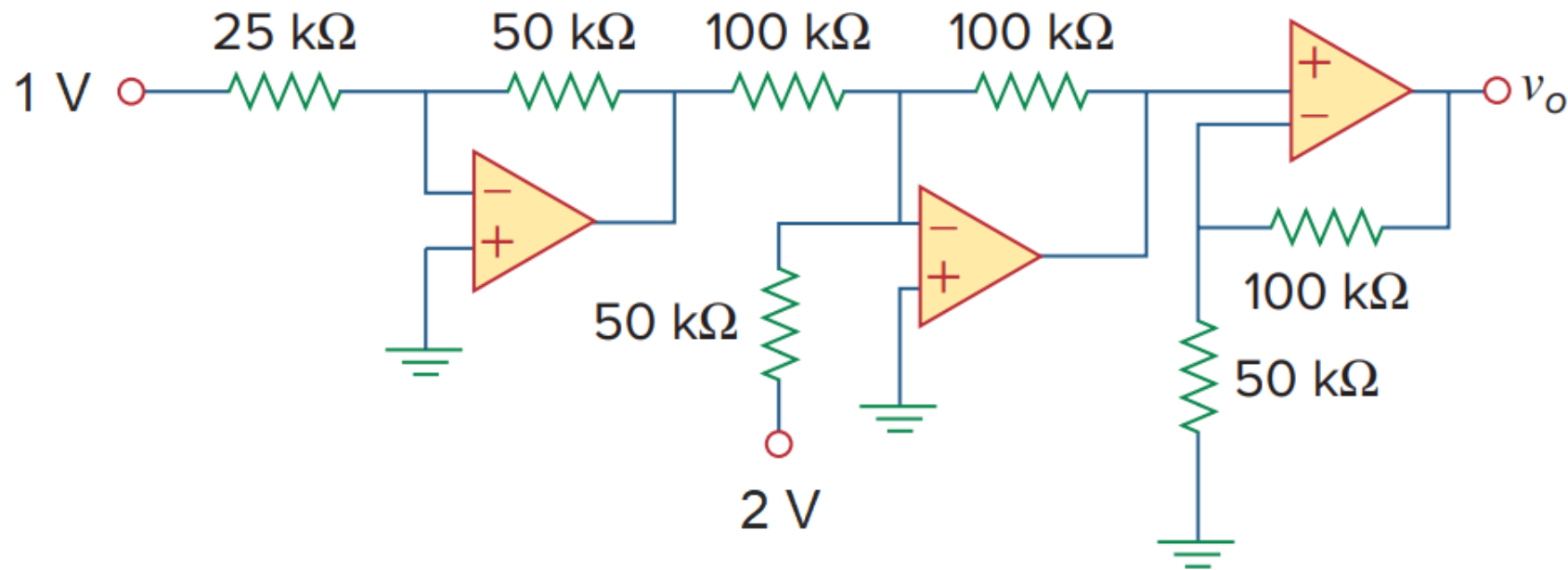Problem 8


- Determine v_o from the circuit shown below.



Ans: $v_o = -6 \text{ V}$

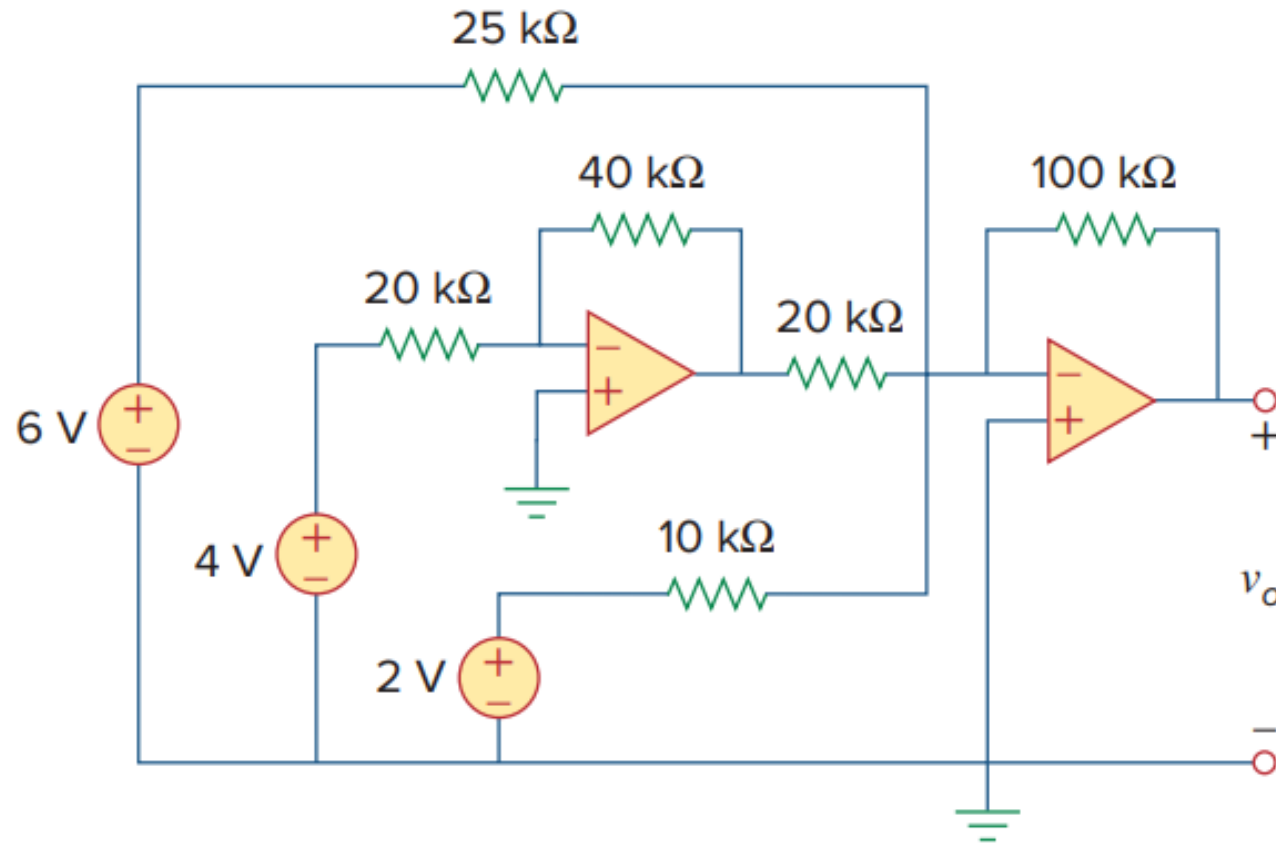Problem 9


- Determine v_o from the circuit shown below.



Ans: $v_o = -4 \text{ V}$

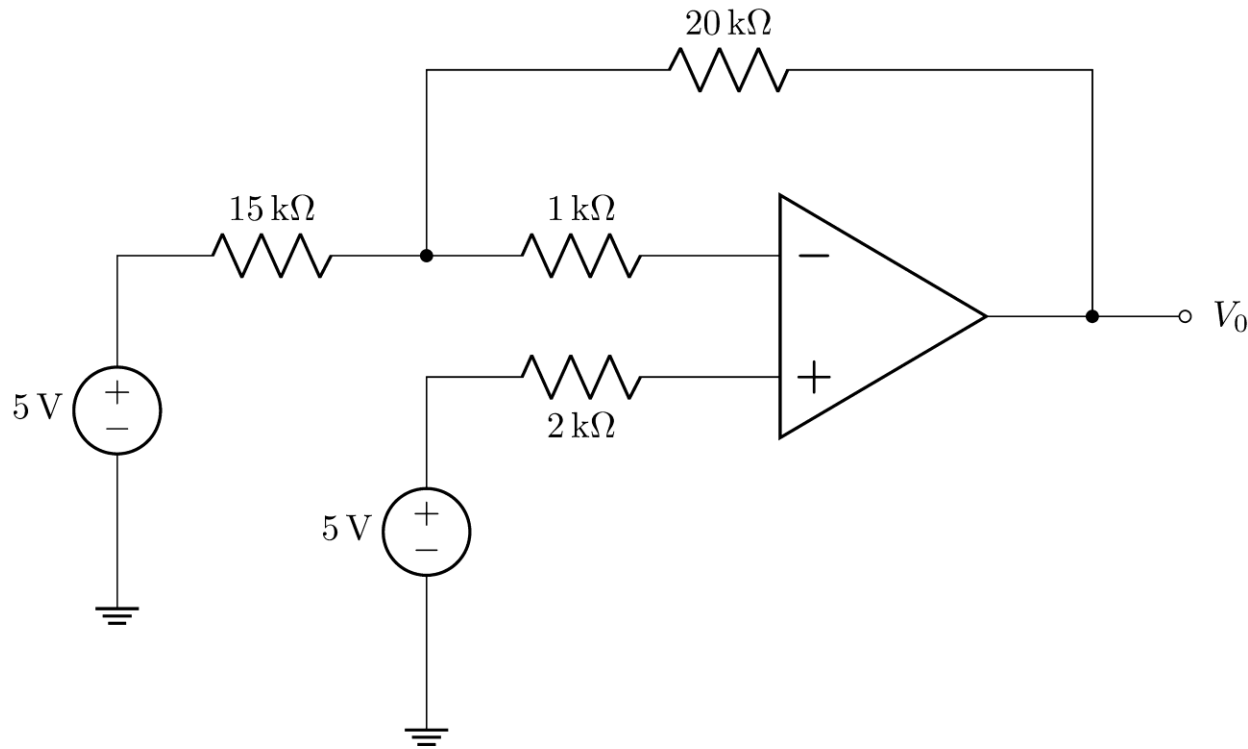Problem 10


- Determine V_o for the circuit shown below.



Ans: $V_o = 5V$

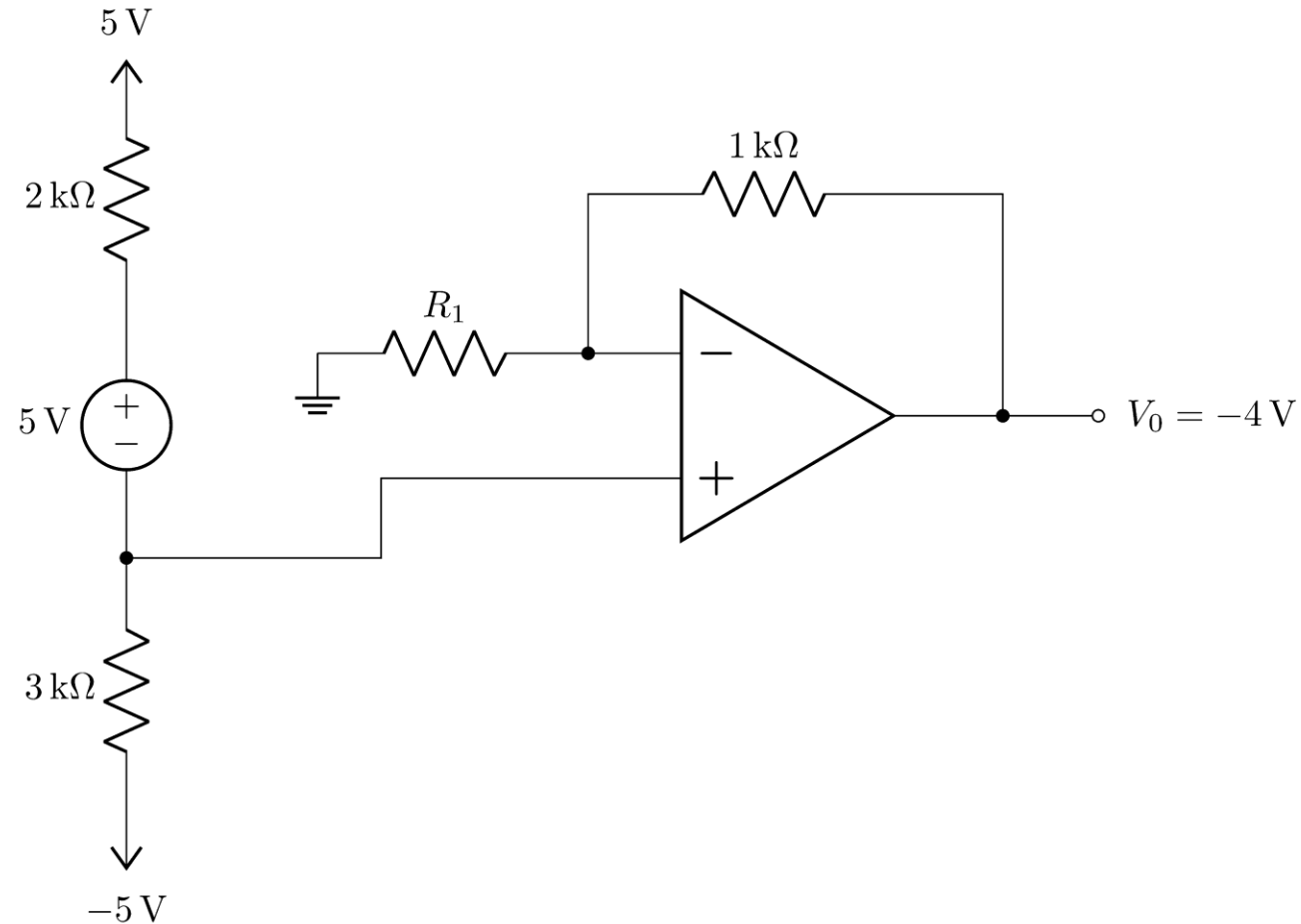Problem 11


- Determine R_1 for the circuit shown below.



Ans: $R_1 = 1\text{ k}\Omega$

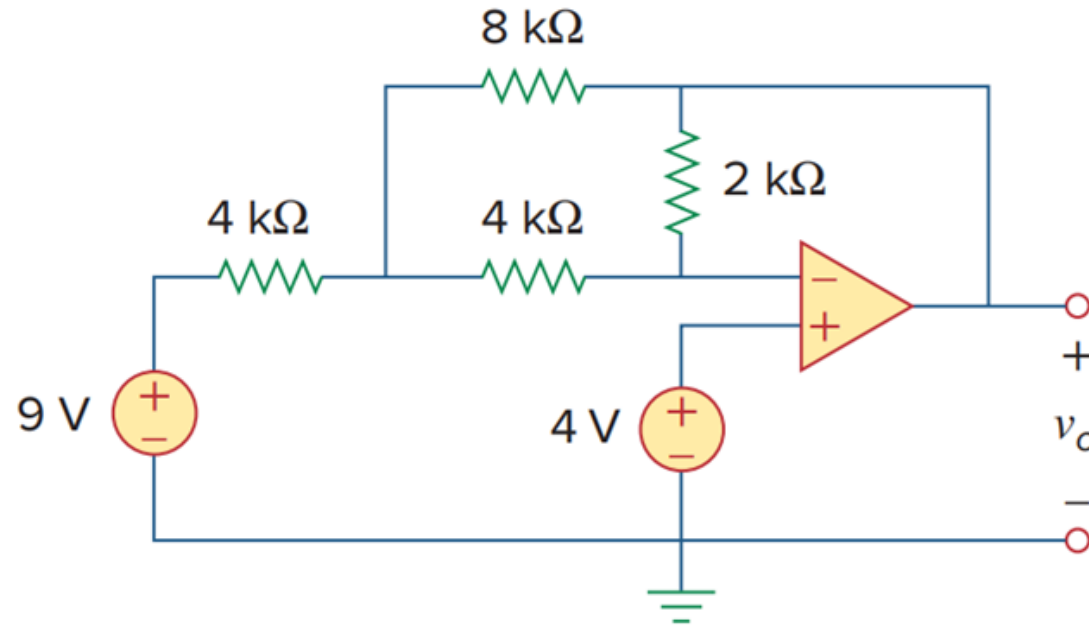Problem 12**

- Determine v_o for the circuits shown below. [Hint: avoid KCL at V_o as op-amp's output current is not known]




Ans: (a) $v_o = 3.09 \text{ V}$

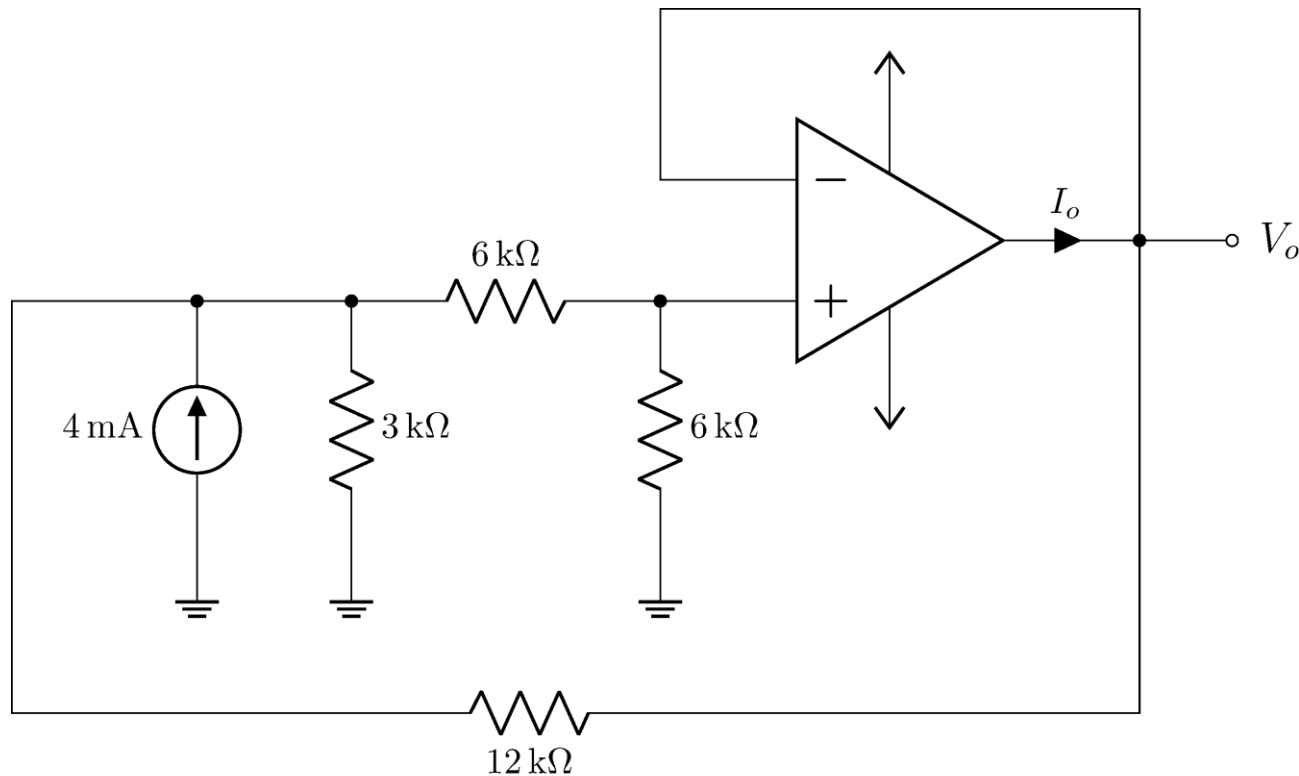Problem 13

- Determine V_o and I_o for the circuit shown below.

[Hint: avoid KCL at V_o as the op-amp's output current is not known]




Ans: $V_o = 4.36 \text{ V}$

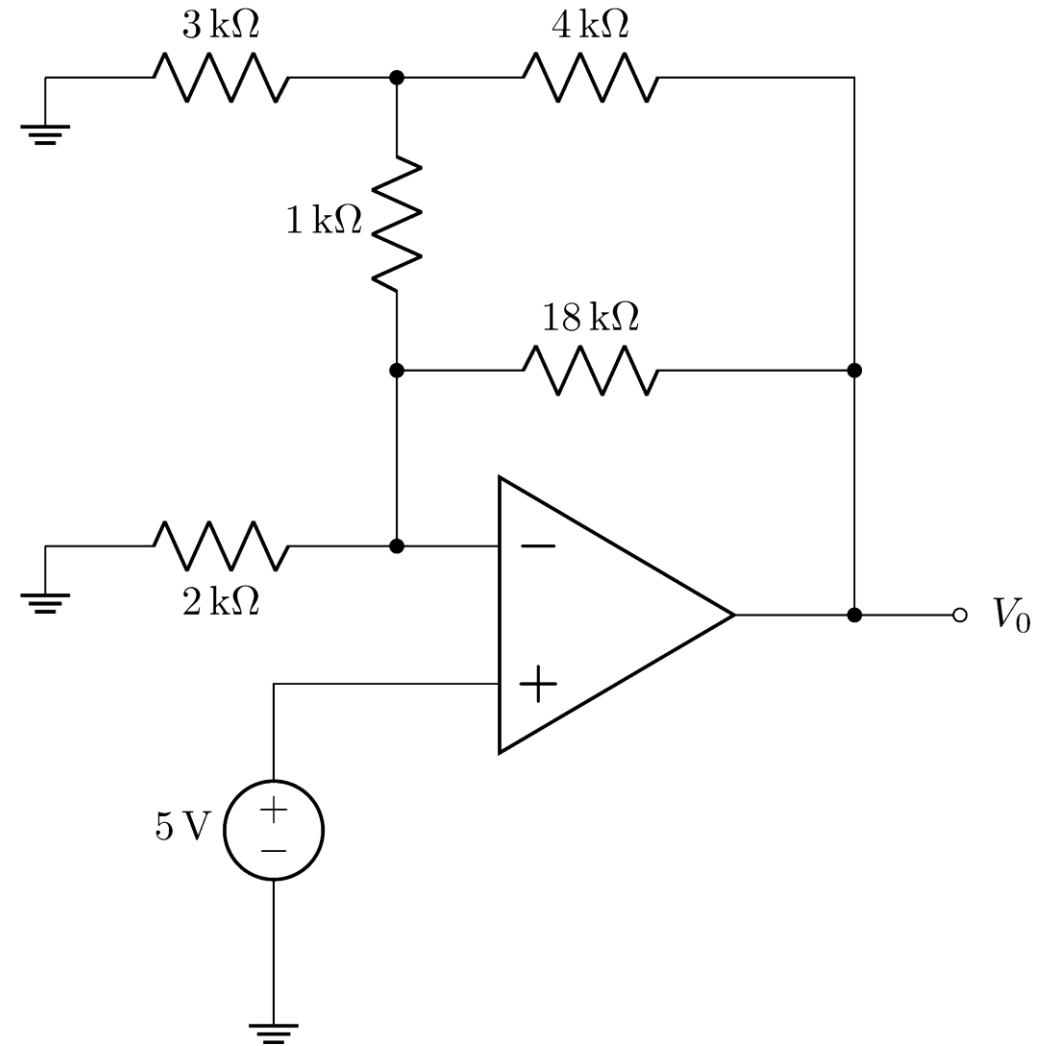Problem 14**

- Determine V_o and I_o for the circuit shown below.


[Hint: avoid KCL at V_o as the op-amp's output current is not known]



Ans: $V_o = 10.4 \text{ V}$

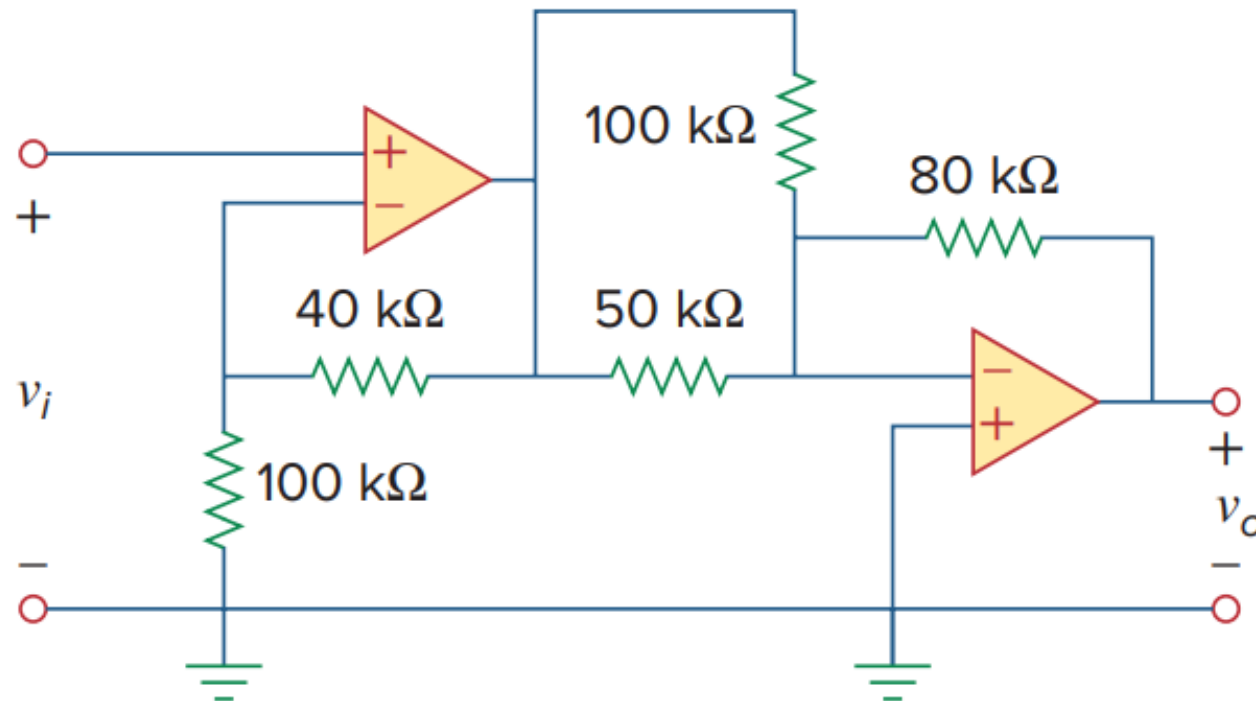Problem 15**

- Determine the gain (v_o/v_i) from the circuit shown below.




Ans: $v_o/v_i = 3.36$

Problem 16**

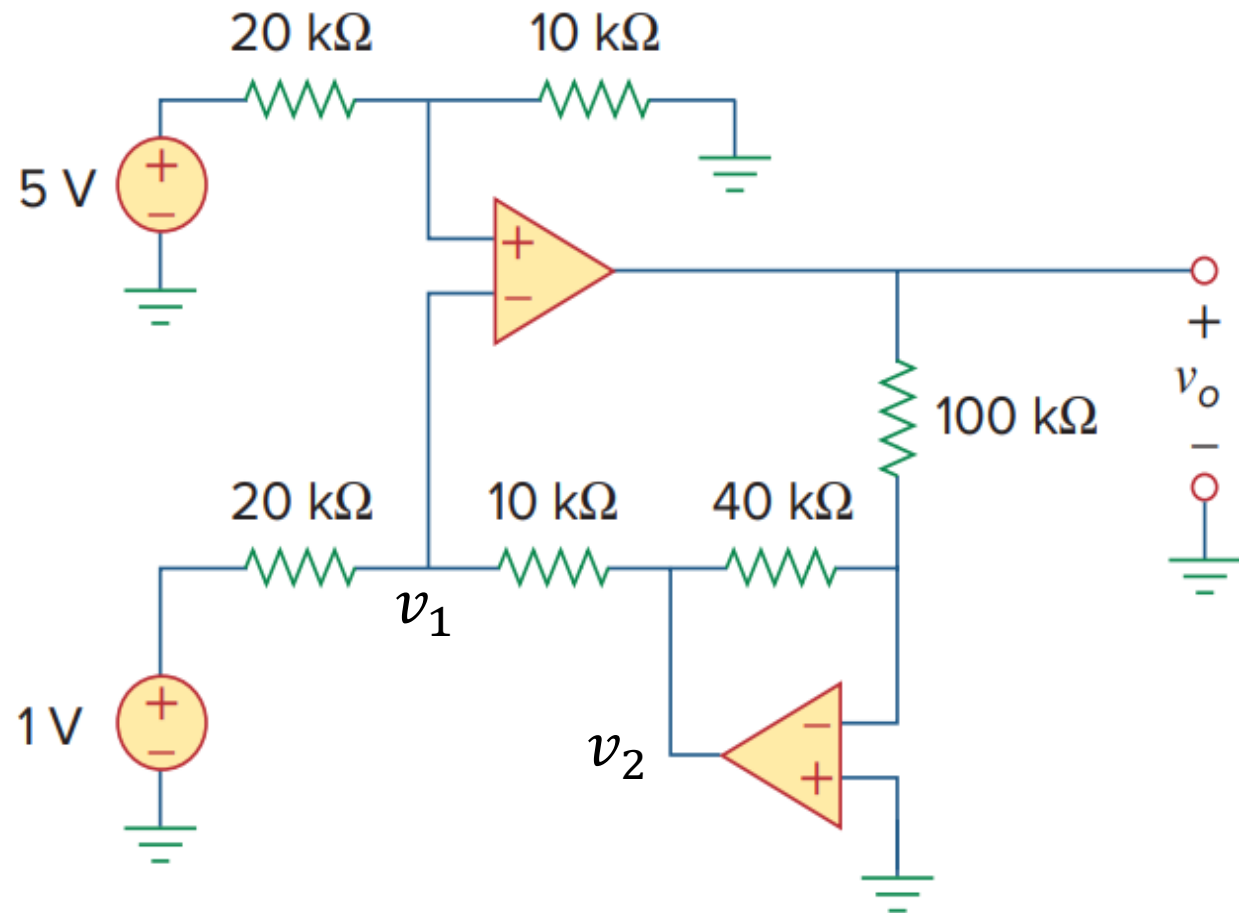- I. Determine v_1 .
- II. Determine v_2 and v_o .


[Hint: avoid KCL at v_o and v_2 as the op-amps' output currents are not known]



Ans: $v_1 = 5/3 \text{ V}$, $v_2 = 2 \text{ V}$, $v_o = -5 \text{ V}$

Problem 17


- Determine V_o .

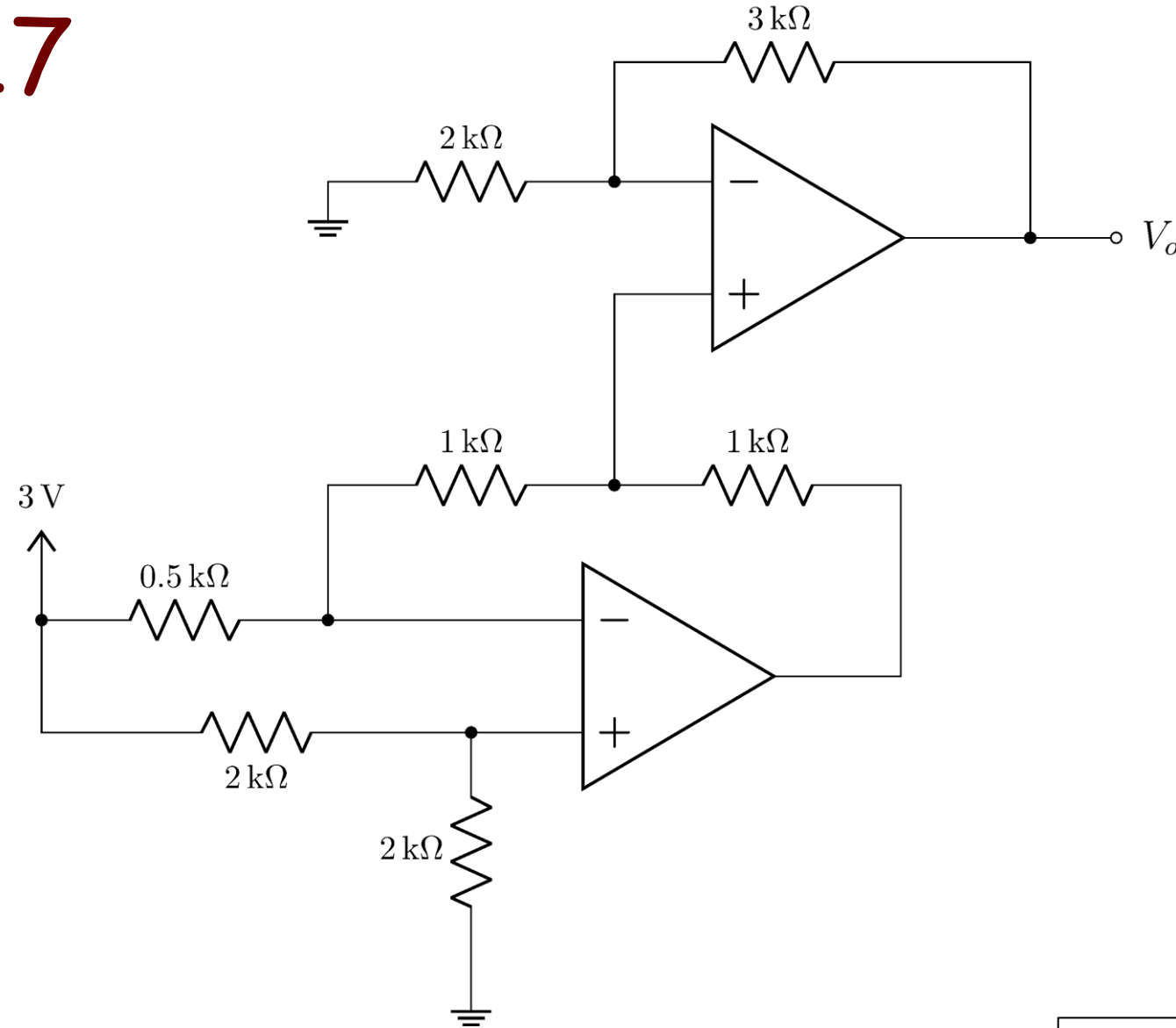

Ans: $V_o = -3.75 \text{ V}$

Problem 18**



- Determine v_o .

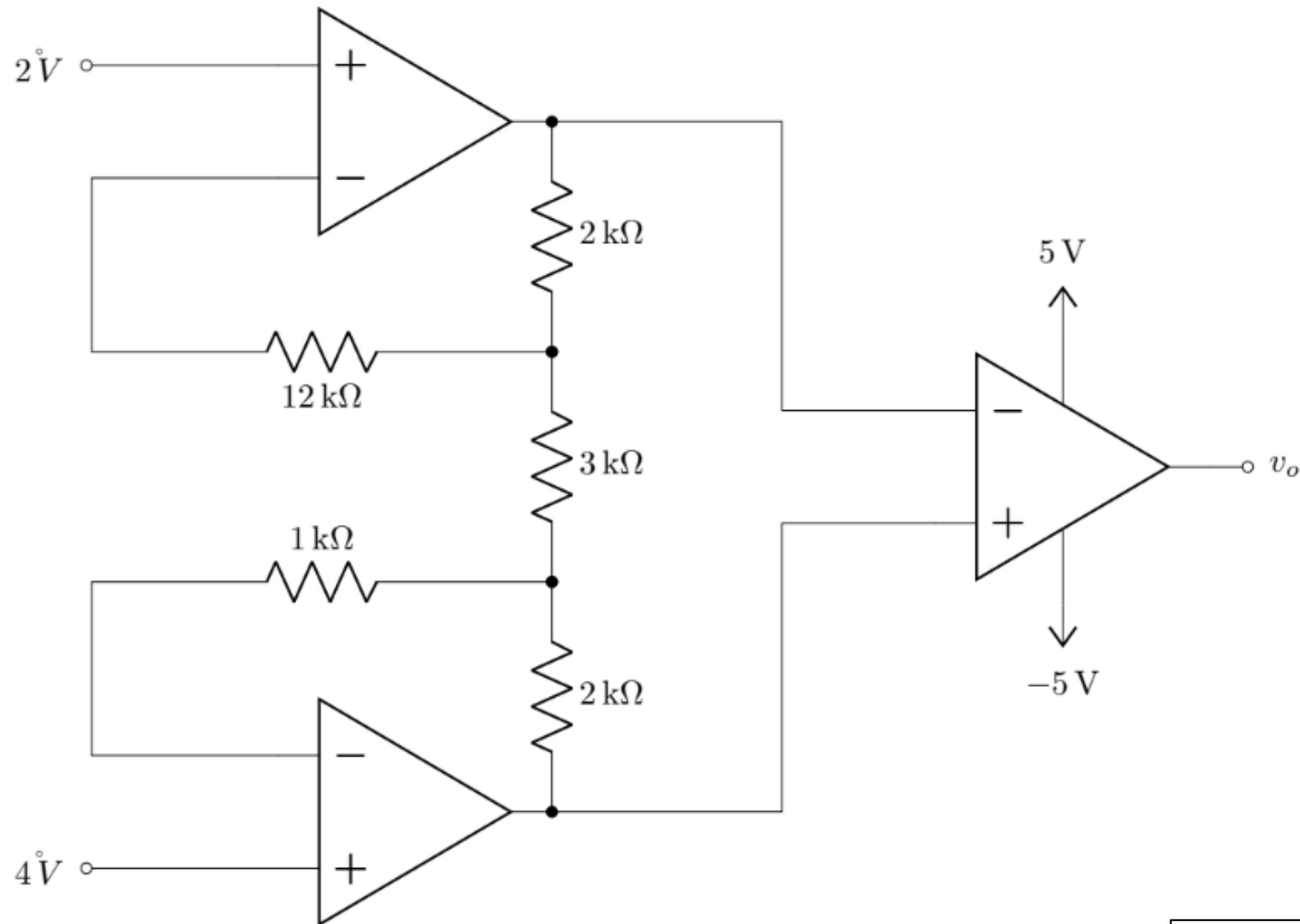

Ans: $v_o = 5V$



Problem 19

- Sketch v_o vs. t , if v_i is as shown in the following plot.

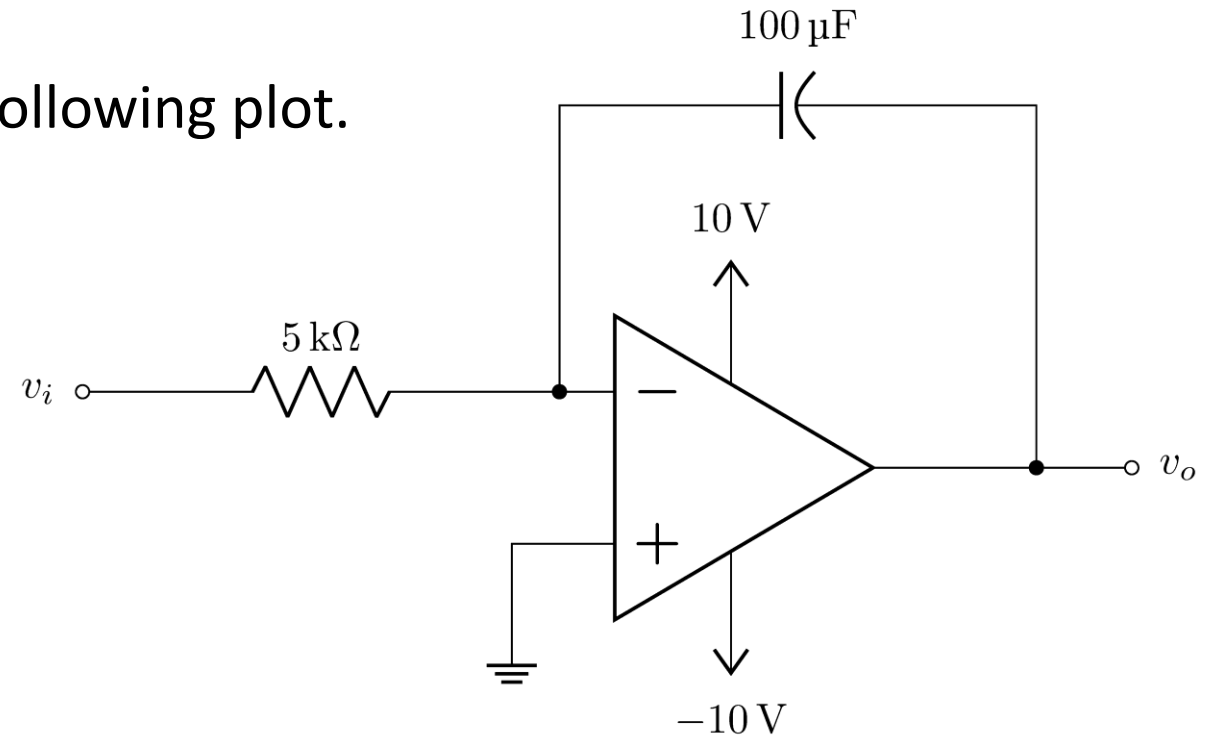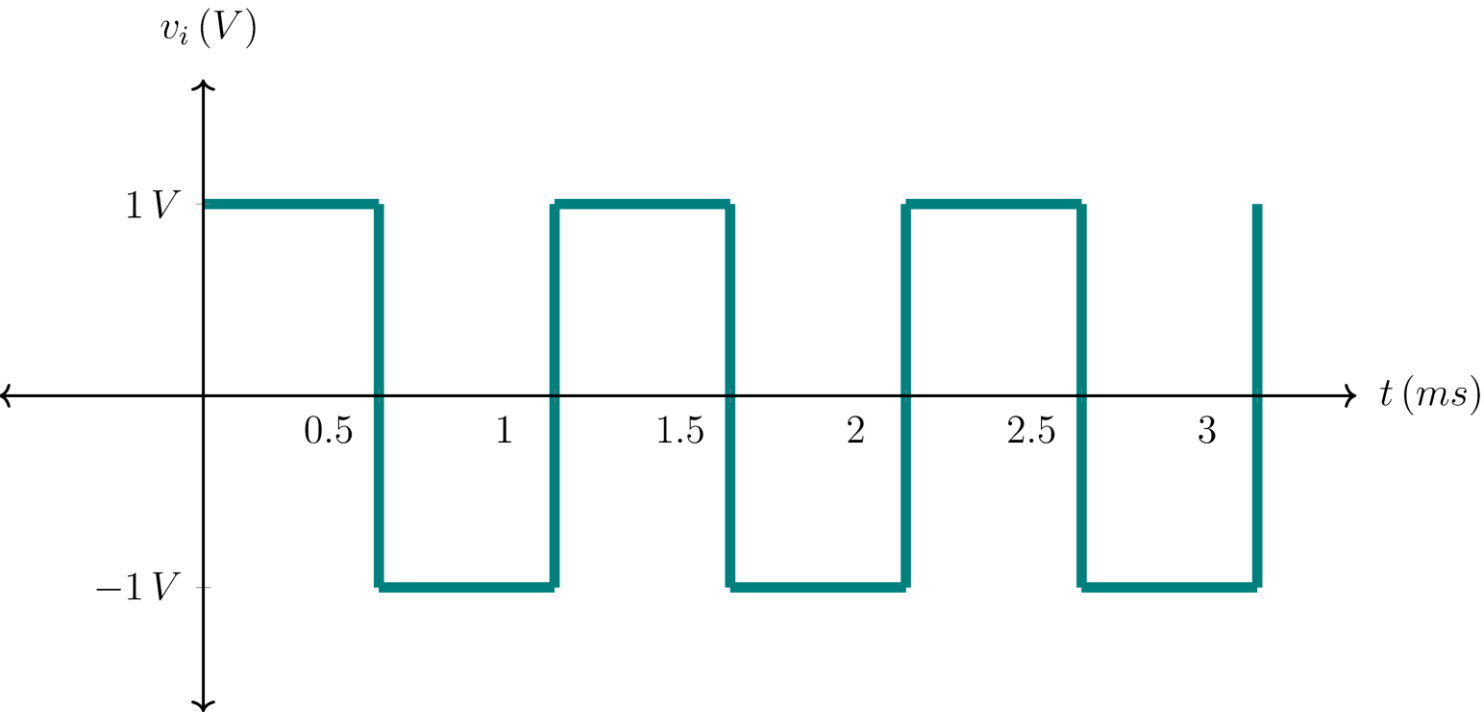



Problem 20

- Sketch v_o vs. t , if v_i is as shown in the following plot. If the bias voltages are $+6\text{ V}$ and -6 V , what will the graph look like.

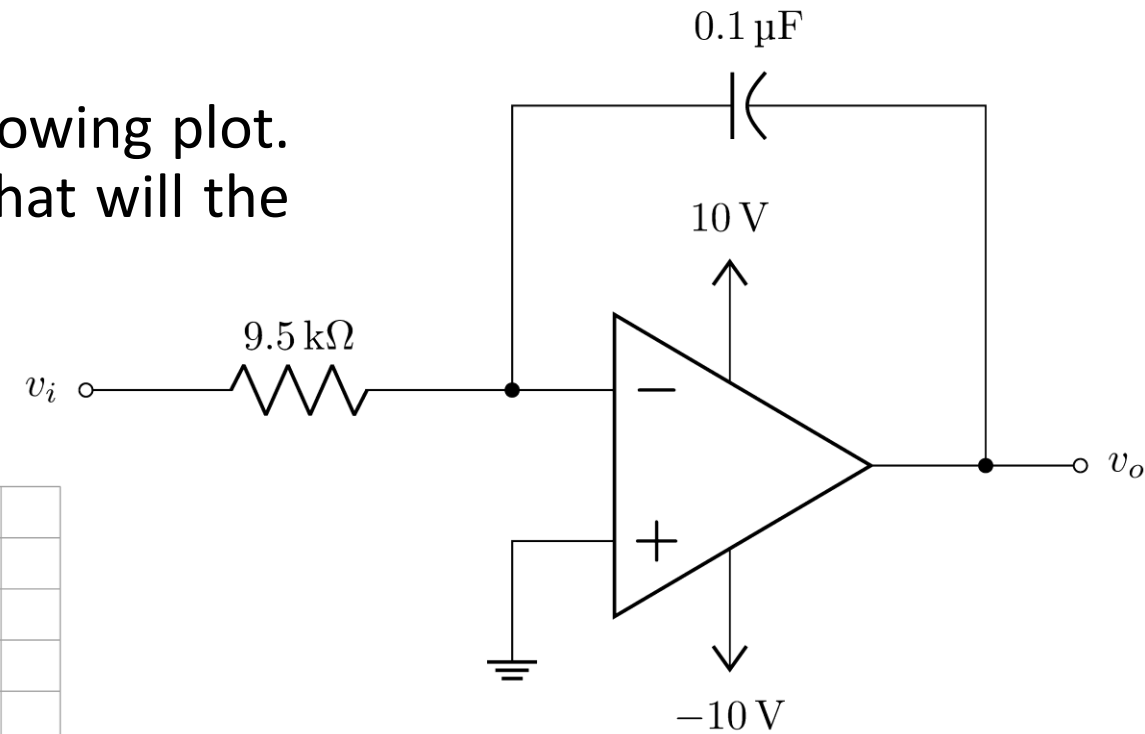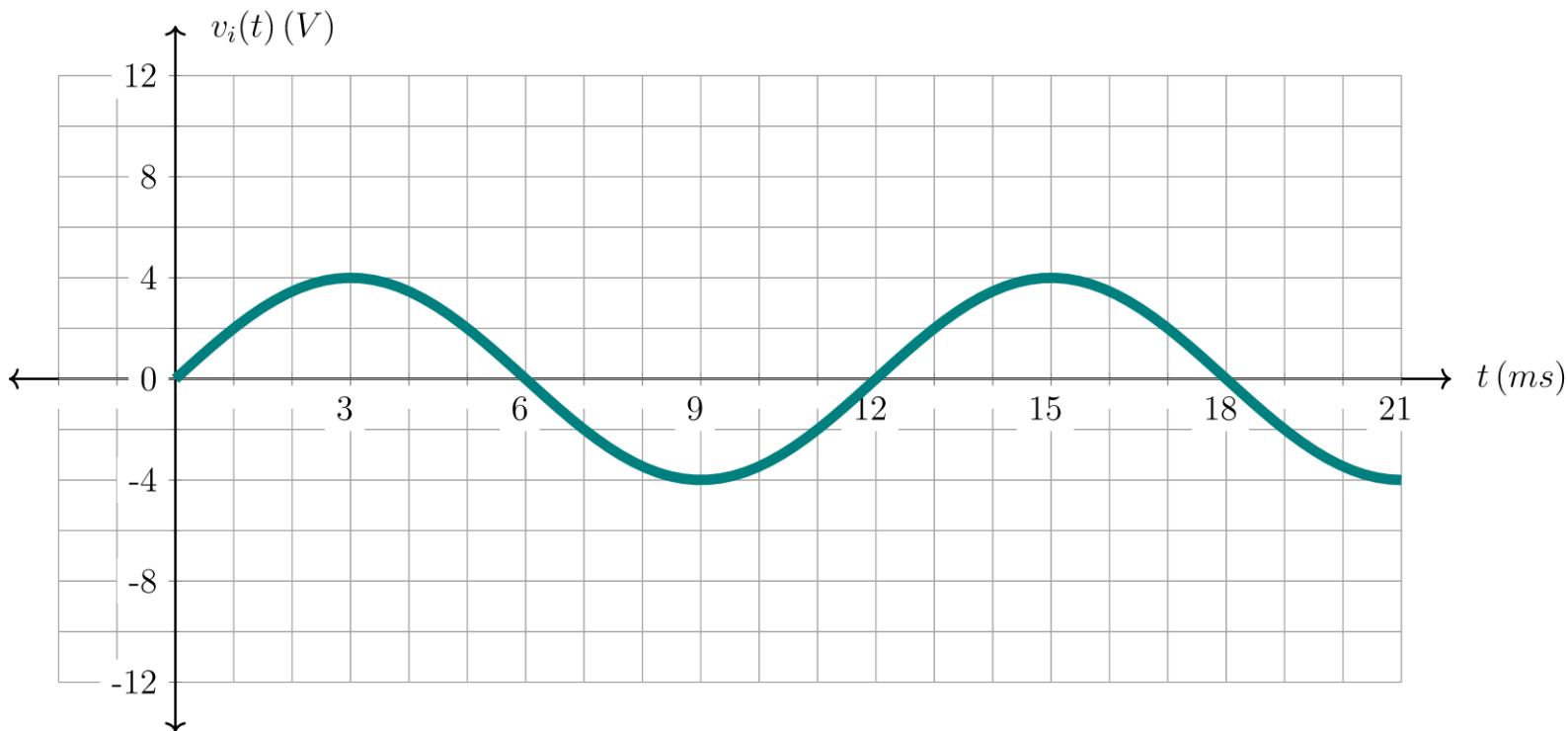



Problem 21

- Sketch v_o vs. t , if v_i is as shown in the following plot.

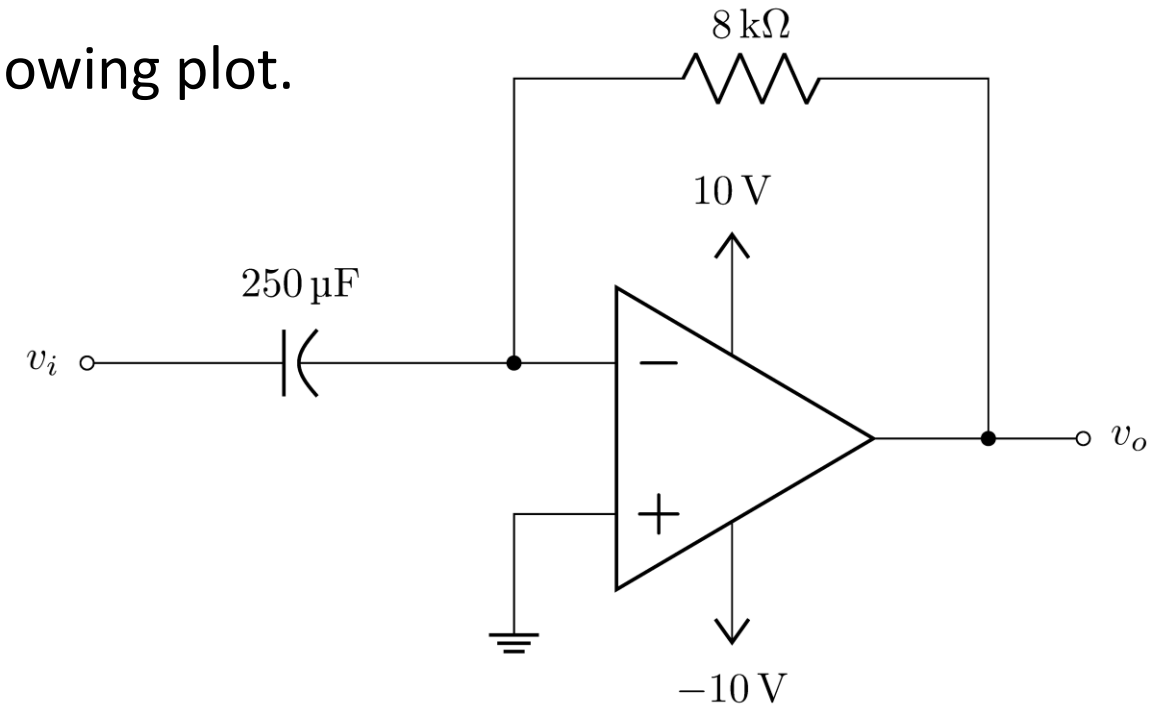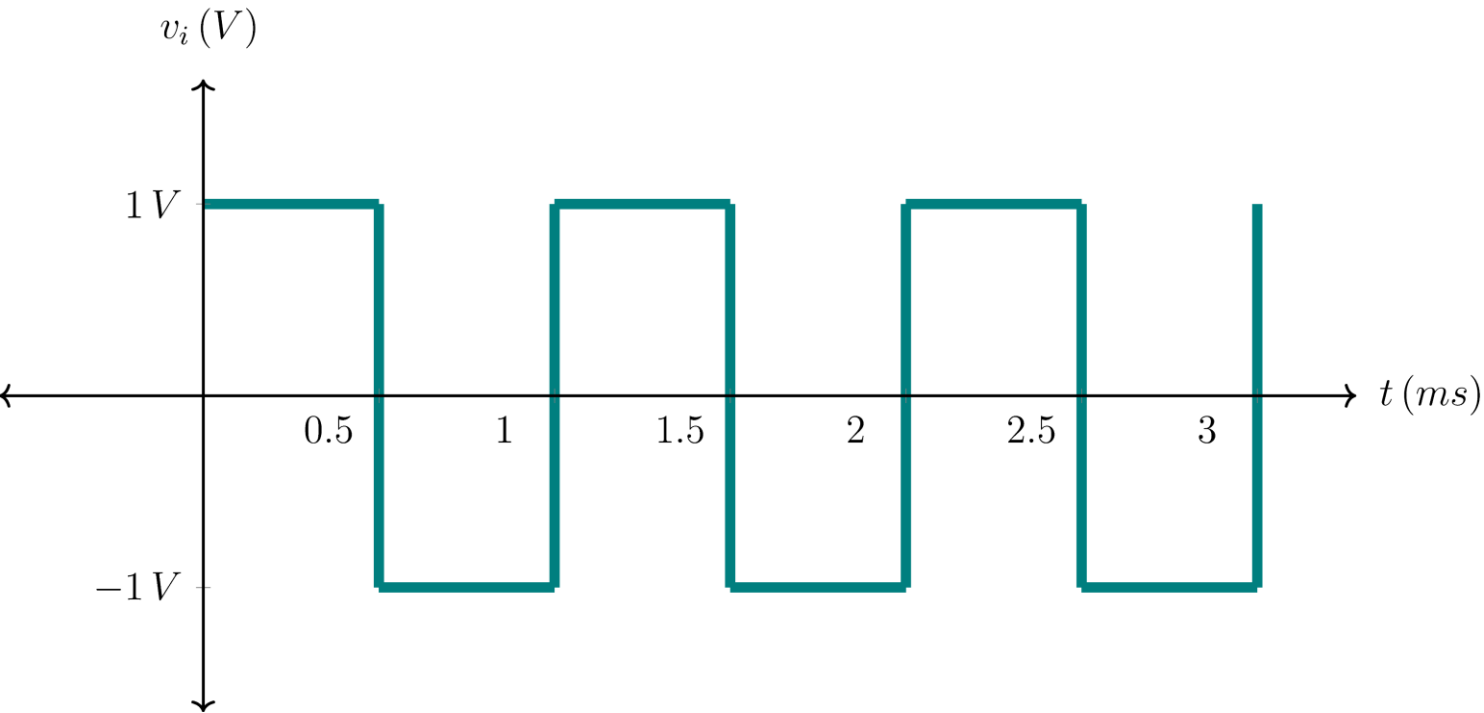


Problem 22

- Sketch v_o vs. t , if v_i is as shown in the following plot.

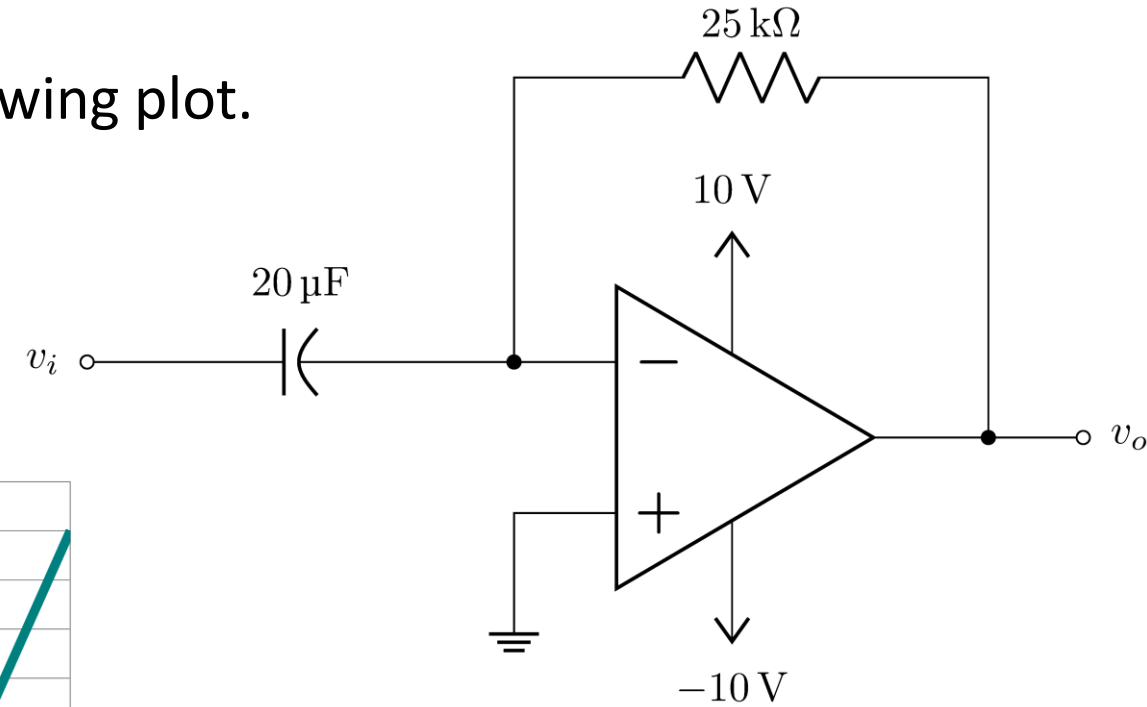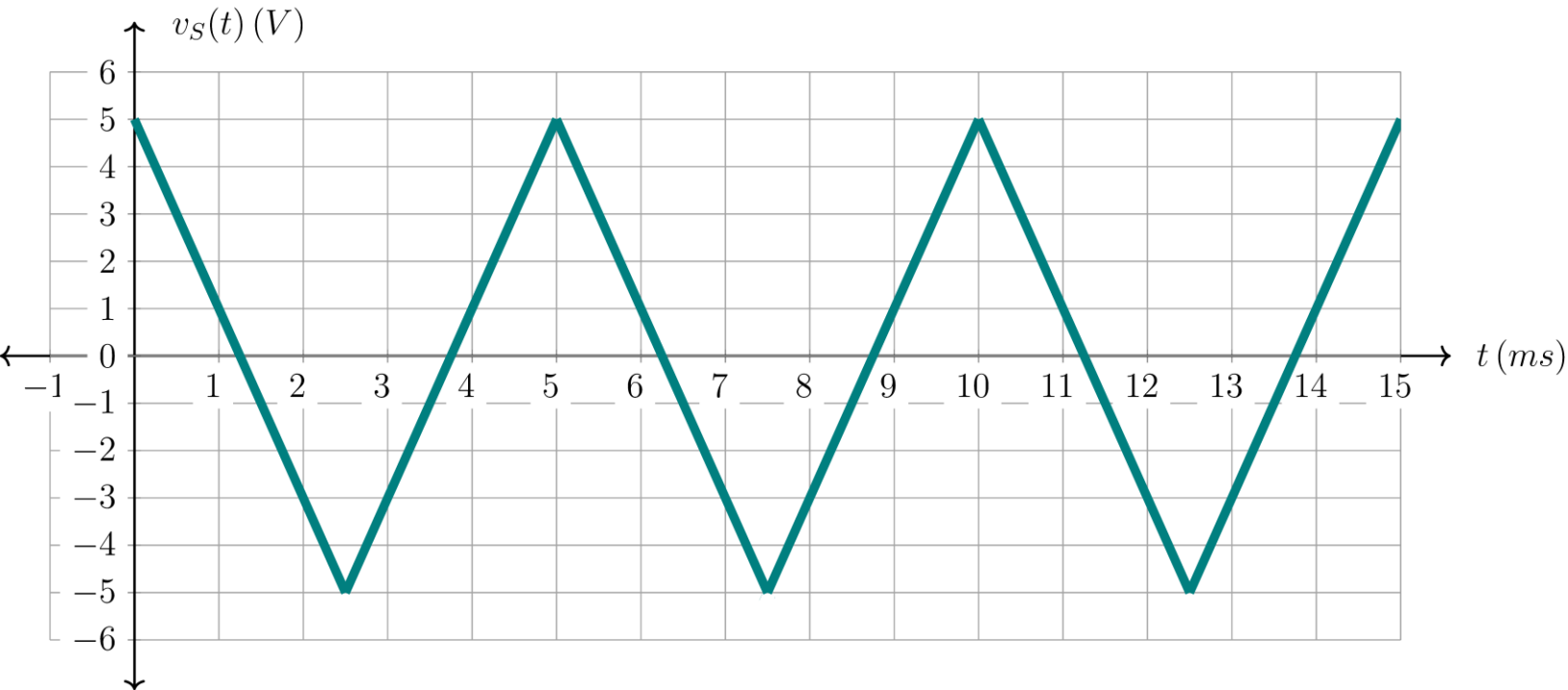



Problem 23

- Sketch i_o vs. t , if v_i is as shown in the following plot.

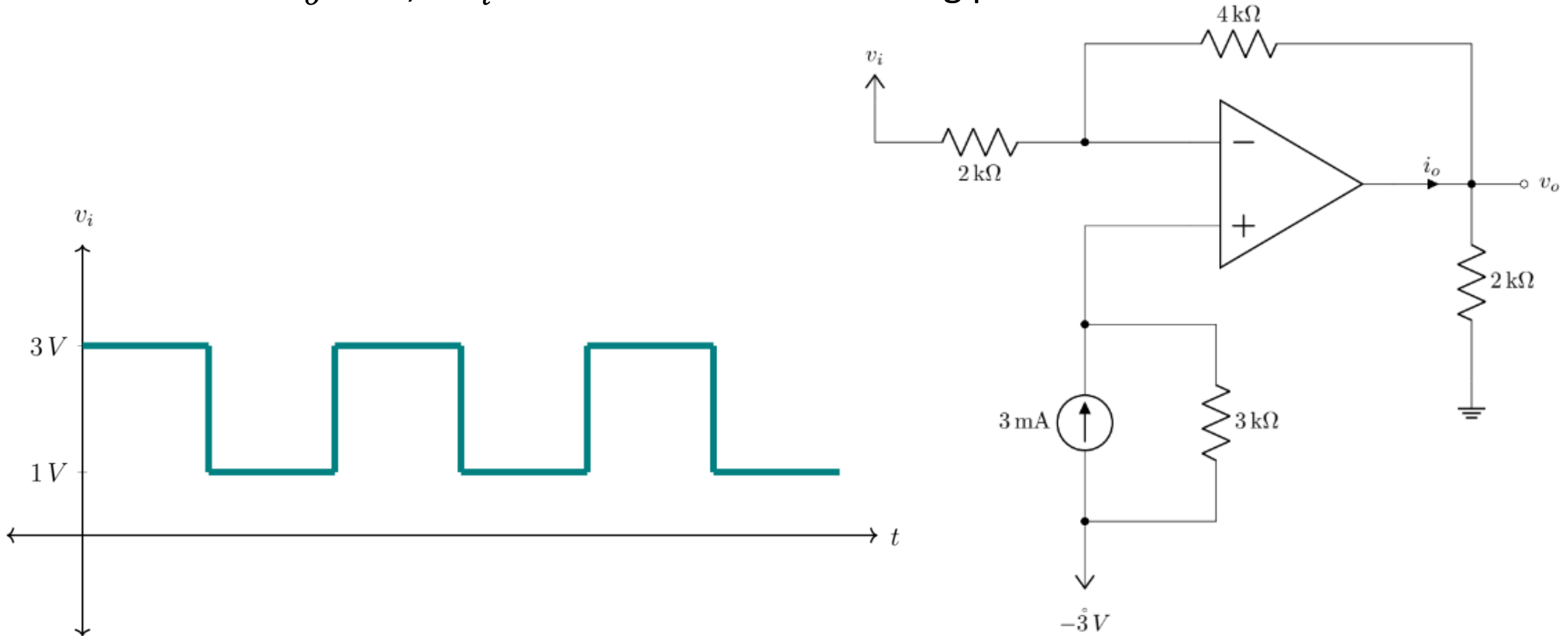



Problem 24

- Sketch V_o vs. t and V_o vs. E_i .

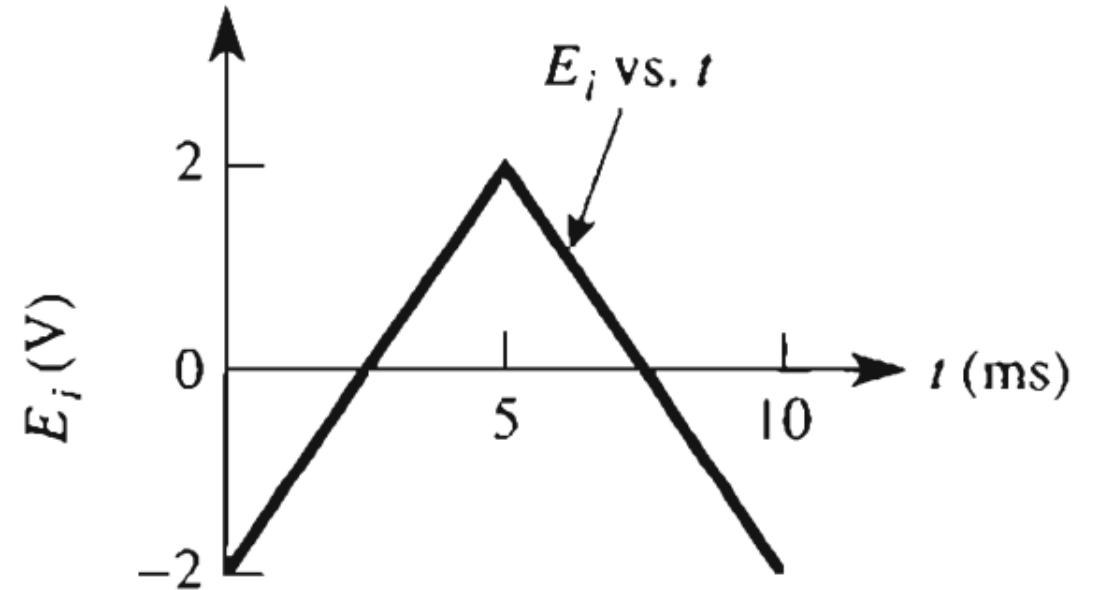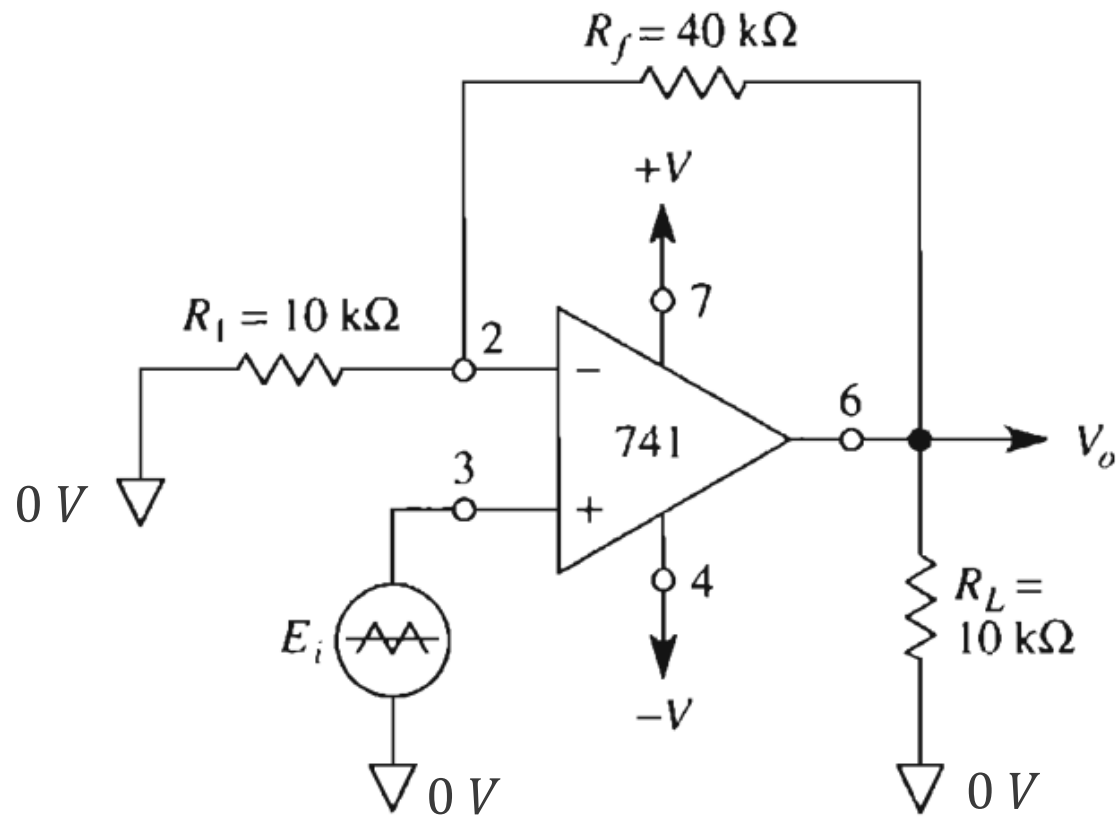


Problem 25

- Sketch V_o vs. t and V_o vs. E_{ac} , if $E_{dc} = -5$ V.

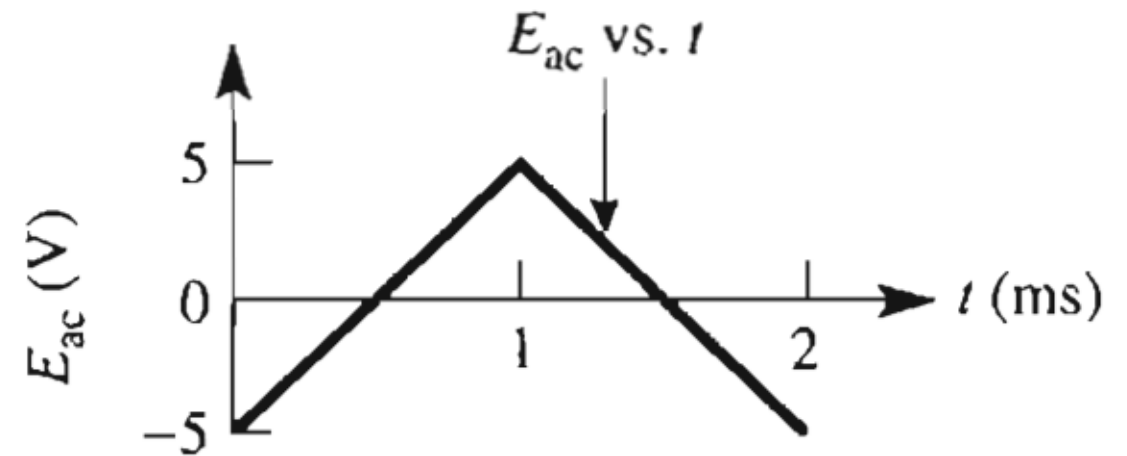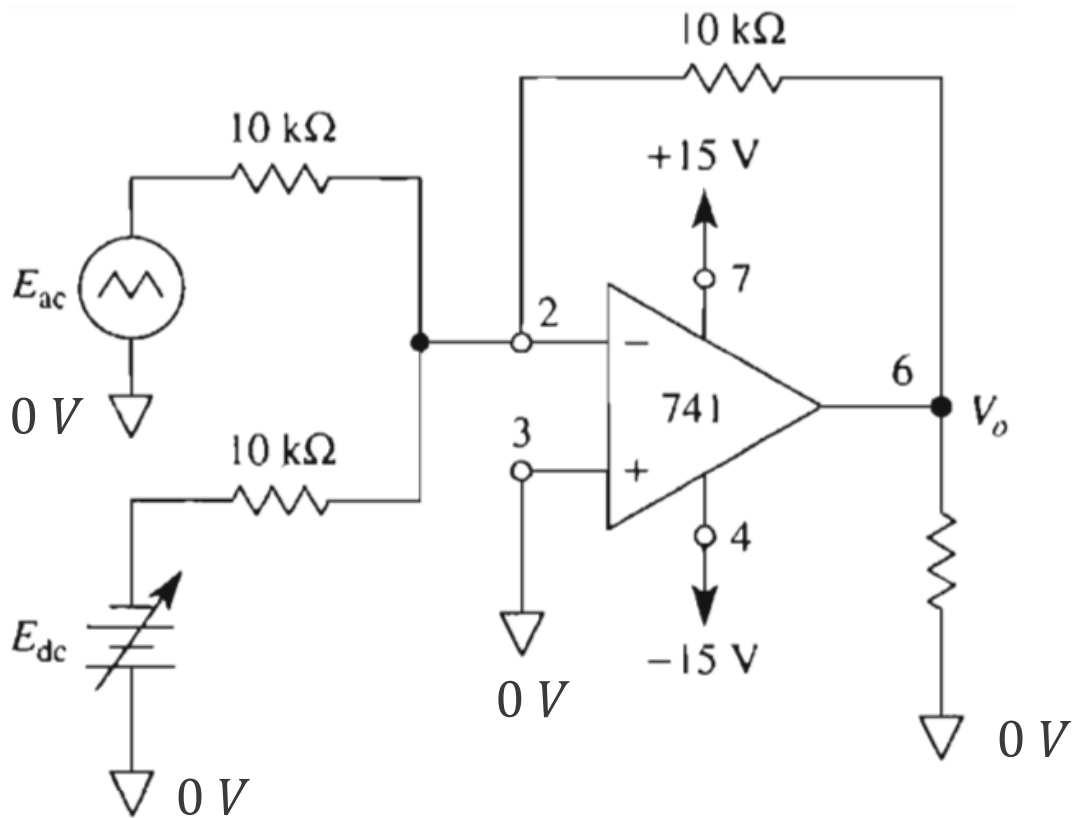


Problem 26

- Design a circuit with a single ideal op-amp for each of the VTC plots shown below. V_{output} and V_{input} are the output voltage and the input voltage respectively.

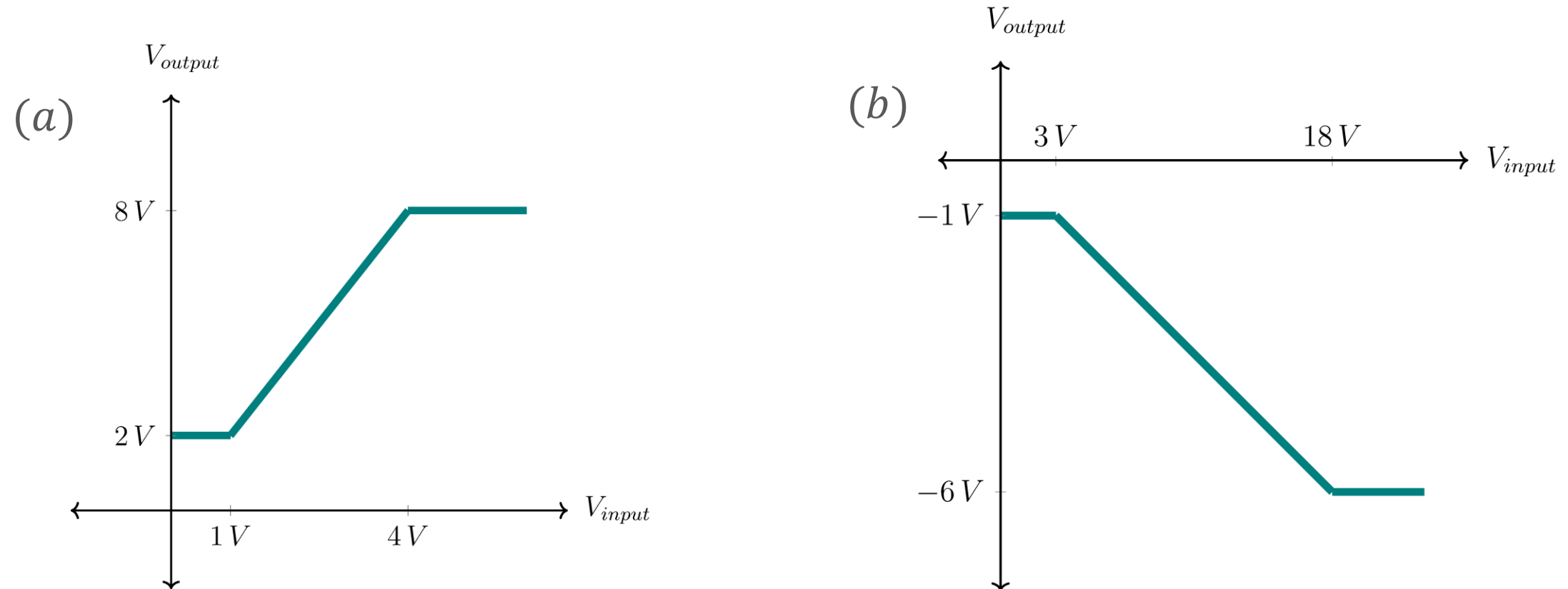

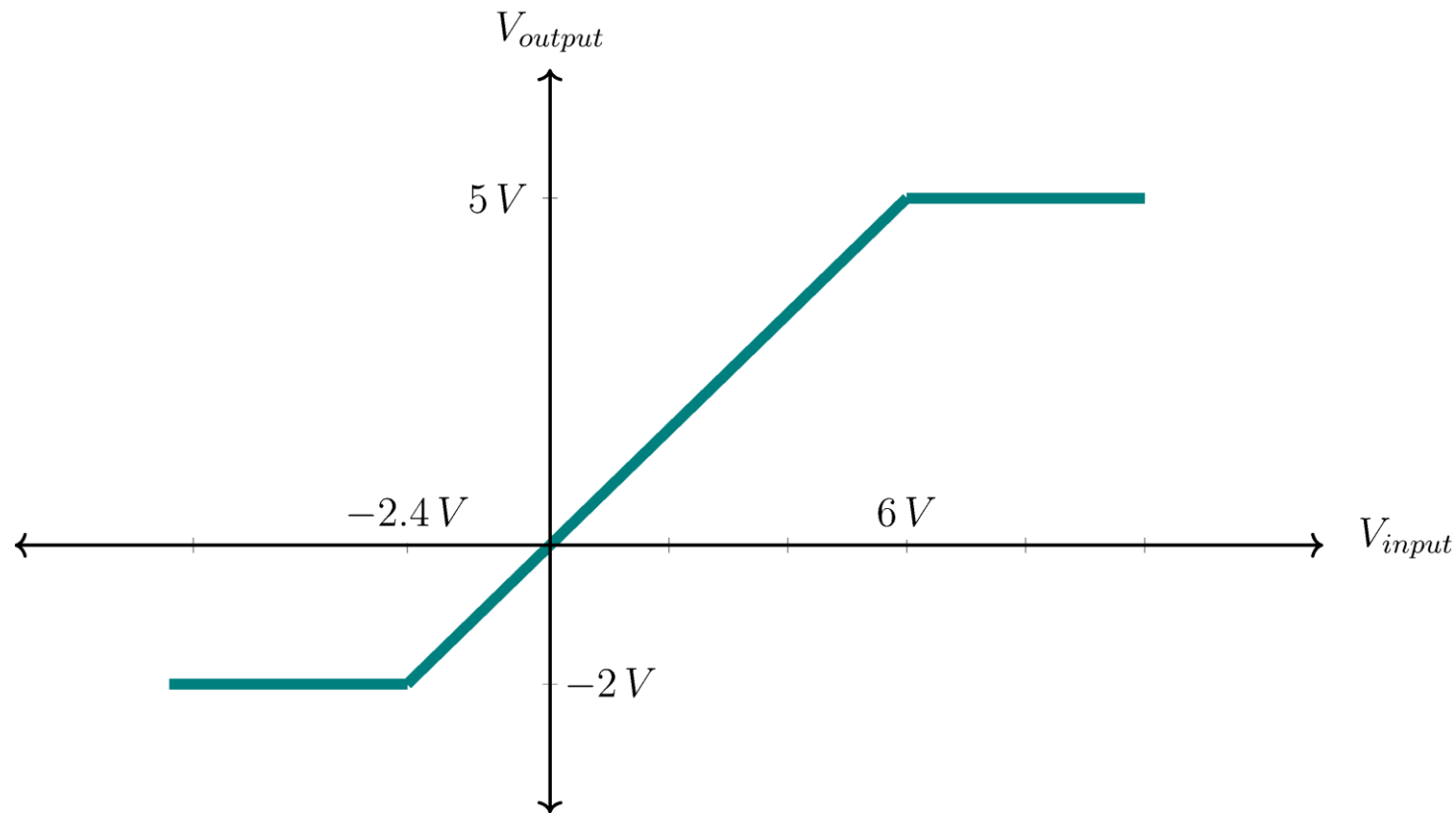Problem 27

- Design a circuit with a single ideal op-amp for the VTC plots shown below. V_{output} and V_{input} are the output voltage and the input voltage respectively.



Acknowledgement and References

Some of the problems in this set are taken or adapted from the following sources:

1. Sedra, A. S., & Smith, K. C., Microelectronic Circuits, Oxford University Press
2. Coughlin, R. F., & Driscoll, F. F., Operational Amplifiers and Linear Integrated Circuits, Pearson
3. Neamen, D. A., Microelectronics: Circuit Analysis and Design, McGraw-Hill