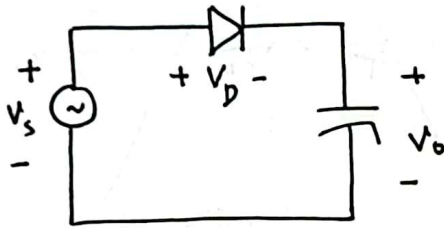



Diode Rectifiers with Capacitors (as filter)

- * Let's look at an impractical circuit to understand how the capacitor works in a rectifier setup.


HW rectifier with C (No load) -



ON: $V_o = V_s - V_{D_0}$

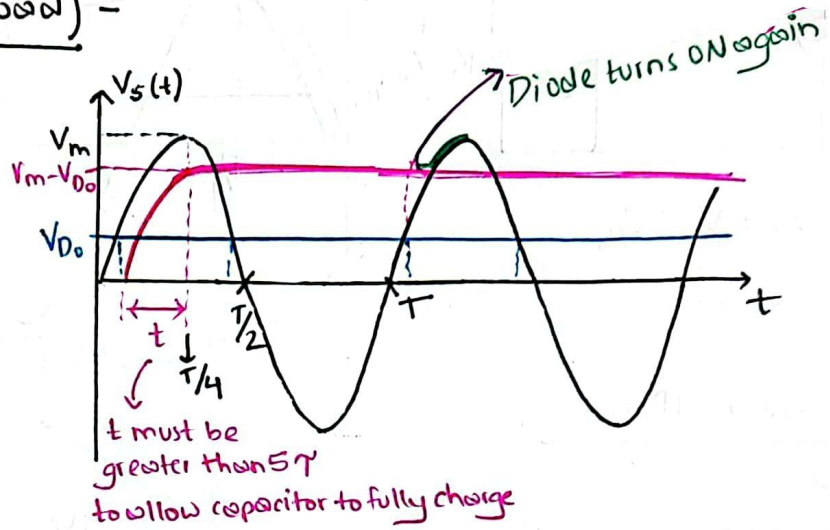

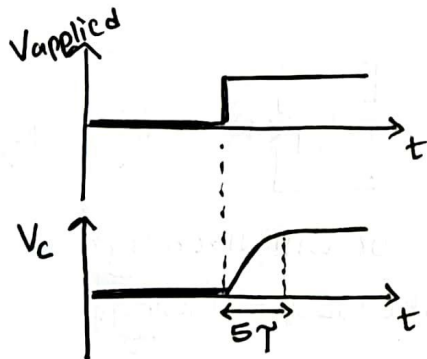- * a capacitor requires $5T$ amount of time for its voltage to reach a steady state value, where $T = RC$.



- * If the capacitor is not given enough time, it will fail to fully follow the applied voltage.

* For the given circuit, $R_{load} = 0$
 $\therefore RC = 0$

The capacitor will be able to follow in no time!

- * $t > 5T$ usually, as $V_s(t)$ is usually at 50 Hz, and RC is sufficiently smaller.

- * After $T/4$, i/p voltage starts decreasing.


- * At and upto $T/4$, $V_D = V_s - V_o > 0 \rightarrow$ diode ON

- * After $T/4$, $V_D = V_s - V_o < 0$, as V_s starts decreasing and V_o is held constant by the capacitor \rightarrow diode slowly turns OFF.

- * As diode turns OFF, there will be no more current flow. Capacitor is unable to discharge as there is no load connected. $V_o \rightarrow$ remains constant.


* connecting a resistive load will affect the capacitor voltage graph.

Half-wave rectifier with C (with load) -


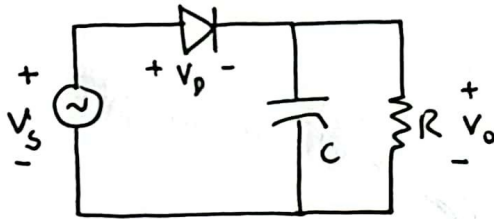


$$V_o = V_s - V_p$$

$$\Delta t = t_2 - t_1 \text{ (graph)}$$

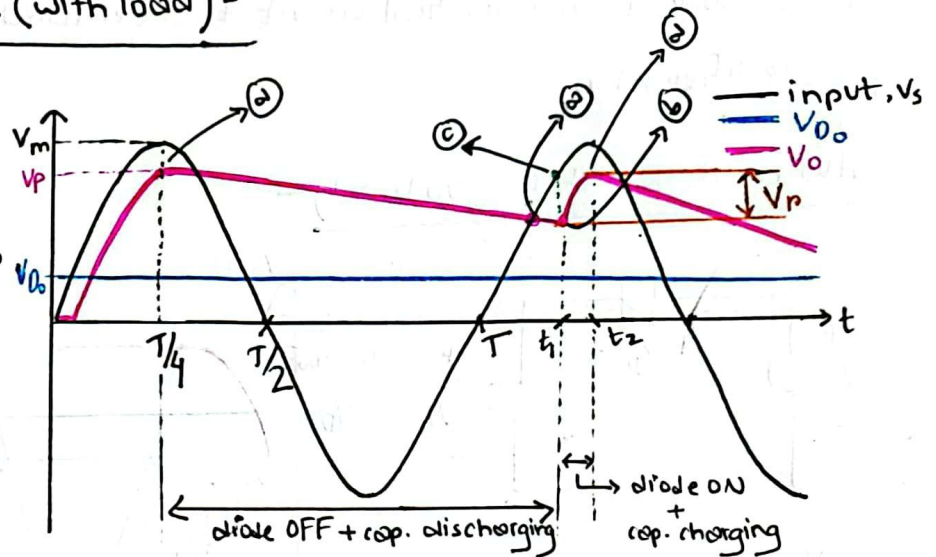

For +ve half cycle,

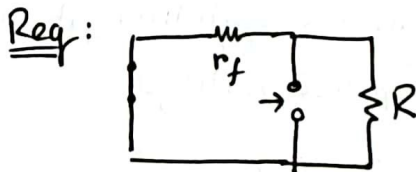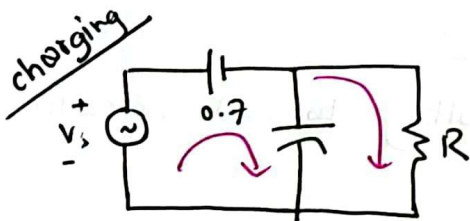

* r_f is the diode resistance ($\ll 50 \Omega$)

* all voltage sources shorted

* R_{eq} is seen from capacitor terminals.

$$\therefore R_{eq} = r_f \parallel R$$

$$R_{eq} < r_f \text{ (given that } r_f \ll R \text{)}$$


* R_{eq} is a very small value.

* Charging time constant, τ_{ch} , is thus very small, so capacitor will charge fully by $T/4$.

discharging

* At/After $T/4$, $V_s - V_o < V_{D0}$

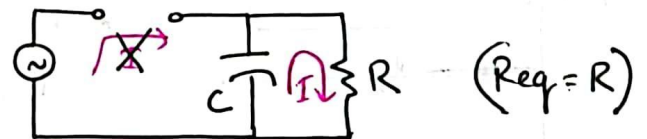* The diode will be reverse biased, thus rendering the circuit -




* The capacitor will discharge through the load following - $5\tau_d = 5RC$.

* One important condition to be met is that $5\tau_d \gg T$.

* The capacitor voltage will decrease following exponential rule.

$$V_c(t) = V_p e^{-t/\tau}$$

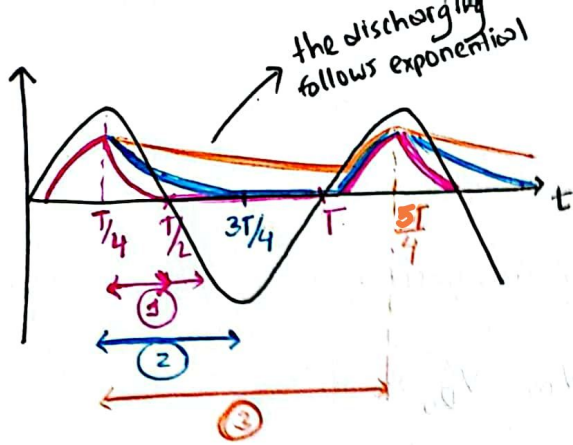

If $5T_d \gg T$ condition is not met, consider the following scenarios -

① $5T_d = \frac{T}{4}$

② $5T_d = T/2$

③ $5T_d = T \rightarrow$ here, the input will charge capacitor again before the capacitor fully manages to discharge

discharging continued

(points have been marked on the graph)

- * At point (a), $V_o > V_{D_0}$ and $V_s = V_o$ (they intersect) + diode still off.
- * After point (a), as V_s increases (while V_o decreases), the diode will eventually become forward biased, turning it on again.
- * This happens when $V_s > V_o + V_{D_0} \rightarrow$ this occurs at point (b)
- * point (c) highlights (in green) that the input at that moment is greater than the ~~cap~~ output by diode voltage drop. ($V_s > V_o + V_{D_0}$)
- (* point (b) ~~and~~ and (c) are the same, just marked on different lines)
- * From point (b) to (d), the diode is biased ON \rightarrow capacitor will charge
- * After point (d), the capacitor will discharge, as the diode is biased OFF. The capacitor will continue discharging until the point (b) is reached in next cycle.
- * The output now is relatively better, as it does not completely go down to 0 V, like it did without a capacitor.
- * The output fluctuates between a max and min level (voltage at point (d) and (b) respectively). This is called the ripple voltage, V_r .

* V_p should be as small as possible.

some points to note -

(i) $\Delta t = t_2 - t_1 \rightarrow$ Diode conducts during this period

(ii) at $t_1 \rightarrow V_o = V_p - V_r$, where $V_p = V_m - V_{D0}$
(point (b))

(iii) at $t_2 \rightarrow V_s = V_m$ and $V_o = V_p$ (both i/p and o/p reach their peak)

$$* I = \frac{V_s - V_{D0} - V_o}{R} = \frac{V_m - V_{D0} - V_p}{R} = \frac{V_m - V_{D0} - (V_m - V_{D0})}{R} = 0$$

(iv) When the diode is off, capacitor discharges through load in an exponential manner.

(v) During discharging phase, $V_o = V_p e^{-(T-\Delta t)/\tau}$
(at point (b))

$t = T - \Delta t$
= discharging duration

$$\Rightarrow V_p - V_r = V_p e^{-(T-\Delta t)/RC}$$

$$\Rightarrow V_p - V_r = V_p \left[1 - \frac{T-\Delta t}{RC} + \left(\frac{T-\Delta t}{RC} \right)^2 \cdot \frac{1}{2!} - \dots \right]$$

Taylor series

using the conditions/approximations: $RC \gg T$
 $\Delta t \ll T$


we can rewrite:

$$\Rightarrow V_p - V_r \approx V_p \left(1 - \frac{T-\Delta t}{RC} \right) \quad [\text{ignore higher order terms}]$$

$$\therefore V_r = \frac{V_p}{fRC}$$

[$f, R \rightarrow$ not changeable]

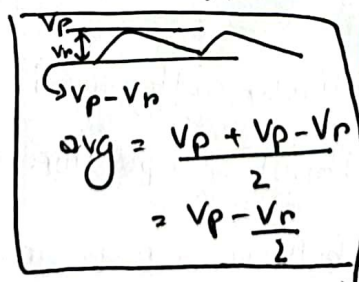
(vi) $V_{dc} = V_{avg} = V_p - \frac{V_r}{2}$



[$C \uparrow, V_r \downarrow \dots$ but $\Delta t \uparrow$]


\downarrow
we don't want,
so we have to
limit how high
 C is.

Full-wave rectifier with C (with load) -

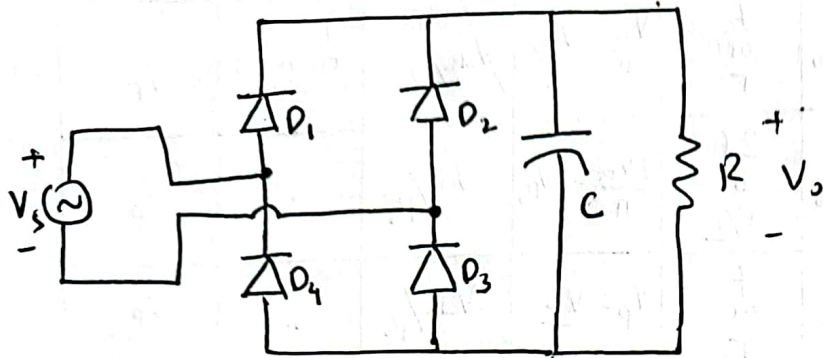

* the analysis is similar to that of half wave rectifier, i.e., capacitor will have charging and discharging phase

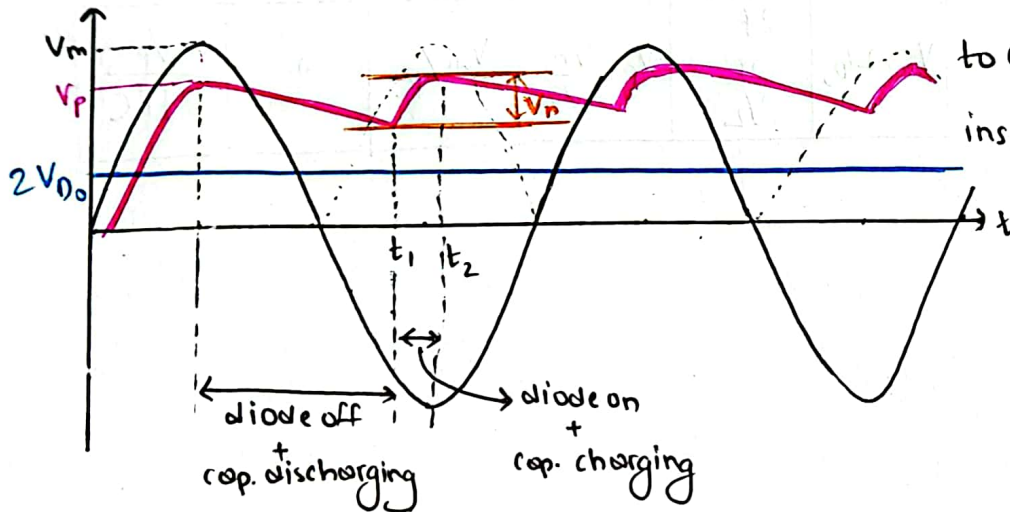* Unlike with HW rectifier, in FW rectifier, capacitor will get to charge every half cycle, instead of every other cycle.



$$V_o = V_s - 2V_r$$

* During discharging phase, time taken = $T/2 - \Delta t$.

$$\Rightarrow V_p - V_r = V_p e^{-(T/2 - \Delta t)/RC}$$

$$\Rightarrow V_p - V_r \approx V_p e^{-T/2RC} \quad [T \gg \Delta t]$$

$$\Rightarrow V_p - V_r \approx V_p \left[1 - T/2RC\right] \quad [RC \gg T]$$

$$\therefore V_r = \frac{V_p}{2fRC} \rightarrow V_r(FW) < V_r(HW)$$

* output for this ckt is better with lower fluctuations.

$$* V_{dc} = V_p - \frac{V_r}{2} \quad (\text{same logic as HW})$$

Summary:

		i/p voltage peak	i/p v. freq/period	o/p v. peak	o/p v. freq/period	o/p V_{dc}	o/p I	V_{rms}	o/p V_r
with out C	HW	V_m	f or, T	$V_m - V_{D0}$	f or T	$\frac{V_m}{\pi} - \frac{V_{D0}}{2}$	V_{dc}/R	no need	V_p
	FW	V_m	f or, T	$V_m - 2V_{D0}$	$2f$ or $T/2$	$\frac{2V_m}{\pi} - 2V_{D0}$	V_{dc}/R	"	V_p
with C	HW	V_m	f or T	$V_m - V_{D0}$	f or T	$V_p - \frac{V_r}{2}$	V_{dc}/R	"	$\frac{V_p}{fRC}$
	FW	V_m	f or T	$V_m - 2V_{D0}$	$2f$ or $T/2$	$V_p - \frac{V_r}{2}$	V_{dc}/R	"	$\frac{V_p}{2fRC}$

↓
Approximation
for $V_D \ll V_m$.

Otherwise, $V_{dc} = \frac{1}{T} \int_0^T v(t) dt$