

Set-01

Question 1:

(a) From the ckt given-

$$V_G = 5V \quad \leftarrow 0.5 \text{ Mark}$$

$$V_D = 6V \quad \leftarrow 0.5 \text{ Mark}$$

Let's assume, $V_S = x$

To operate in saturation-


$$V_{DS} \geq V_{GS} - V_T$$

$$\Rightarrow V_D - V_S \geq V_G - V_S - V_T$$

$$\Rightarrow \boxed{6 - x \geq 5 - x - 1}$$

This condition is always true. Hence the MOSFET will operate in Sat.

(b)

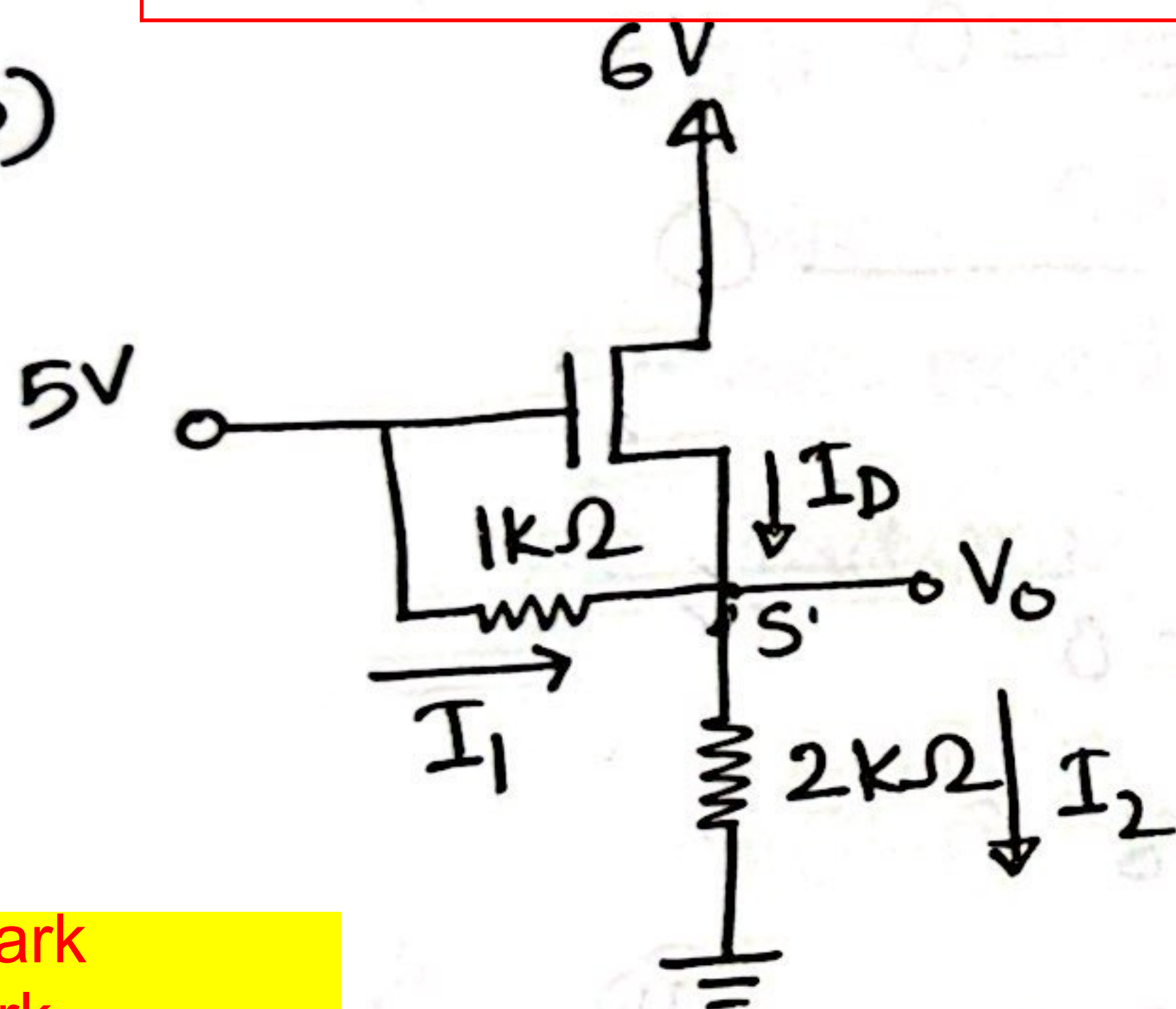

Previously we proved the mosfet will operate in saturation.

So,

$$I_D = \frac{1}{2} K (V_{GS} - V_T)^2$$

$$[K_{eff} \text{ at } S' \text{ node}] \quad I_2 - I_1 = \frac{1}{2} \times 1 (5 - x - 1)^2 \quad [Assuming V_S = x]$$

$$\Rightarrow \frac{x}{2} - \left(\frac{5-x}{1}\right) = \frac{1}{2} (4-x)^2$$

$$\Rightarrow x - 10 + 2x = 16 - 8x + x^2$$

$$\Rightarrow x^2 - 11x + 26 = 0$$

$$\Rightarrow x = 7.56, 3.43$$

not acceptable for Saturation.

$$\therefore V_O = V_S = x = 3.43V$$

$$I_1 = \frac{5 - 3.43}{1k\Omega} = 1.57 \text{ mA}$$

$$I_D = I_2 - I_1 = 0.145 \text{ mA}$$

$$I_2 = \frac{3.43}{2} = 1.72 \text{ mA}$$

Validation:

$$\left. \begin{array}{l} V_{DS} = 6 - 3.43 = 2.57 \\ V_{GS} = 5 - 3.43 = 1.57 \end{array} \right\} \boxed{V_{DS} > V_{GS} - V_T}$$

1 Mark


Total - 2 Marks

KCL - 1 Mark
VO - 1 Mark
I1 - 1 Mark
I2 - 1 Mark
ID - 1 Mark
Verification - 1 Mark

Total - 6 Marks

Give 3 marks for
wrong assumption
but correct procedure

(c)

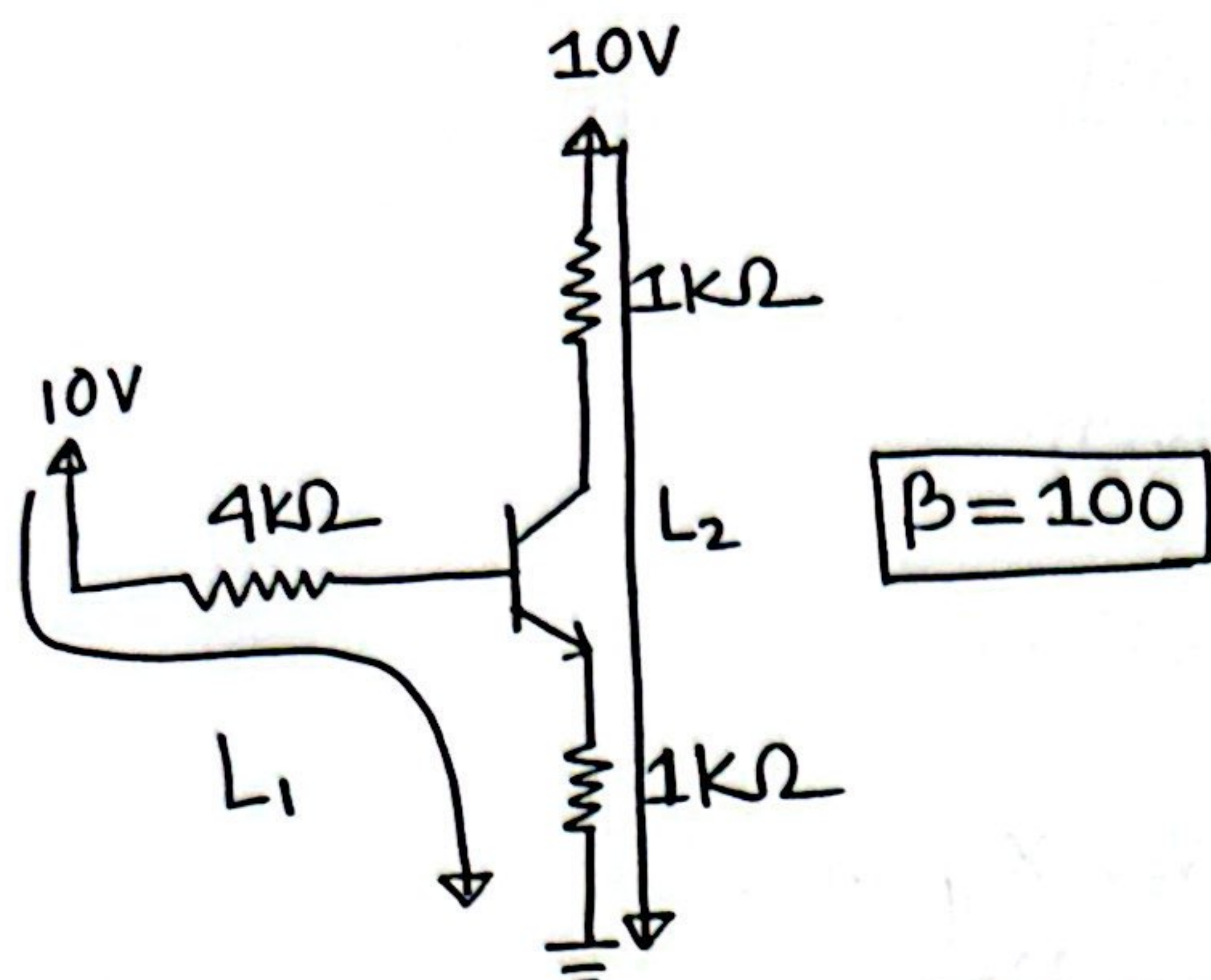

KVL in L1 - 1 mark
 KVL in L2 - 1 mark
 IB - 1 mark
 IC - 1 mark
 IE - 1 mark
 VC - 1 mark
 VE - 1 mark
 Verification - 1 mark

total - 8 marks

Give 4 marks for wrong assumption but correct procedure

Let's assume the ~~me~~ BJT is in Saturation.

$$\therefore V_{BE, \text{sat}} = 0.8 \text{ V}$$

$$V_{CE, \text{sat}} = 0.2 \text{ V}$$

Applying KVL along ~~the~~ L1

$$-10 \text{ V} + 4I_B + 0.8 + I_E = 0$$

$$\Rightarrow 4I_B + I_E = 9.2 \quad \text{--- (I)}$$

Applying KVL along L2

$$-10 + I_C + 0.2 + I_E = 0$$

$$\Rightarrow I_E - I_B + I_E = 9.8$$

$$\Rightarrow 2I_E - I_B = 9.8 \quad \text{--- (II)}$$

from (I) and (II)

$$I_B = 0.95 \text{ mA}$$

$$I_E = 5.37 \text{ mA}$$

$$\therefore I_C = 4.42 \text{ mA}$$

$$V_E = (5.37 \text{ mA} \times 1) = 5.37 \text{ V}$$

Validation:

$$\frac{I_C}{I_B} < \beta$$

$$\Rightarrow \boxed{\frac{4.42}{0.95} < 100} \rightarrow \text{This is TRUE}$$

2

(d) From the graph-

$$T = (1.25 - 0.25) \text{ ms} \\ = 1 \text{ ms}$$

1 mark

Total - 4 marks

$$\therefore f_{\text{out}} = \frac{1}{T} = 1 \text{ kHz}$$

1 mark

$$V_{\text{avg}} = 5 + \frac{(10-5)}{2}$$

2 mark

$$V_{\text{avg}} = 7.5 \text{ V}$$

Question 2:

Given,

$$V_{\text{in}} = 10 \sin(200\pi t)$$

$$f_{\text{in}} = 100 \text{ Hz}$$

1 mark

Total - 10 marks

$$f_{\text{out}} = 200 \text{ Hz}$$

So, we need to design a F.W. rectifier.

1 mark

$$V_{\text{out(max)}} = 10 - 2 \times V_{\text{D0}} \\ = 8.6 \text{ V}$$

1 mark

$$V_{\text{D(P-P)}} = 0.43 \text{ V.}$$

1 mark

We know-

$$V_{\text{D(P-P)}} = \frac{V_{\text{out(max)}}}{f_{\text{out}} RC}$$

1 mark


Let's assume - $R = 5 \text{ k}\Omega$

1 mark

$$\therefore C = \frac{8.6}{0.43 \times 200 \times 5 \times 10^3} \\ = 20 \mu\text{F}$$

1 mark

Designed ckt:

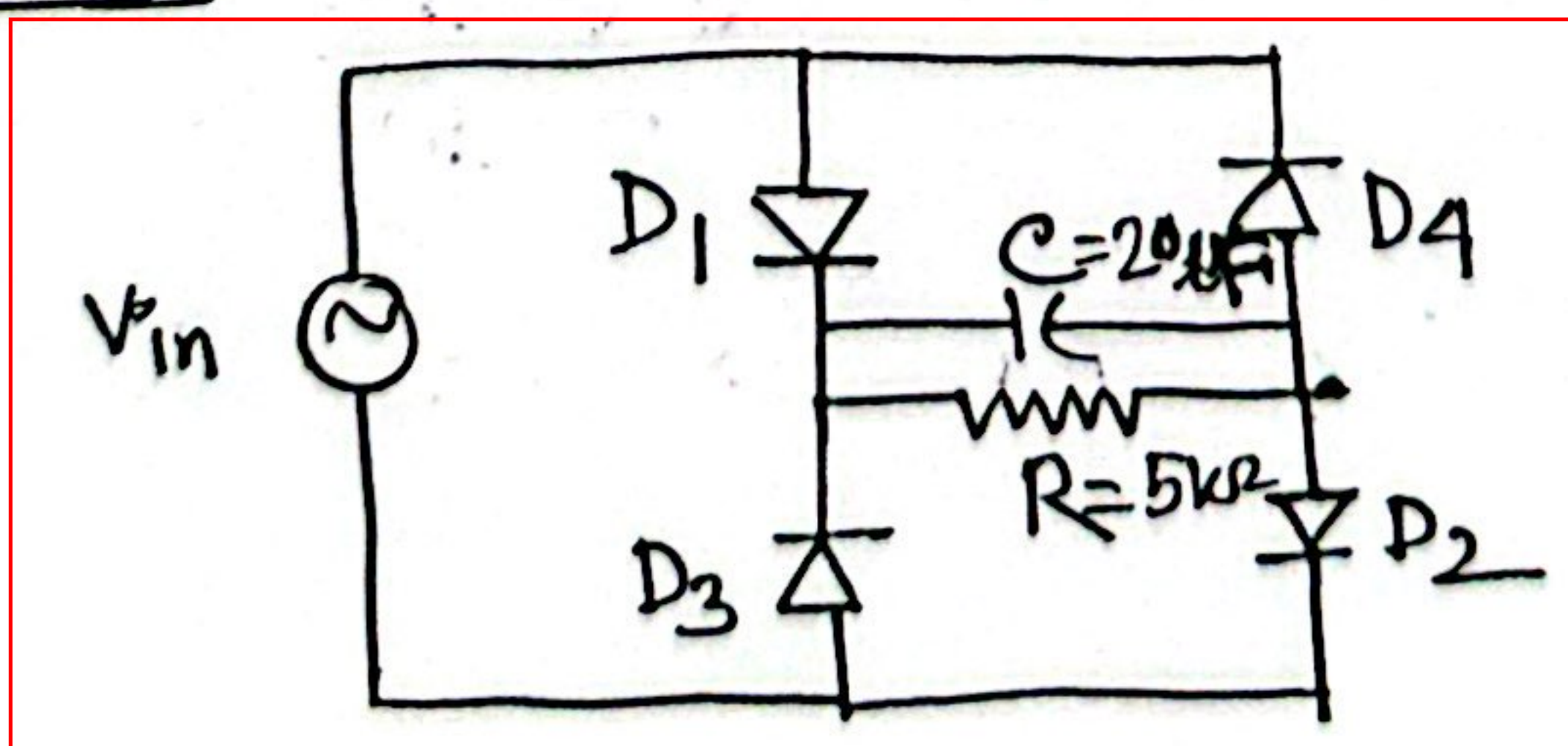

3 marks





⑥ $f = \bar{A}B + \bar{B}C + \bar{C}A$
 $= O_1 + O_2 + O_3$

④

This circuit is drawn differently & it's valid. You may have taught a different way of drawing logic circuits.

Give partial marks according to your judgement.


Total - 10 marks

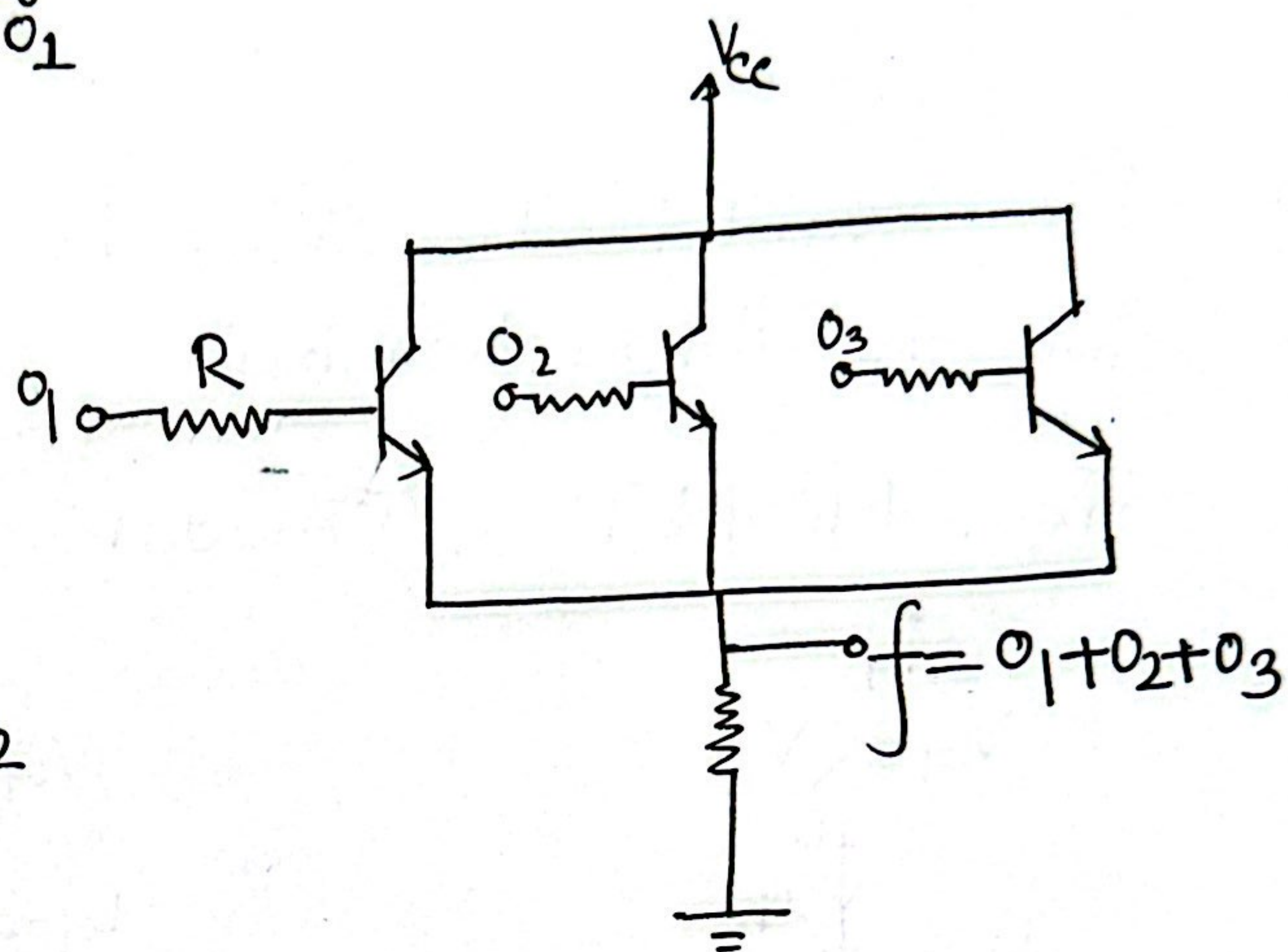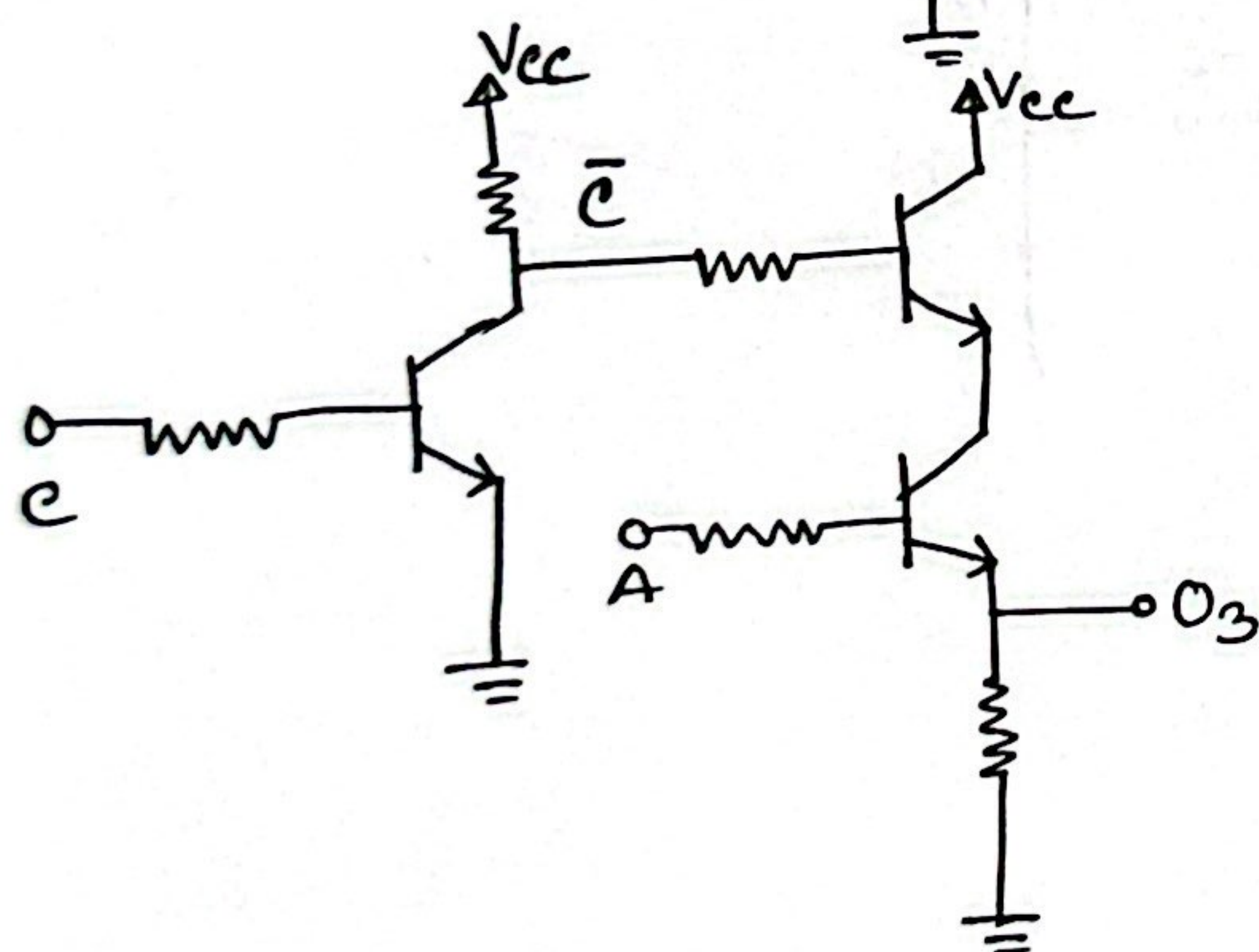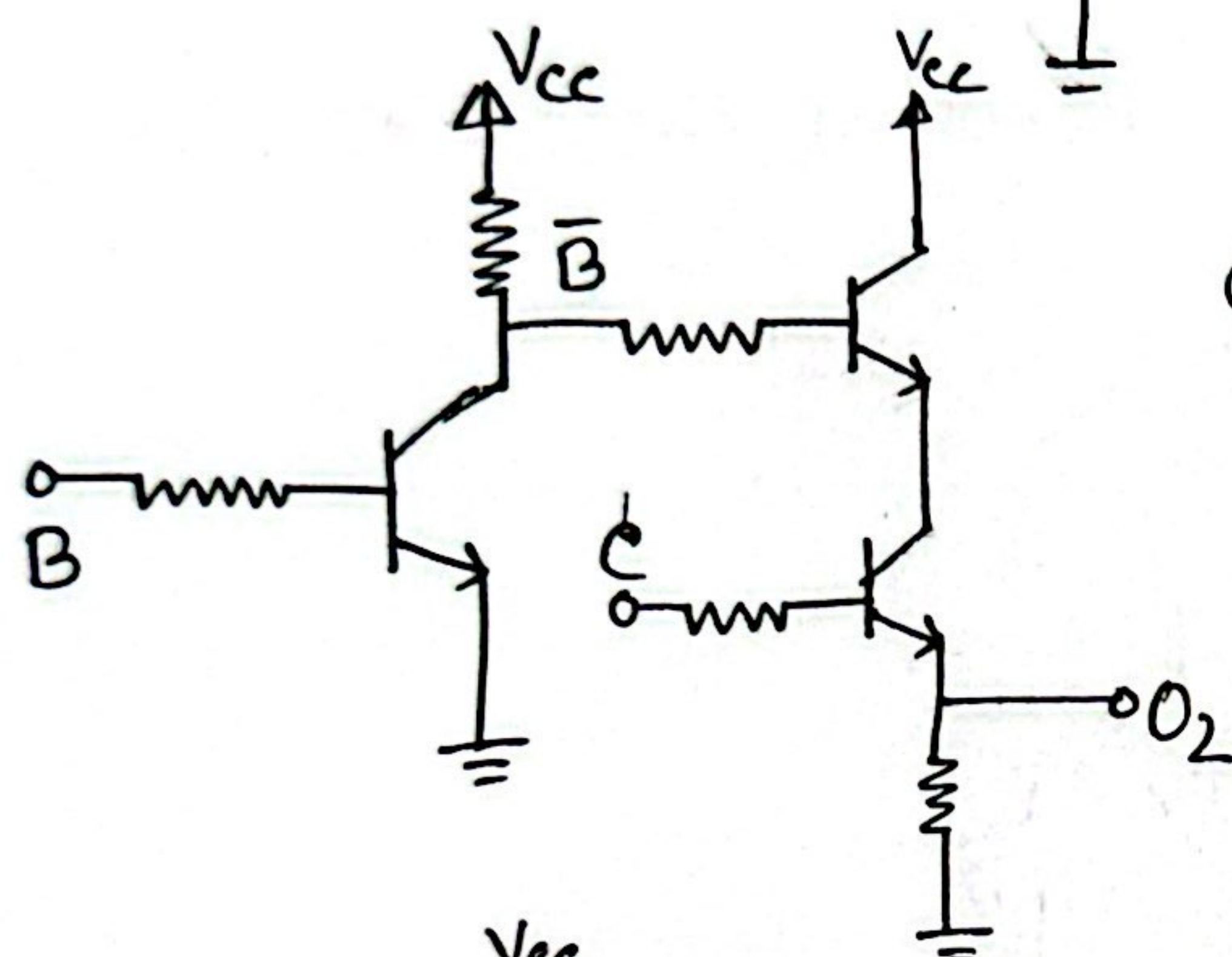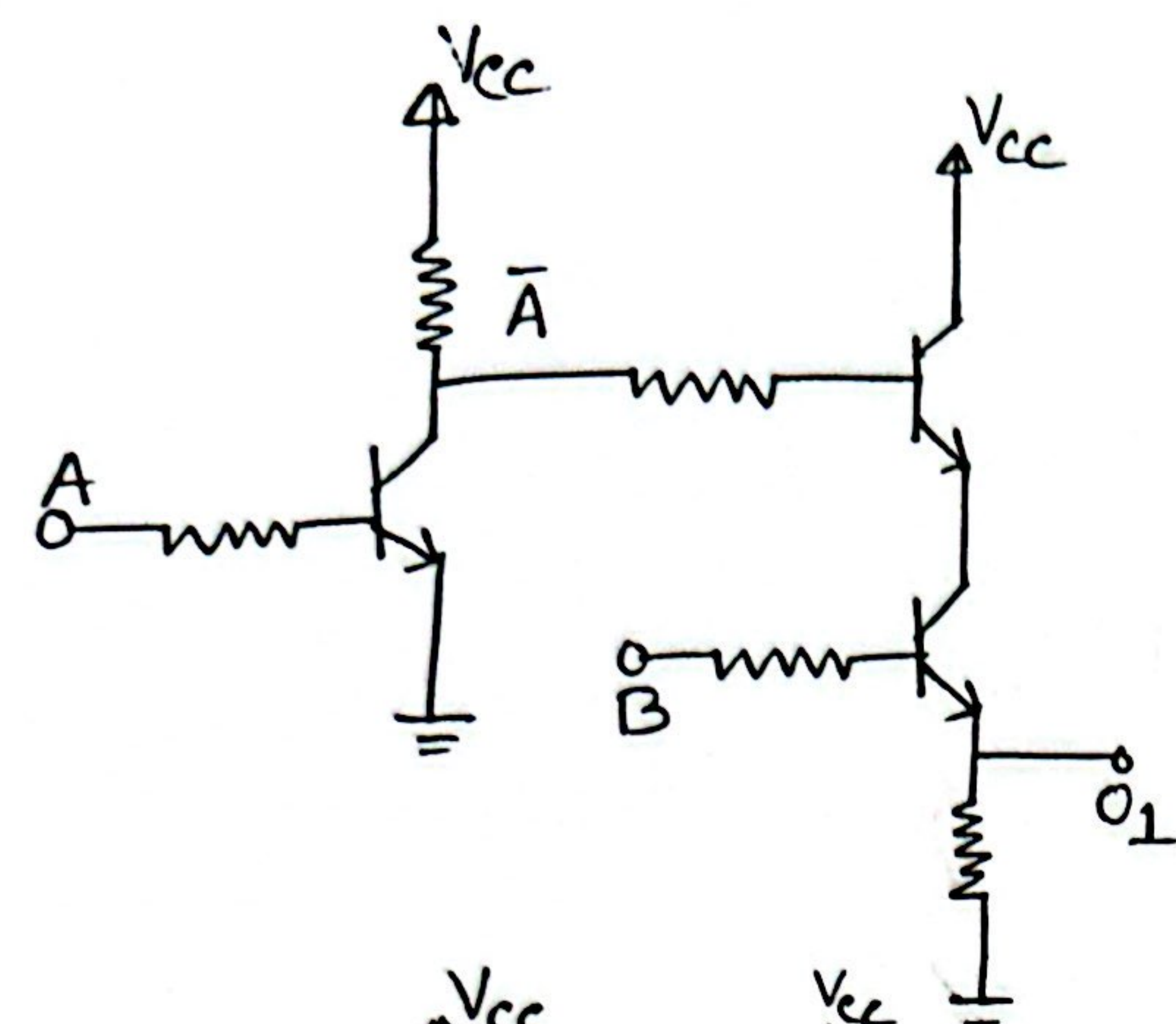

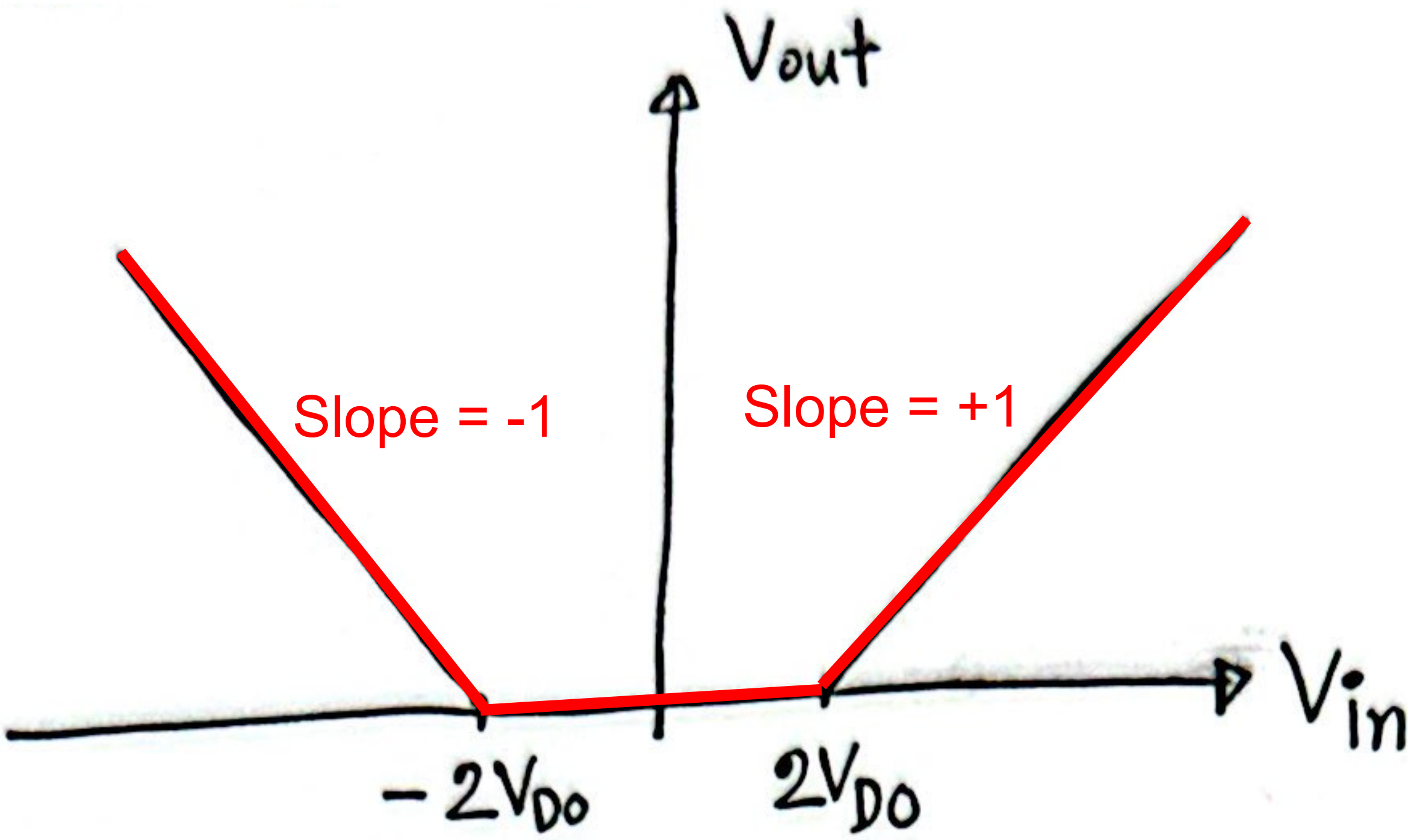Question 3

(a)

Graph - 2 marks
Label - 2 marks
total - 4 marks




(b)

MOSFET is an electronic device. The "Triode" & "Cutoff" region in the I-V graph of a MOSFET is almost similar to the "ON" state & the "OFF" state in the I-V graph of a switch respectively. This resemblance allows MOSFETs to act like switches by turning current flow ON or OFF electronically. Hence, MOSFETs can be used as an electronic switches.

total - 2 marks
give partial marks according to the answer

(c)

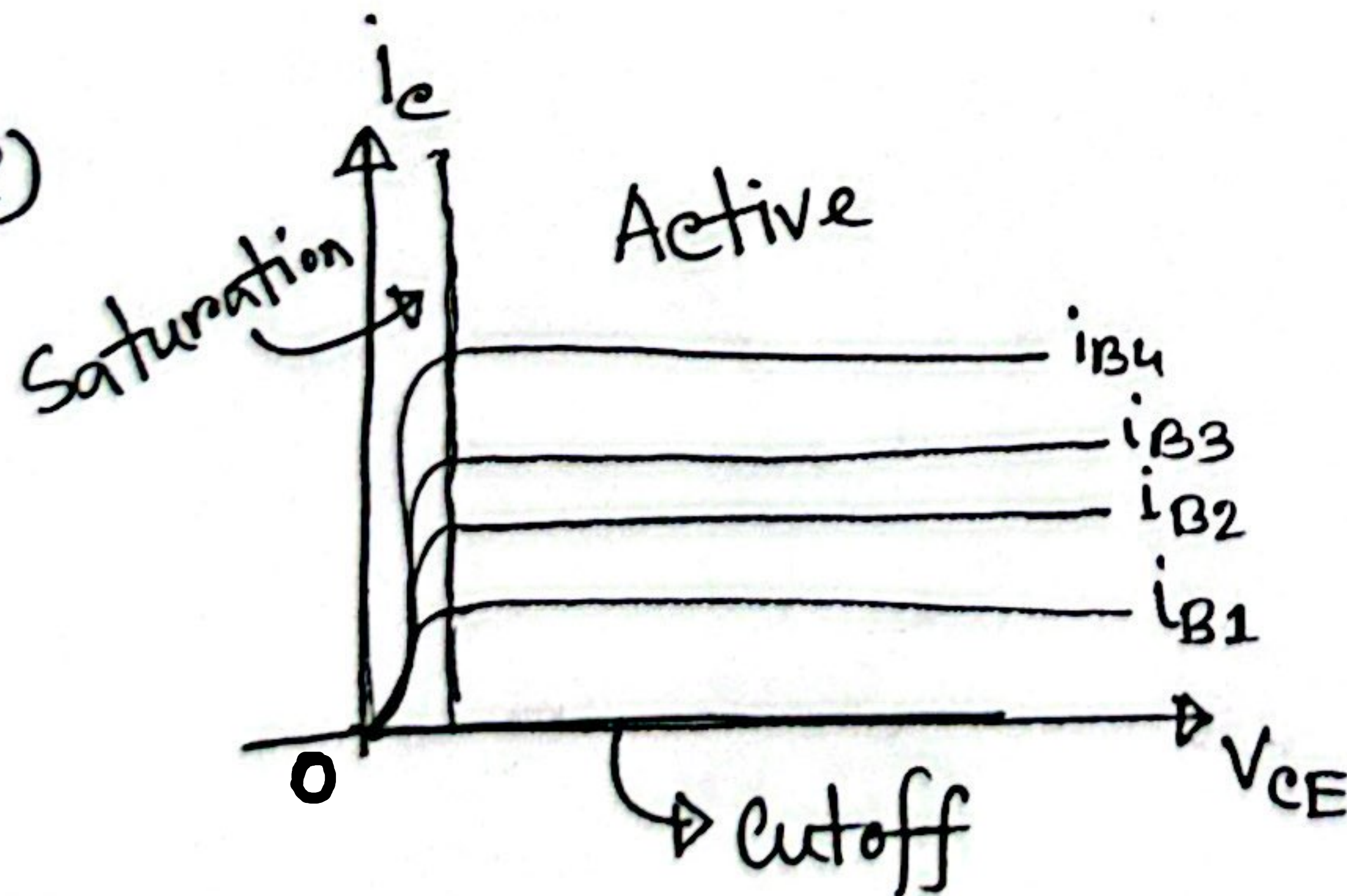


Graph - 1.5 marks
Label - 1 mark
Identifying Operating Regions - $3 \times 0.5 = 1.5$ marks
Total - 4 marks

Question 1:

(a) Same as set-01 1(a)

(b)

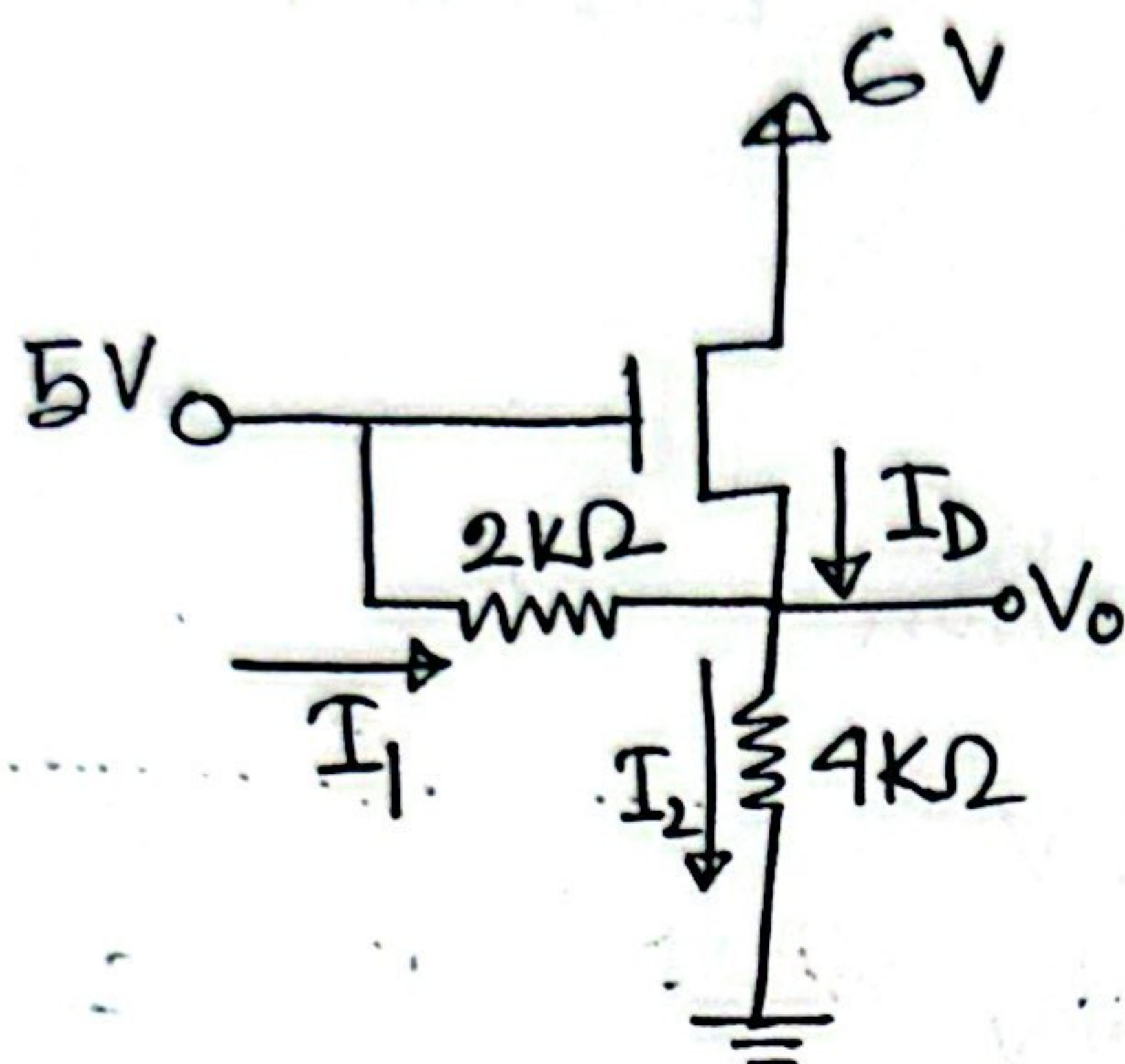

Assumption — saturation

$$I_D = \frac{1}{2} K (V_{GS} - V_T)^2$$

$$\Rightarrow I_2 - I_1 = \frac{1}{2} \times \frac{1}{2} (5 - x - 1)^2 \quad [\text{Assuming } V_S = x]$$

$$\Rightarrow \frac{x}{4} - \left(\frac{5-x}{2}\right) = \frac{1}{4} (4-x)^2$$

$$\Rightarrow x - 10 + 2x = 16 - 8x + x^2$$

$$\Rightarrow x = 7.56, 3.43$$

↓
not acceptable

$$V_0 = V_S = x = 3.43 \text{ V}$$

$$I_1 = \frac{5 - 3.43}{2k} = 0.785 \text{ mA}$$

$$I_D = I_2 - I_1 = 0.0725 \text{ mA}$$

$$I_2 = \frac{3.43}{4k} = 0.8575 \text{ mA}$$


Validation:

$$V_{DS} = 6 - 3.43 = 2.57 \text{ V}$$

$$V_{GS} = 5 - 3.43 = 1.57 \text{ V}$$

$$V_{DS} > V_{GS} - V_T$$

(c)

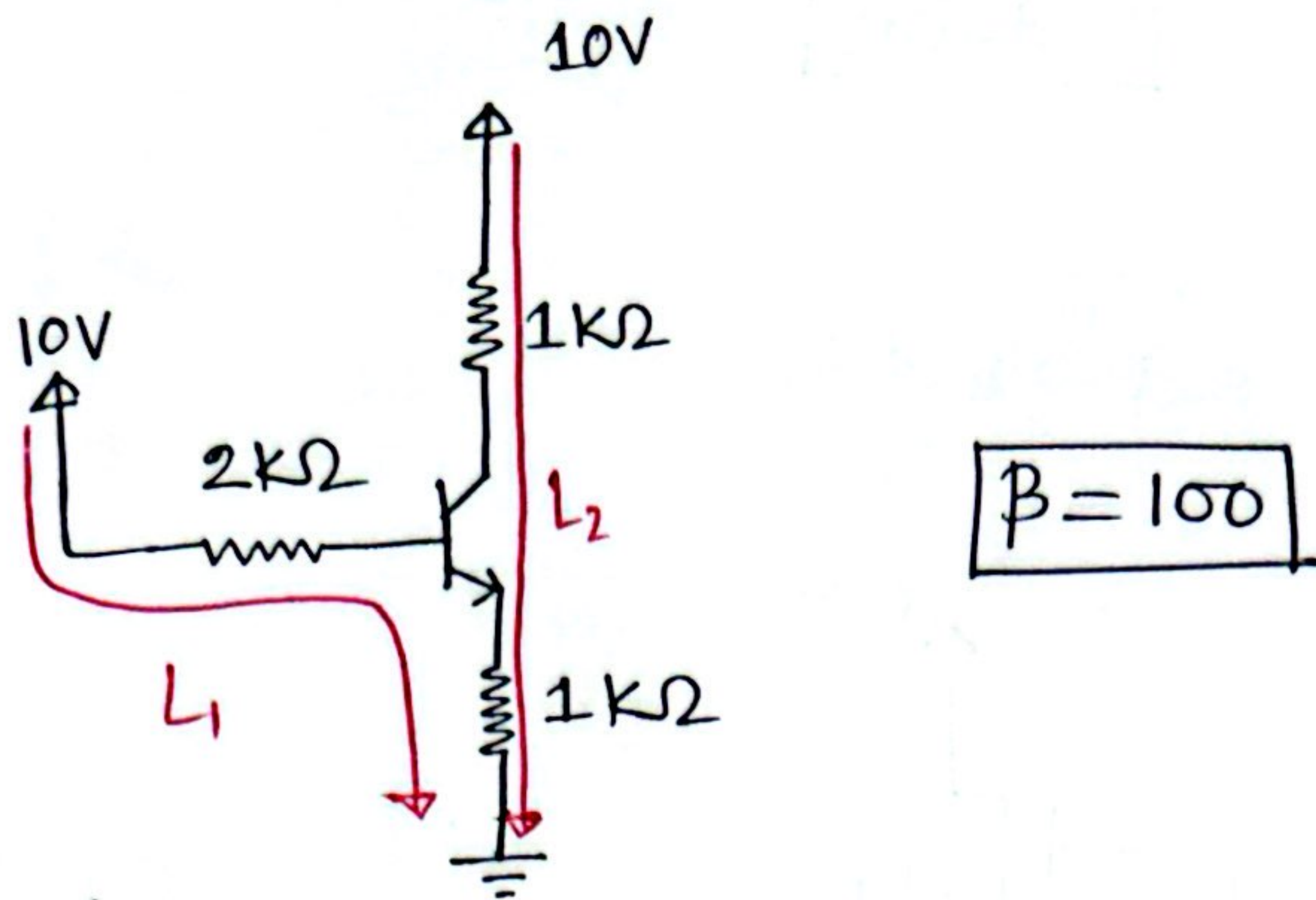

Assumption — Saturation

$$V_{BE, \text{sat}} = 0.8 \text{ V}$$

$$V_{CE, \text{sat}} = 0.2 \text{ V}$$

Applying KVL along L_1

$$-10 + 2I_B + 0.8 + I_E = 0$$

$$\Rightarrow 2I_B + I_E = 9.2 \quad \text{--- ①}$$

Applying KVL along L_2

$$-10 + I_C + 0.2 + I_E = 0$$

$$\Rightarrow I_E - I_B + I_E = 9.8$$

$$\Rightarrow 2I_E - I_B = 9.8 \quad \text{--- ②}$$

Solving ① & ②

$$I_B = 1.72 \text{ mA}$$

$$I_E = 5.76 \text{ mA}$$

$$\therefore I_C = 4.04 \text{ mA}$$

$$V_E = 5.76 \text{ V}$$

Validation:

$$\frac{I_C}{I_B} < \beta$$

$$\Rightarrow \frac{4.04}{1.72} < 100 \quad \boxed{\text{TRUE}}$$

(d) $T = (1.25 - 0.25) \text{ ms}$
 $= 1 \text{ ms}$

$f_{\text{out}} = 1 \text{ kHz}$

$V_{\text{avg}} = 10 + \left(\frac{20 - 10}{2} \right)$

$V_{\text{avg}} = 15 \text{ V}$

Question 2

Given,

$V_{\text{in}} = 10 \sin(200\pi t)$

$f_{\text{in}} = 100 \text{ Hz}$

$f_{\text{out}} = 100 \text{ Hz}$

Design requirement:- H.W. rectifier

$V_{\text{out(max)}} \Rightarrow 10 - 0.7 = 9.3 \text{ V}$


$V_{\text{p-p}} = 0.93 \text{ V}$

$V_{\text{p-p}} = \frac{V_{\text{out(max)}}}{f_{\text{out}} RC}$

Assuming $R = 5 \text{ k}\Omega$



$C = \frac{9.3}{0.93 \times 100 \times 5 \times 10^3}$
 $= 20 \mu\text{F}$

Designed ckt:

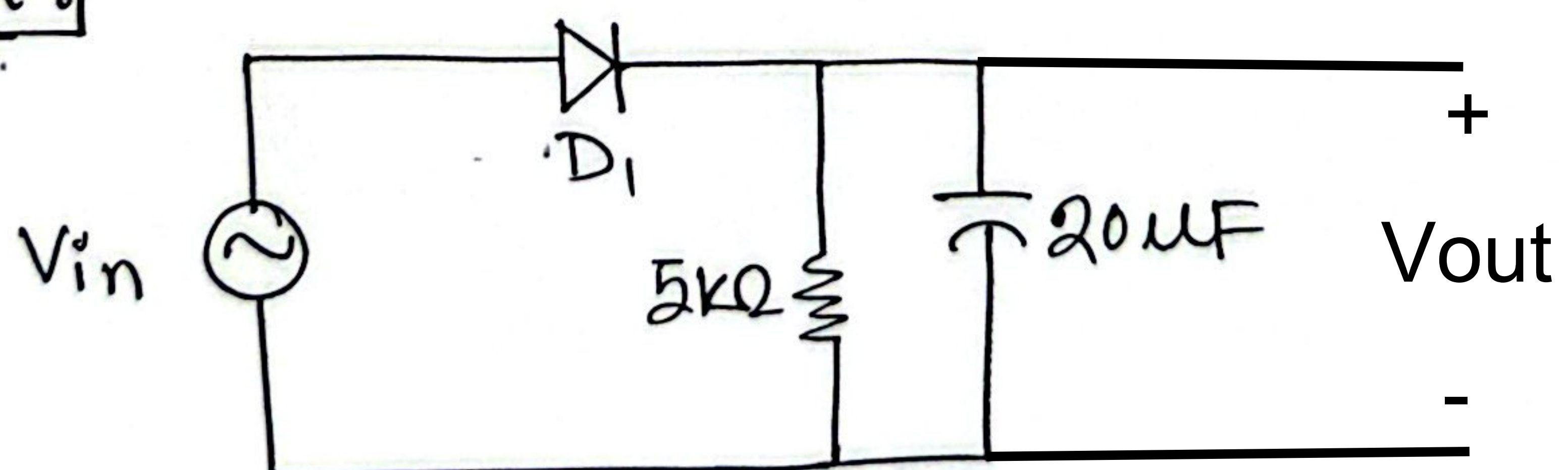


(b) $f = \bar{C}A + \bar{A}B + \bar{B}C = O_1 + O_2 + O_3$

④

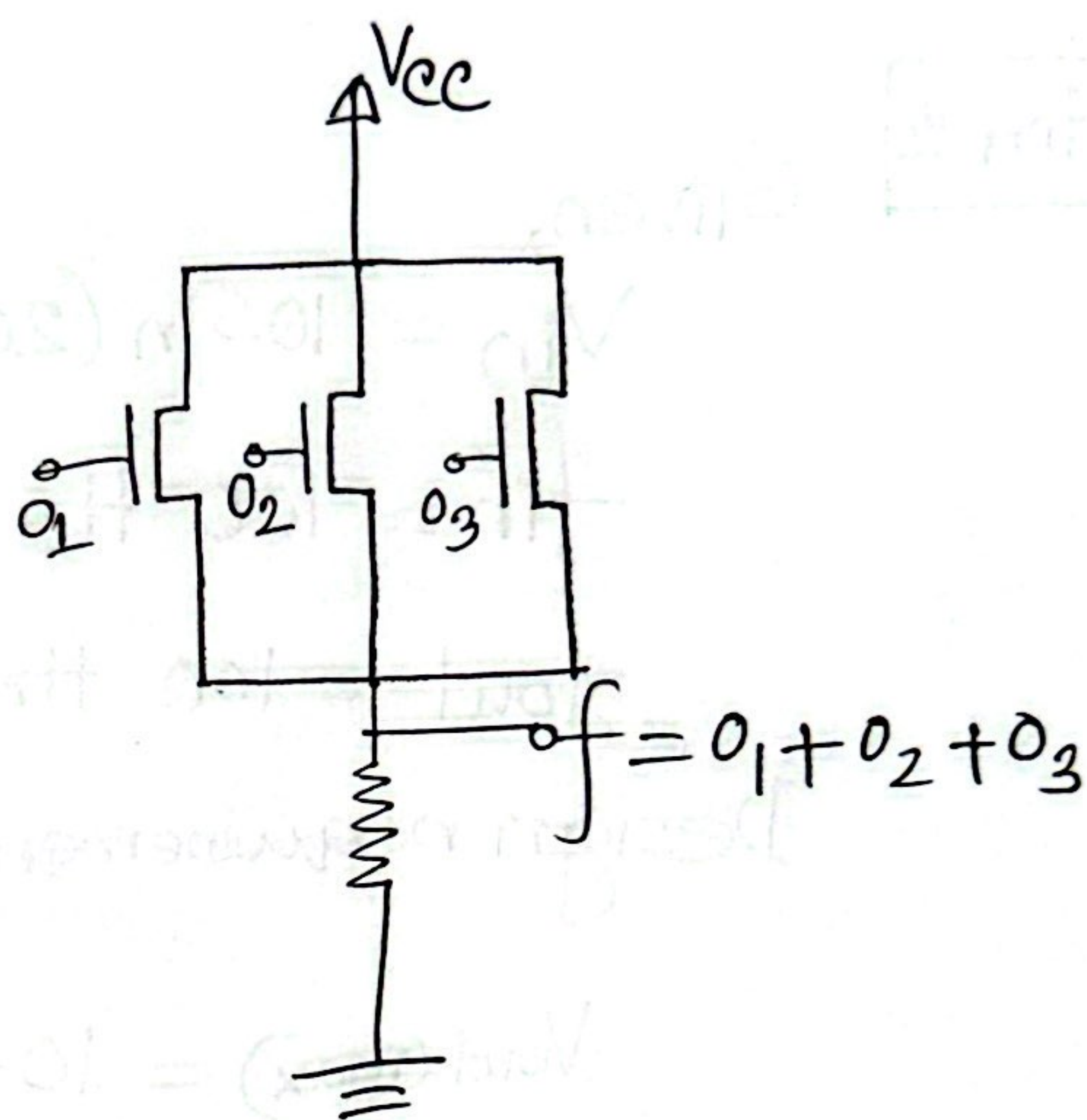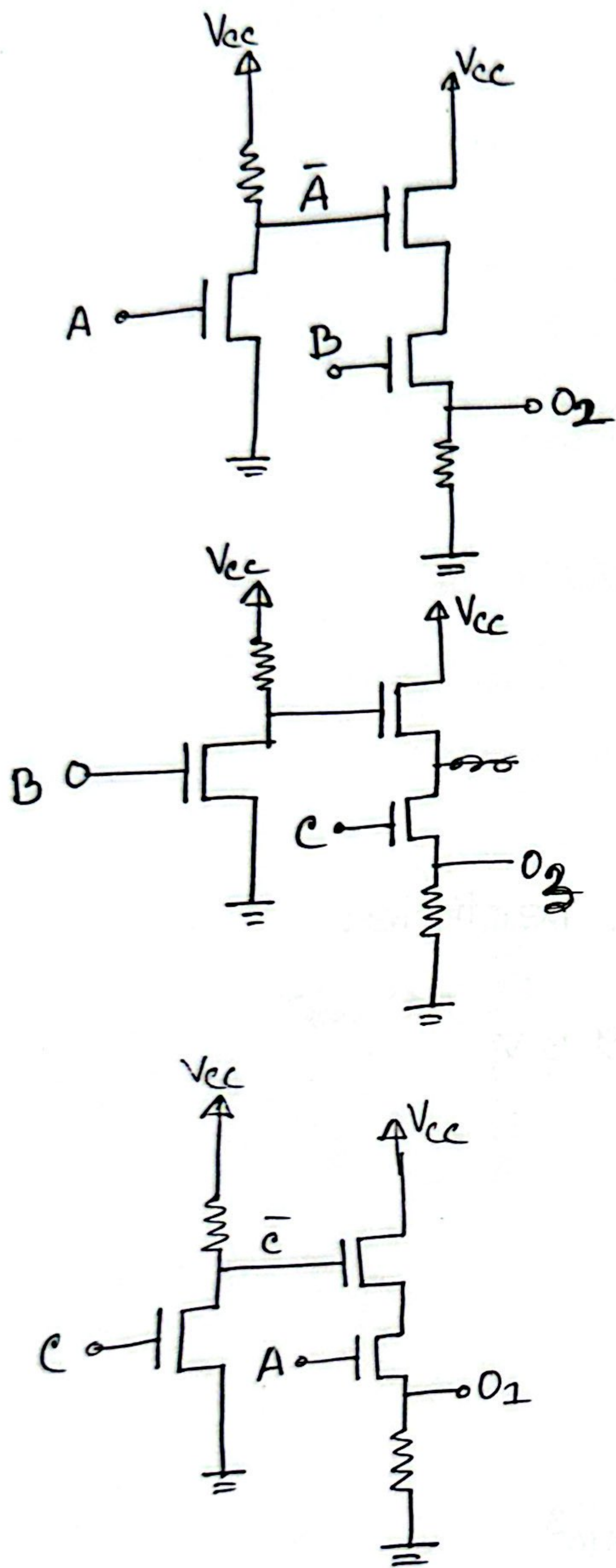

Question 3

(a)

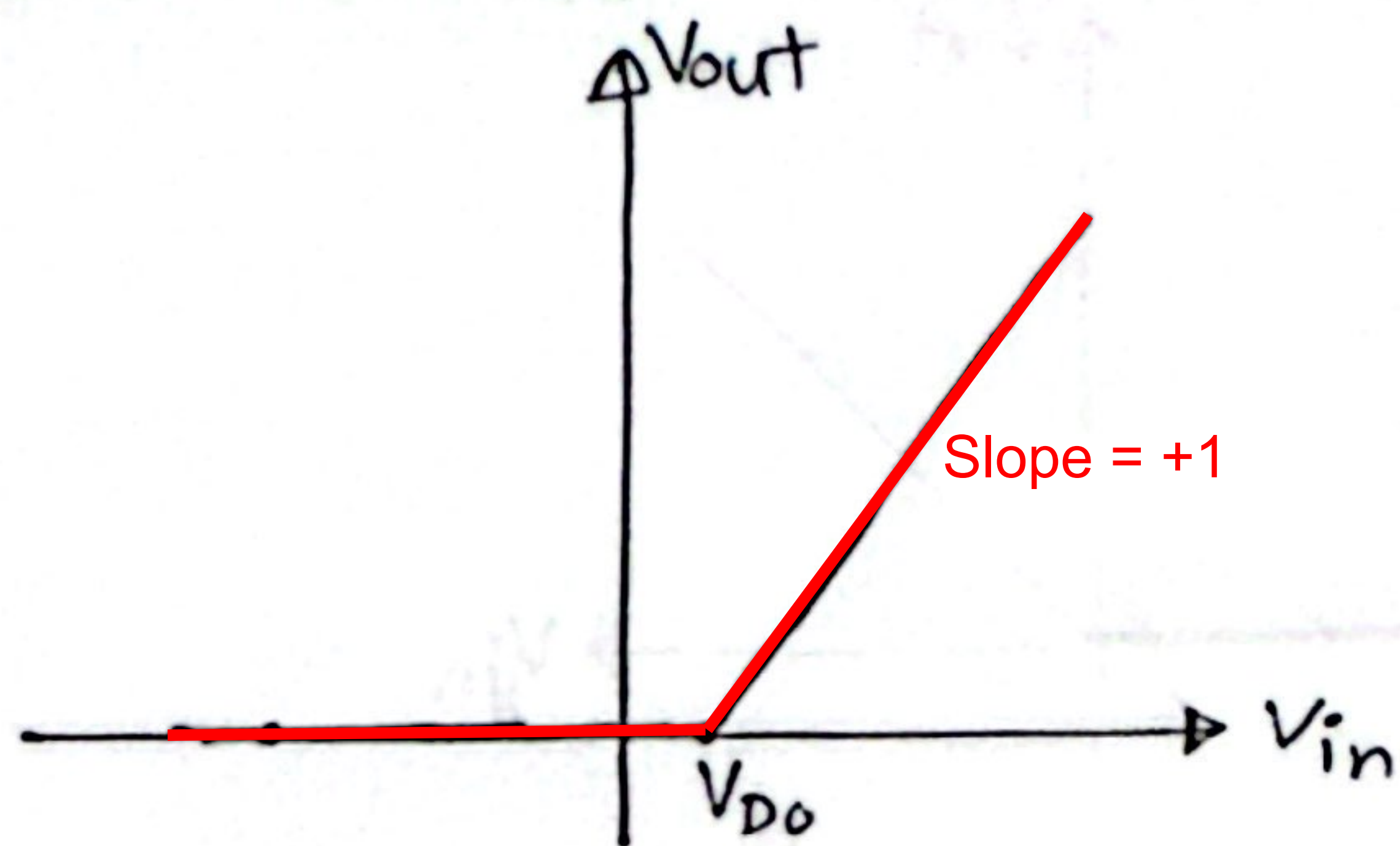

(b) BJT is an electronic device. The "Saturation" & "Cutoff" region in the I-V graph of a BJT is almost similar to the "ON" state & the "OFF" state in the I-V graph of a switch respectively. This resemblance allows BJTs to act like switches by turning current flow ON or OFF electronically. Hence, BJTs can be used as an electronic switches.

(c)

