Section: 07 Faculty: TAV




Assessment: Quiz 2 Duration: 30 minutes Date: July23, 2025 Full Marks: 20


No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed. At the end of the exam, both the answer script and the question paper must be returned to the invigilator. All the questions are compulsory. Marks allotted for each question are mentioned beside each question. Symbols have their usual meanings.

Question 1 of 2

For the circuits shown below, using ideal diode model, find the values of the voltages and currents indicated.

[CO3] [10 marks]

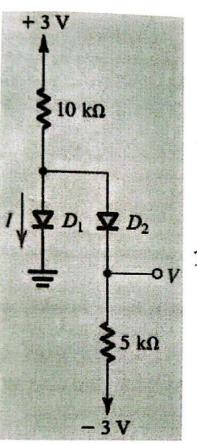

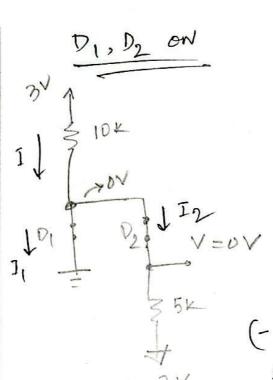

$$I = \frac{3-0}{10}, I_2 = \frac{0-(-3)}{5}$$


$$I = 0.3, I_2 = 0.6$$

$$I = I_1 + I_2$$

$$\Rightarrow I_1 = I - I_2$$

$$= 0.3 - 0.6 = 8 - 0.3 \text{ mA}$$

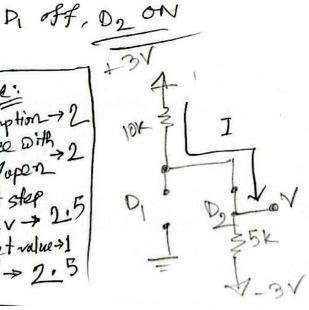(- II) flows from n to p. so, assumption arong



$$J = \frac{3^{-V}}{10} = \frac{V - (-3)}{5}$$

$$\Rightarrow 3^{-V} = 2V + 6$$

$$\Rightarrow 3V = -3$$

$$\Rightarrow V = -1$$

$$\therefore j = \frac{3 - (-1)}{10} = 0.4m A$$


$$J \text{ positive } \rightarrow D_2 \text{ oN}$$

$$D_1 \Rightarrow V_{\eta} - V_{\rho} = 0 - (-1) = 1 \rightarrow so. \text{ of } D_{\eta}$$

Question 2 of 2

[CO3] [5+5 marks]

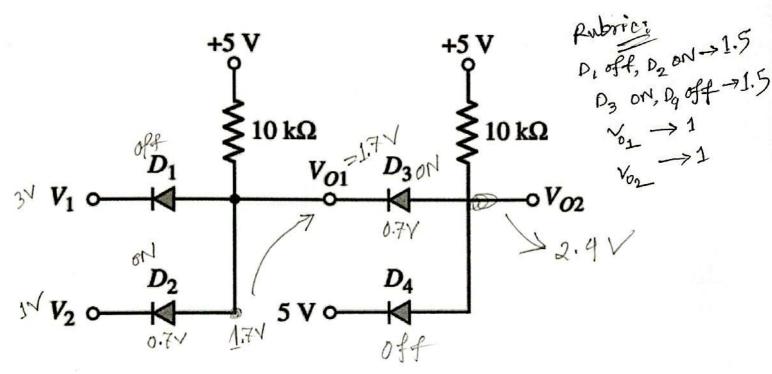(a) Design a circuit to implement (A+B).C.D using diodes
(b) Determine Vo2 for the circuit below if V1 = 3V and V2 = 1 V. Use CVD model with VDo= 0.7 V.



(b) both AND Gate structure.

