

Practice Problem Set 1

CSE251 - Electronic Devices and Circuits

ALTERNATIVE REPRESENTATION OF CIRCUITS

Circuit drawing, KCL, and KVL


[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)


Problem 1

- Draw an alternative representation of the following circuit minimizing the number of floating voltage sources.

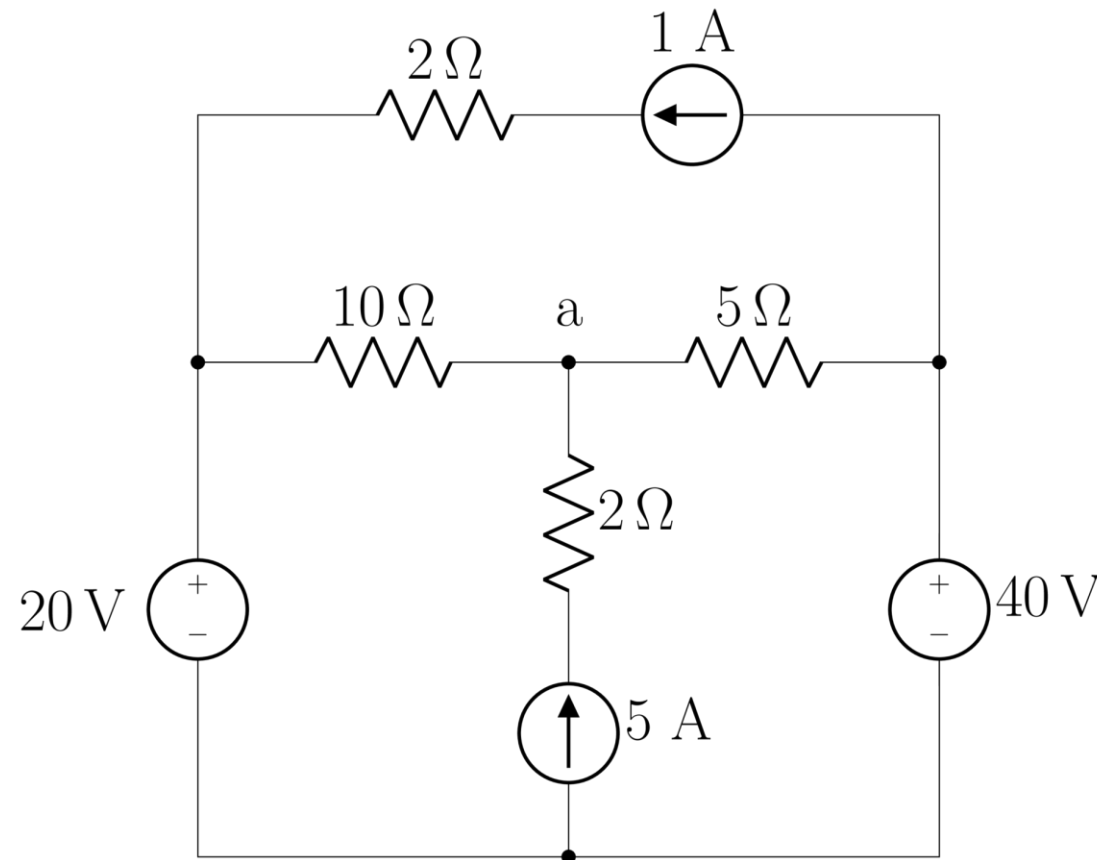


Problem 2

- Draw an alternative representation of the following circuit minimizing the number of floating voltage sources.
- Using KCL, solve for I_x and I_y .

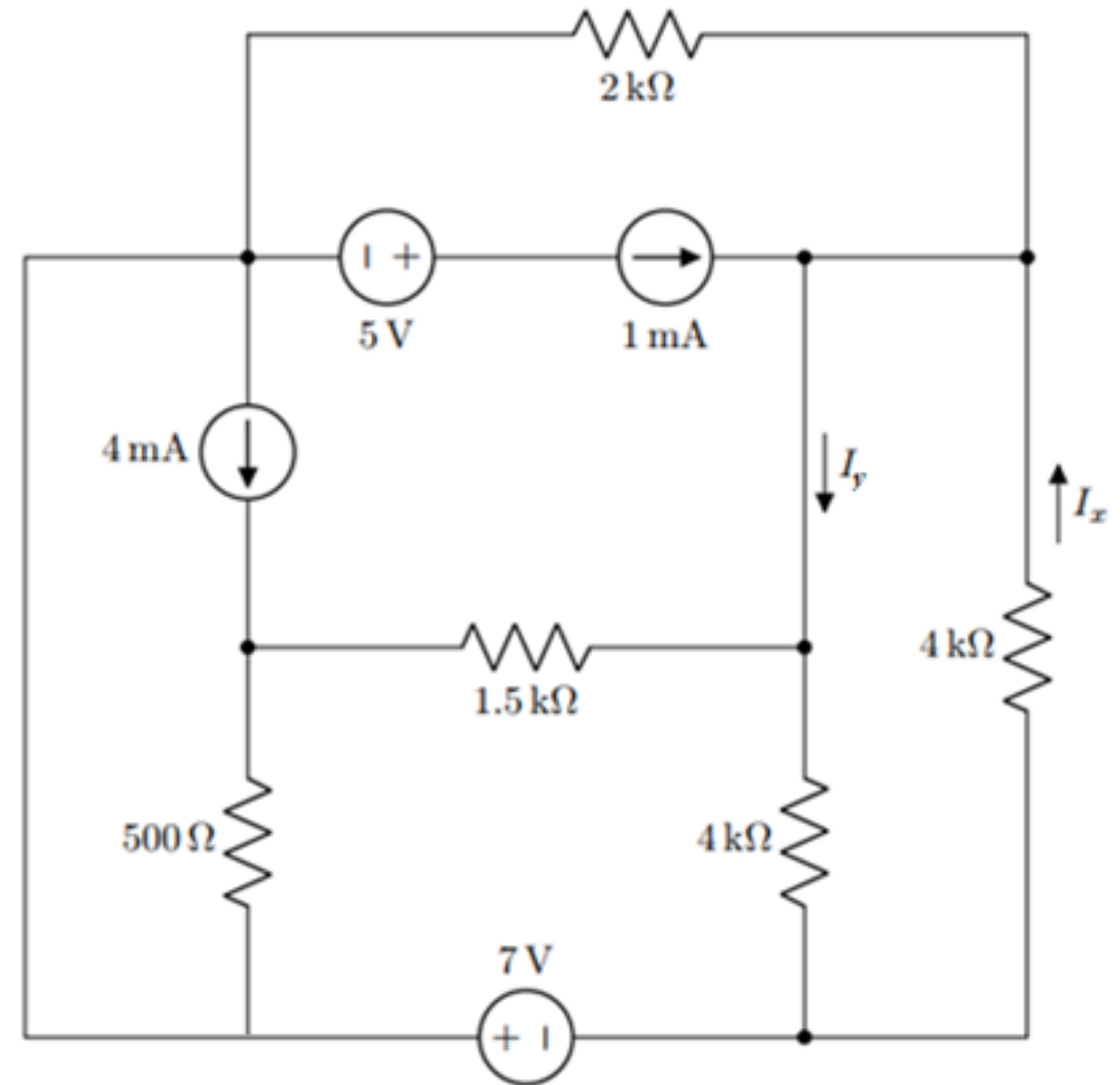


Problem 3

- Draw an alternative representation of the following circuit minimizing the number of floating voltage sources. Using KCL, determine i_x .

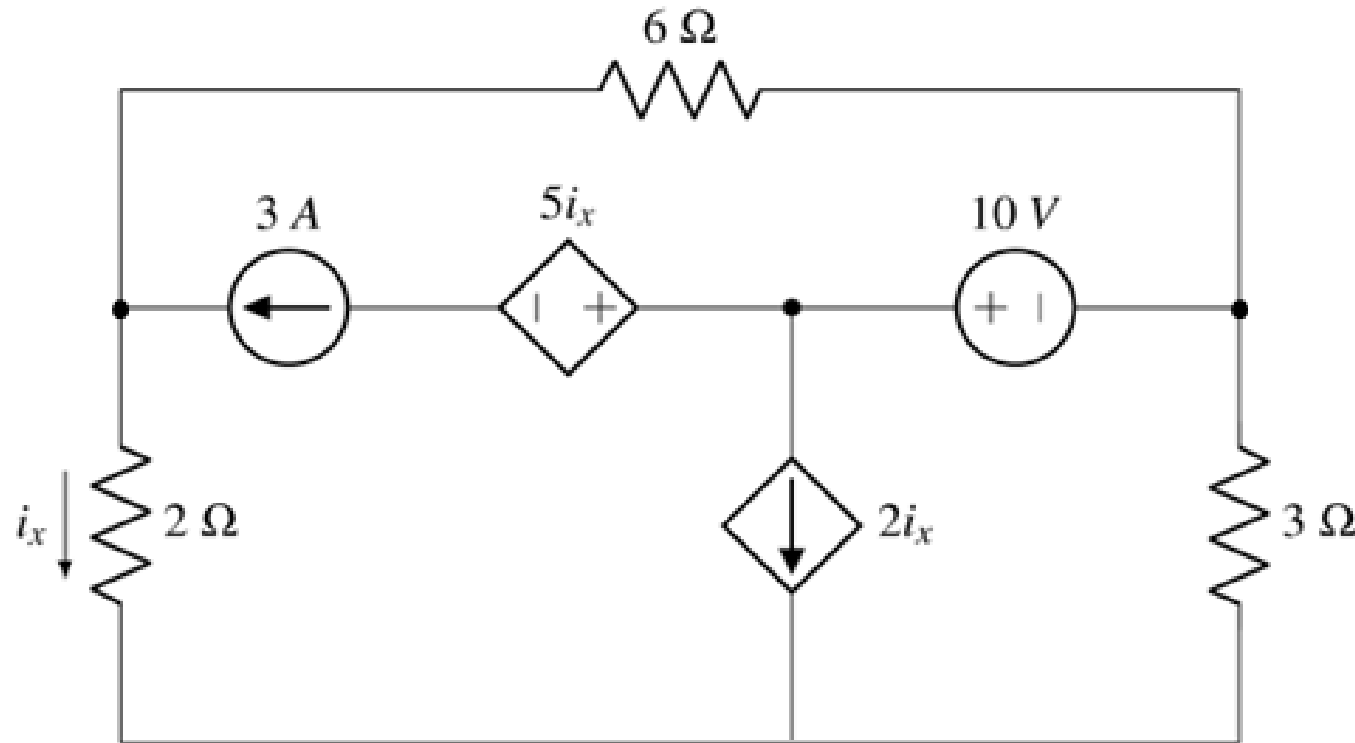


Problem 4

- Draw an alternative representation of the following circuit minimizing the number of floating voltage sources. Write all the KCL equations needed to solve this circuit.

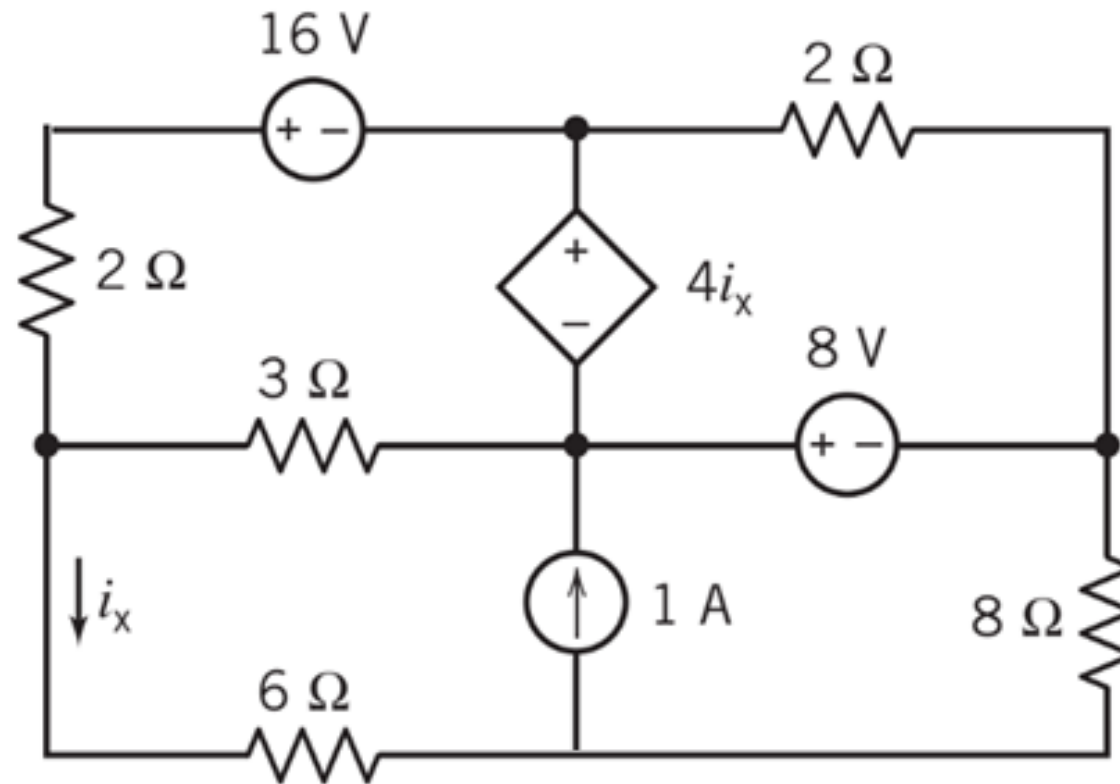


Problem 5

- Draw an alternative representation of the following circuit minimizing the number of floating voltage sources. Using KVL, solve for i_x .

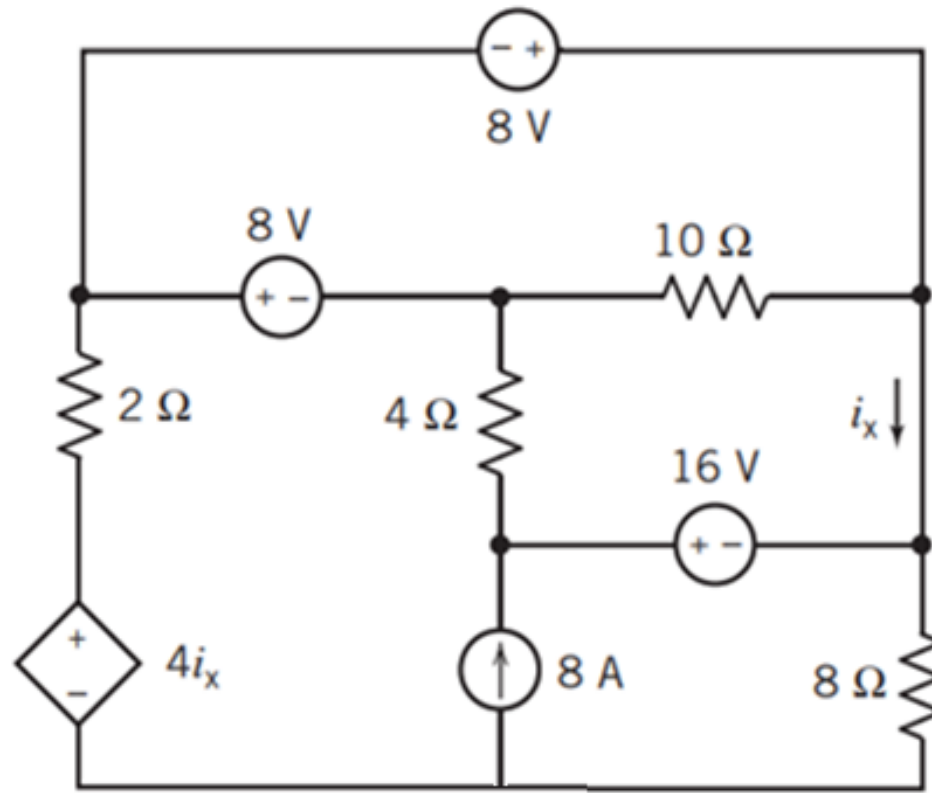


Problem 6

- How many KVL equations we can derive from the following circuit that are solvable? Draw an alternative representation minimizing the number of floating voltage sources. Solve for i_o using circuit laws as necessary.

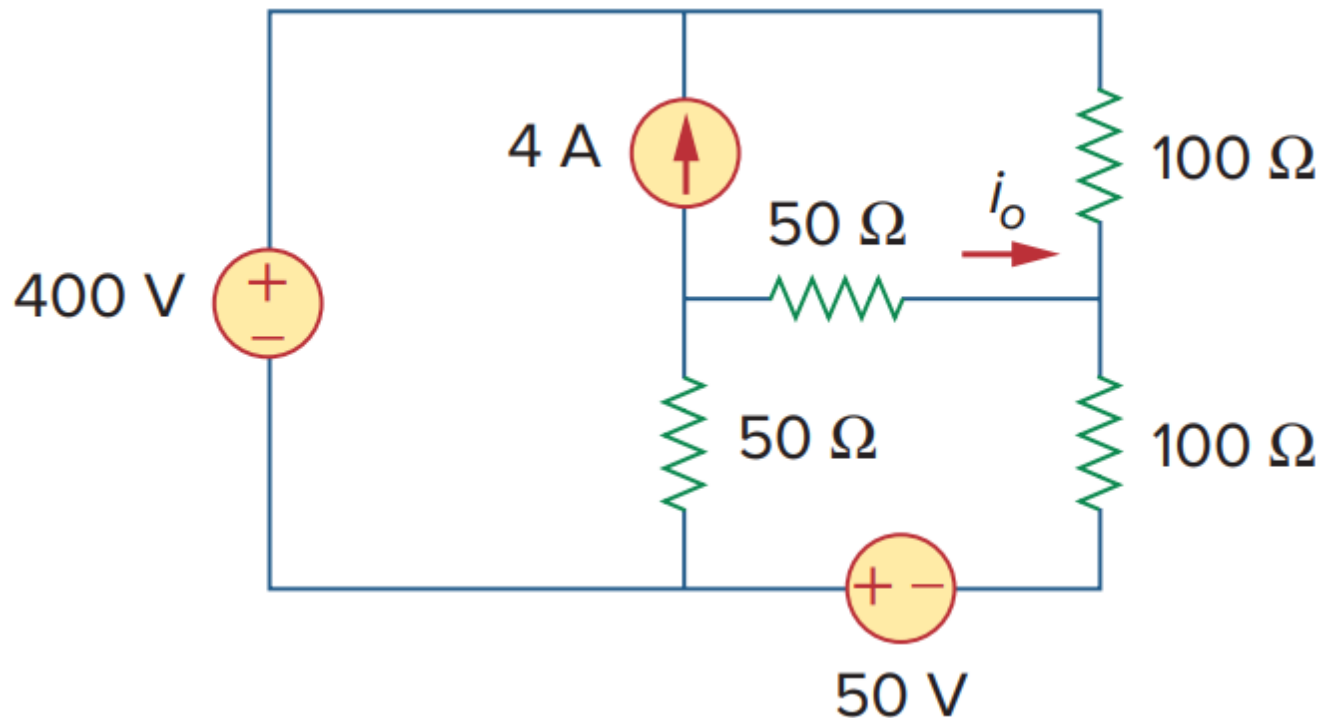


Problem 7

- Draw a loop representation of the adjacent circuit.

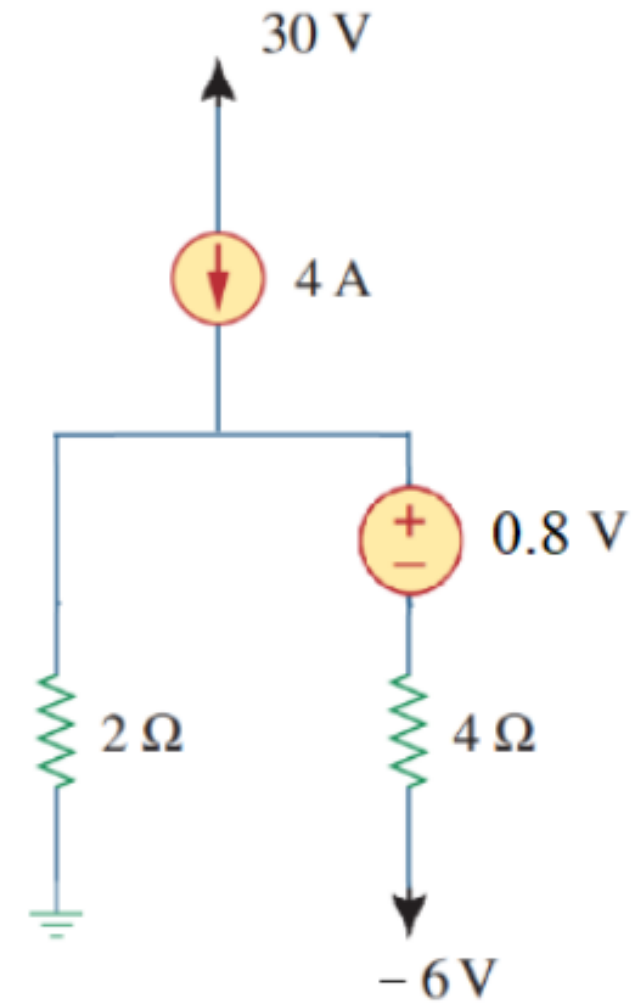


Problem 8

- Determine V_1 using KCL.
- Draw a loop representation of the circuit.

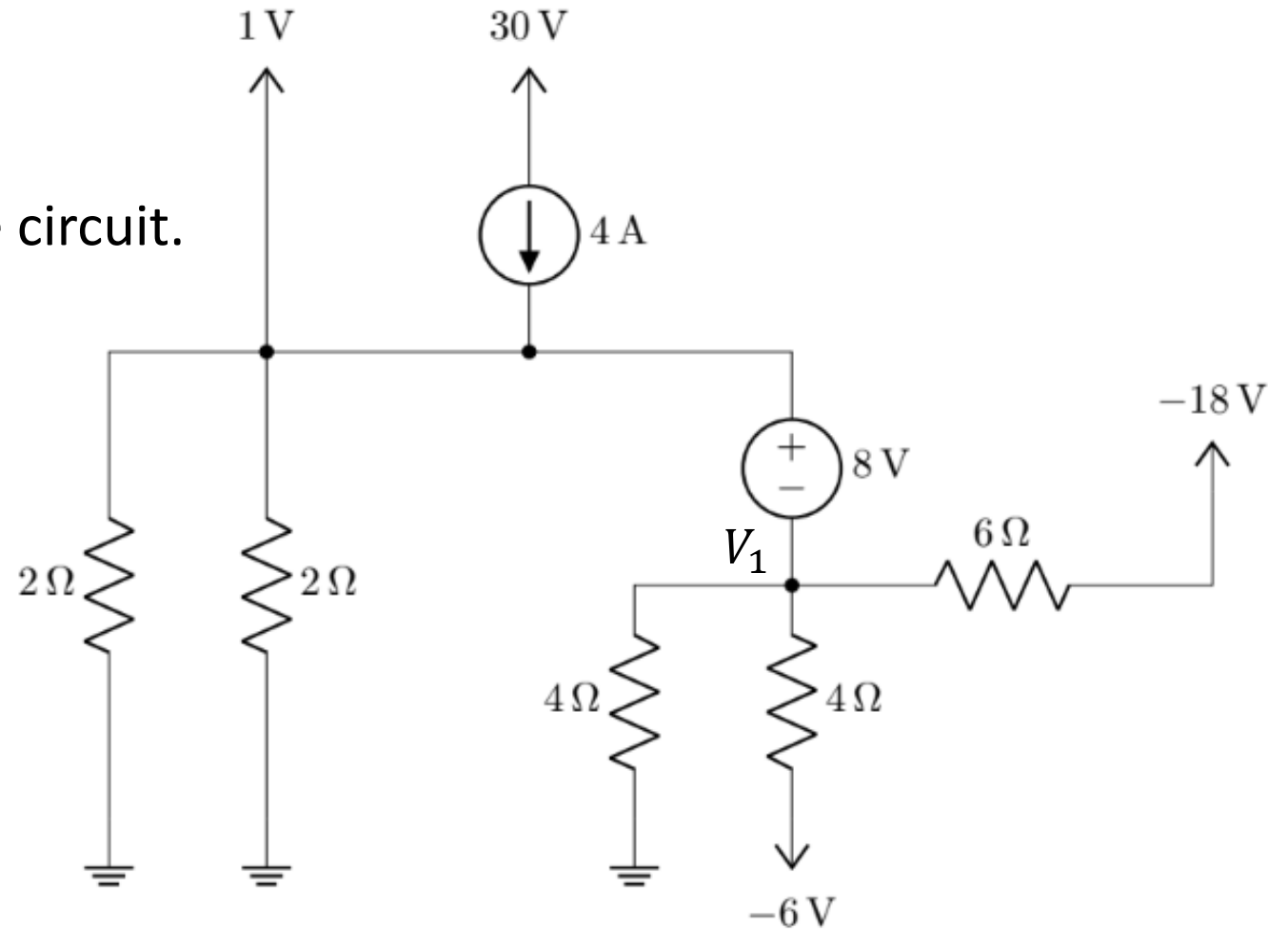


Problem 9

- Write KVL equations along the indicated arrows: **maroon** and **blue**.

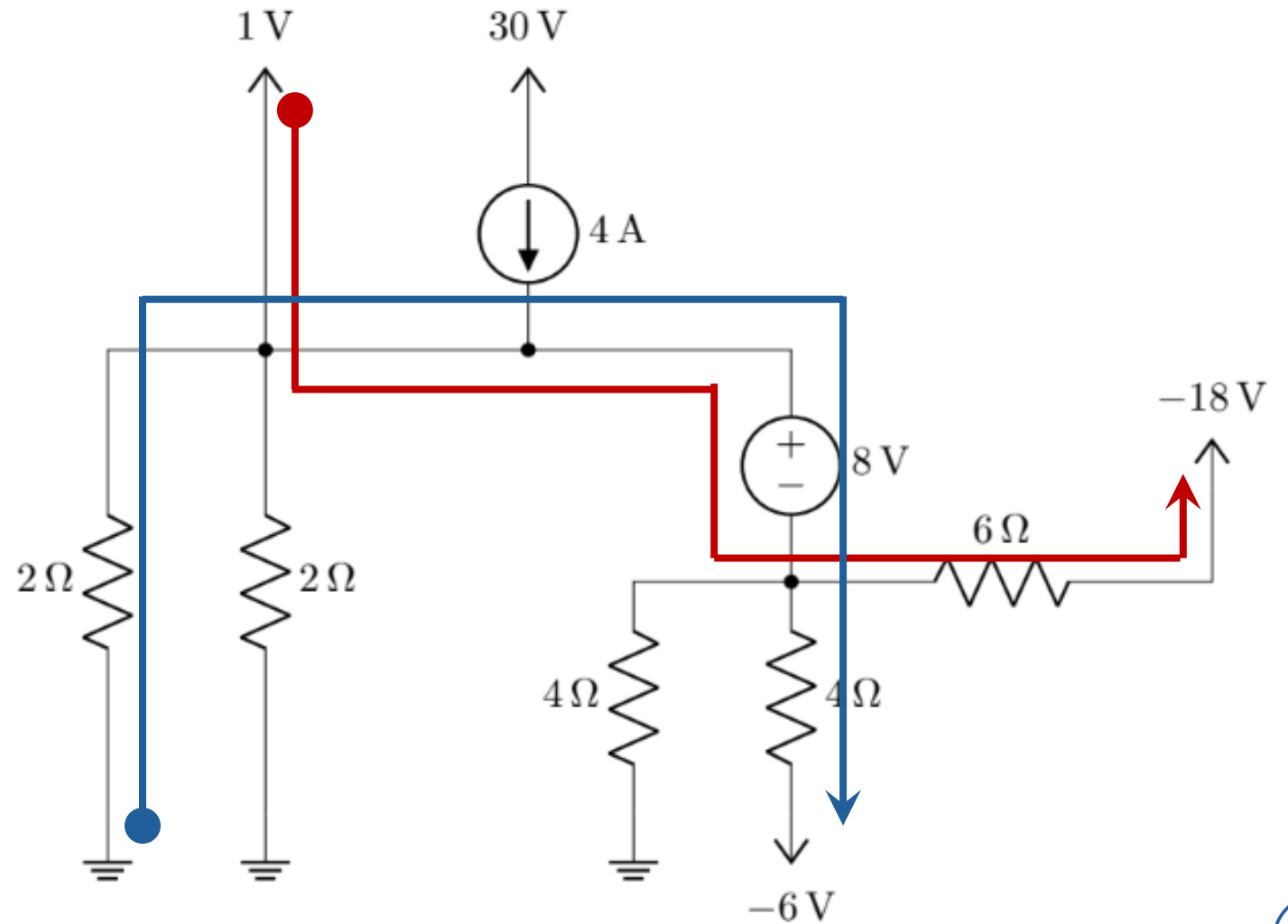


Problem 10

- Determine the voltage V_o and the voltage across the 5 A source using KCL.
- Can you solve it using KVL only? If not, why?

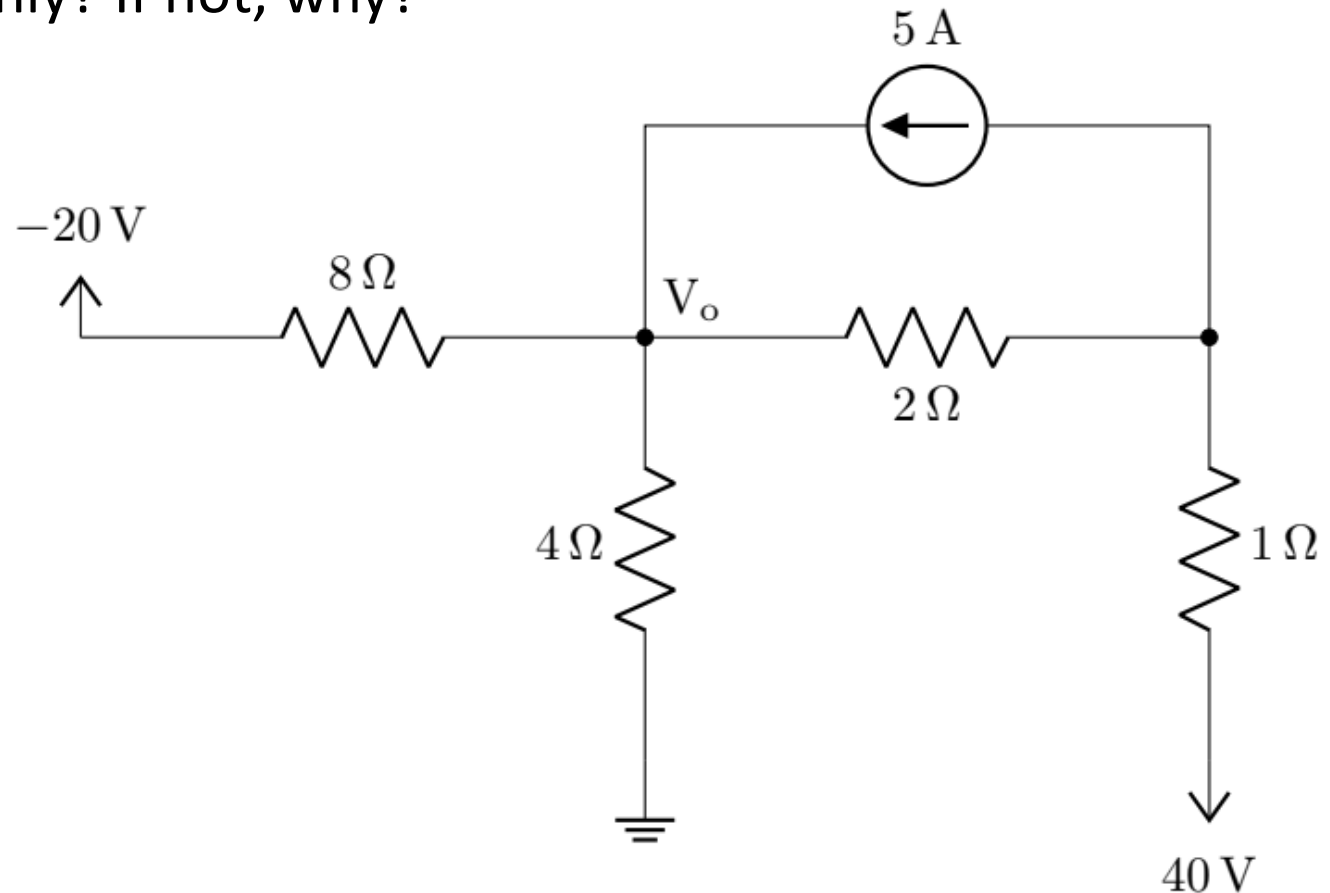


Problem 11

- For the circuit shown below, determine the voltage across the 1 mA current source using KVL. Do not use KCL.

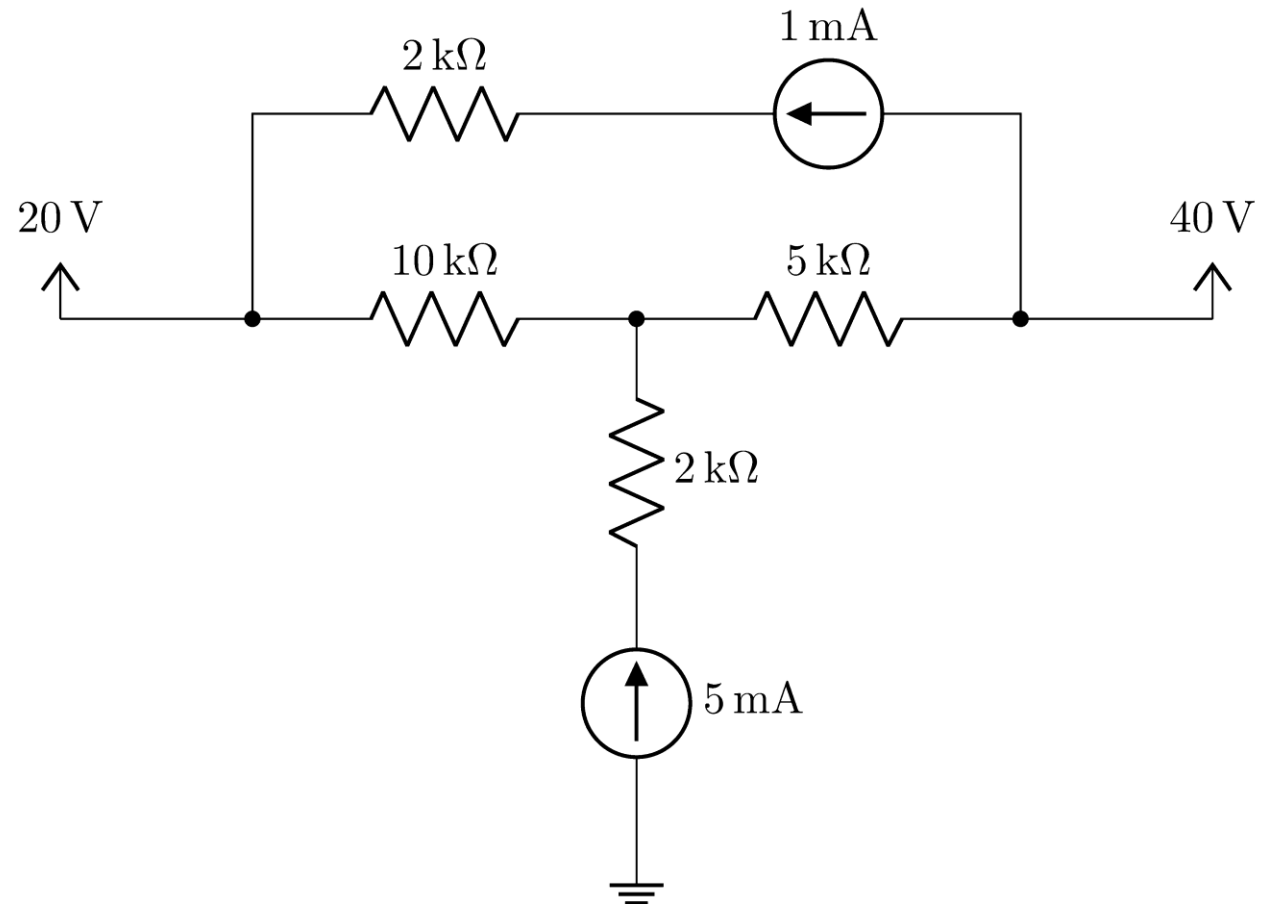

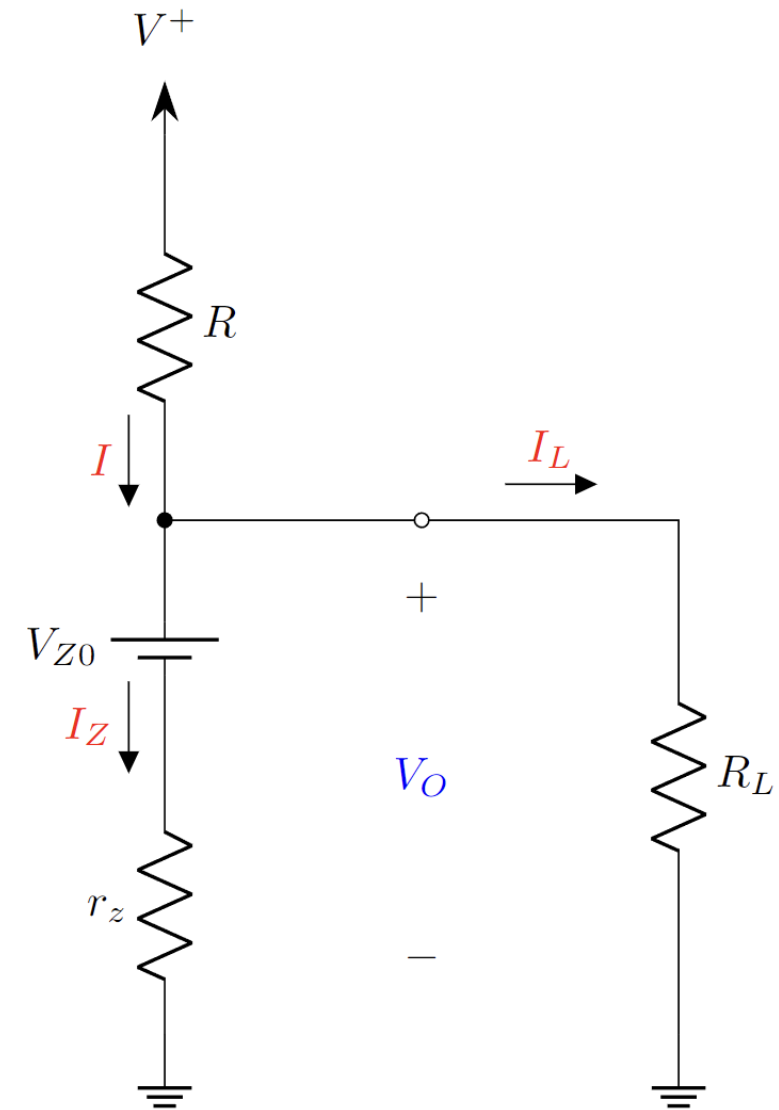Problem 12

- For $R = 100\ \Omega$, $R_L = 10\ \text{k}\Omega$, $r_z = 20\ \Omega$, $V_{Z0} = 3\ \text{V}$, and $I_Z = 1\ \text{mA}$, determine V_o , I_L , I , and V^+ .



Acknowledgement and References

Some of the problems in this set are taken or adapted from the following sources:

1. Sadiku, M. N. O., Fundamentals of Electric Circuits, McGraw-Hill
2. Dorf, R. C., & Svoboda, J. A., Introduction to Electric Circuits, Wiley