

Practice Problem Set 3.2

CSE251 - Electronic Devices and Circuits

DIODE CIRCUIT MODELS

Method of assumed states, Exponential Model, and
Piecewise Linear Models: CVD+R and CVD


[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)

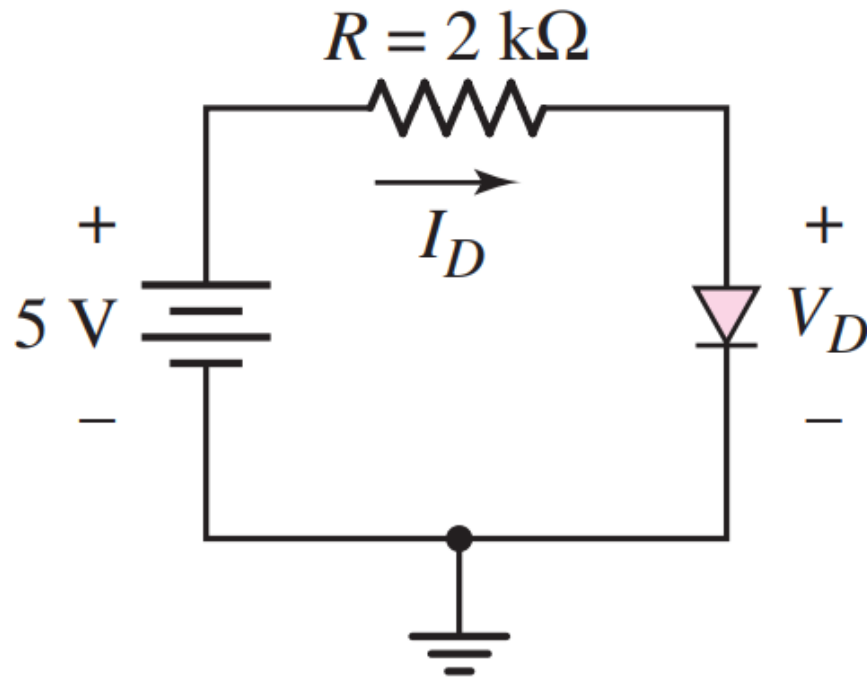Problem 1

- If the diode in the following circuit has a reverse saturation current $I_o = 10^{-13} \text{ A}$, follow an iterative approach and write a program to determine I_D and V_D . Assume the ideality factor $\eta = 1$ and the thermal voltage $V_T = 25 \text{ mV}$.





Hint: There will be two simultaneous equations: one is the diode's current-voltage relation and the other is the result of applying KVL around the loop.

$$I_D = I_o \left(e^{\frac{V_D}{\eta V_T}} - 1 \right) \text{ and } I_D = -\frac{1}{2} V_D + \frac{5}{2}$$

Take an array of V_D with values in a reasonable range. For example, from 0.400 V to 0.800 V . For each V_D , evaluate I_D using both the equations. The value of V_D for which both the equations of I_D yields the closest value is the answer.

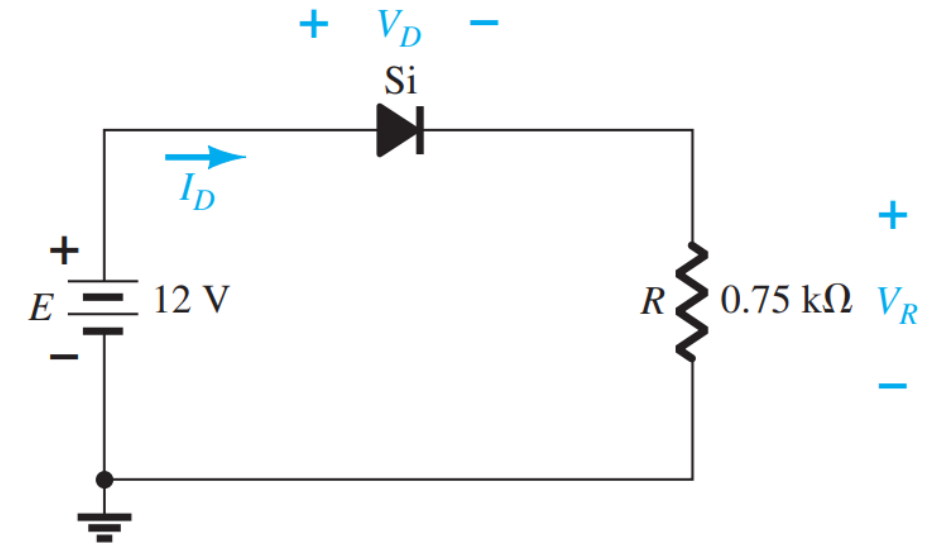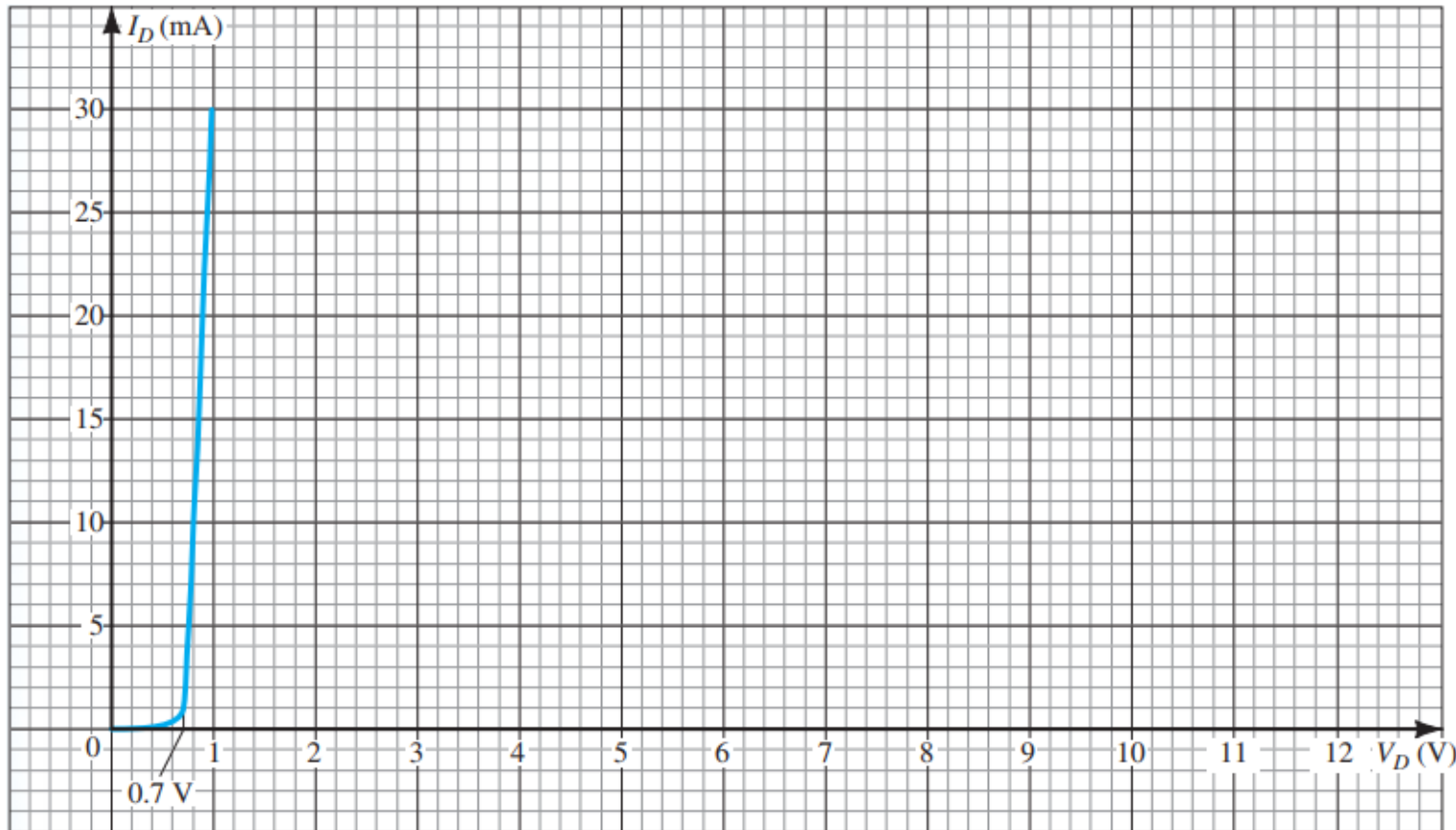Problem 2


- The $I - V$ characteristic of the diode in the following circuit has been plotted below. Determine I_D and V_D .



Ans: $I_D = 15 \text{ mA}$, $V_D = 0.82 \text{ V}$

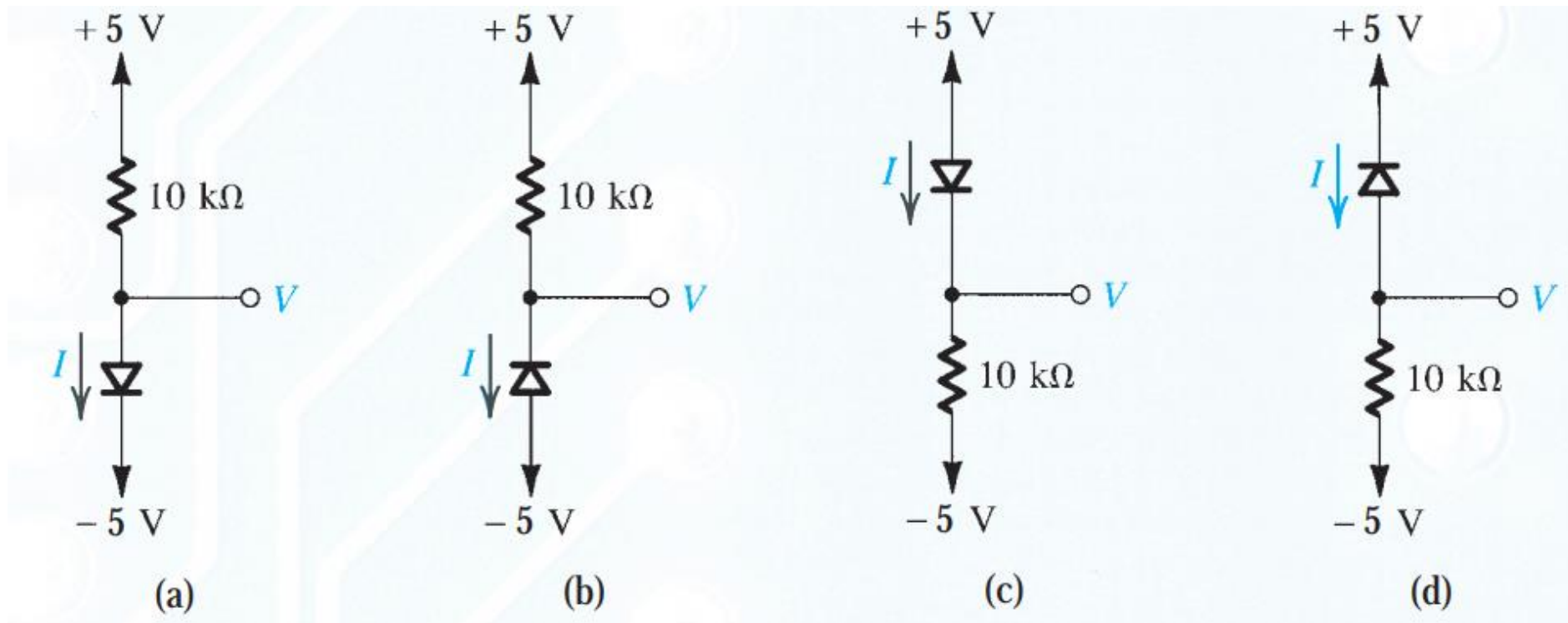Problem 3



- For the circuits shown below, using ideal diode model, find the values of the voltages and currents indicated.



Ans: (a) $I = 1\text{ mA}$, $V = -5\text{ V}$; (b) $I = 0\text{ mA}$, $V = 5\text{ V}$; (c) $I = 1\text{ mA}$, $V = 5\text{ V}$; (d) $I = 0\text{ mA}$, $V = -5\text{ V}$

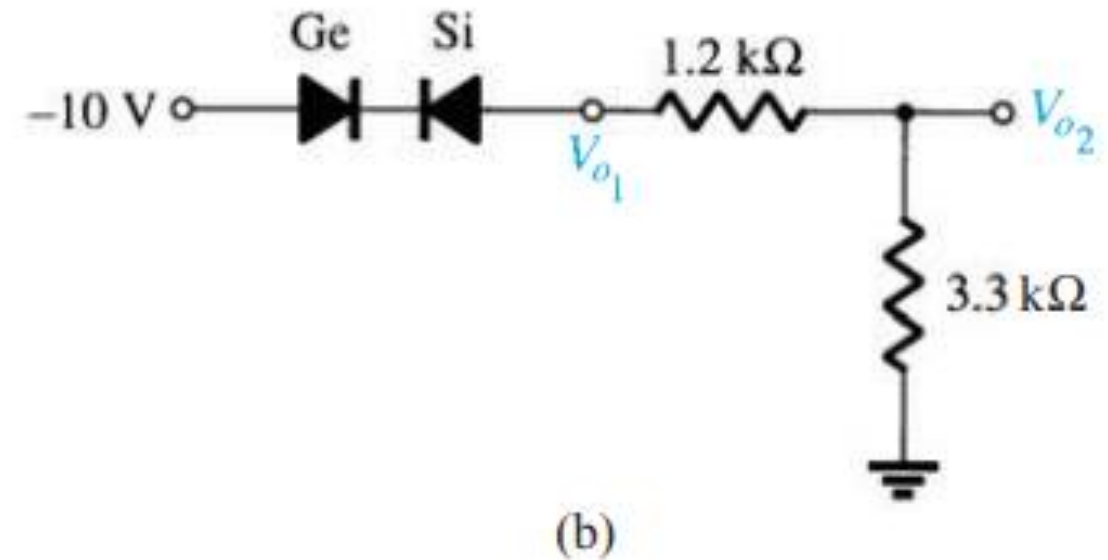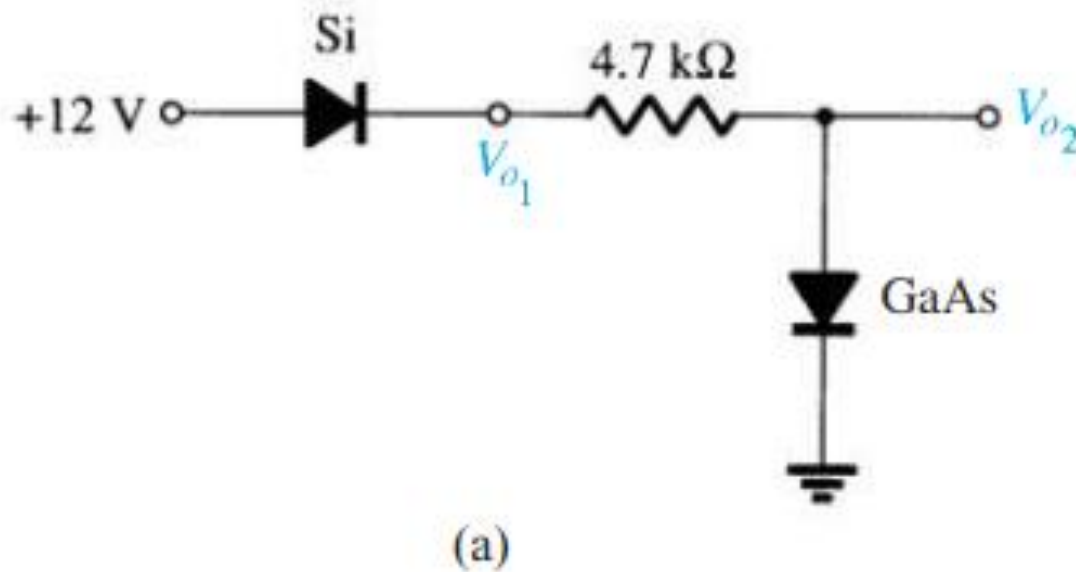Problem 4



- Determine V_{o1} and V_{o2} for the circuits shown below. Use $CVD + R$ Model with $V_{D_{o, Si}} = 0.7\text{ V}$, $r_o = 20\ \Omega$, $V_{D_{o, Ge}} = 0.3\text{ V}$, $r_o = 10\ \Omega$, and $V_{D_{o, GaAs}} = 1.2\text{ V}$, $r_o = 5\ \Omega$.



Ans: (a) $V_{o1} = 11.3\text{ V}$, $V_{o2} = 1.21\text{ V}$; (b) $V_{o1} = 0\text{ V}$, $V_{o2} = 0\text{ V}$

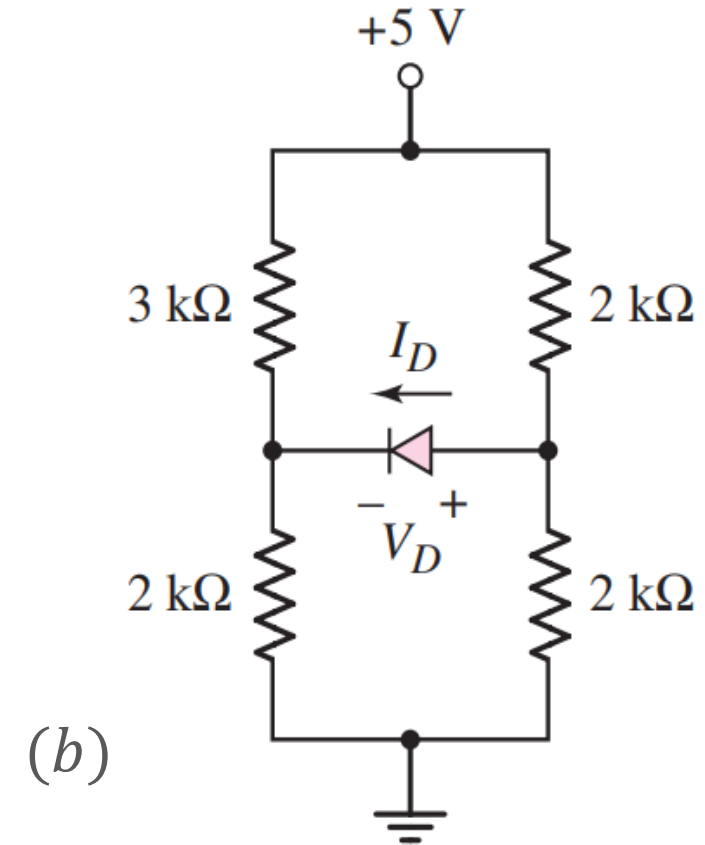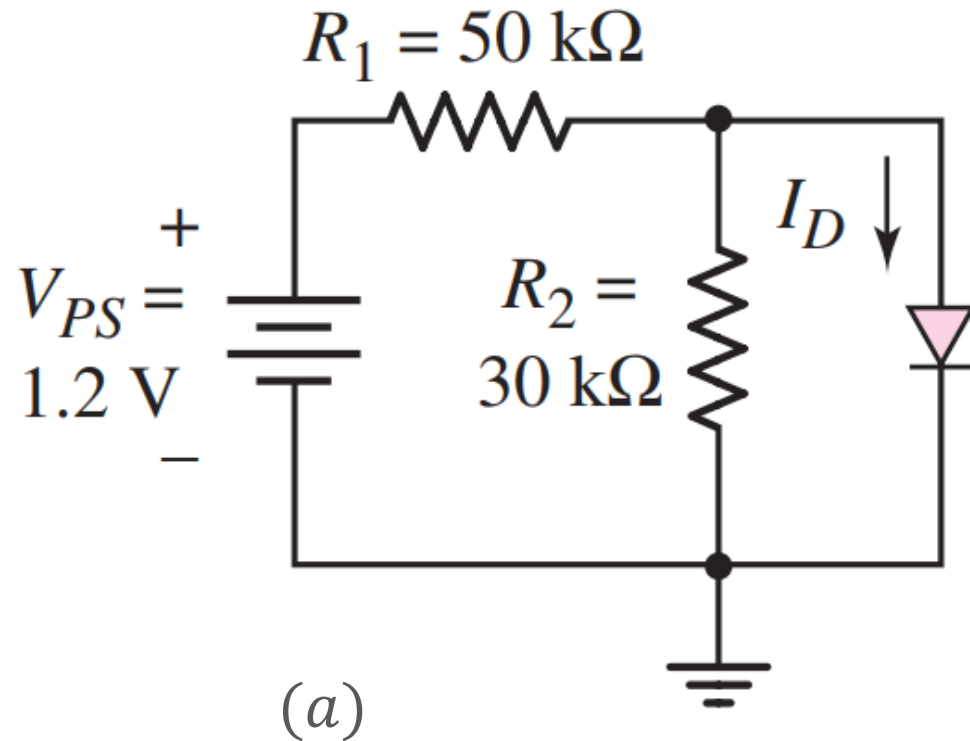Problem 5


- For the circuits shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), find I_D .



Ans: (a) $I_D = 0\text{ mA}$; (b) $I_D = 0\text{ mA}$

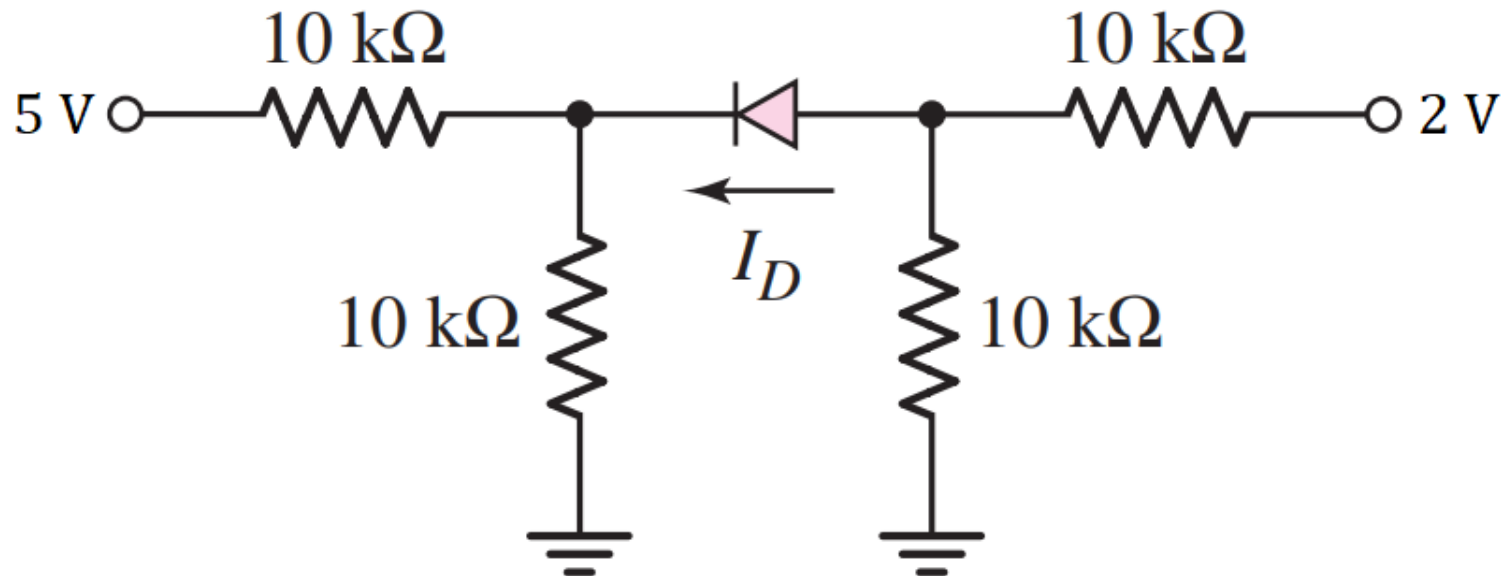Problem 6



- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine I_D .



Ans: $I_D = 0\text{ mA}$

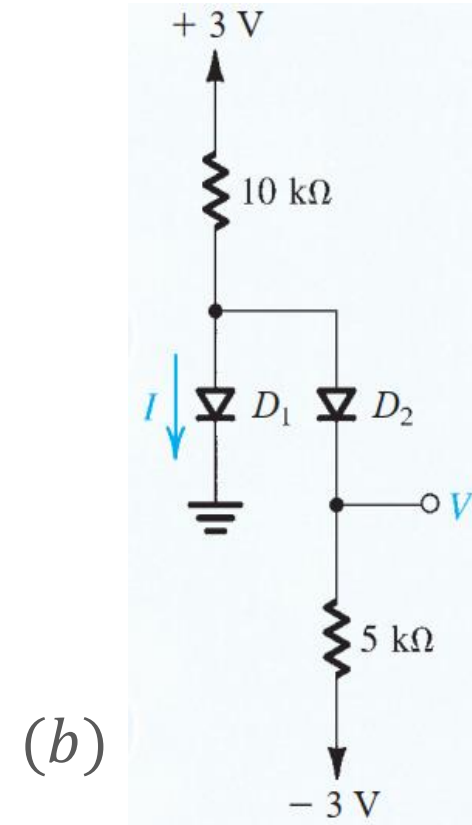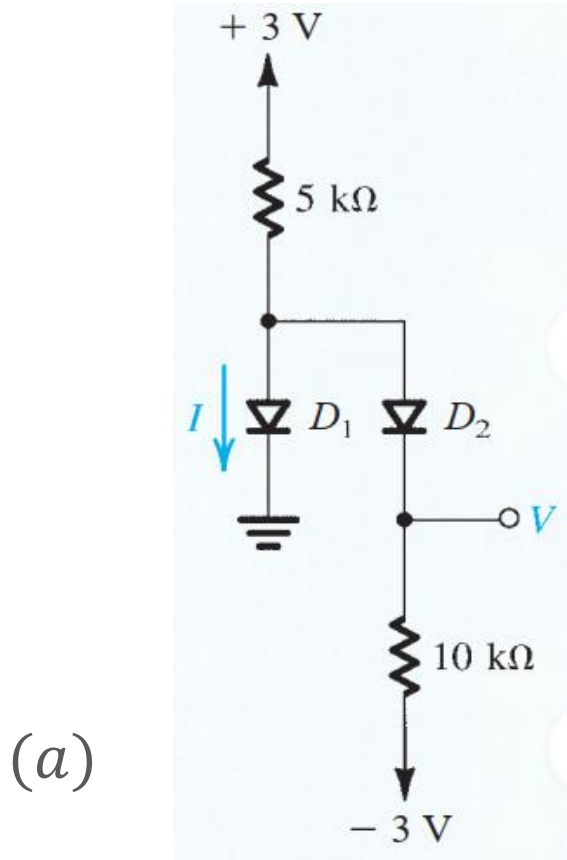Problem 7


- For the circuits shown below, using ideal diode model, find the values of the voltages and currents indicated.



Ans: (a) D_1 ON, D_2 ON, $I = 0.3 \text{ mA}$, $V = 0 \text{ V}$; (b) D_1 OFF, D_2 ON, $I = 0 \text{ mA}$, $V = -1 \text{ V}$

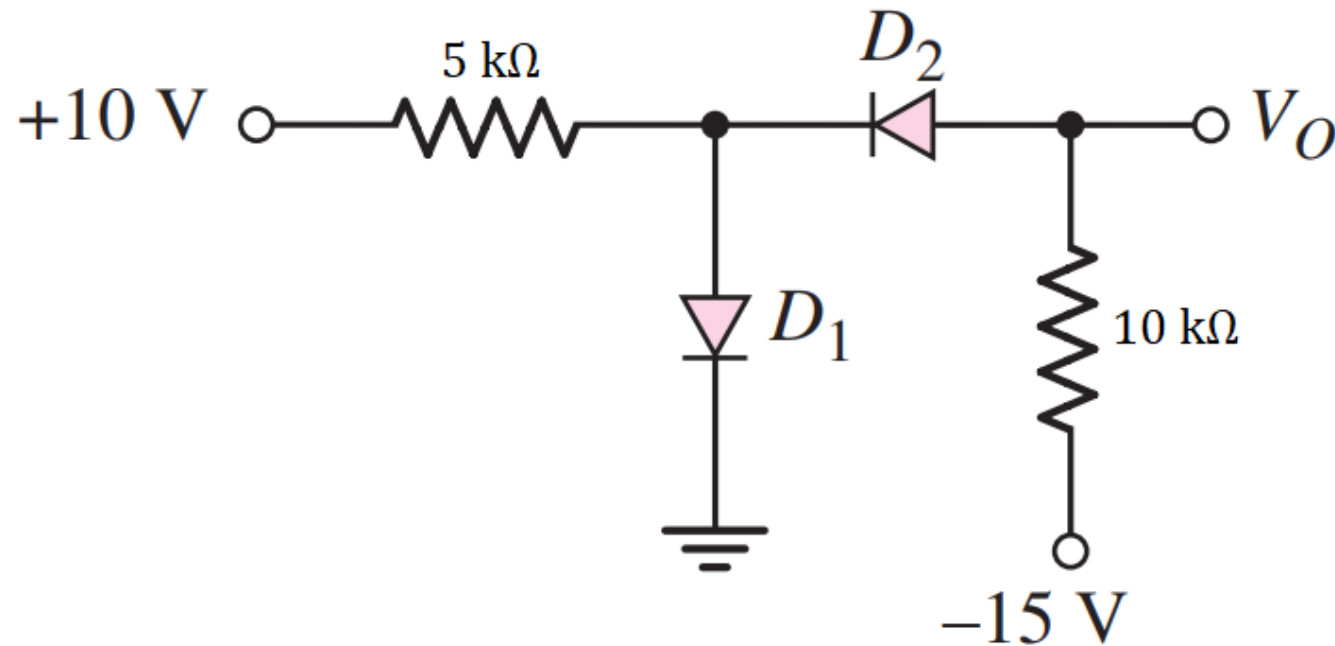Problem 8


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_O .



Ans: D_1 ON, D_2 OFF, $V_O = -15\text{ V}$

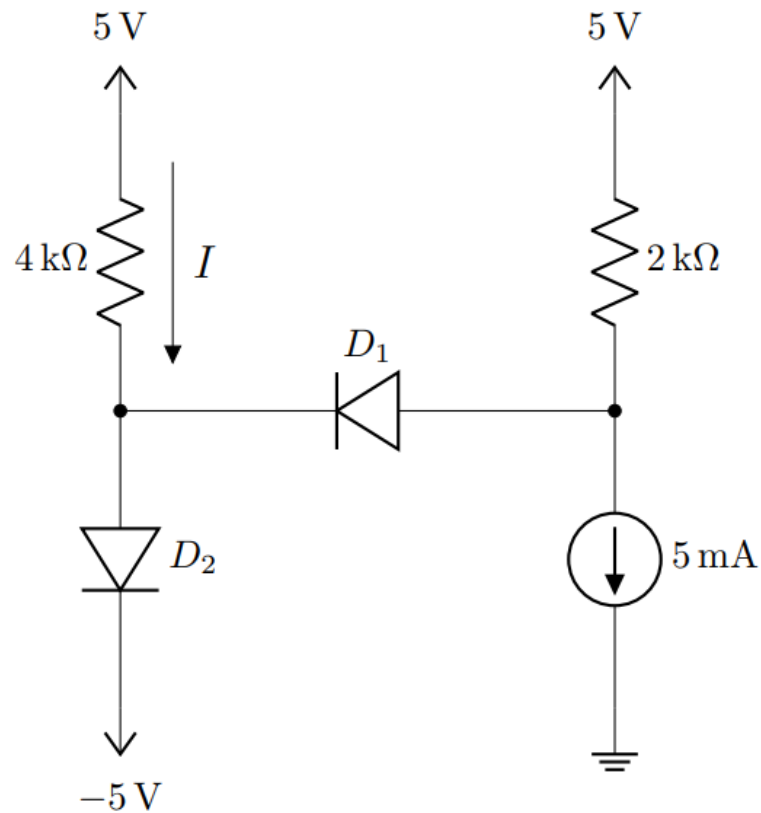Problem 9


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine I .



Ans: D_1 OFF, D_2 ON, $I = 2.325\text{ mA}$

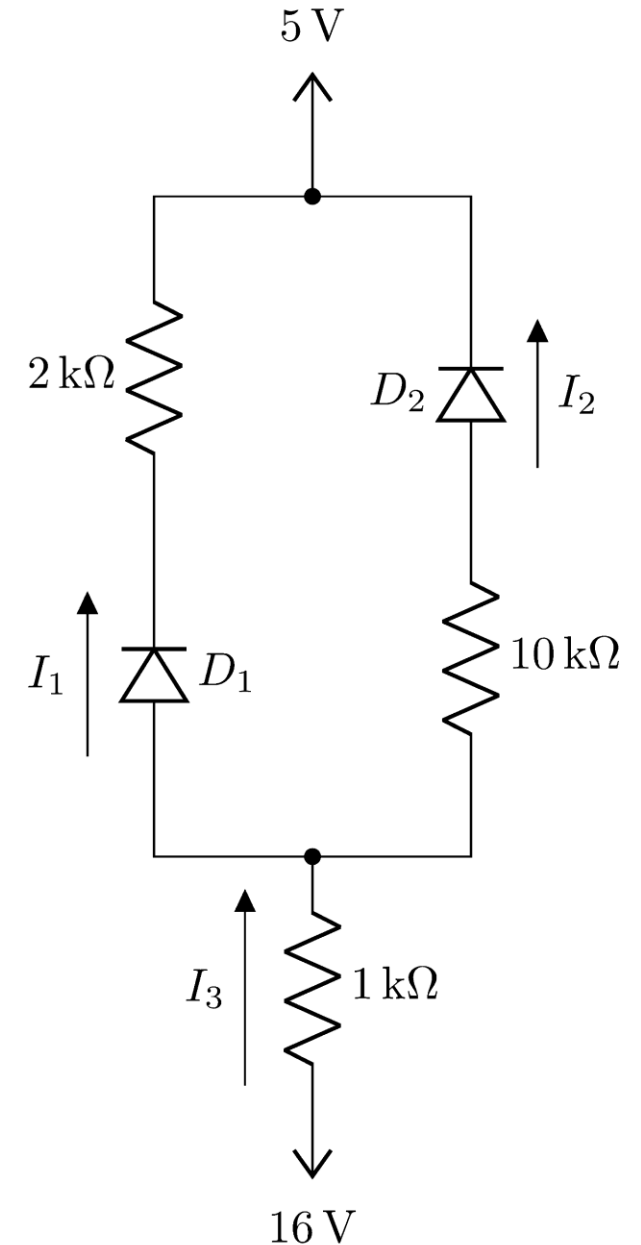Problem 10


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine I_1 , I_2 , and I_3 .



Ans: D_1 ON, D_2 ON, $I_1 = 3.22\text{ mA}$, $I_2 = 0.64\text{ mA}$, $I_3 = 3.86\text{ mA}$

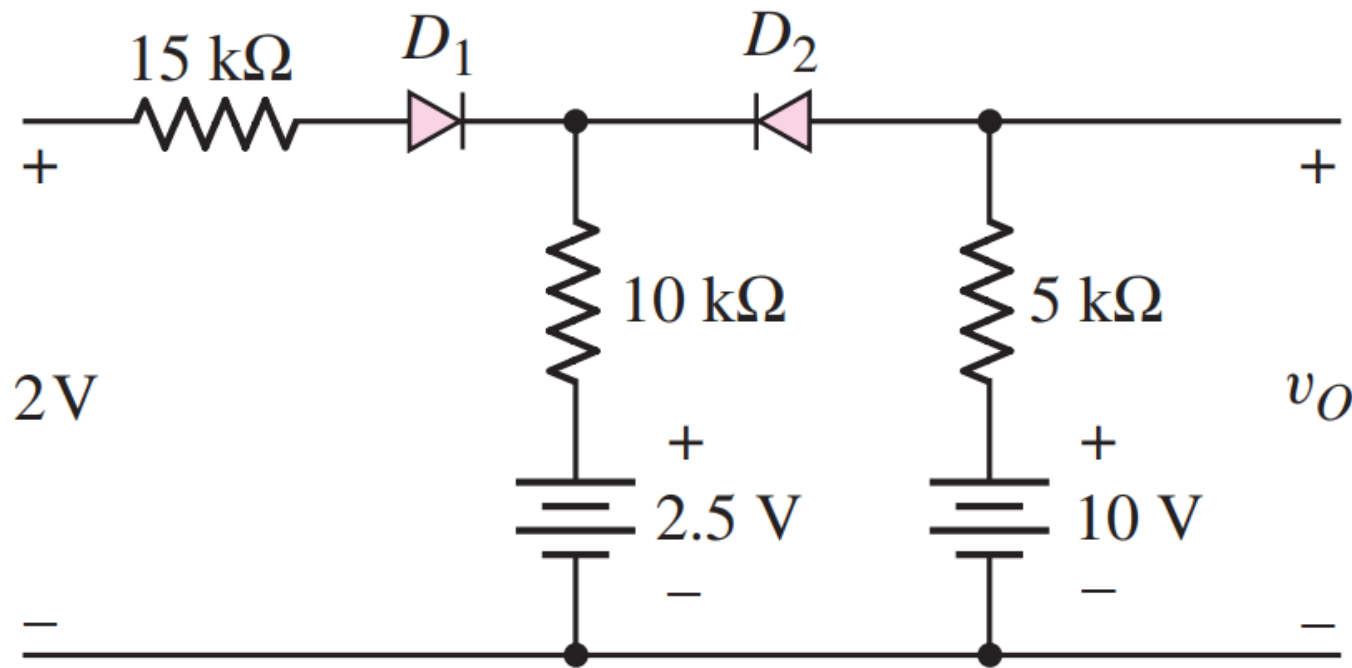Problem 11


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine v_O .



Ans: D_1 OFF, D_2 ON, $v_O = 7.735\text{ V}$

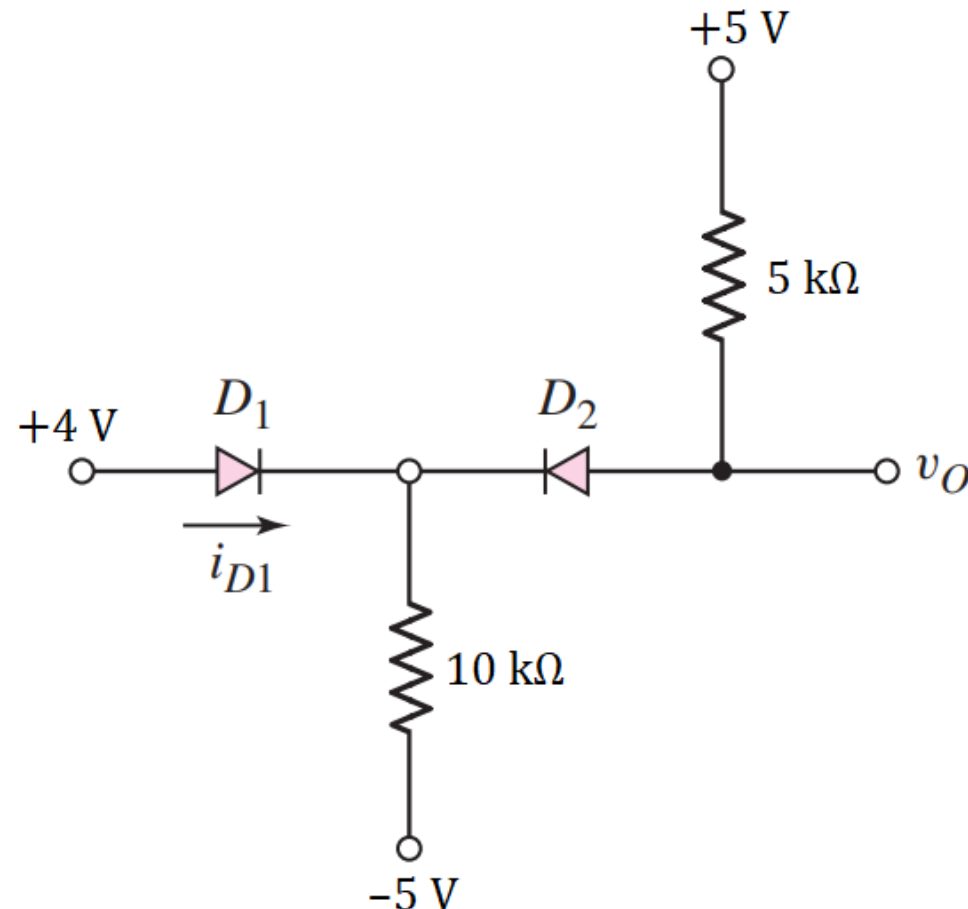Problem 12


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine v_o .



Ans: D_1 ON, D_2 ON, $v_o = 4\text{ V}$

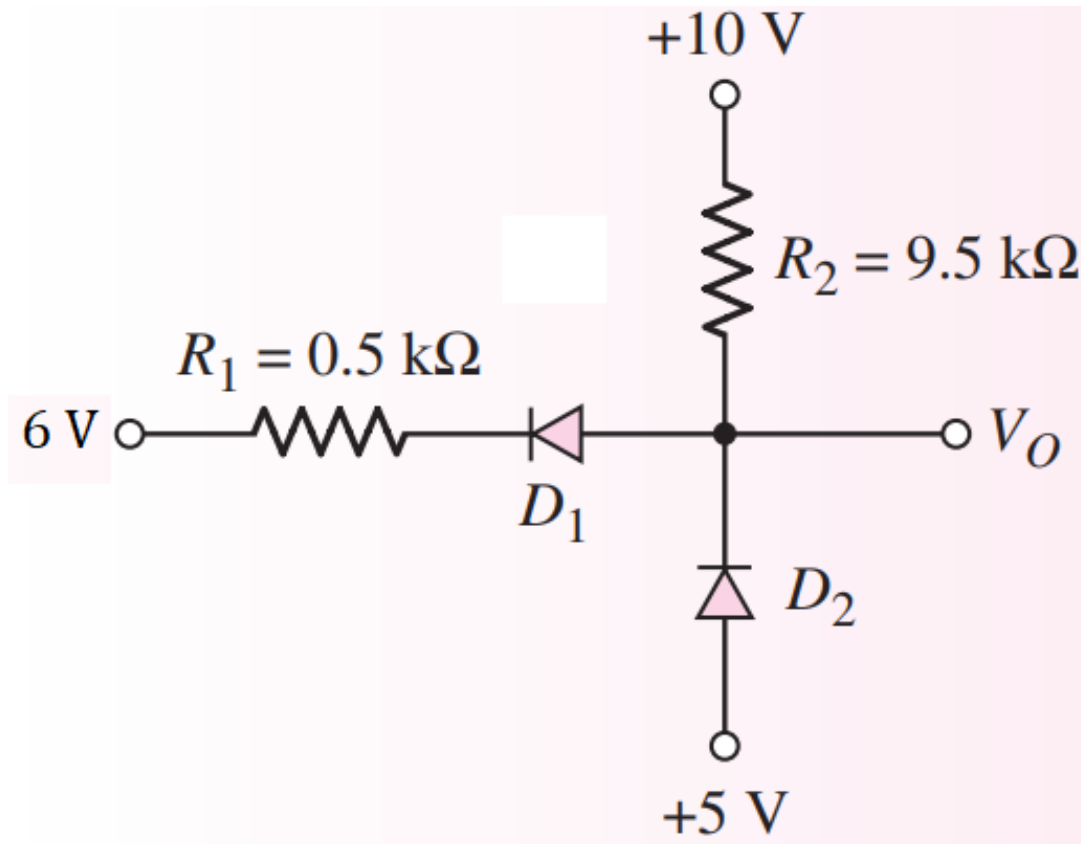Problem 13


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_O .



Ans: D_1 ON, D_2 OFF, $V_O = 6.865\text{ V}$

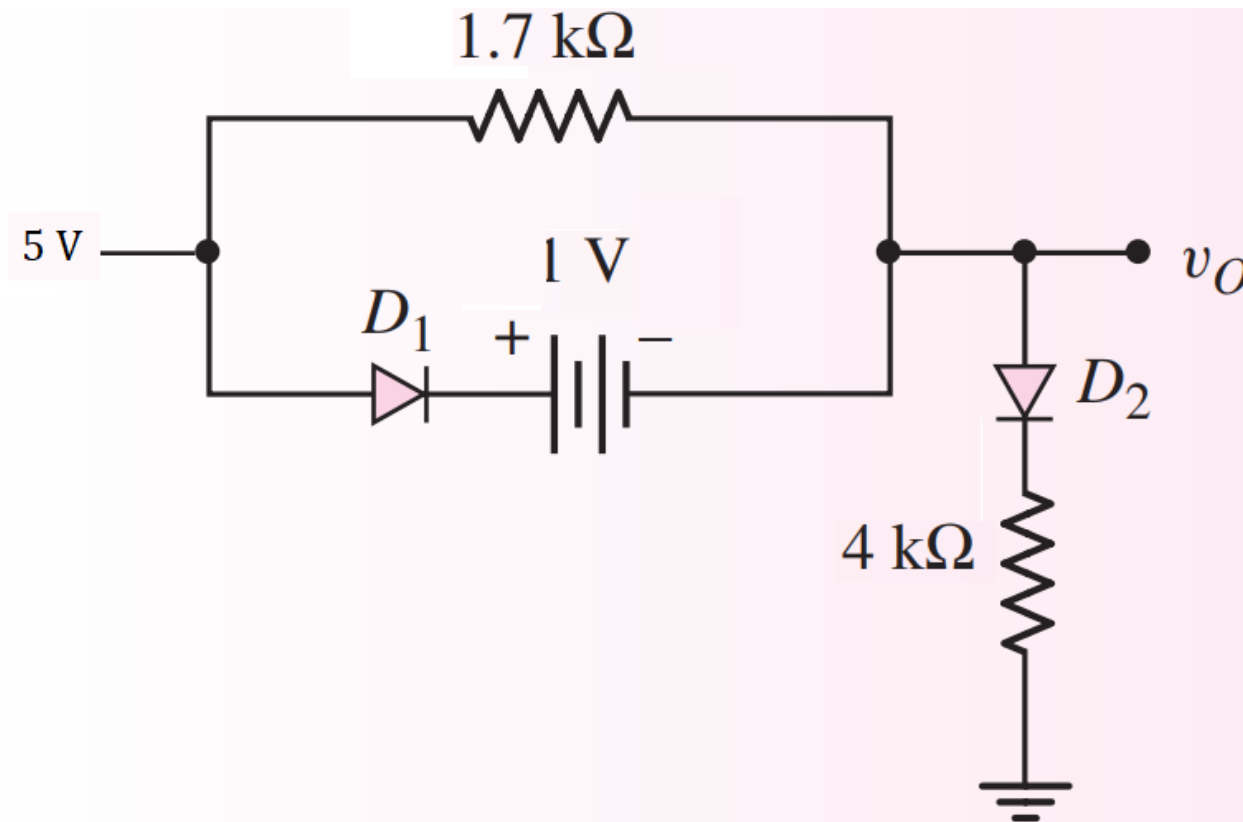Problem 14


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine v_O .



Ans: D_1 OFF, D_2 ON, $v_O = 3.72\text{ V}$

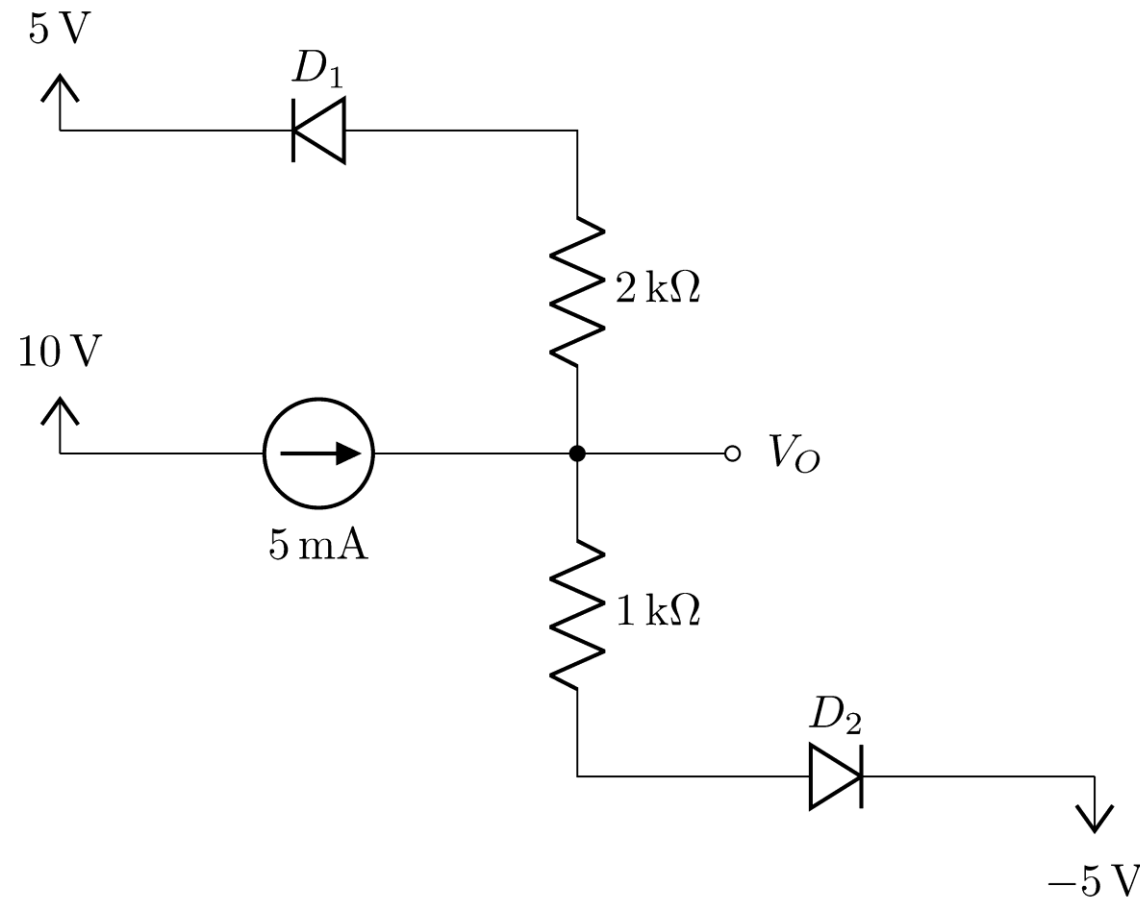Problem 15


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_O .



Ans: D_1 OFF, D_2 ON, $V_O = 0.7\text{ V}$

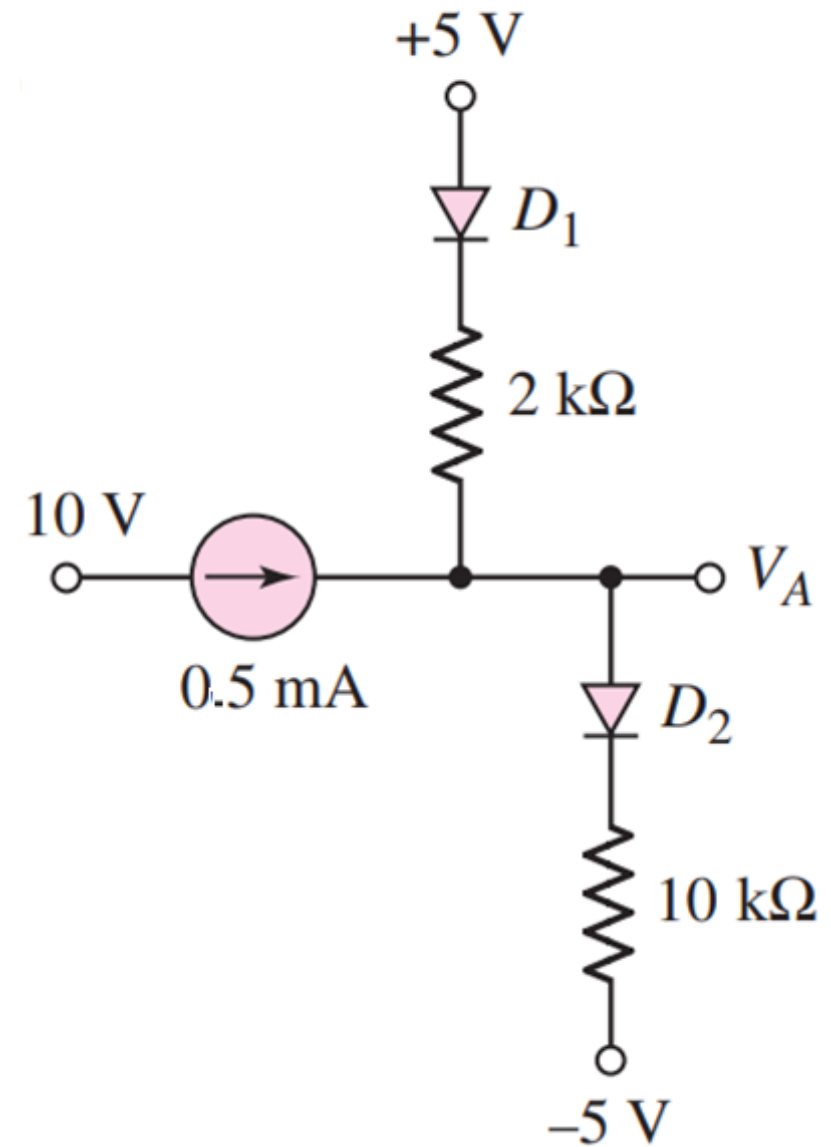Problem 16


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_A .



Ans: D_1 ON, D_2 ON, $V_A = 3.7\text{ V}$


Problem 17

- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), show that all the diodes remain off.

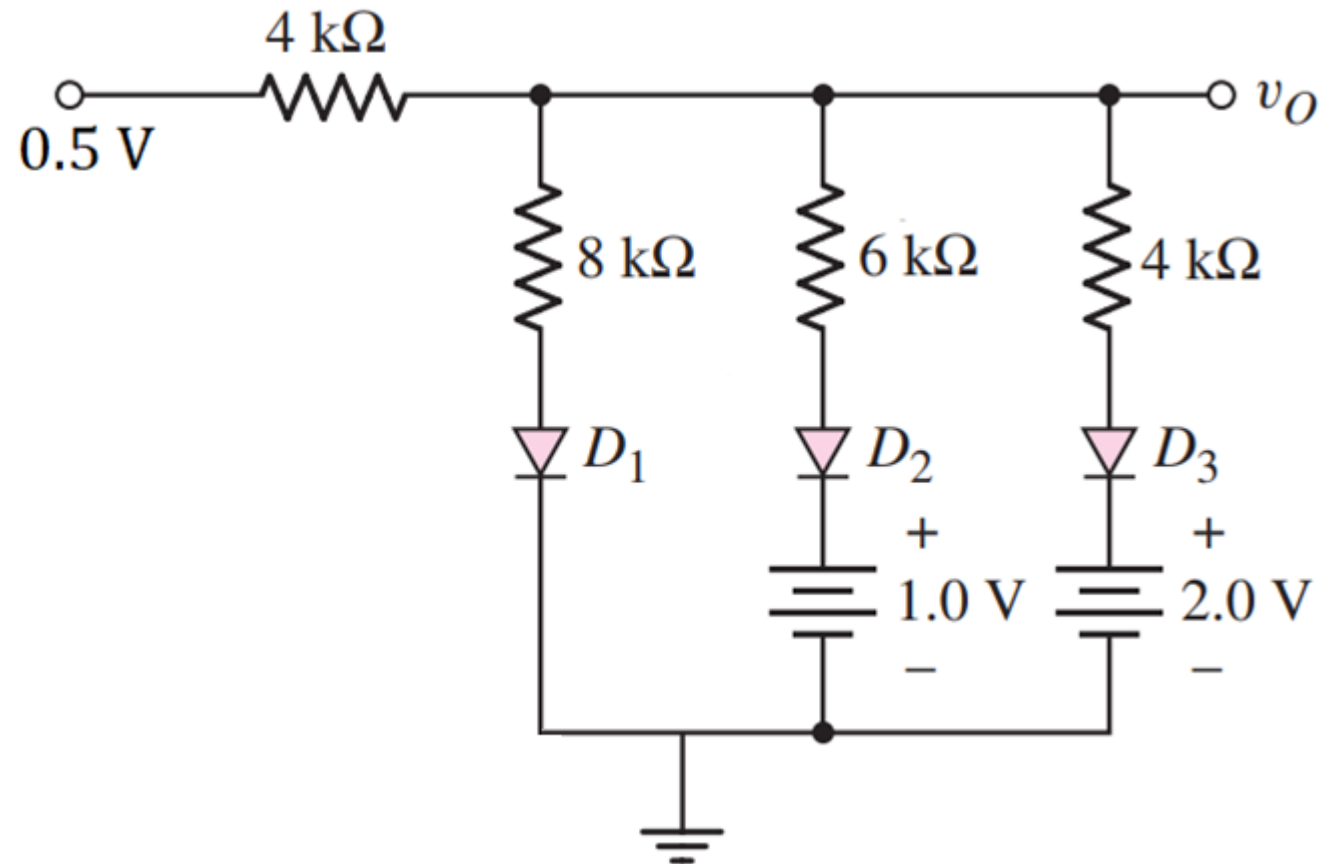

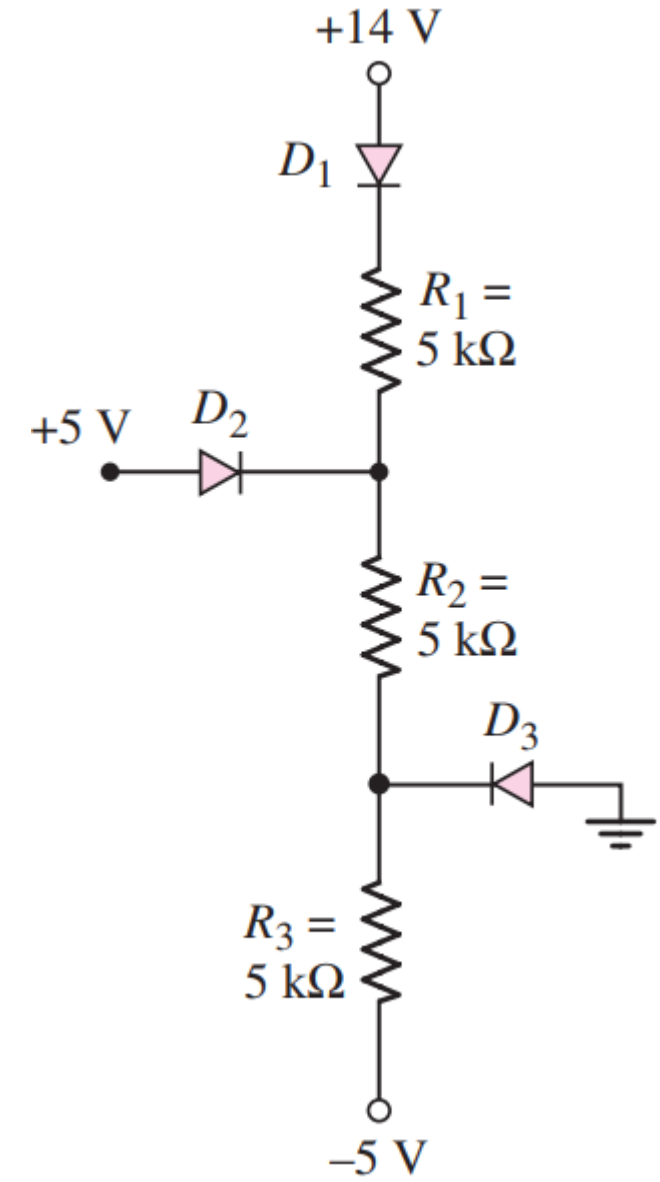Problem 18


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine the voltage across R_2 .



Ans: D_1 ON, D_2 OFF, D_3 OFF, $V_{R_2} = 6.11\text{ V}$

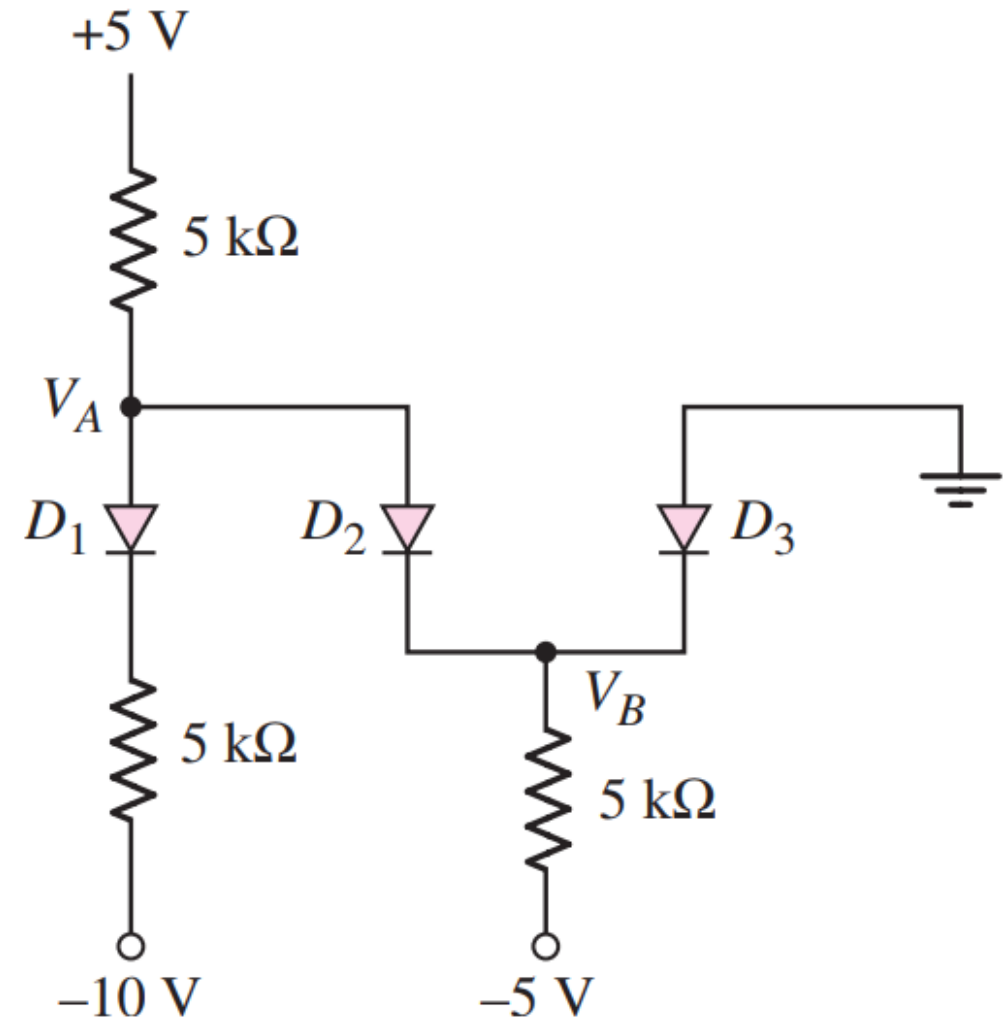Problem 19


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_A and V_B .



Ans: D_1 ON, D_2 OFF, D_3 ON, $V_A = -2.16\text{ V}$, $V_B = -0.65\text{ V}$

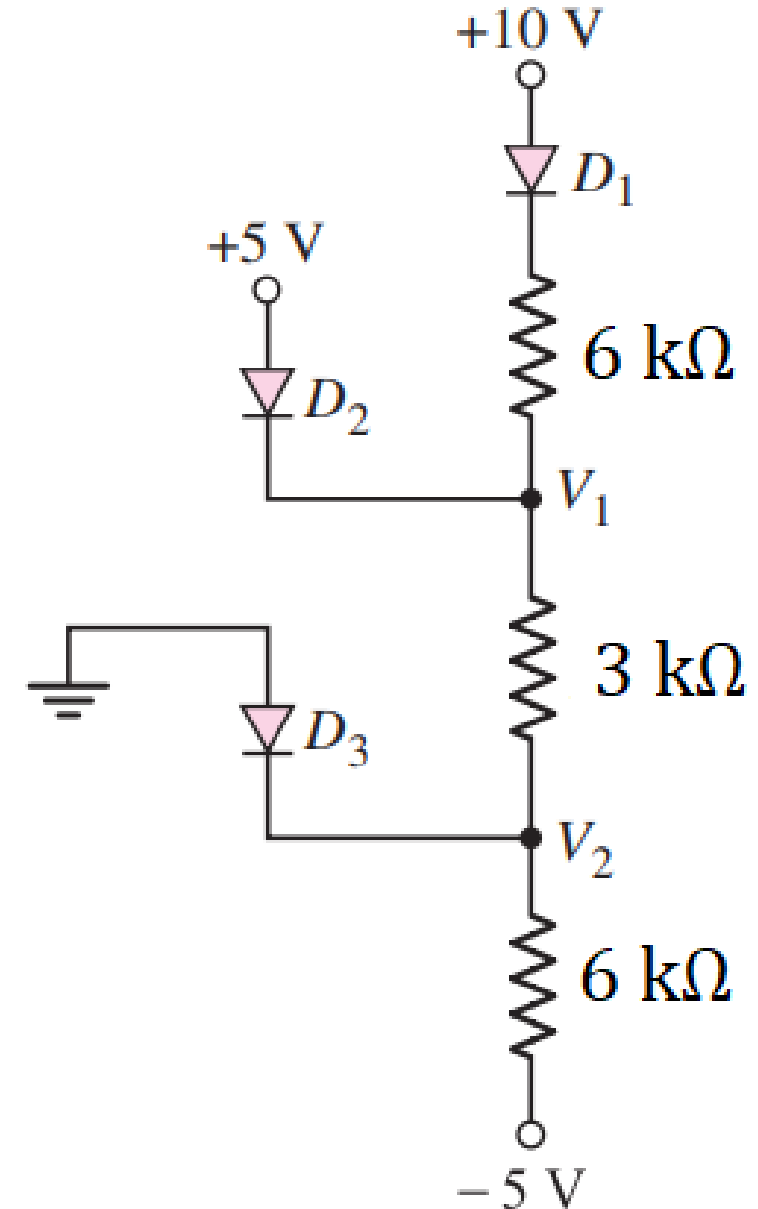Problem 20


- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_1 and V_2 .



Ans: D_1 ON, D_2 ON, D_3 OFF, $V_1 = 4.38\text{ V}$, $V_2 = 1.23\text{ V}$

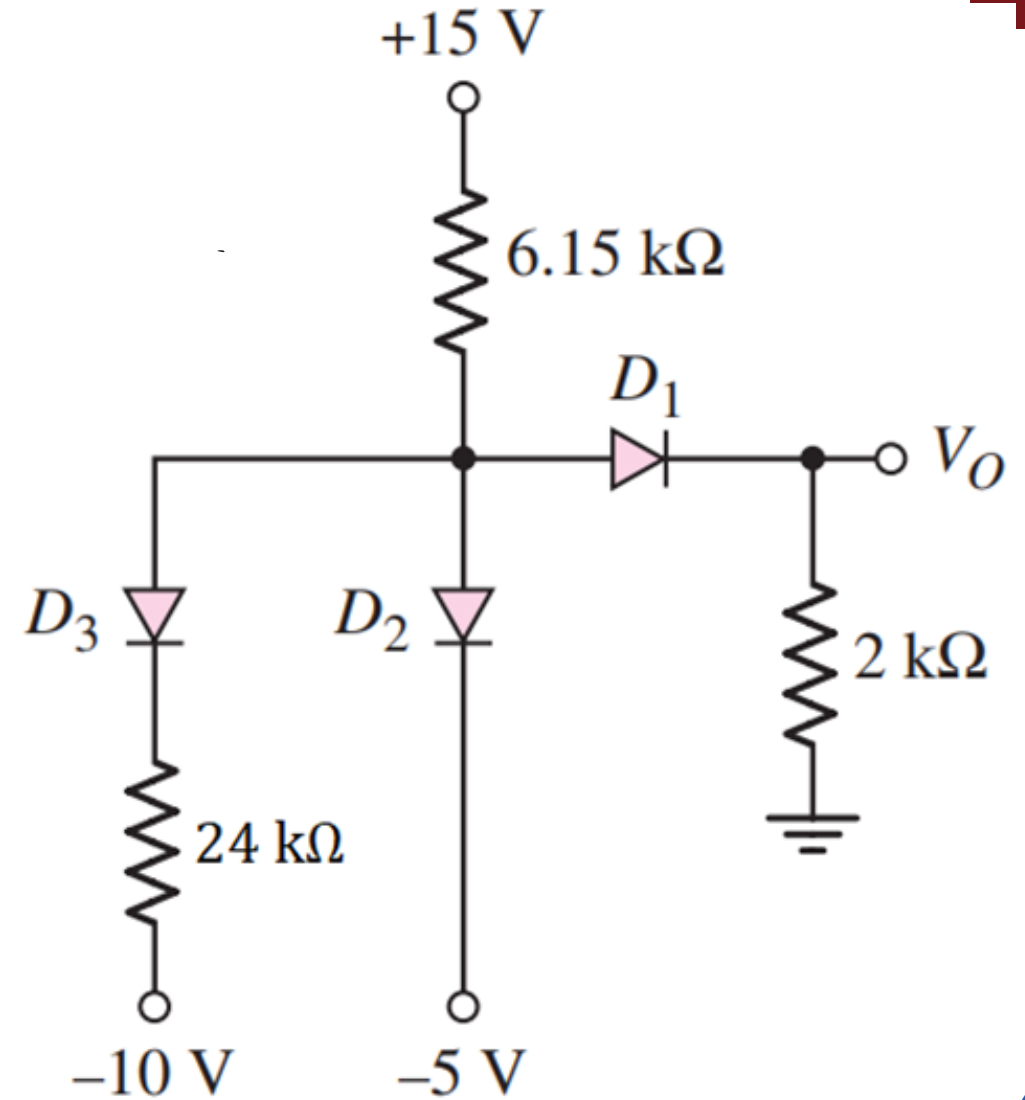Problem 21

- For the circuit shown below, using CVD model (with $V_{D_o} = 0.7\text{ V}$), determine V_O .



Ans: D_1 OFF, D_2 ON, D_3 ON, $V_O = 0\text{ V}$