

Brac University

Semester: Spring 2024

Course Code: CSE251

Electronic Devices and Circuits

Section: 01-23

Set
01

Assessment: *Midterm Exam*

Duration: 1 hour 30 minutes

Date: 08 March, 2024


Full Marks: 30

Instructions: Answer any 3 out of 4 questions.


■ Question 1 of 4 [CO1, CO2, CO3] [10 marks]

The adjacent truth table represents a logic circuit implemented with ideal diodes and a 5 V supply voltage. 'A' and 'B' are the boolean input variables of the circuit and 'f' is the boolean output variable of the circuit. V_A and V_B are the input voltages corresponding to 'A' and 'B'. The voltage level corresponding to the output variable 'f' is denoted by V_f .

A	B	f
0	0	0
0	1	0
1	0	0
1	1	1

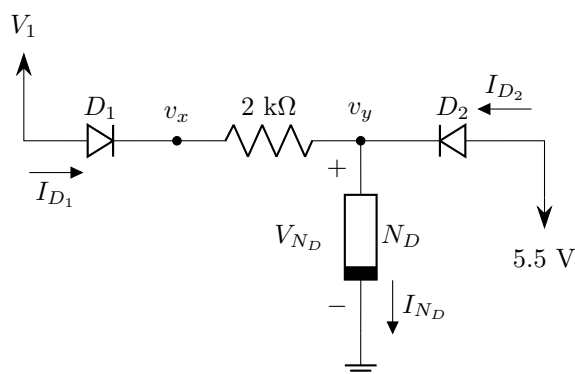

(a) Circuit-1

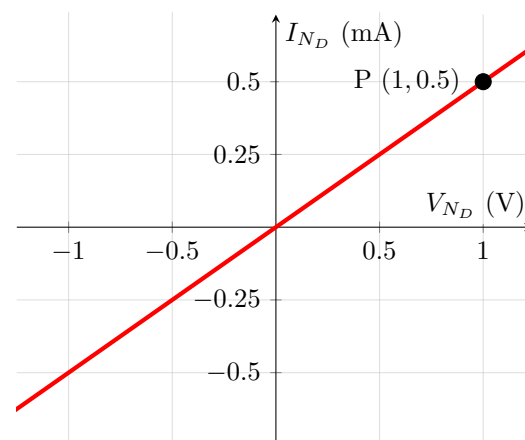

(b) I-V Characteristics of the device N_D

- [1 mark] **Deduce** the logical function f and **draw** the mentioned logic circuit.
- [1 mark] **Calculate** the value of 'f' when $V_A = 4$ V and $V_B = 5$ V.
- [2 marks] **Identify** the equivalent circuit model for the I-V characteristics of the unknown device, N_D in Fig. (b). **Calculate** the model parameters.
- [6 marks] **Assume**, D_2 is 'ON' and $V_1 = V_f$. **Redraw** Circuit-1 by replacing N_D with the equivalent circuit model found in part-(c). Now, **analyze** Circuit-1 to **determine** the values of I_{D1} , I_{D2} , v_x , and v_y . You must **validate** your assumptions. Here, the forward voltage drop of both of the diodes is, $V_{D0} = 0.5$ V.


■ Question 2 of 4 [CO1, CO2, CO3] [10 marks]

The input voltage of a half-wave rectifier is a **Sine** wave with amplitude $V_M = 10$ V and 40 Hz frequency. The output load resistance is $R = 50$ k Ω . A silicon diode is used in this circuit whose forward voltage drop is $V_{D_0} = 0.6$ V.

- [4 marks] Briefly **explain** the purpose of a rectifier. **Draw** the input and output waveforms of the mentioned rectifier with proper labeling. **Draw** the Voltage Transfer Characteristic (VTC) curve of the rectifier.
- [1 mark] **Calculate** the DC value of the output voltage, V_{DC} .
- [3 marks] After connecting a capacitor parallel to the load, V_{DC} changes to $V_{DC(Cap)}$ and the new output voltage can be expressed as $V_{out} = V_{DC(Cap)} \pm 0.5$ V. **Calculate** the peak-to-peak ripple voltage $V_{r(p-p)}$, and **determine** the ripple frequency, f_r . Now, **calculate** the value of the capacitor, C .
- [1 mark] **Calculate** the DC value of the output voltage after connecting the capacitor, $V_{DC(Cap)}$.
- [1 mark] **Compare** $V_{DC(Cap)}$ with V_{DC} determined in part-(b) and briefly **explain** their difference.

■ Question 3 of 4 [CO1, CO2, CO3] [10 marks + 2 marks (bonus)]

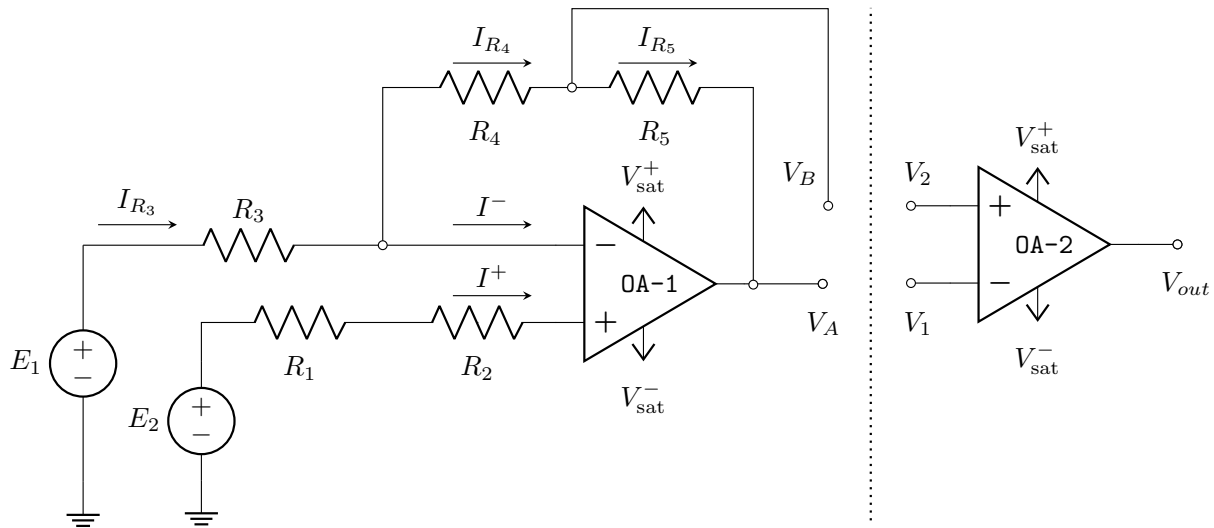The ‘ideal’ operational amplifiers (Op-Amp) below have been connected to saturation voltages $V_{sat}^+ = +8$ V and $V_{sat}^- = -8$ V. The resistor values are given as: $R_1 = R_2 = 1$ k Ω , and $4R_4 = 10R_5 = 20$ k Ω .



- [1 mark] **State** the current values of I^- and I^+ .
- [4 marks] If $E_1 = 5$ V, $E_2 = 0$ V, and $R_3 = 10$ k Ω , **determine** V_A and V_B .
- [2 marks] **Find** the value of V_{out} if $V_1 = V_A$ and $V_2 = V_B$.
- [3 marks] For $E_1 = 0$ V and $E_2 = 2.2$ V, we measure V_A to be 5.13 V. Showing necessary calculations, **select** what value of R_3 will make this possible.
- [2 marks (bonus)] After obtaining R_3 in question (d), find the value of V_B .

■ Question 4 of 4 [CO1, CO2, CO3] [10 marks]

Answer questions (a-d) based on **Figure 1** and question (e) based on the data shown in **Figure 2**.

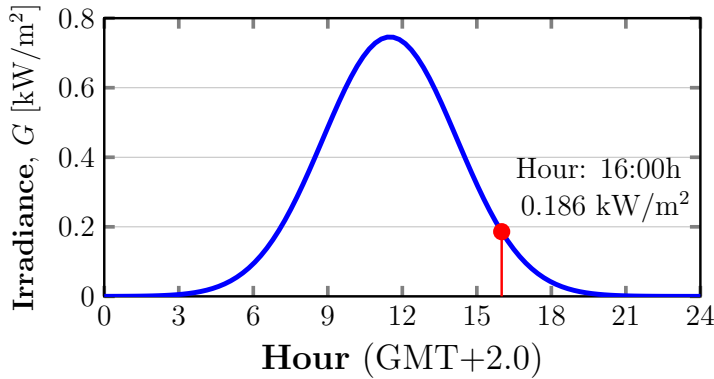


Figure 1: For questions (a-d)

$$V_O = X_1 V_1 - X_2 \int V_2 dt$$

Where, $X_1 = 1 + \text{last digit of student ID}$

$X_2 = 1 + \text{2nd last digit of student ID}$

Figure 2: For question (e) only.

Figure 1 shows the variation of direct solar irradiance, G (in units of kW/m^2) throughout the day in Egypt. The irradiance is 0.186 kW/m^2 at 16:00 hours. A photodetector generates a voltage of V_S by converting solar irradiance G (in units of kW/m^2) according to the following equation:

$$V_S(G) = 6G^2 + 7G \quad (1)$$

You have to design an automatic system with an Op-Amp comparator circuit. This system will take V_S as an input from a photodetector and control a street lamp, ensuring it meets the following conditions:

- The lamp switches ON after 16:00 hours.
- The lamp switches ON when system output is 5 V.
- The lamp switches OFF when system output is 0 V.

Based on the above scenario, answer the following questions:

- [1 mark] Calculate the photodetector voltage V_S at 16:00 hours. Determine how V_S changes before and after 16:00 hours.
- [1 mark] Show how the changes in irradiance G and subsequently V_S - with respect to the value obtained in part (a) - should affect the street lamp operation (ON / OFF states).
[Hint: Observe the graph in Fig. 1 and Equation (1)]
- [2 marks] Determine whether the Op-Amp comparator circuit of the system should be in an inverting or non-inverting configuration. Justify your choice by explaining briefly how this configuration meets the conditions mentioned above.
- [3 marks] Draw the completed Op-Amp comparator circuit clearly marking the input and output terminals and the positive and negative saturation voltages. Also clearly indicate the reference voltage against which the input of the comparator is compared.
- [3 marks] Design a circuit with Op-Amps that implements the function shown in **Figure 2**. Clearly indicate the input, output, and circuit parameters.