

Student ID:	22299173	Lab Section:	07
Name:	Anika Tabassum	Lab Group:	3

## Experiment-06

### Study of I-V Characteristics of MOSFET and Implementation of Logic Functions



CSE251 - Electronic Devices and Circuits Lab

## Objective

1. To observe and understand the I-V characteristics of MOSFET.
2. To implement a NAND gate and a Logic Function using MOSFETs and verify the truth tables.

## Equipments

1. MOSFET (IRF 540) - ( $\times 3$ )
2. Resistances:  $4.7\text{ k}\Omega$  ( $\times 1$ ),  $100\text{ k}\Omega$  ( $\times 1$ )
3. DC power supply
4. Oscilloscope
5. Trainer Board
6. Breadboard
7. Chords and Wire

## Background Theory

### Introduction to MOSFET

Three-terminal devices are far more useful than two-terminal ones (such as Diodes) because they can be used in a multitude of applications, ranging from signal amplification to digital logic and memory. The basic principle involved is the use of the voltage between two terminals to control the current flowing in the third terminal. In this way a three-terminal device can be used to realize a controlled source.

The control signal can be used to cause the current in the third terminal to change from zero to a large value, thus allowing the device to act as a switch. Switch is the basis for the realization of the logic inverter, which is a basic element of digital circuits.

There are two major types of three-terminal semiconductor devices: (i) MOSFET (Metal-Oxide Semiconductor Field-Effect Transistor) and (ii) BJT (Bipolar Junction Transistor). Although both of them offer unique features and areas of application, MOSFET has become by far the most widely used electronic device, especially in the design of integrated circuits (ICs).

There are two kinds of MOSFET: (i) NMOS and (ii) PMOS. In this experiment, we will study about the I-V characteristics of NMOS and design an NAND gate and a Boolean Logic Function using the NMOS transistor. The figure above shows the IC and the circuit diagram of a MOSFET (NMOS).

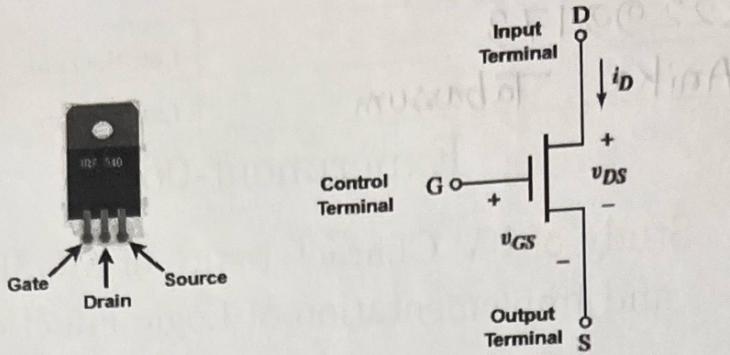


Figure 1: NMOS IC (IRF540) and Circuit Diagram

### MOSFET as a Switch

MOSFET is a three-terminal device with a control terminal, an input terminal, and an output terminal. The control terminal of the MOSFET is called its gate G, the input terminal its drain D, and the output terminal its source S. MOSFET can act as a switch depending upon the applied voltage in the input terminal. A simple circuit model known as 'Switch Model' or 'S-Model' is used to model this behavior.

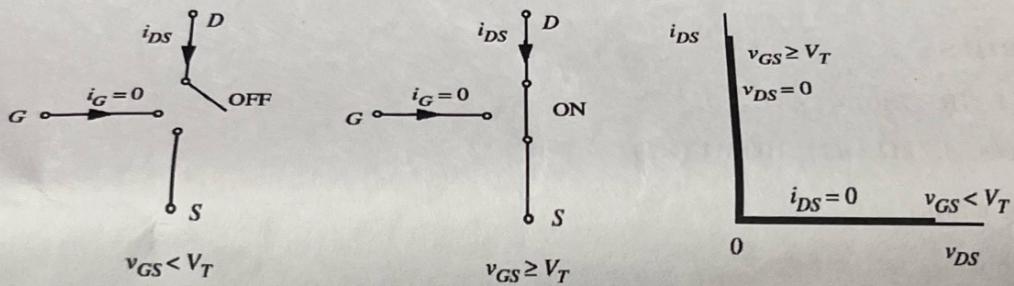


Figure 2: S-Model of MOSFET

Note that the current  $I_G = 0$ . We can summarize the S-model of the MOSFET in algebraic form as:

when  $\rightarrow v_{GS} < V_T$ , then  $\rightarrow i_{DS} = 0$  and when  $\rightarrow v_{GS} \geq V_T$ , then  $\rightarrow v_{DS} = 0$

### MOSFET Switch Implementation of Logic Gates and Logic Functions

Switches can be used to build logic gates. As we can use MOSFET as a switch, logic gates can be built using MOSFETs. The following subsections discuss two logic gates, NOT gate and NAND gate, which are implemented using MOSFETs. We can also implement various Logic Functions using MOSFETs. To demonstrate this thing, a logic function will be implemented in Task-01.

#### NOT Gate/Inverter Using MOSFET

Consider the circuit shown in following figure, which comprises a MOSFET and a load resistor powered by a supply voltage  $V_S$ . This circuit acts as a NOT Gate/Inverter.

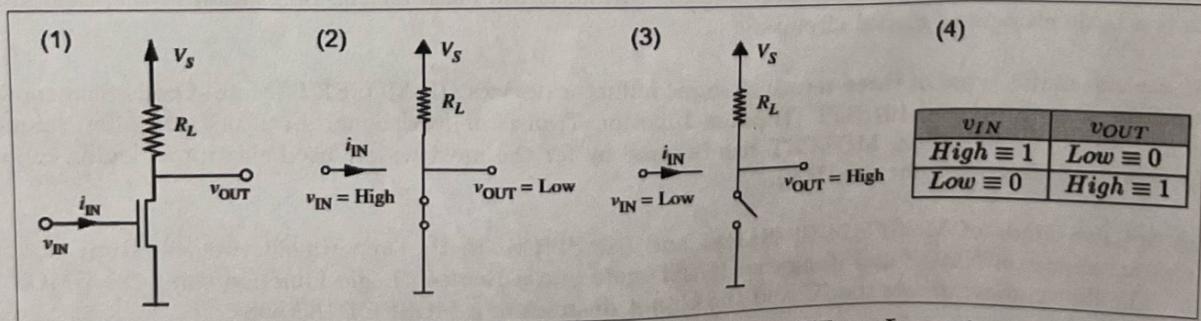


Figure 3: (1) MOSFET NOT Gate (2) When Input is '1' (3) When Input is '0' (4) Truth Table

## NAND Gate Using MOSFET

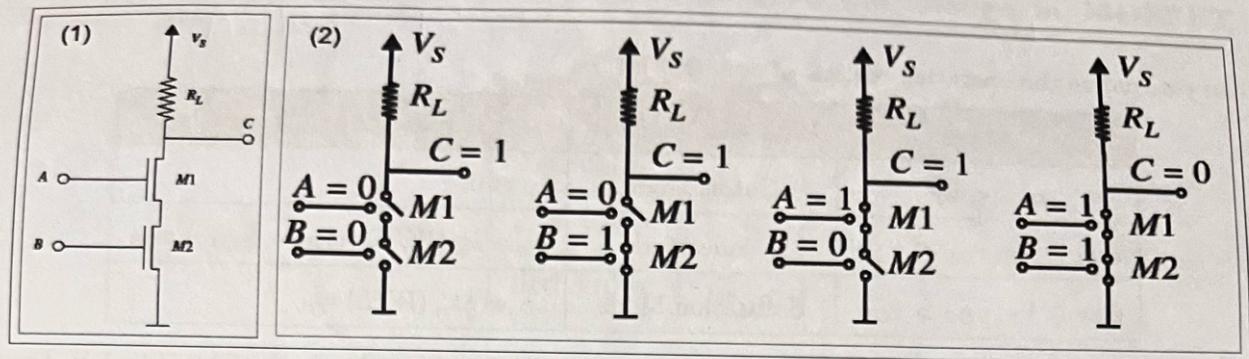


Figure 4: (1) MOSFET NAND Gate (2) Equivalent Circuits for Different Inputs

Consider the circuit shown in the figure above, which comprises a two MOSFETs and a load resistor powered by a supply voltage  $V_S$ . This circuit acts as a NAND gate. NAND gate is a universal gate that can be used to implement any Logic Function.

## Logic Function Using MOSFET

We can use combinations of MOSFETs to implement various logic functions. The circuit shown in Figure-5 implements  $f = \overline{xy + z}$ .

### I-V Characteristics of a MOSFET

The S-model of a MOSFET is a simplification of the actual I-V characteristics of a MOSFET which helps us understand the behavior of a MOSFET as a switch. But the actual I-V characteristics is very different from it.

**Figure-6** represents the actual I-V characteristics of a MOSFET. There are 3 operating regions in the I-V characteristics graph: **Cutoff**, **Triode**, **Saturation**. The first two are useful if we want to use MOSFET as a switch. On the other hand, if we want to use MOSFET as an amplifier, we must operate it in the saturation region.


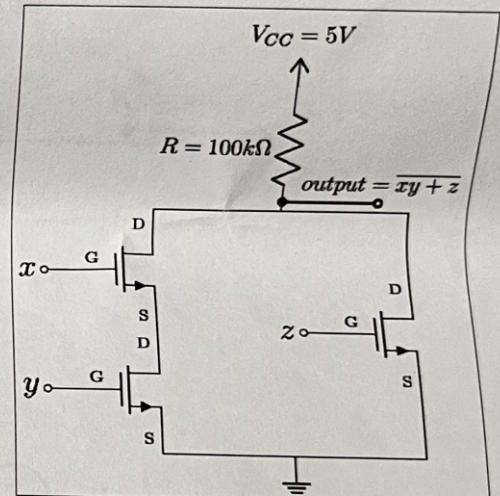


Figure 5: Logic Function using MOSFET

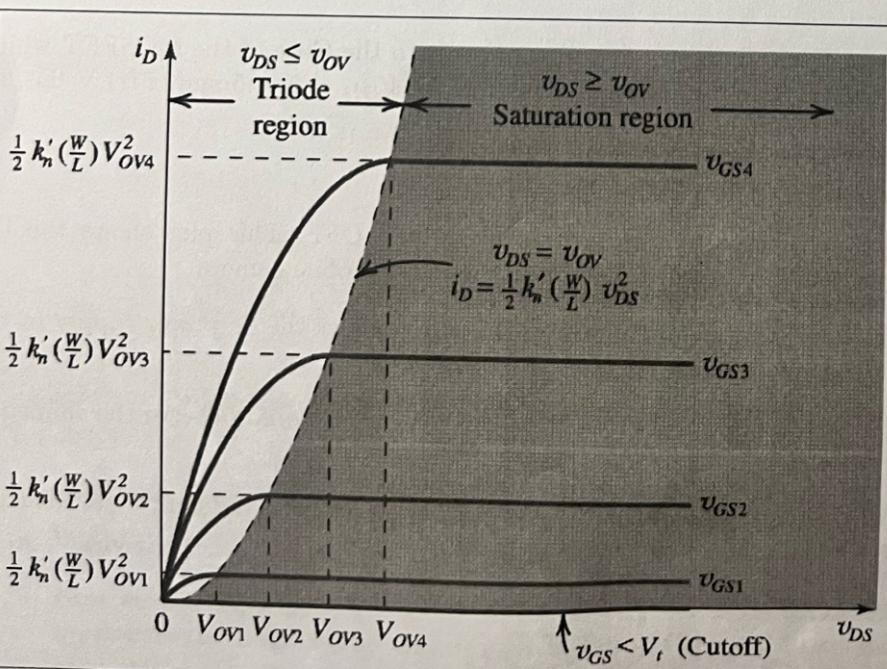

In this graph

$V_T$  = Threshold Voltage

$v_{OV}$  = Overdrive voltage

$L$  = Channel Length

$W$  = Channel Width

$k'_n$  = Process Transconductance Parameter

$$v_{GS} = v_G - v_S$$

$$v_{DS} = v_D - v_S$$

$$v_{OV} = v_{GS} - V_T$$

Figure 6: I-V Characteristics of a MOSFET


We can summarize the operating regions of a MOSFET as:

When	Operating Mode	Equation of Current
$v_{GS} < V_T$	Cutoff Mode	$i_D = 0$
$v_{GS} \geq V_T, v_{DS} \leq v_{OV}$	Triode Mode	$i_D = k'_n (W/L) (v_{OV} - \frac{1}{2}v_{DS}) v_{DS}$
$v_{GS} \geq V_T, v_{DS} > v_{OV}$	Saturation Mode	$i_D = \frac{1}{2}k'_n (W/L) v_{OV}^2$

The value of  $V_T$  is controlled during device fabrication and typically lies in the range of 0.3 V to 1 V. From the graph, we see that, for the same value of  $v_{DS}$ ,  $i_{DS}$  increases if we increase  $v_{GS}$ . Also, for a lower value of  $v_{GS}$ , the MOSFET operates in Saturation for a lower value of  $v_{DS}$  and for higher value of  $v_{GS}$ , the MOSFET goes into Saturation for a higher value of  $v_{DS}$ .
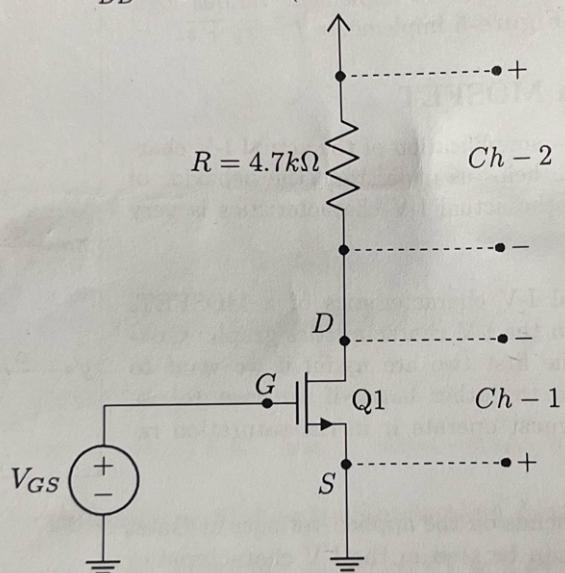
## Task-01: I-V Characteristics of a MOSFET

$$V_{DD} = 5 + 5 \sin(2\pi ft) \text{ V [i.e. } 0\text{V to } 10\text{V]}$$



### Procedure


1. Construct the circuit shown above. Use a data switch and connect it to the Gate of the MOSFET which will provide necessary voltage for  $V_{GS}$ . Use the function generator for  $V_{DD} = 5 + 5 \sin(2\pi ft) \text{ V}$  [i.e. an AC voltage that varies from 0V to 10V] and set  $f = 50 \text{ Hz}$ .
2. Set the oscilloscope in X-Y mode. Invert the Channel-1.
3. Observe the plot in the oscilloscope when the data switch is ON and OFF. This plot shows the I-V characteristics of a MOSFET as a switch. Capture the plots using your mobile camera.
4. Now, disconnect the data switch from the gate of the MOSFET and connect the dc power supply to the gate terminal so that we can increase or decrease  $V_{GS}$ .
5. Rotate the voltage knob of the dc power supply slowly from 0V to 5V. You should observe the change in the I-V characteristics.
6. Use your mobile camera to capture the image of the I-V characteristics graphs for 3 different  $V_{GS}$ . Measure the values of  $V_{GS}$  of the captured images and write them in Data Table 1.

**Data Table 1: Different Values of  $V_{GS}$  to observe the change in MOSFET I-V Characteristics**

Values of $V_{GS}$	
1st Value	0
2nd Value	2.5
3rd Value	5

## Task-02: Logic Gate and Logic Function Implementation


$$V_{CC} = 5V$$

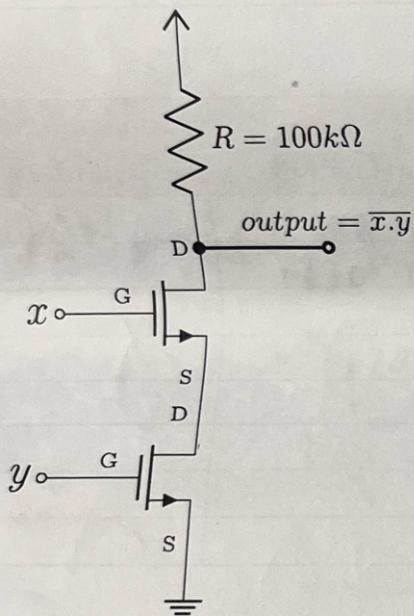

*Circuit-1*

NAND Gate using MOSFET

$$V_{CC} = 5V$$

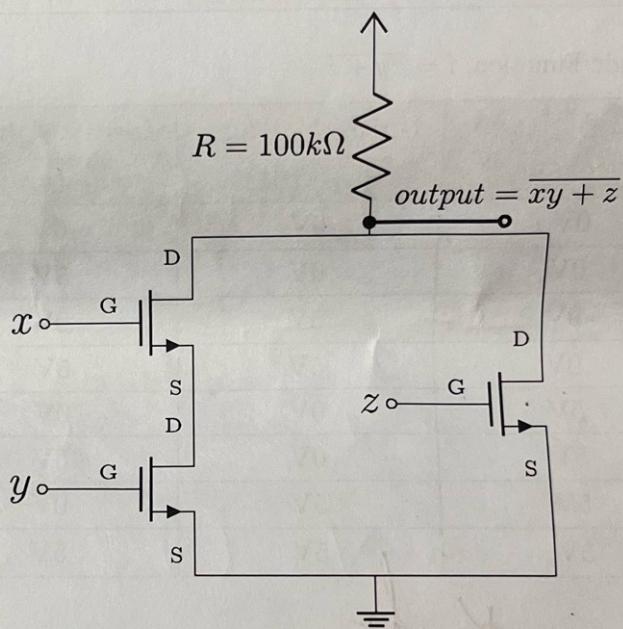

*Circuit-2*

Logic Function,  $f = \overline{xy} + z$  using MOSFET

## Procedure

1. On a trainer board, setup the Circuit 1.
2. Connect the gate terminals (input x and y) to data switches. Those switches provide 5V approximately.
3. Keeping  $V_{CC}$  constant at 5V, at first turn off the data switches connected to the gate terminal. This implies you are now applying  $V_x = 0V$ ,  $V_y = 0V$ . Measure the corresponding output voltage,  $V_{out}$  which should be approximately 5V which corresponds to boolean 1.
4. The boolean outputs can also be determined by the state of an LED. Connect  $V_{out}$  to one of the LEDs and check it. When the LED is ON, the boolean output is 1. Similarly, when the LED is OFF, the boolean output is 0.
5. Next, use the input voltage combinations of Data Table 1 and observe the state of LED again.
6. Verify the truth table of the NAND gate.
7. Now we will implement a Logic Function,  $f = \overline{xy} + z$  using MOSFET. Circuit 2 in the figure shown above represents the Logic Function  $f = \overline{xy} + z$ . Setup Circuit 2 in a similar way to the procedure followed for Circuit 1.

8. Keeping  $V_{DD}$  constant at 5V, observe the state of the LED for different combinations of the inputs  $x$ ,  $y$  and  $z$  as shown in Data Table 1.
9. Verify the truth table of the Logic Function,  $f = \overline{xy + z}$ .

**Data Table 2: Verification of the Truth Tables of Logic Gate and Logic Function**

1. NAND Gate

Input Voltage, $V_x$ (volt)	Input Voltage, $V_y$ (volt)	State of LED (On/Off)	Boolean Output (0 or 1)
0V	0V	ON	1
0V	5V	OFF	0
5V	0V	OFF	0
5V	5V	OFF	0

2. Logic Function,  $f = \overline{xy + z}$

Input Voltage, $V_x$ (volt)	Input Voltage, $V_y$ (volt)	Input Voltage, $V_z$ (volt)	State of LED (On/Off)	Boolean Output (0 or 1)
0V	0V	0V	on	1
0V	0V	5V	off	0
0V	5V	0V	on	1
0V	5V	5V	off	0
5V	0V	0V	on	1
5V	0V	5V	off	0
5V	5V	0V	on	1
5V	5V	5V	off	0

*Suman Kumar*  
29.08.25

Signature of the lab faculty

## Report Submission Guidelines

1. Attach the signed Data Sheet (if any)
2. Attach the captured images (if any)
3. Answer the questions in the "Test Your Understanding" section
4. Add a brief Discussion regarding the experiment. For the Discussion part of the lab report, you should include the answers of the following questions in your own words:
  - What did you learn from this experiment?
  - What challenges did you face and how did you overcome the challenges? (if any)
  - What mistakes did you make and how did you correct the mistakes? (if any)
  - How will this experiment help you in future experiments of this course?

## Test Your Understanding

Answer the following questions:

1. We can use the MOSFET as a switch. Which operating regions do we need for this purpose and why?


Answer: When we use MOSFET as a switch, we operate 2 regions.

i) Cutoff: Here the gate - source voltage is less than the threshold voltage. For this current doesn't flow from drain to source. This acts like an open switch.

ii) Saturation Region: Here the gate to source voltage is greater than the threshold voltage and drain to source voltage is high enough to keep the MOSFET fully on. This acts like closed switch.


2. Draw the VTC ( $V_{DS}$  vs  $V_{GS}$ ) graph of a MOSFET operating as a switch.

Answer:

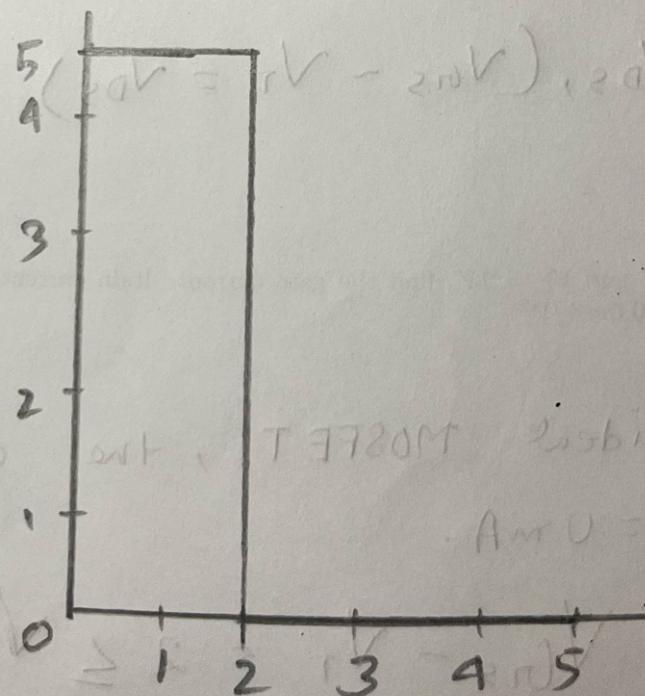

3. Draw a circuit using MOSFETs that implements the following logic function,  $f = (x+y)z$

Answer:

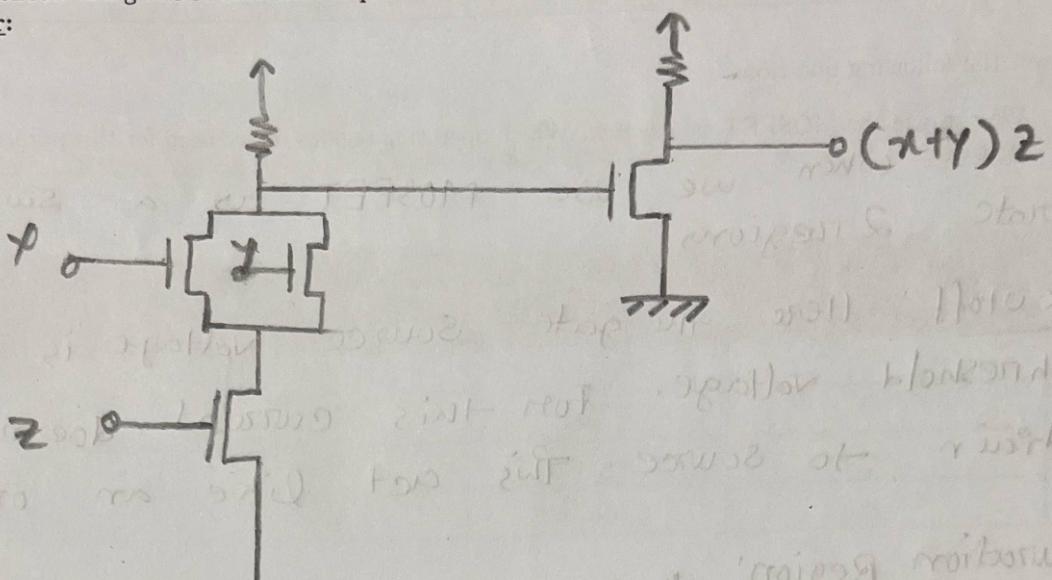

4. When a MOSFET is in triode mode, does it display zero, finite or infinite resistance? Justify your answer.

Answer:

When a MOSFET is in triode mode, it shows finite resistance in triode mode.

$$\# V_{DS} < V_T$$

$$\# V_{GS} > V_{DS}, (V_{GS} - V_T = V_{DS})$$

5. If  $V_{DS} = 3V$ ,  $V_{GS} = 3V$  and  $V_T = 1V$ , find the gate current, drain current and source current of a MOSFET given that  $k = 0.5mA/V^2$ .

Answer:


For an ideal MOSFET, the gate current is zero, so  $I_{Gn} = 0mA$ .

Now,

$$V_{DS} = 3V, V_{GS} - V_T = 2 \leq V_{DS} \text{ (saturation)}$$

$$I_D = \frac{k}{2} (V_{GS} - V_T)^2 = \frac{0.5}{2} (3-1)^2 = 1mA$$

$$I_S = I_D + I_{Gn} = 1mA$$

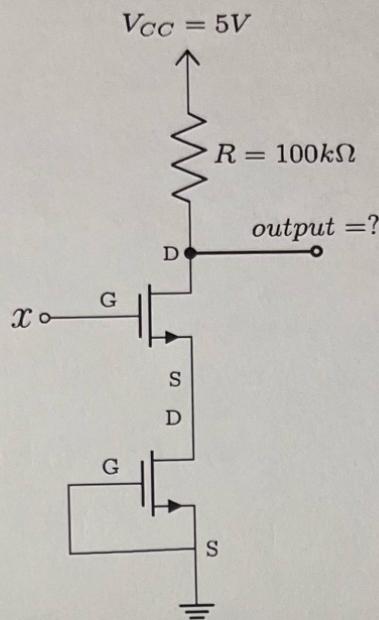

6. What is the value of the output of the circuit above?

Answer: assume ,  $V_s = 0V$

# the top N-MOS has  $V_{GS} = 0$  , so it is off .


# output = 5V


**GW INSTEK GDS-1102B**

Digital Storage Oscilloscope  
100 MHz 1 GS/s

VPO  
Variable-Persistence Oscilloscope

HARDCOPY

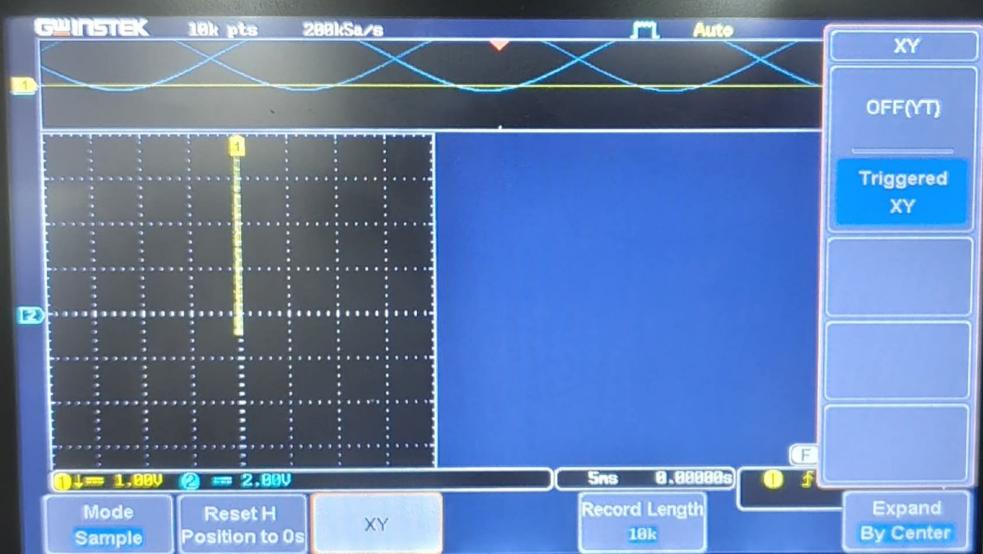

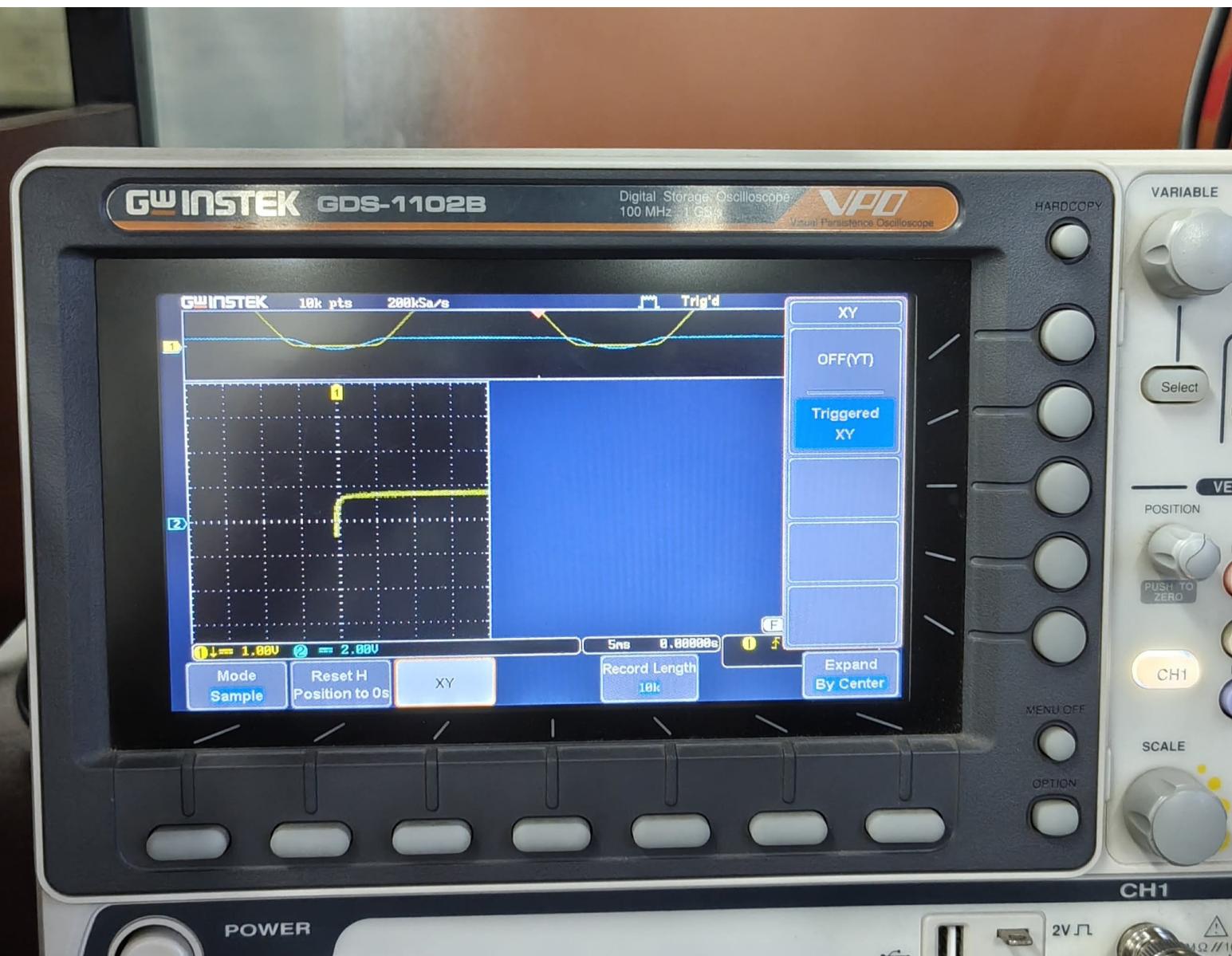


**GWINSTEK GDS-1102B**

Digital Storage Oscilloscope  
100 MHz 1 GS/s

VPO  
Visual Persistence Oscilloscope

HARDCOPY

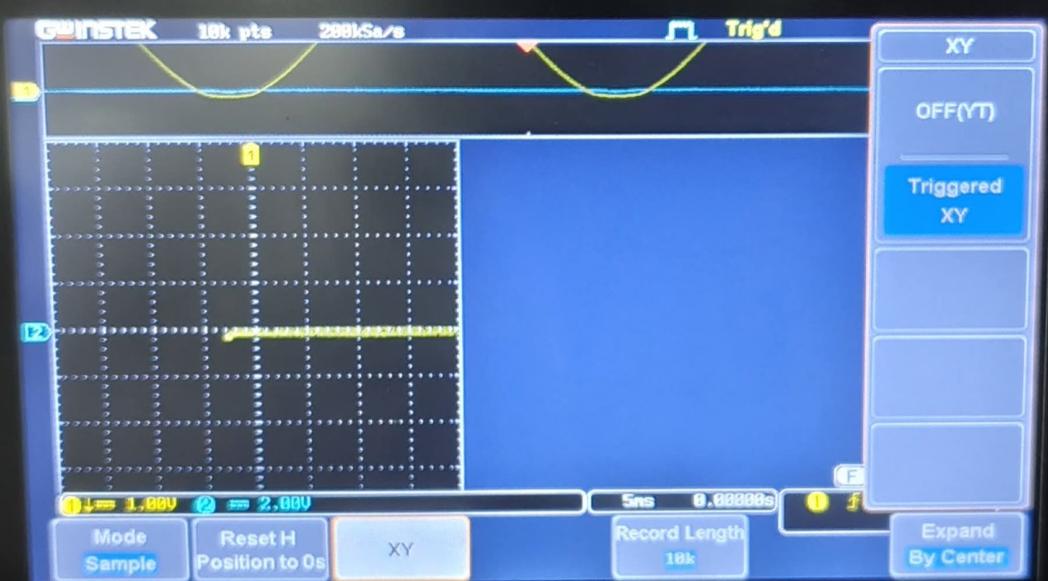

POWER

MENU OFF

OPTION

CH1