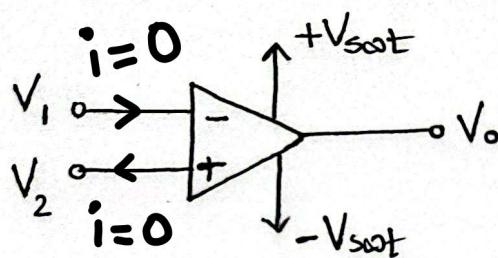


## 2.1 Op-Amp OL Practice Problem Solution



$V_0$  = output terminal

$V_1$  = inverting terminal

$V_2$  = non-inverting terminal

$$\text{gain equation} \Rightarrow V_0 = A V_0 \\ = A(V_2 - V_1)$$

### Problem 1

I.  $V_2 = -40 \mu\text{V}$

$A = 150,000$

$V_0 = +15 \text{ V}$

$V_1 = ?$

Use,


$$V_0 = A(V_2 - V_1)$$

$$\Rightarrow 15 = 150,000(-40 \times 10^{-6} - V_1)$$

$$\therefore V_1 = -1.4 \times 10^{-4} \text{ V}$$

$$= -140 \mu\text{V}$$

II.

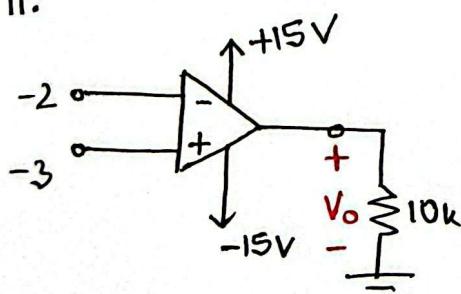

$$V_0 = A(V_2 - V_1)$$

$$= 10^4(-3 - (-2))$$


$= -10,000 \text{ V} \rightarrow \text{not possible.}$

Output will go to negative saturation.

$$\therefore V_0 = -15 \text{ V}$$
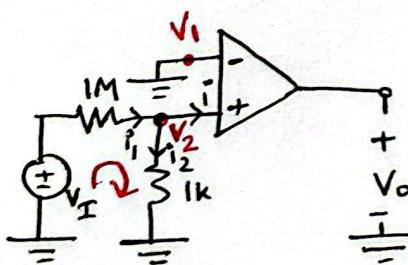
## Problem 2

A common mistake in problems like these -  
 many of you will consider that  $V_I$  is being applied to the non-inverting terminal directly,  
 but  $V_I \neq V_2$ , as there is a  $1k\Omega$  resistor.



KCL at  $V_2$ ,

$$i_1 = i + i_2 \quad (\text{but } i=0)$$

$$\therefore i_1 = i_2, \text{ so } V_I, 1M\Omega, 1k\Omega$$

are all in series with each other.

KVL at highlighted loop,

$$-V_I + (1M \times i_1) + (1k \times i_1) = 0$$

$$i_1 = \frac{V_I}{1M + 1k}$$

$$= \frac{2.0}{10^{16} + 10^3} = 1.998 \mu A$$

$$\therefore V_2 = i_2 \times 1k$$

$$= 1.998 \mu A \times 1k$$

$$= 1.998 mV$$

Alternative to this KVL,

$$V_2 = \frac{1k}{1k + 1M} \times V_I$$

$$= 1.998 mV$$

(voltage divider rule)


We know,

$$V_o = A(V_2 - V_I)$$

$$\Rightarrow A = A(1.998 mV - 0)$$

$$\therefore A = 2002$$


\*\* If the problem looked like -

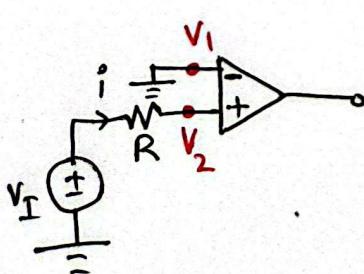

We know that  $i = 0$  here ( $\text{as } R_i = \infty$ ), but we can define  $i$  as -

$$i = \frac{V_I - V_2}{R} = 0 \Rightarrow V_I = V_2$$
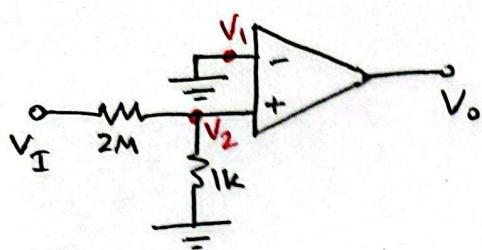
### Problem 3 → A variation of problem 2.



Using voltage divider rule,

$$V_2 = \frac{1k}{1k + 2M} \times V_I$$

$$V_I = \frac{(1k + 2M) \times V_2}{1k}$$

$$\text{Given, } A = 10^4,$$

$$V_o = -2.0V,$$

$$V_s = 0 \text{ (grounded)}$$

$$= \frac{(10^3 + 2 \times 10^6) \times (-2 \times 10^{-4})}{10^3}$$

$$= -0.4002 V$$

$$\Rightarrow V_o = A(V_2 - V_1)$$


$$\Rightarrow -2 = 10^4(V_2 - 0)$$

$$\therefore V_2 = -2 \times 10^{-4} V$$


### Problem 4

For problems like these, write these conditions first :  $V_2 > V_1, V_o = +V_{sat}$   
 $V_2 < V_1, V_o = -V_{sat}$

$V_o$  vs.  $t$ ,

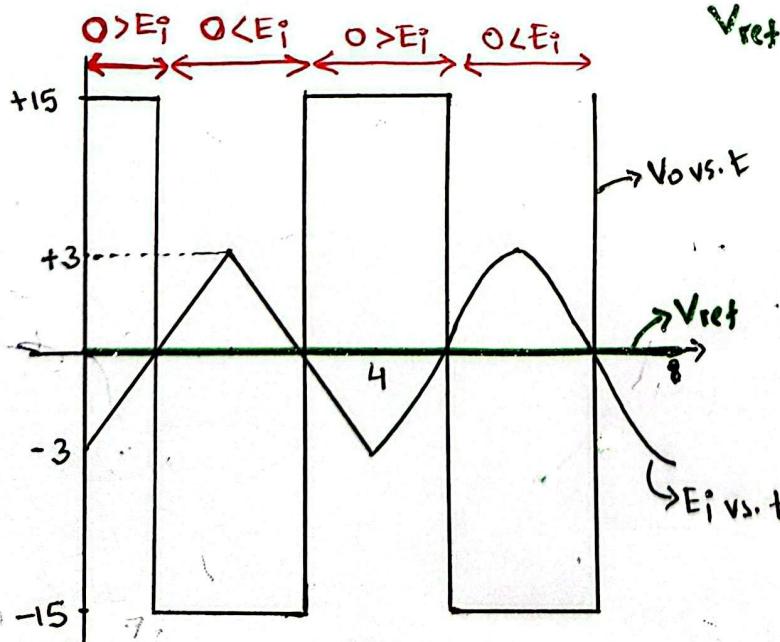

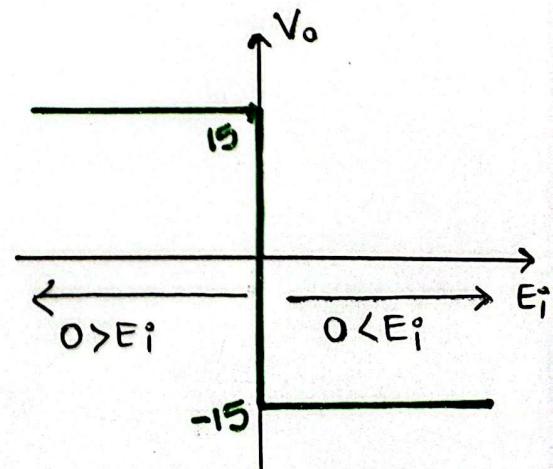
$$V_{ref} = 0 \left\{ \begin{array}{l} \therefore 0 > E_i, V_o = +15V \\ 0 < E_i, V_o = -15V \end{array} \right.$$



## Problem 5

- I. Given that  $V_i > +5V$ ,  $V_o = +15V \rightarrow V_2 > V_1$ ,  $V_o = +V_{sat}$
- input signal crosses  $+5V$  in the positive direction.
- $+4 +5 +6 +7$
- $\rightarrow V_o = +V_{sat}$
- or,  $V_2 < V_1$ ,  $V_o = -V_{sat}$
- $\rightarrow V_o = +V_{sat}$
- for  $V_2 > V_1$

Circuit:

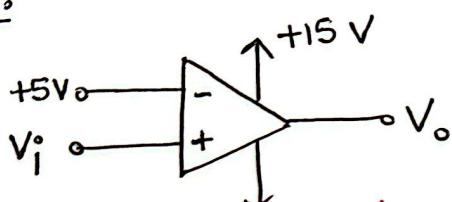

(this is an arbitrary value. You can consider anything less than 0, as question states 'output voltage will go positive to...')

$$\therefore V_2 = V_i, V_1 = +5$$

- II. Given that  $V_i < -4$ ,  $V_o = +15V$  (and  $V_i > -4$ ,  $V_o = -15V$ )

input signal is below  $-4V$ .


$$\rightarrow V_2 > V_1, V_o = +V_{sat} \checkmark$$

$$V_2 < V_1, V_o = -V_{sat}$$

$$-4 > V_i, V_o = +15V$$

$$\therefore V_2 = -4, V_1 = V_i$$

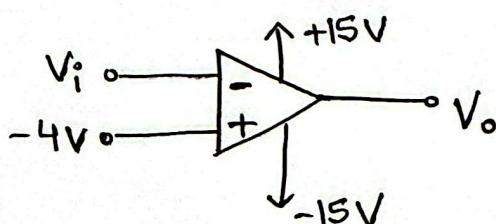\* this time, both  $\pm V_{sat}$  were specified in the question.



Circuit:

## Problem 6


$$\left. \begin{array}{l} V_2 > V_1, V_o = +V_{sat} \\ V_2 < V_1, V_o = -V_{sat} \end{array} \right\} \text{given, } V_2 = V_{temp} = 4 \quad \rightarrow \quad \begin{array}{l} 4 > E_C, V_o = +15 V \\ 4 < E_C, V_o = 0 V \end{array}$$

$$V_1 = E_C$$

$$+V_{sat} = +15 V$$

$$-V_{sat} = 0 V$$

a)  $V_o$  vs.  $E_C$

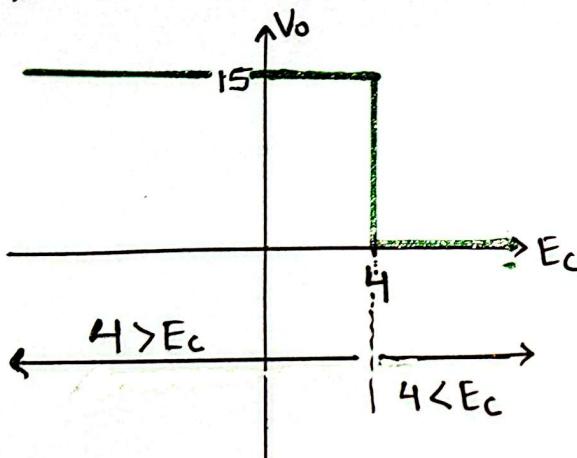

c) [optional]

Find the straight line equation for  $E_C$ .

Two data points  $(t, V) = (0, 0)$  and  $(20 \text{ ms}, 10 \text{ V})$


$$\Rightarrow V - 0 = \frac{10 - 0}{20 - 0} (t - 0)$$

$$\therefore V = \frac{1}{2} t \quad (t \text{ is in ms})$$

The first intersection occurs when  $V = 4$ ,

$$\Rightarrow 4 = \frac{1}{2} t$$

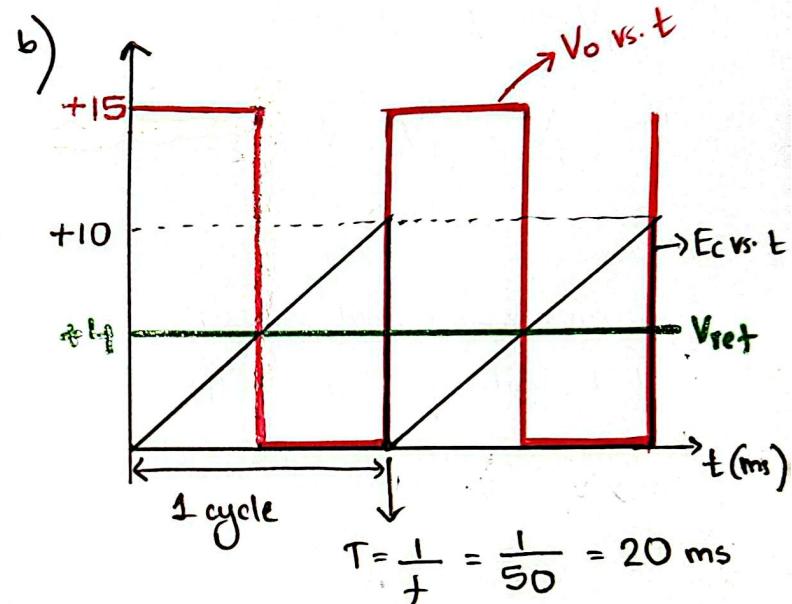$t = 8 \text{ ms} \rightarrow \text{HIGH TIME, as from 0 to 8 ms, } V_o = +15 \text{ V.}$



$$T = \frac{1}{f} = \frac{1}{50} = 20 \text{ ms}$$



## Problem 7 → variation of problem 6

$$\left. \begin{array}{l} V_2 > V_1, V_o = +V_{sat} \\ V_2 < V_1, V_o = -V_{sat} \end{array} \right\} \text{given } V_2 = E_C$$

$V_1 = V_{temp} = +3V \rightarrow E_C > 3, V_o = +15V$   
 $+V_{sat} = 15V$   
 $-V_{sat} = 0V$

$E_C < 3, V_o = -15V$

a)  $V_o$  vs.  $E_C$

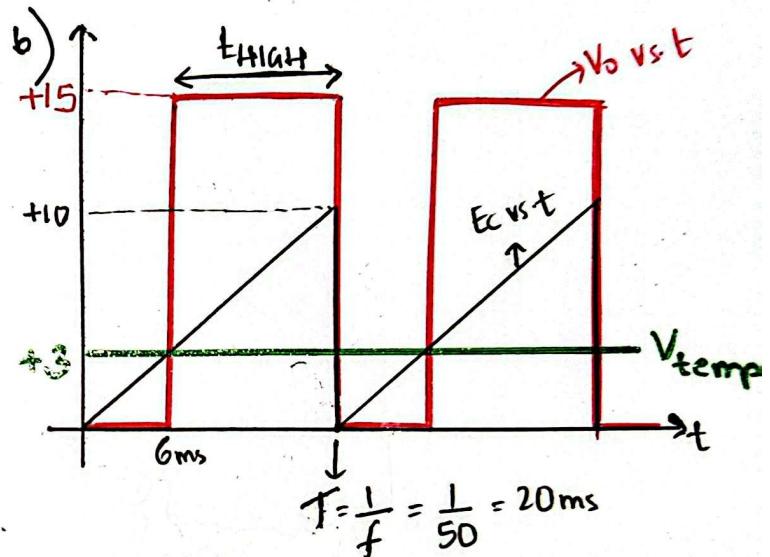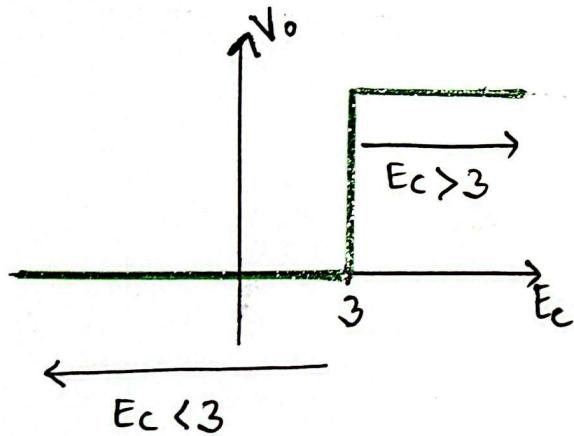

c) [optional]  $V = \frac{1}{2}t$  [see problem 6]


$$\text{at } V = 3, 3 = \frac{1}{2}t$$

$$t = 6 \text{ ms}$$


↳ LOW TIME

$$\therefore t_{HIGH} = 20 - 6 = 14 \text{ ms}$$

## Problem 8

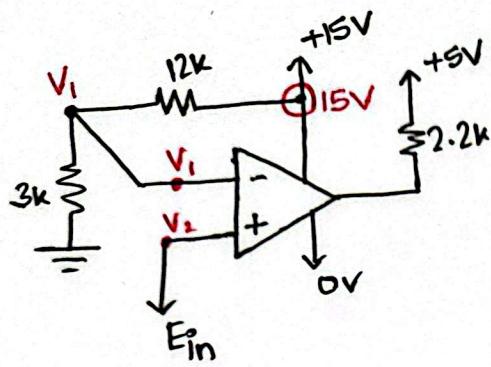

simplify →

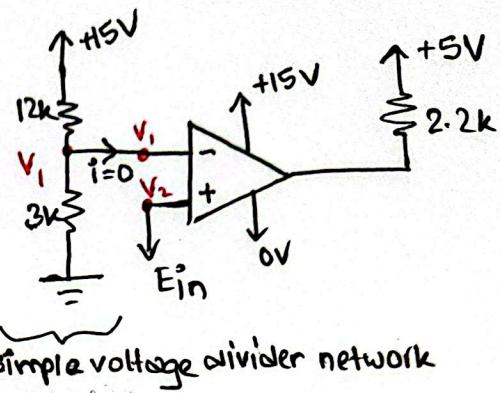


a) Write the conditions:

$$\left. \begin{array}{l} V_2 > V_1, V_o = +V_{sat} \\ V_2 < V_1, V_o = -V_{sat} \end{array} \right\} \rightarrow$$

$$V_1 = \frac{3}{12+3} \times 15 = 3V$$


$$E_{in} > 3, V_o = +V_{sat} = +15V$$

$$E_{in} < 3, V_o = -V_{sat} = 0V$$

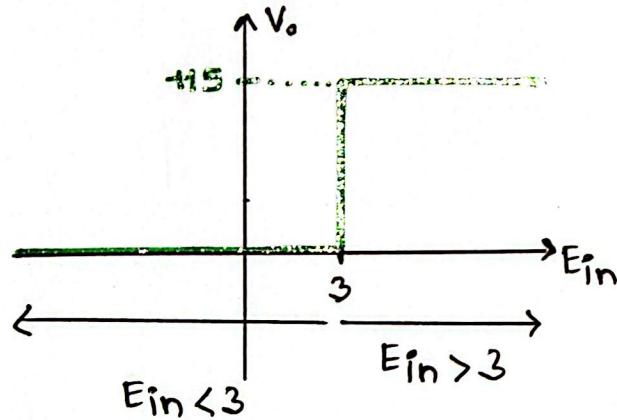


b)  $E_{in}$  = triangular wave with 5V amplitude and 100Hz frequency



important for axis intersection points

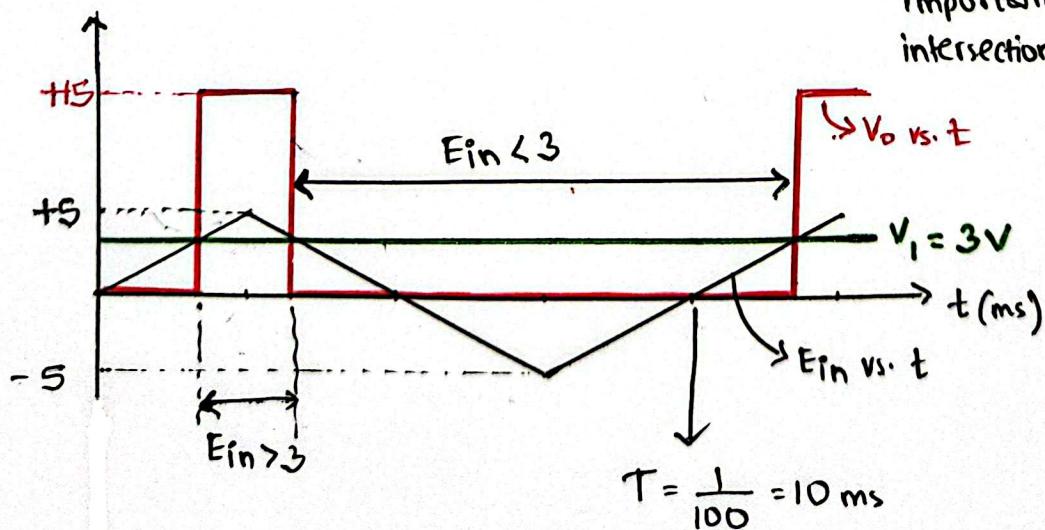

$$T = \frac{1}{100} = 10ms$$

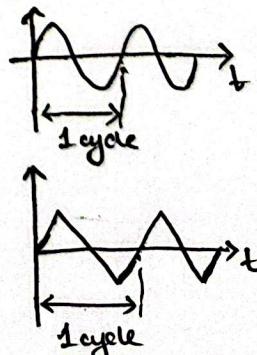


## Problem 9

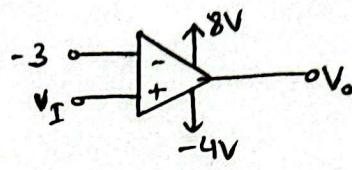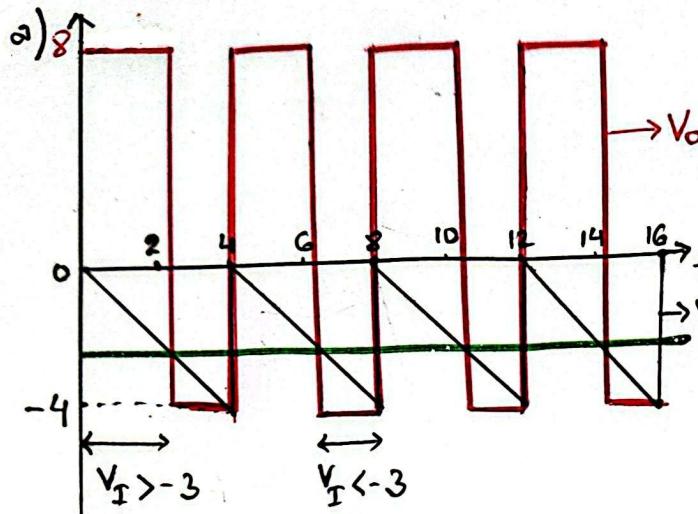

$$\left. \begin{array}{l} V_2 > V_1, V_o = +V_{sat} \\ V_2 < V_1, V_o = -V_{sat} \end{array} \right\}$$

$$V_I > -3, V_o = +8V$$

$$V_I < -3, V_o = -4V$$

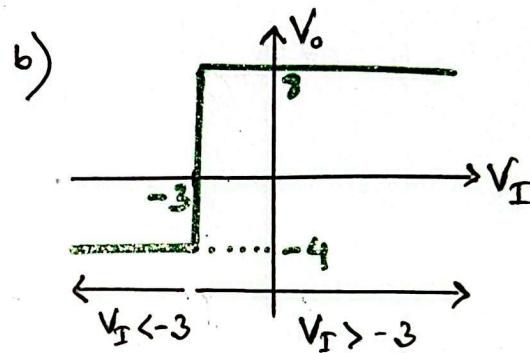

## Problem 10

From circuit,  $V_2 = -3V$

$$V_1 = V_I$$


$$+V_{sat} = +15V$$

$$-V_{sat} = -15V$$


$$\left. \begin{array}{l} V_2 > V_1, V_o = +V_{sat} \\ (-3 > V_I, V_o = +15V) \end{array} \right\}$$

$$V_2 < V_1, V_o = -V_{sat}$$

$$(-3 < V_I, V_o = -15V)$$

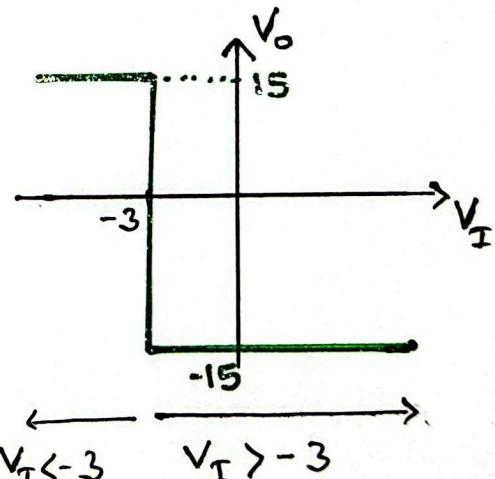

## Problem 11

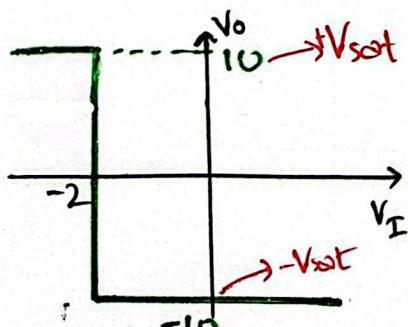

$$\left. \begin{array}{l} V_I < -2, V_o = +10 \\ V_I > -2, V_o = -10 \end{array} \right.$$


Write the conditions:

$$V_2 > V_1, V_o = +V_{sat}$$


$$V_2 < V_1, V_o = -V_{sat}$$

matches.

$$\therefore V_2 = -2, V_1 = V_I$$

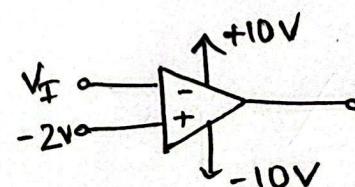

## Problem 12

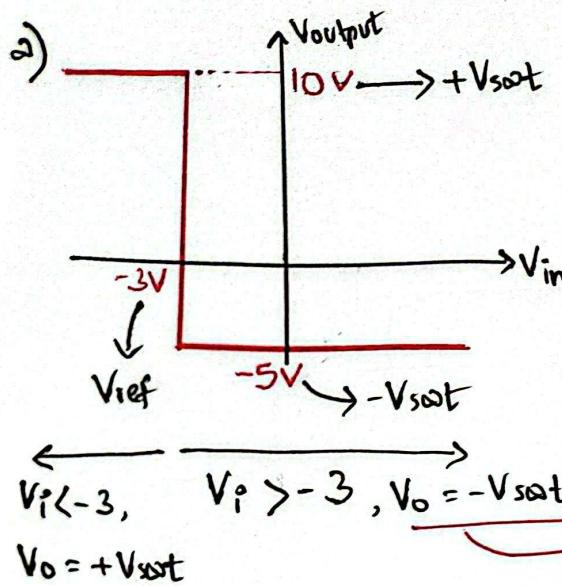

Write the conditions,



$$V_2 > V_1, V_o = +V_{\text{sat}}$$

$$-3 > V_i, V_o = +10V$$

$$V_2 < V_1, V_o = -V_{\text{sat}}$$

$$V_i > -3, V_o = -5V$$

∴ circuit:

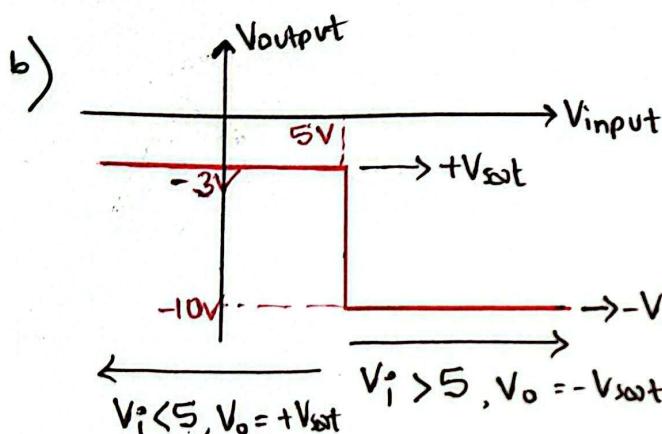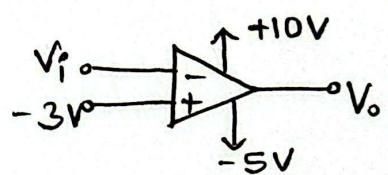


$$V_2 > V_1, V_o = +V_{\text{sat}}$$


$$V_2 < V_1, V_o = -V_{\text{sat}}$$

$$\therefore V_2 = 5, V_1 = V_i$$

∴ circuit:

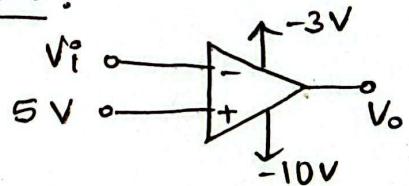

## Problem 13

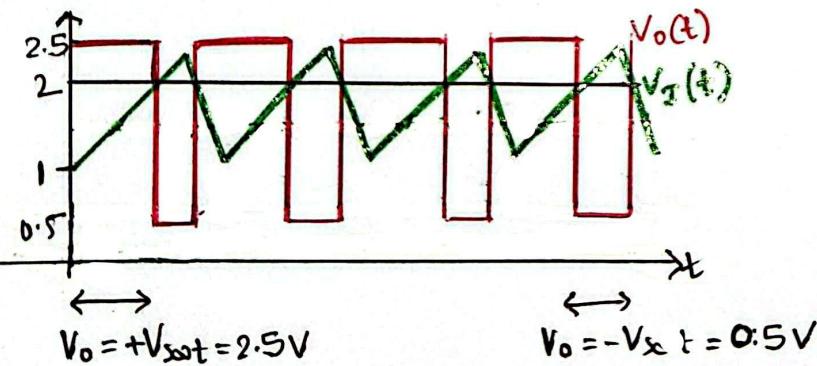

when  $V_{\text{ref}} = 2V > V_I(t)$

when  $2V < V_I(t)$

$$a) V_2 > V_1, V_o = V_{\text{sat}}$$

$$V_o = 2.5 \text{ for } 2V > V_I(t)$$

$$\therefore V_2 = 2, V_1 = V_I$$

