

ID:	Name:
-----	-------



## Brac University

Semester: Summer 2024

Course Code: CSE251

Electronic Devices and Circuits

Section: 01-27

Set
01

Assessment: *Midterm Exam*

Duration: 1 hour 40 minutes


Date: 13 July, 2024

Full Marks: 30


**Instructions:** Answer any 3 out of 5 questions. Read the questions carefully.
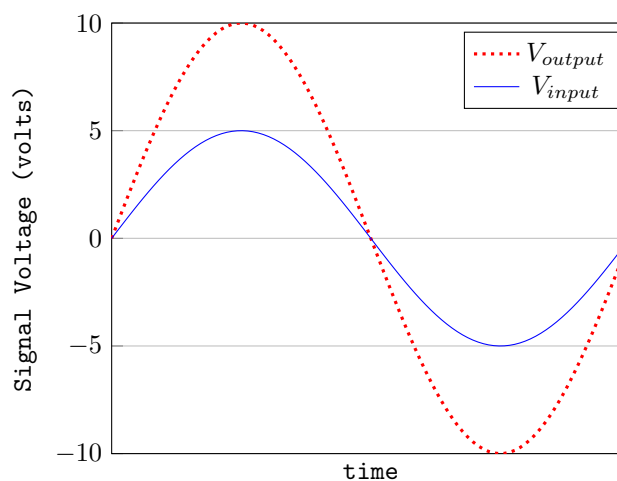
### ■ Question 1 of 5 [CO1, CO2, CO3] [10 marks]

Michael Scott wants to make a phone call to his assistant, Dwight Schrute, but the outdated phone system keeps failing as the signal is too weak by the time it reaches Dwight. Dwight plans on designing a device to help Michael make the call. The device will take the weak signal as input and give a strong signal at its output without changing the waveshape and polarity of the signal as shown in the following figure.



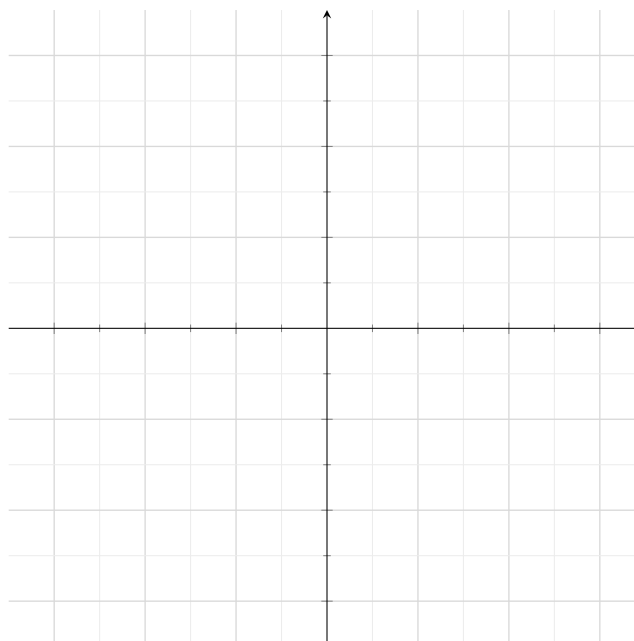- (a) [1 mark] What is a virtual ground? **Explain** briefly.
- (b) [2 marks] **Analyze** the figure above and **draw** the VTC graph of the device in the graph given below. **Label** the graph properly.




- (c) [3 marks] **Design** circuit for the device based on the waveshapes in the figure shown above.
- (d) [4 marks] Dwight calculates his yearly sales using the following function. **Design** a device to help Dwight implement the function,  $f$  where  $x$ ,  $y$ , and  $z$  will be the inputs of the device.

$$f = -3 \frac{dz}{dt} + 6x + 9 \int (y) dt$$


### ■ Question 2 of 5 [CO1, CO2, CO3] [10 marks]

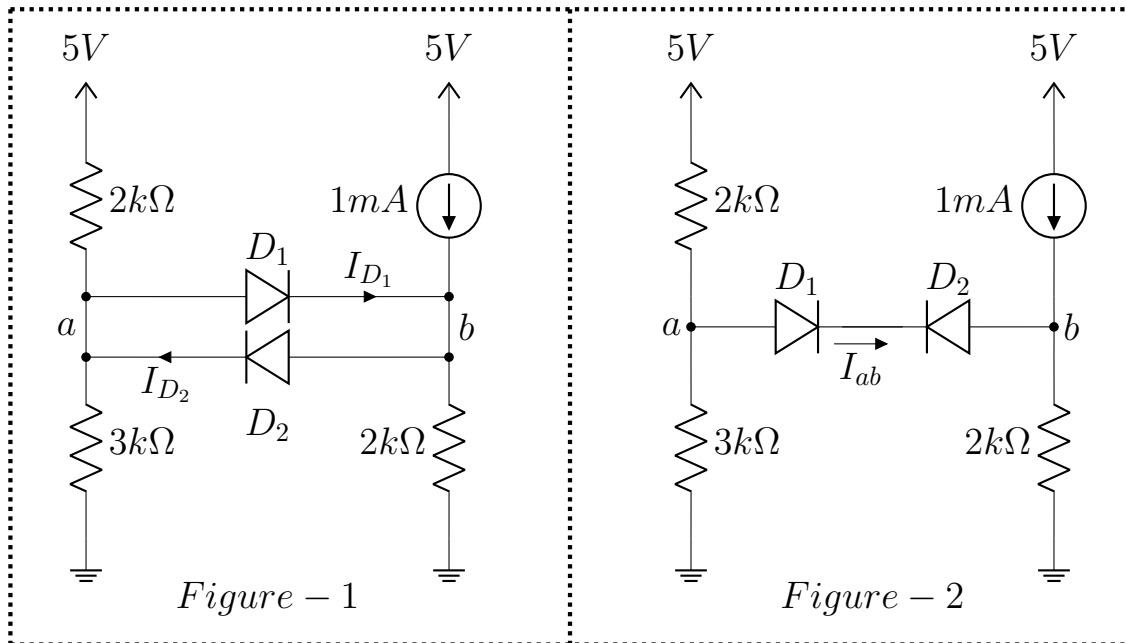- (a) [2 marks] **State** the conditions to verify the assumptions regarding the operating states of an ideal diode model.
- (b) [2 marks] **Calculate** the voltages at node a and b in Figure-1 if both of the diodes are disconnected.
- (c) [4 marks] **Analyze** the circuit in Figure-1 and **calculate**  $I_{D_1}$  and  $I_{D_2}$  using the method of assumed states. You must **validate** your assumptions. **Use** the CVD model with  $V_{D_0} = 0.7V$  for both diodes.
- (d) [2 marks] **Analyze** the circuit in Figure-2 and **calculate**  $I_{ab}$ .


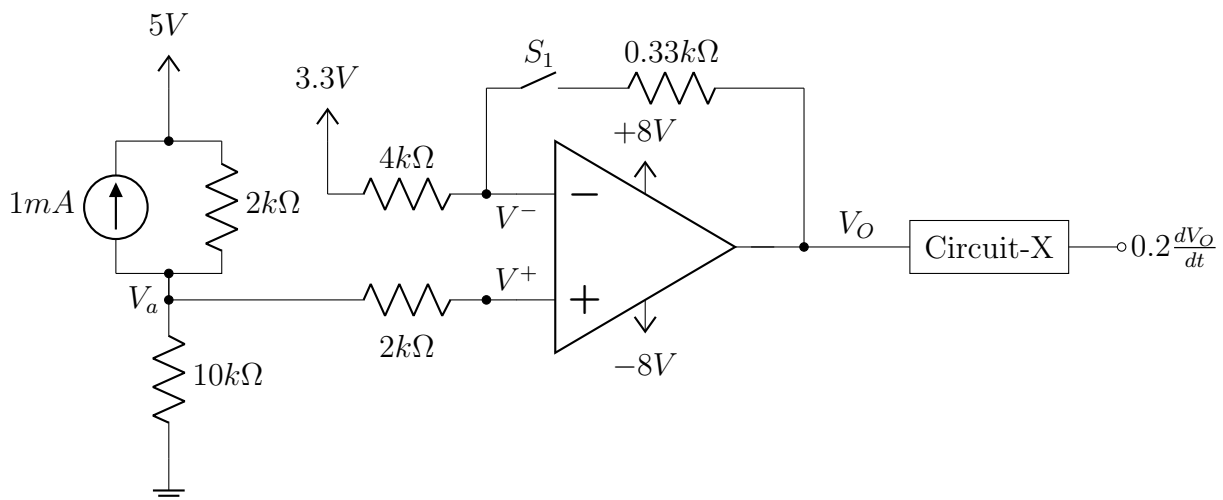
### ■ Question 3 of 5 [CO1, CO2, CO3] [10 marks]


The circuit diagram has a switch  $S_1$  which is shown to be 'open' in the figure. The output  $V_O$  is passed through an unknown block of 'Circuit-X' and a differentiated result is generated.



- (a) [1 mark] **State** the equation of gain of an inverting amplifier.
- (b) [3 marks] **Calculate** the values of  $V_a$  and  $V_+$ .
- (c) [2 marks] **Determine**  $V_O$  when the switch  $S_1$  is closed.
- (d) [2 marks] **Determine**  $V_O$  when the switch  $S_1$  is open.
- (e) [2 marks] **Design** the 'Circuit-X'. **Assume** any value if necessary.
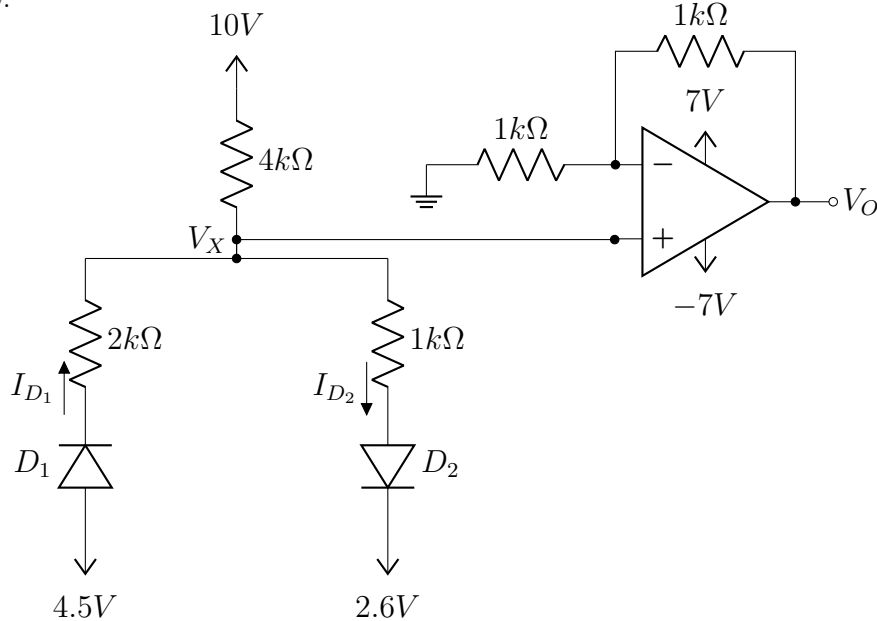
### ■ Question 4 of 5 [CO1, CO2, CO3] [10 marks]

Consider the following circuit with an ideal op-amp and two diodes. The diodes  $D_1$  and  $D_2$  have  $V_{D_0}$  of 0.5V and 0.6V respectively.



- [1 mark] **State** the equivalent circuit model of an ideal diode in reverse bias.
- [7 marks] **Analyze** the circuit and **calculate**  $V_X$ ,  $I_{D1}$ , and  $I_{D2}$ . **Use** method of assumed states. You must **validate** your assumptions.
- [2 marks] **Determine** the output voltage,  $V_O$ .

### ■ Question 5 of 5 [CO1, CO2, CO3] [10 marks]

In the adjacent circuit  $V_{DD} = 5V$  and other parameters are as follows:

#### Input Voltages      Diode Barrier Voltages

$V_1 = 2.0V$       For D1:  $V_{D1} = 0.3V$

$V_2 = 2.2V$       For D2:  $V_{D2} = 0.7V$

$V_3 = 2.4V$       For D3:  $V_{D3} = 0.5V$

$V_4 = 2.5V$       For D4:  $V_{D4} = 0.9V$

For D5 & D6:  $V_{D5} = V_{D6} = 1V$

Based on the given circuit, answer the following questions.

- [2 marks] **Draw** the I-V characteristics of a diode using the constant voltage drop with resistance (CVD+R) model. Clearly indicate the different operating modes on your graph.
- [3 marks] **Determine** the values of  $V_{O1}$  and  $V_{O2}$ .
- [2 marks] **Calculate** the value of  $V_O$ .
- [3 marks] Solve the circuit to find  $V_O$ , assuming  $V_3 = -2V$  and  $V_4 = -3V$ , while all other voltages remain unchanged. **Identify** the states of the diodes D3 and D4. [Hint: You may need to use the method of assumed states in order to determine  $V_{O2}$ .]

