

## Brac University

Semester: Fall 2024

Course Code: CSE251

Electronic Devices and Circuits

Section: 01-28

Set
01

Assessment: *Midterm Exam*

Duration: 1 hour 15 minutes

Date: 22 November, 2024

Full Marks: 30

**Instructions:** Answer all the questions and read the questions carefully.

### ■ Question 1 of 3 [CO1] [6 marks]

- [1.5 marks] **State** the assumptions for the parameters of an ideal op-amp.
- [1 mark] **State** the equation of the output of an op-amp integrator circuit.
- [1.5 marks] Why is a diode considered a non-linear device? **Explain** briefly.
- [2 marks] **State** the conditions to verify the assumptions regarding the operating states of the CVD model of a diode.

### ■ Question 2 of 3 [CO2] [11 marks]

- [5 marks] **Analyze** the circuit in *Figure-1*, and **calculate** the value of  $V_X$ . Now, **draw** the waveform of  $V_O$ , and **label** the graph properly.
- [5 marks] **Analyze** the circuit in *Figure-2*, and **calculate**  $V_X$ ,  $V_Y$ ,  $I_{D1}$ , and  $I_{D2}$  using the method of assumed states. You must **validate** your assumptions. Use  $V_{D0} = 0.7V$  for both diodes.
- [1 mark] **Analyze** the circuit in *Figure-3*, and **determine** the boolean logic function,  $f$  with the boolean inputs  $x$ ,  $y$ ,  $z$ . **Assume**, ideal diodes are used here.

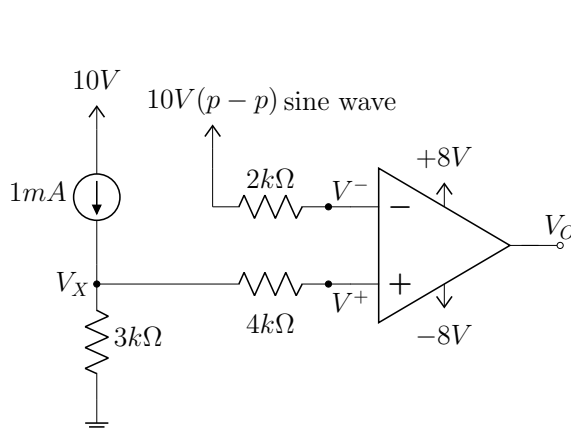


Figure-1

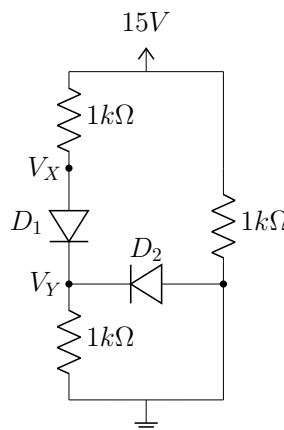


Figure-2

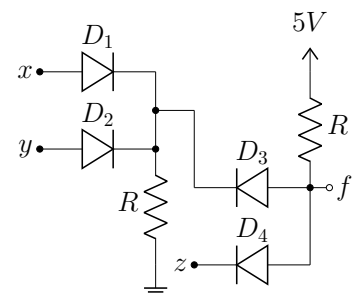


Figure-3

### ■ Question 3 of 3 [CO3] [13 marks]

- [6 marks] **Design** a device to implement the following function,  $f$  where  $x$ ,  $y$ , and  $z$  are the inputs of the device. **Assume** any value if necessary.

$$f = \frac{d^2x}{dt^2} + 10y + \int (10z - 9)dt$$

- [3 marks] **Design** the circuits with the boolean inputs  $A$ ,  $B$ ,  $C$ ,  $D$  using Ideal Diodes to implement the following boolean logic functions,

- $f = A + C + B.D$
- $f = A.C + B + D$

- (c) [2 marks] **Analyze** the graph in *Figure-4*, and **design** a circuit that implements the relationship between the voltage waveforms,  $V_{input}$  and  $V_{output}$ . **Assume** any value if necessary.

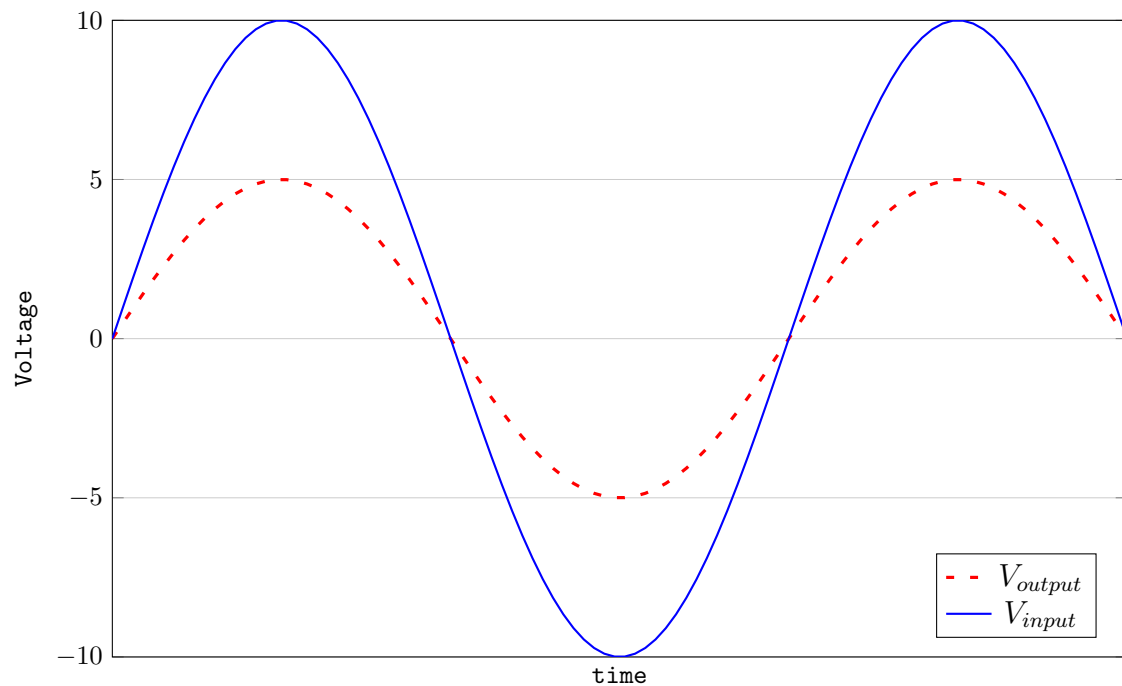


Figure-4

- (d) [2 marks] Now, **modify** the circuit you designed in the previous question so that  $V_{output(modified)}$  represents the output waveform of the modified circuit as shown in *Figure-5*. **Assume** any value if necessary.

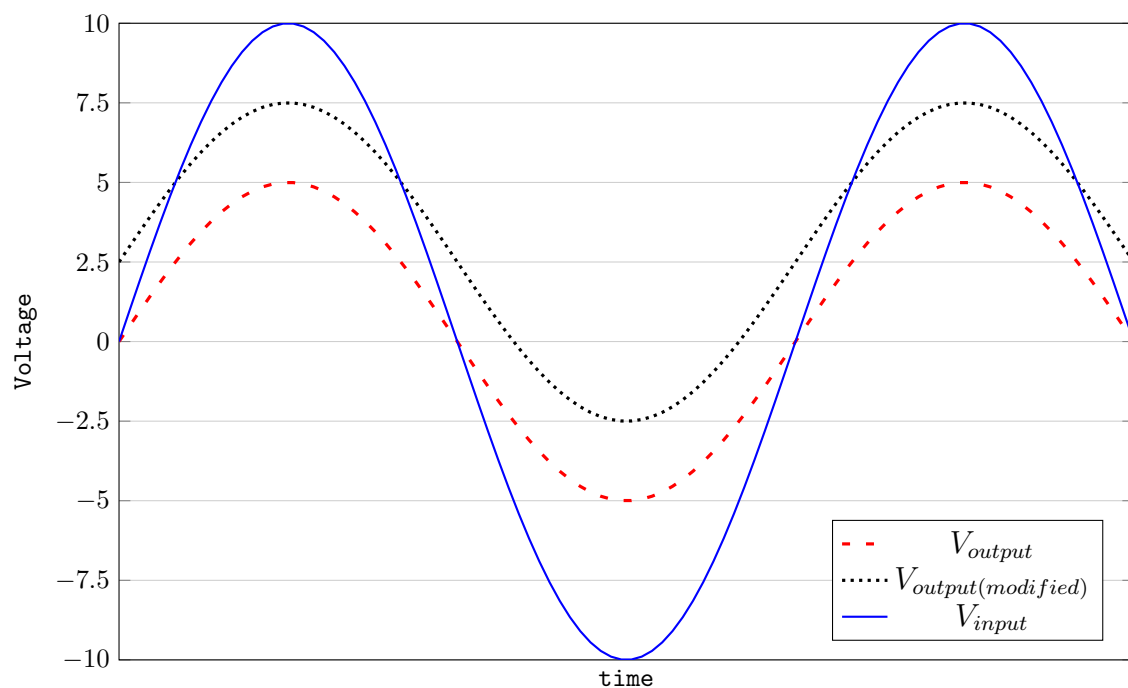


Figure-5