
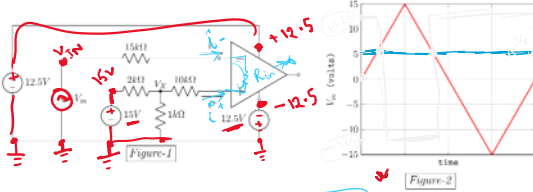


■ Question 1 [CO2] [7.5 marks]

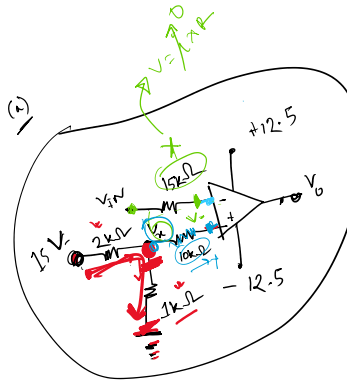- (a) [2.5 marks] Show the alternative representation (i.e. line representation/diagram) of the circuit in Figure-1.
(b) [1 mark] State the values of i^+ and i^- of the circuit shown in Figure-1.
(c) [1.5 marks] Analyze the circuit in an alternative representation from part-(a), and calculate V_X .
(d) [2.5 marks] Analyze the circuit in an alternative representation from part-(a) & the waveform of V_{in} in Figure-2, and draw the waveform of the output voltage on Figure-2. Label the graph properly.




$i^+ = i^- = 0$



(c) $V_X = 0 = \frac{1}{1+2} \times 15 = 5V$
 $V_o = A(V_+ - V_-)$
 $V_- = V_X$
 $V_+ = 5V$
 $V_o = 12.5V$
 $V_o = -12.5V$


■ Question 3 [CO2] [7.5 marks]

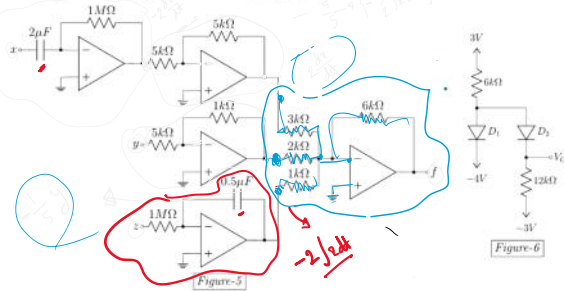- (a) [2 marks] Analyze the circuit in Figure-5, and determine the expression of the function, f where x , y and z are the input of the circuit.
(b) [4 marks] Analyze the circuit in Figure-6, and calculate I_{D1} , I_{D2} , & V_O using the method of assumed states. You must validate your assumptions. Here, $V_{D0} = 0.7V$.
(c) [1.5 marks] Draw the Voltage Transfer Characteristics (VTC) of a non-inverting amplifier with Gain = 1.5, $V_{sat}^+ = 8V$, and $V_{sat}^- = -8V$. Label the graph properly.



$V_o = -\frac{1}{R_0} V_{sat}$

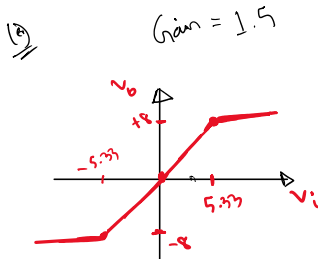Adder,
 $V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$
 $= -6 \left(\frac{2 \frac{dx}{dt}}{3} + \frac{-4}{2} + \frac{2 \frac{dx}{dt}}{1} \right)$



non-inv
 $V_o = \left(1 + \frac{R_2}{R_1} \right) V_i$
 $V_{sat}^+ = 8V$
 $V_{sat}^- = -8V$
 $\frac{1 + \frac{R_2}{R_1}}{\frac{R_2}{R_1}} = 1.5$
 $\frac{R_2}{R_1} = \frac{1}{2} \left[R_2 = 1k\Omega, R_1 = 2k\Omega \right]$

$V_o = 0 \rightarrow V_i = 0$
 $V_o = 8 \rightarrow 8 = 1.5 V_i \rightarrow V_i = \frac{8}{1.5} = \frac{16}{3} = 5.33$
 $V_o = -8 \rightarrow -8 = 1.5 V_i \rightarrow V_i = \frac{-8}{1.5} = -\frac{16}{3} = -5.33$

■ Question 4 [CO1] [5 marks]


- (a) [1 mark] State the relation between the input and output voltages of an ideal op-amp.
(b) [2 marks] What is a linear amplifier? Explain the reason for the saturation of the output voltage of an amplifier briefly.

$V_o \propto V_i$

$V_o = A(V_+ - V_-)$

■ Question 5 [CO3] [5 marks]

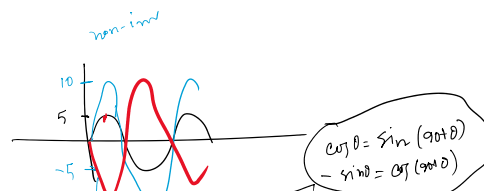- (a) [3 marks] Analyze the graph in Figure-7, and design a circuit that implements the relationship between the voltage waveforms, $V_{input} = 5 \sin(t)$ and V_{output} . Assume any value if necessary.
(b) [2 marks] Design the circuits with the boolean inputs A, B, C, D using Ideal Diodes to implement the following boolean logic functions:
(i) $f = A.B.C + D$ (ii) $f = (A+B+C).D$



the voltage waveforms, $V_{input} = \sin(t)$ and V_{output} . Assume any value if necessary.

- (b) [2 marks] Design the circuits with the boolean inputs A, B, C, D using Ideal Diodes to implement the following boolean logic functions:
(i) $f = A.B.C + D$ (ii) $f = (A+B+C).D$

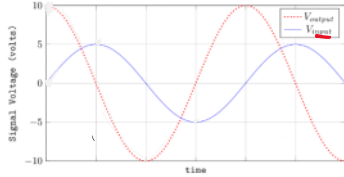


Figure-7


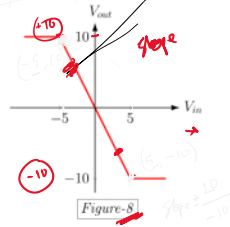


Figure-8

Question 6 [CO3] [5 marks]

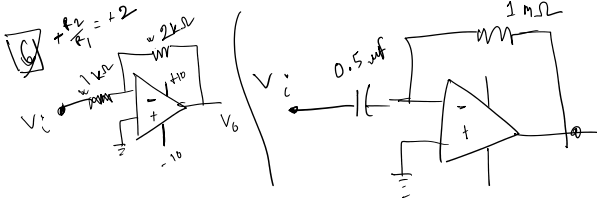- (a) [2 marks] Analyze the graph in Figure-8, and design a circuit that implements the relationship between V_{in} and V_{out} . Assume any value if necessary.
(b) [3 marks] Design a device to implement the following function, f where x , y , and z are the input of the device. Assume any value if necessary.

$$f = 5 \int (x+y) dt - 3 \frac{dz}{dt}$$




$$V_o = 10 \cos t$$

$$V_o = \left(-\frac{1}{RC} \int V_i dt \right) - 5 \cos t$$

$$\frac{1}{RC} = 2 \Rightarrow RC = \frac{1}{2}$$
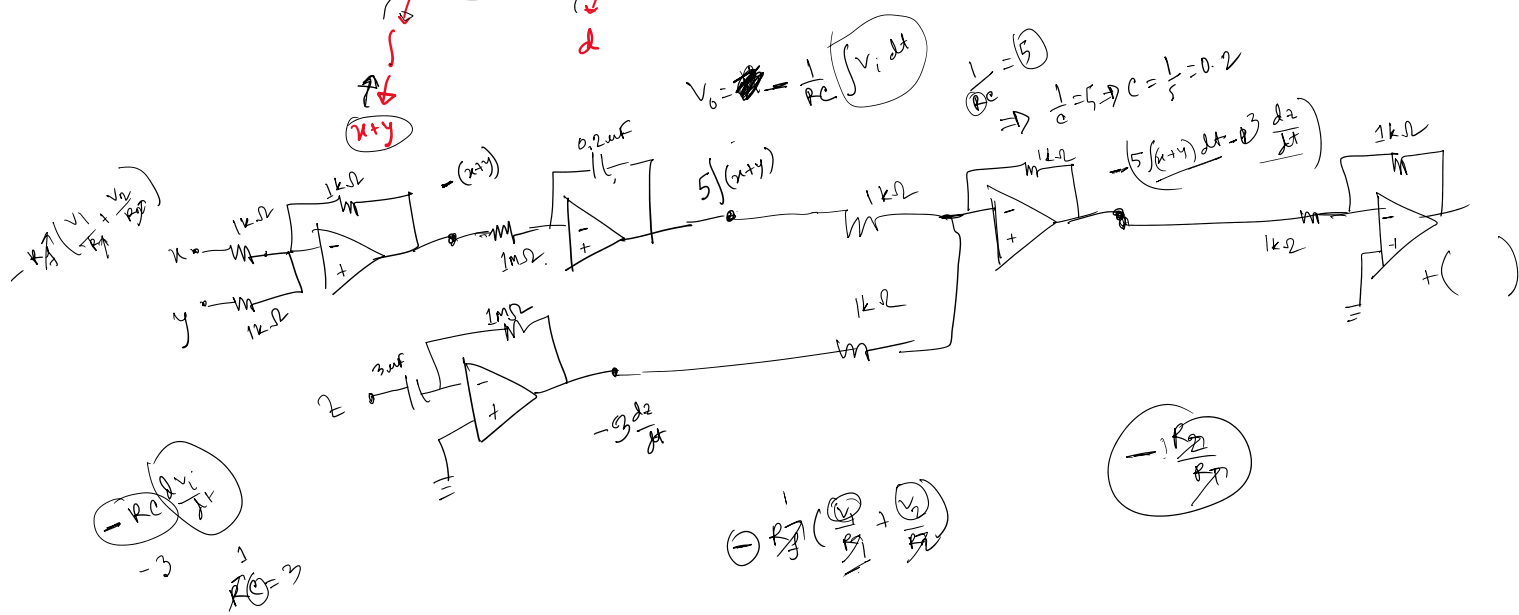
$$f = 5 \int (x+y) dt - 3 \frac{dz}{dt}$$



Question 7 [CO3] [5 marks]

- (a) [4 marks] The Voltage Transfer Characteristics (VTC) of an ideal NOT gate can be represented by the graph in Figure-9. Analyze the graph in Figure-9, and design a circuit using an op-amp comparator that can work as an ideal NOT gate. Assume any value if necessary.
(b) [1 mark] Design a circuit with the boolean inputs A, B using Ideal Diodes to implement the boolean logic function, $f = \bar{A}.B + A.B$


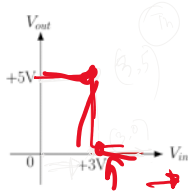


Figure-9

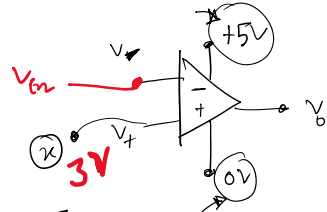

$$V_o = 5V - V_i$$

$$\Rightarrow 0 = 5 - V_i \Rightarrow V_i = 5V$$

$$V_o = 5V - V_i = 0$$


$$\Rightarrow V_i = 5V$$

$$\begin{aligned} x > V_{in} &\rightarrow +5 \\ x < V_{in} &\rightarrow 0 \end{aligned}$$

Summer 24


■ Question 1 of 5 [CO1, CO2, CO3] [10 marks]

Michael Scott wants to make a phone call to his assistant, Dwight Schrute, but the outdated phone system keeps failing as the signal is too weak by the time it reaches Dwight. Dwight plans on designing a device to help Michael make the call. The device will take the weak signal as input and give a strong signal at its output without changing the waveshape and polarity of the signal as shown in the following figure.

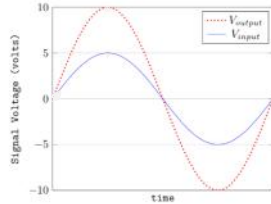


(a) [1 mark] What is a virtual ground? Explain briefly.

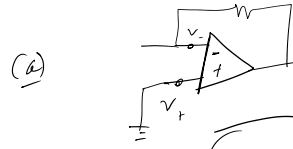(b) [2 marks] Analyze the figure above and draw the VTC graph of the device in the graph given below. Label the graph properly.




(b) Gain $\rightarrow 2$

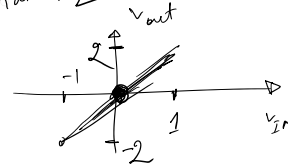

Slope = 2
Gain = 2

$$\frac{\Delta y}{\Delta x} = 2$$

$$\Delta y = \Delta x \times 2$$

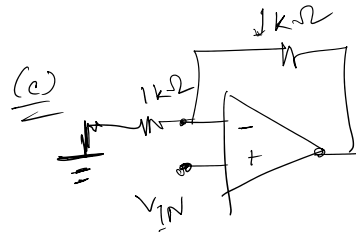

$$\left(1 + \frac{R_2}{R_1}\right) = 2$$


$$\frac{R_2}{R_1} = 1$$

(d) [4 marks] Dwight calculates his yearly sales using the following function. Design a device to help Dwight implement the function, f where x , y , and z will be the inputs of the device.

$$f = -3 \frac{dz}{dt} + 6x + 9 \int (y) dt$$

■ Question 3 of 5 [CO1, CO2, CO3] [10 marks]

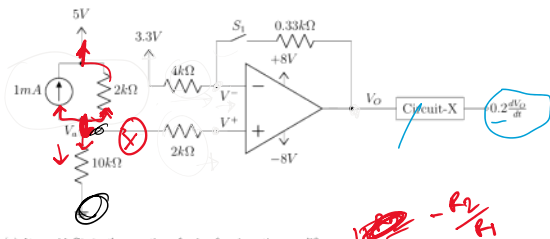The circuit diagram has a switch S_1 which is shown to be 'open' in the figure. The output V_O is passed through an unknown block of 'Circuit-X' and a differentiated result is generated.



(a) [1 mark] State the equation of gain of an inverting amplifier.


(b) [3 marks] Calculate the values of V_a and V_+ .

(c) [2 marks] Determine V_O when the switch S_1 is closed.

(d) [2 marks] Determine V_O when the switch S_1 is open.

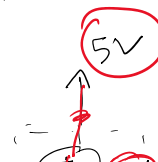
(e) [2 marks] Design the 'Circuit-X'. Assume any value if necessary.

$$1 + \frac{V_a - 5}{2} + \frac{V_a - 0}{10} = 0$$




$$5 - V_a = 2$$

$$\Rightarrow V_a = 3V$$

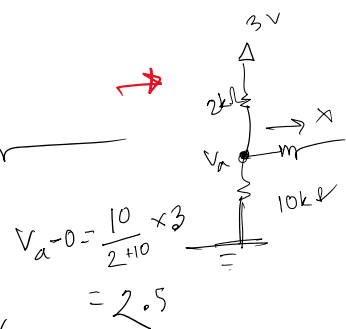

$$V_a - 0 = \frac{10}{2+10} \times 3$$

$$= 2.5$$

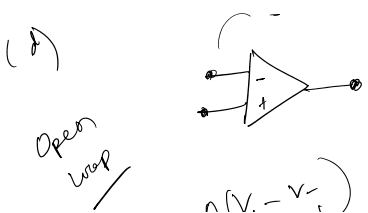


$$V_O = -8V$$

Open Loop

$$V_0 = A(V_+ - V_-)$$


2.5V (-) 3.3V

$$V_0 = -8V$$

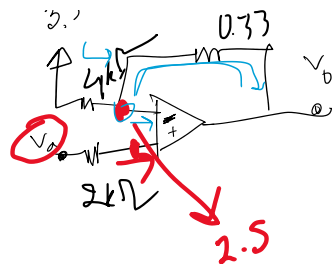

$$= 2.5$$
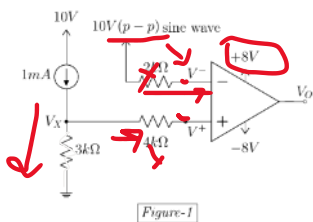
$$\frac{3.3 - 2.5}{4} = \frac{2.5 - V_0}{0.33}$$



(a) [5 marks] Analyze the circuit in Figure-1, and calculate the value of V_X . Now, draw the waveform of V_O , and label the graph properly.

$$V_X - 0 = 1 \times 3 = 3V$$

